

Chapter 4

Coupled Microstrip Line

National Taiwan University of
Science and Technology


Chun-Long Wang

Outline

- Literature Examples
- Motivations
- Coupled Microstrip Line
- Coupled Microstrip Line Using Front-End Decoupling Capacitor
- Coupled Microstrip Line Using Distributed Decoupling Capacitors
- Conclusions

Literature Examples

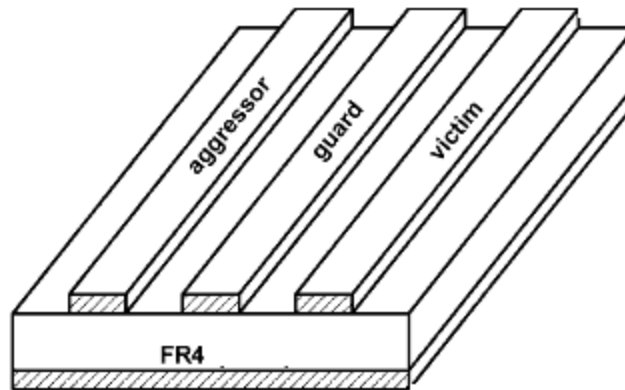
- Coupled Microstrip Line Using Guard Trace [1]
 - Advantages
 - Easy Implementation with the PCB process
 - Disadvantages
 - Slight reduction of the far-end crosstalk noise



[1] D. Brooks, *Signal Integrity Issues and Printed Circuit Board Design*. New York: Prentice Hall, pp. 233–234, 2003.

Literature Examples

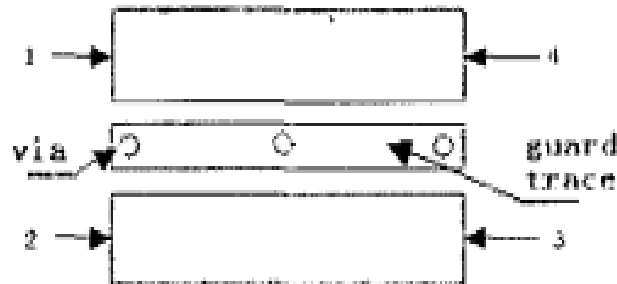- Coupled Microstrip Line Using Grounded Guard Trace [2]
 - Advantages
 - Efficient reduction of the far-end crosstalk noise
 - Disadvantages
 - Layout areas are limited due to via placement



[2] L. Zhi, W. Qiang, and S. Changsheng, "Application of guard traces with vias in the rf pcb layout," in *Proc. IEEE 3rd International Symposium on Electromagnetic Compatibility*, pp. 771-774, May, 2002.

Literature Examples


- Coupled Microstrip Line Using Grounded Guard Trace and Dielectric Overlay [3]

- Advantages

- Efficient reduction of far-end crosstalk noise with only two vias

- Disadvantages

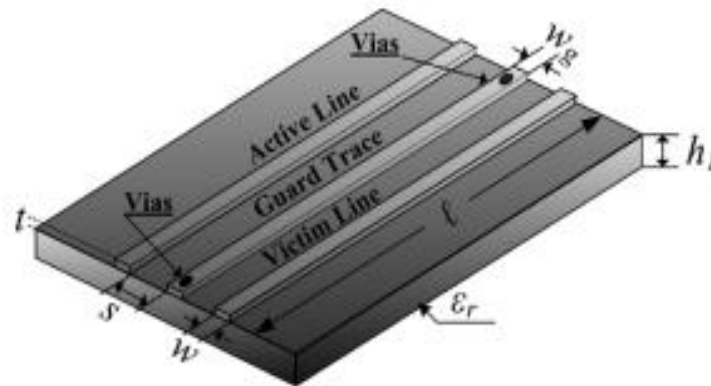- Additional cost of the dielectric overlay



[3] Y. S. Cheng, W. D. Guo, C. P. Hung, R. B. Wu, and D. D. Zutter, "Enhanced microstrip guard trace for ringing noise suppression using a dielectric superstrate," *IEEE Trans. Adv. Packag.*, vol. 33, no. 4, pp. 961–968, Nov. 2010.

Literature Examples


- Coupled Microstrip Line Using Serpentine Guard Trace [4]

- Advantages

- Efficient reduction of far-end crosstalk noise without using any vias and dielectric overlay

- Disadvantages

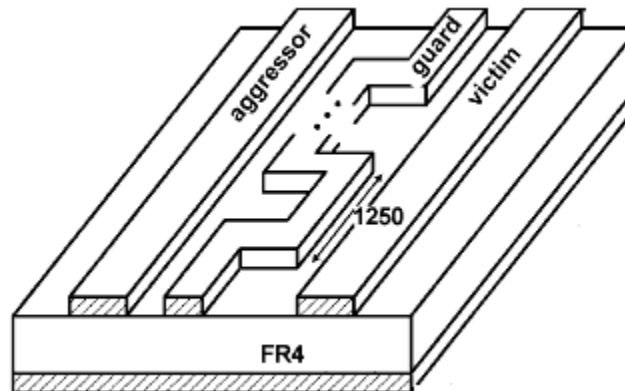- Large area are needed for the serpentine guard trace



[4] K. Lee, H. B. Lee, H. K. Jung, J. Y. Sim, and H. J. Park, "A serpentine guard trace to reduce the far-end crosstalk voltage and the crosstalk induced timing jitter of parallel microstrip lines," *IEEE Trans. Adv. Packag.*, vol. 31, no. 4, pp. 809–817, Nov. 2008.

Literature Examples


- Coupled Microstrip Line Using Alternately Open-Circuited Stubs [5]

- Advantages

- Efficient reduction of the areas spent by the serpentine guard trace

- Disadvantages

- Large reflection

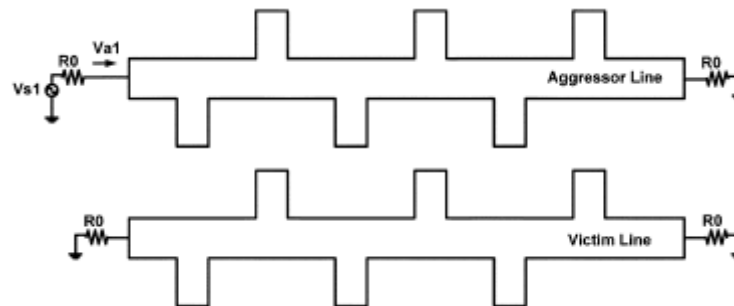

[5] S. K. Lee, K. Lee, H. J. Park, and J. Y. Sim, "FEXT-eliminated stub-alternated microstrip line for multi-gigabit/second parallel links," *Electron. Lett.*, vol. 44, no. 4, pp. 272–273, Feb. 2008.


Motivations

- To Save the Cost
 - Elimination of the Need of Dielectric Overlay
- To Increase the Routing Flexibility
 - Elimination of the Need of Vias
- To Save the Area
 - Elimination of the Need of Serpentine Guard Trace
- To Reduce the Reflection
 - Elimination of the Need of Alternately Open-Circuited Stubs



Coupled Microstrip Line

- Topology

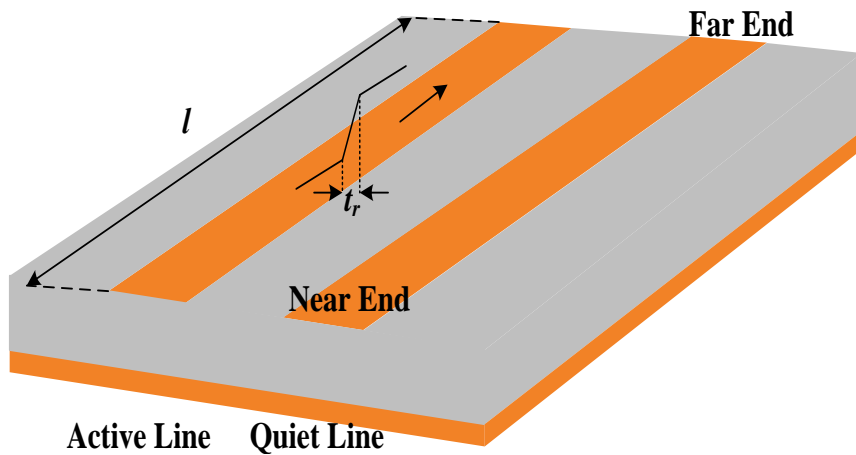
- FR4 Substrate with $\epsilon_r=4.4$ and $\tan\delta=0.02$



3-D view

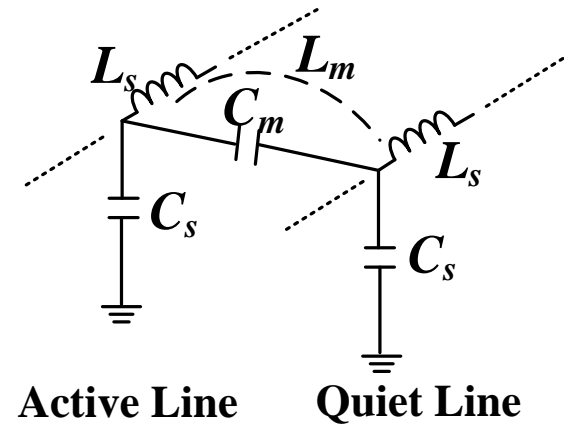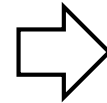

Equivalent circuit

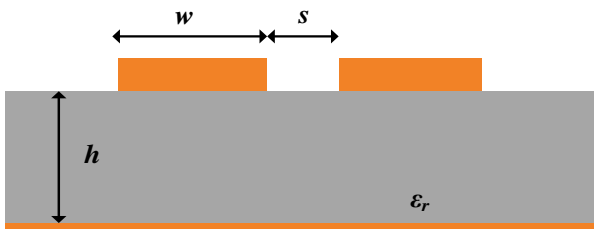


Cross-sectional view

| w (mm) | s (mm) | h (mm) | l (mm) |
|----------|----------|----------|----------|
| 1.42 | 0.7 | 0.8 | 40 |

Dimensions


Coupled Microstrip Line

- Even- and Odd-Mode Equivalent Circuits

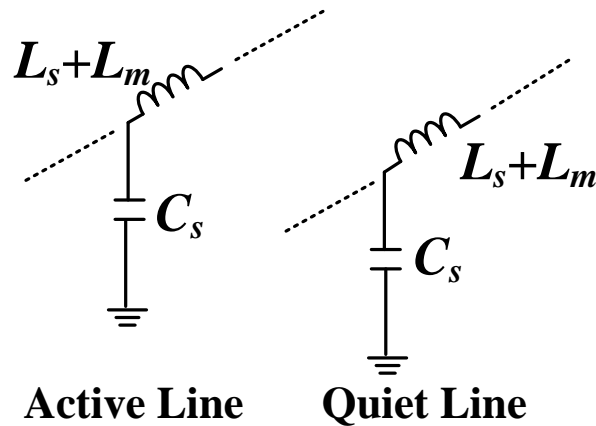

Even-mode equivalent circuit

$$TD_{even} = l\sqrt{(L_s + L_m)(C_s)}$$

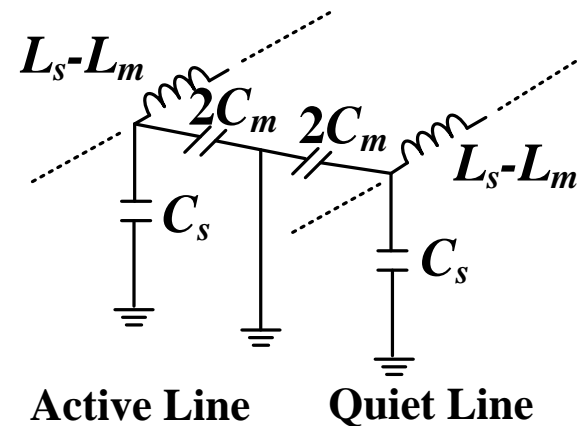


Odd-mode equivalent circuit

$$TD_{odd} = l\sqrt{(L_s - L_m)(C_s + 2C_m)}$$

Coupled Microstrip Line

- FEXT and NEXT

- Even-and Odd-mode Decomposition

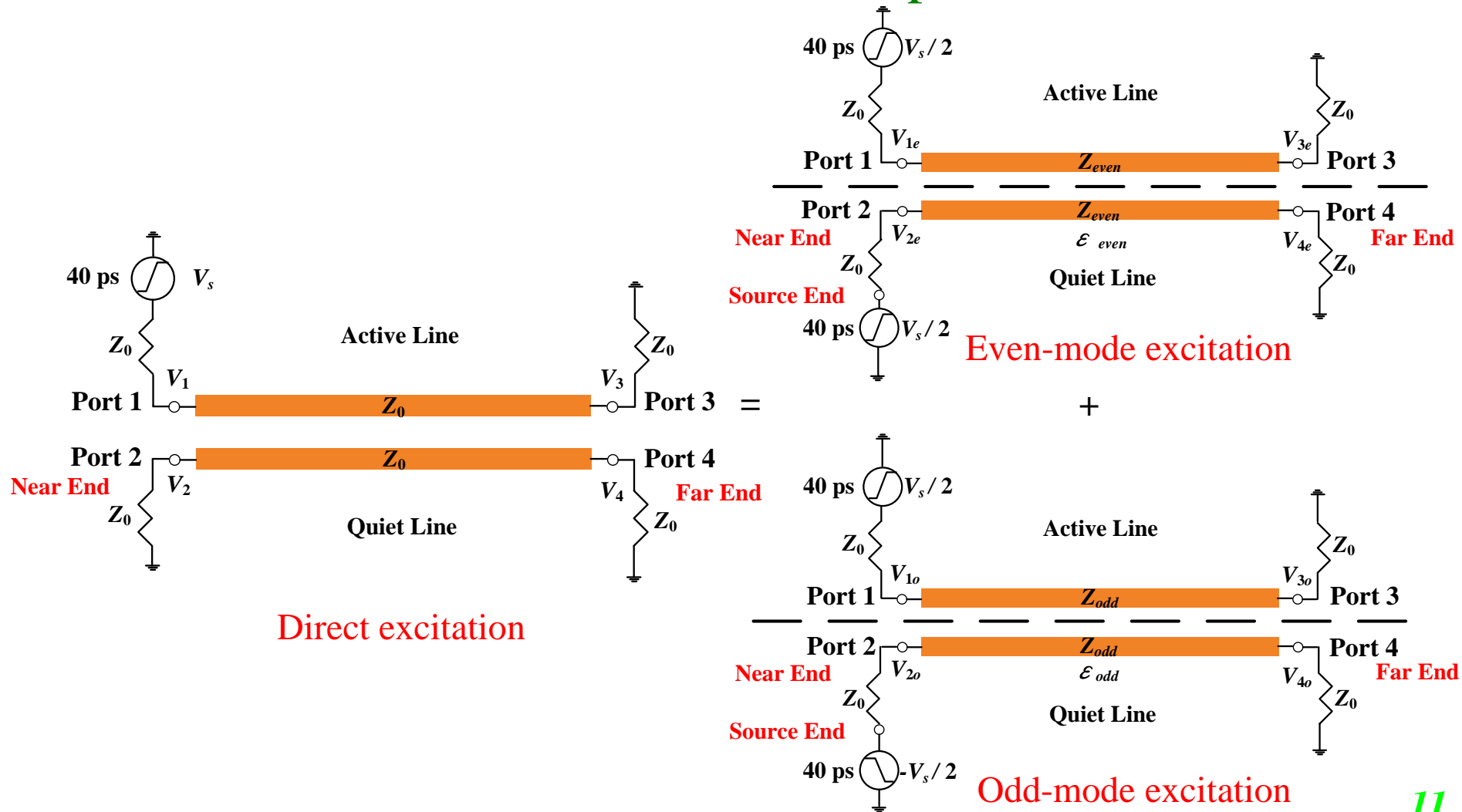


Coupled Microstrip Line


- FEXT and NEXT
 - Ideal Coupled Line

| TD_{even} (ps) | TD_{odd} (ps) | T_d (ps) |
|------------------|-----------------|------------|
| 253.614 | 229.202 | 24.412 |

| Far-end crosstalk noise (volt) | 0.076 |
|--------------------------------|-------|
|--------------------------------|-------|

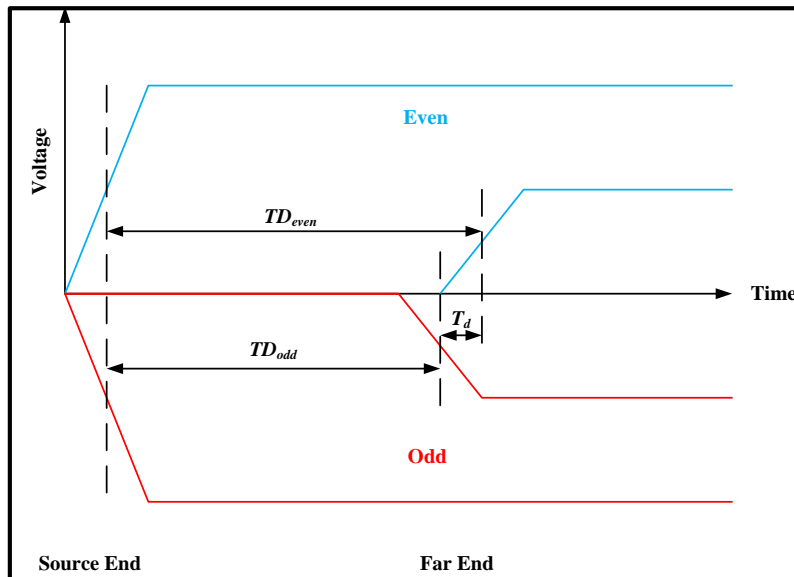


FEXT: $V_{4e}(t)$ and $V_{4o}(t)$

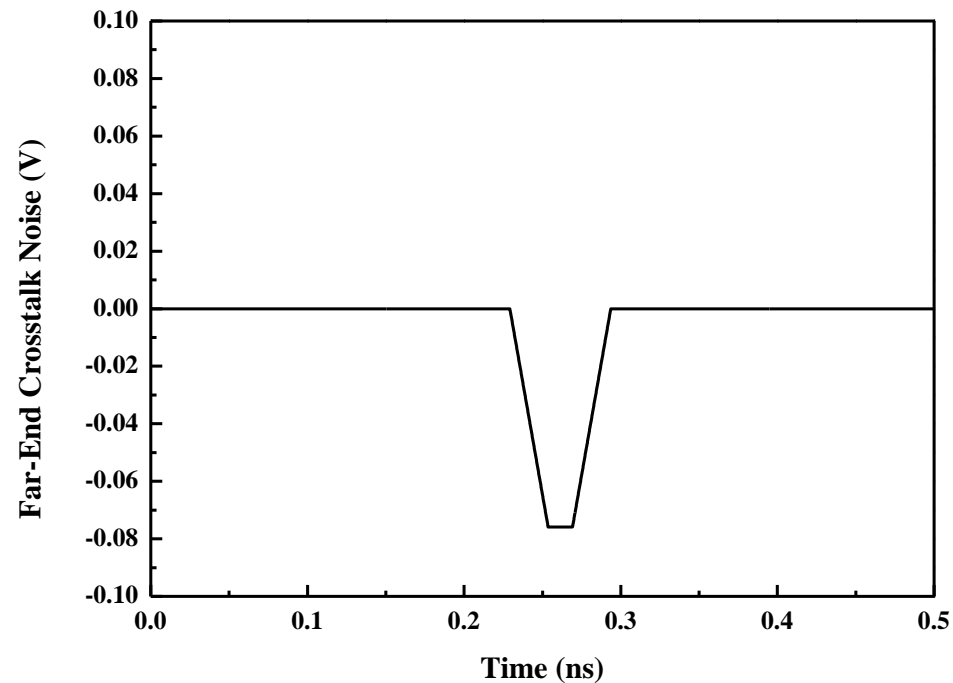

FEXT: $V_4(t)$

Coupled Microstrip Line

- FEXT and NEXT
 - Ideal Coupled Line

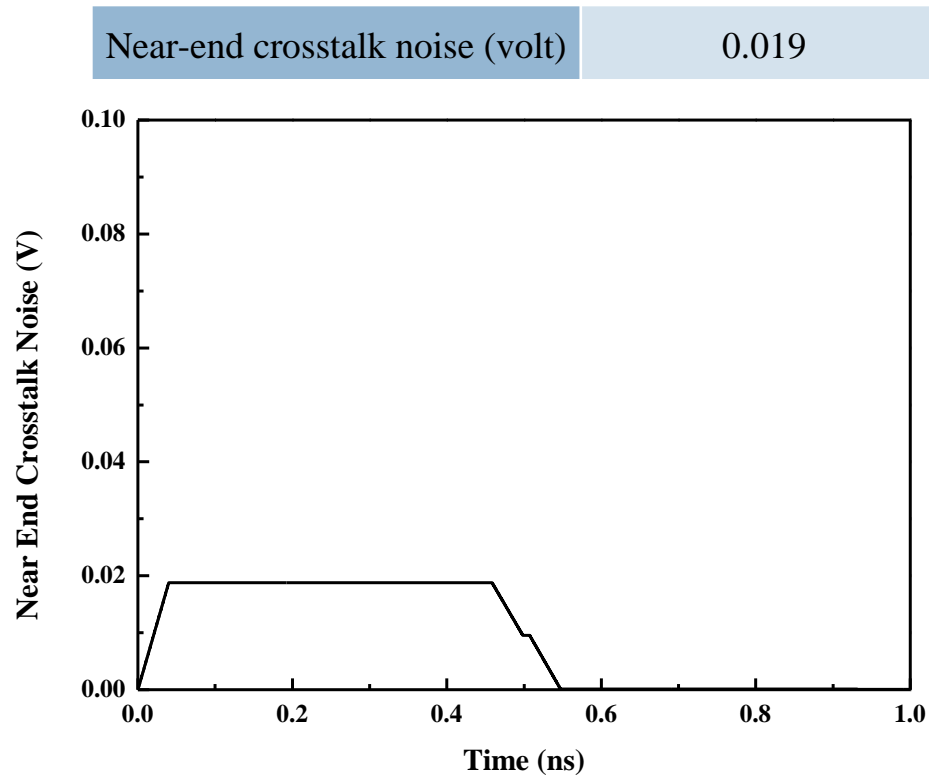

NEXT: $V_2(t)$

Coupled Microstrip Line

- FEXT and NEXT

- Estimation Equations

- Peak of NEXT occurs at $t=t_r$

$$V_2(t_r) = V_{2e}(t_r) + V_{2o}(t_r)$$

$$V_{2e}(t_r) = \frac{V_s}{2} \left(\frac{Z_{even}}{Z_{even} + Z_0} \right)$$

$$V_{2o}(t_r) = -\frac{V_s}{2} \left(\frac{Z_{odd}}{Z_{odd} + Z_0} \right)$$

- Peak of FEXT occurs at $t=TD_{even}$

$$V_4(t) = V_{4o}(t) + V_{4e}(t)$$

$$|V_4(TD_{even})| = V_{max} \min\left(\frac{T_d}{t_r}, 1\right)$$

$$V_{max} = \frac{Z_0}{Z_{even} + 2Z_0 + Z_{odd}} V_s$$


Coupled Microstrip Line

- FEXT and NEXT


- Lossless Coupled Microstrip Line

| TD_{even} (ps) | TD_{odd} (ps) | T_d (ps) |
|------------------|-----------------|------------|
| 254.414 | 234.002 | 20.412 |

| Far-end crosstalk noise (volt) | 0.0641 |
|--------------------------------|--------|
|--------------------------------|--------|

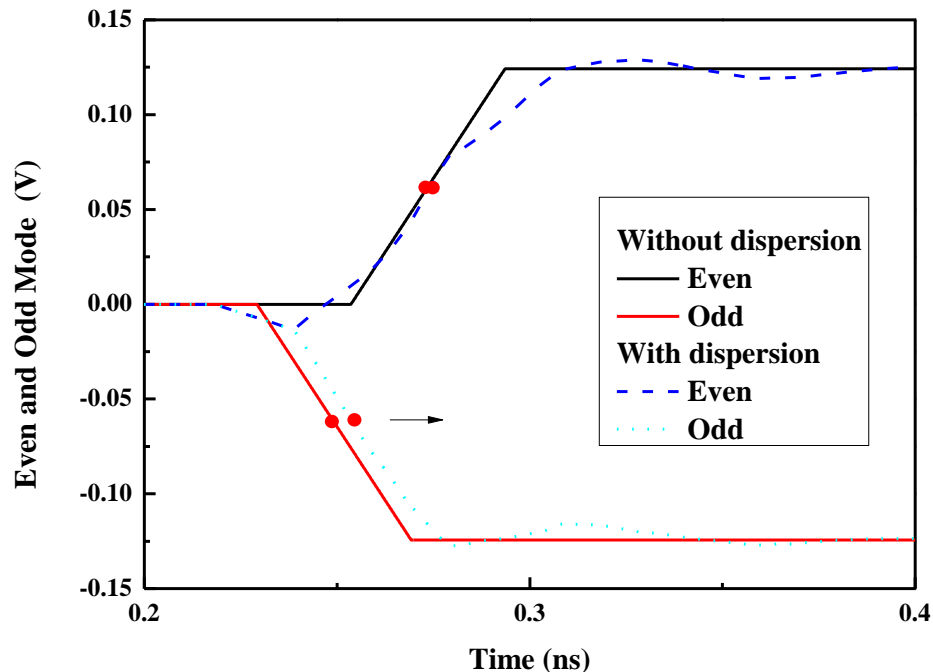

FEXT: $V_{4e}(t)$ and $V_{4o}(t)$

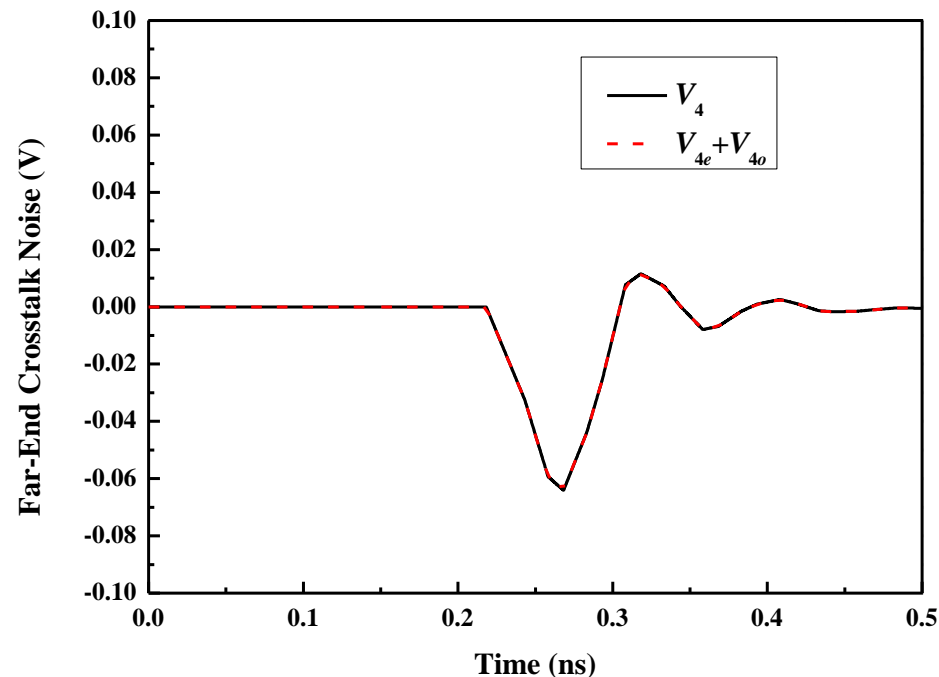


FEXT: $V_4(t)$

Coupled Microstrip Line

- FEXT and NEXT
 - Lossless Coupled Microstrip Line

Near-end crosstalk noise (volt)

0.0169

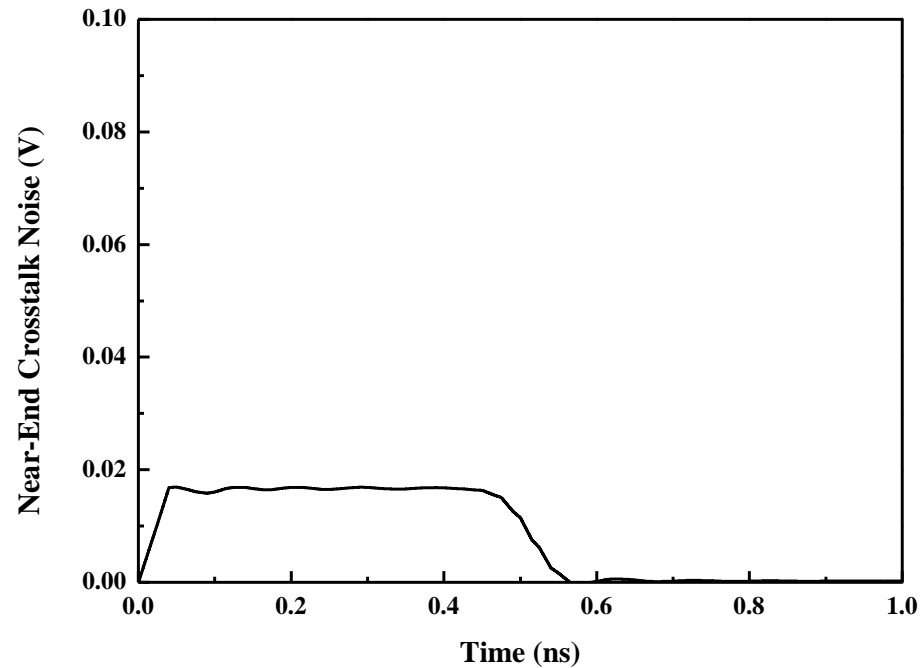

NEXT: $V_2(t)$


Coupled Microstrip Line

- FEXT and NEXT


- Lossy Coupled Microstrip Line

| TD_{even} (ps) | TD_{odd} (ps) | T_d (ps) |
|------------------|-----------------|------------|
| 258.814 | 238.202 | 20.612 |

| Far-end crosstalk noise (volt) | Simulation | 0.063 |
|--------------------------------|-------------|-------|
| | Measurement | 0.055 |

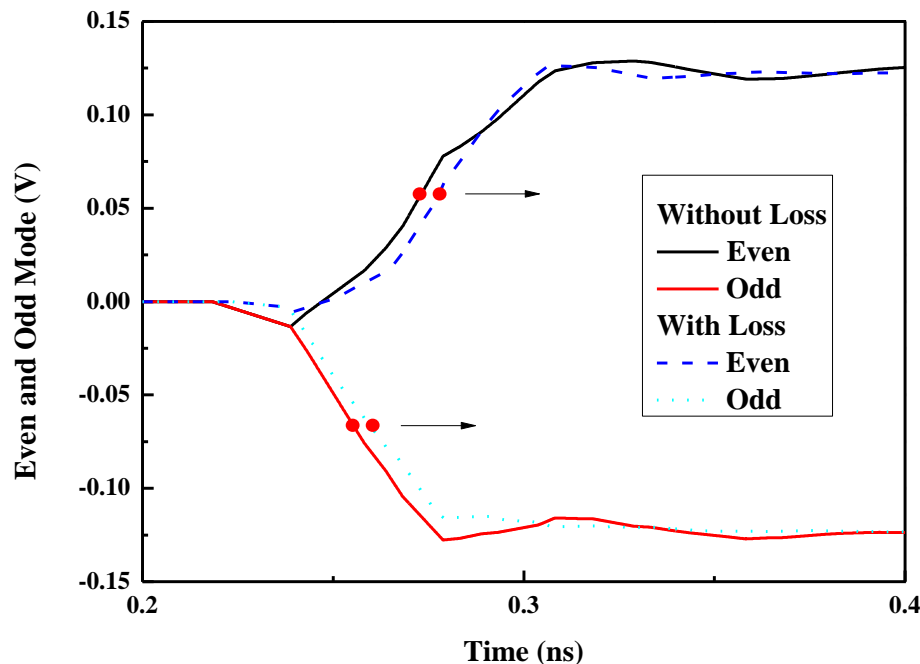


FEXT: $V_{4e}(t)$ and $V_{4o}(t)$

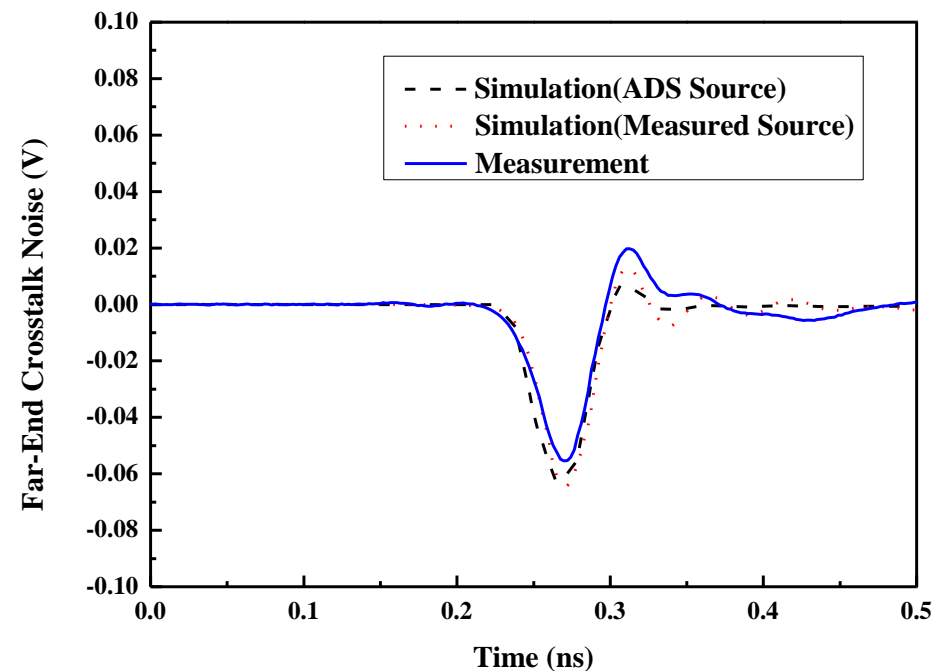

FEXT: $V_4(t)$


Coupled Microstrip Line

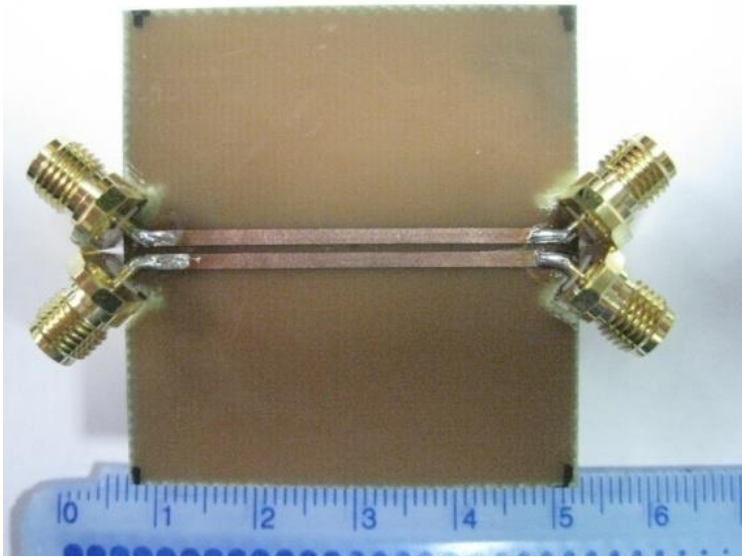- FEXT and NEXT
 - Lossy Coupled Microstrip Line



Real circuit

| | | |
|---------------------------------|-------------|--------|
| Near-end crosstalk noise (volt) | Simulation | 0.0180 |
| | Measurement | 0.0163 |

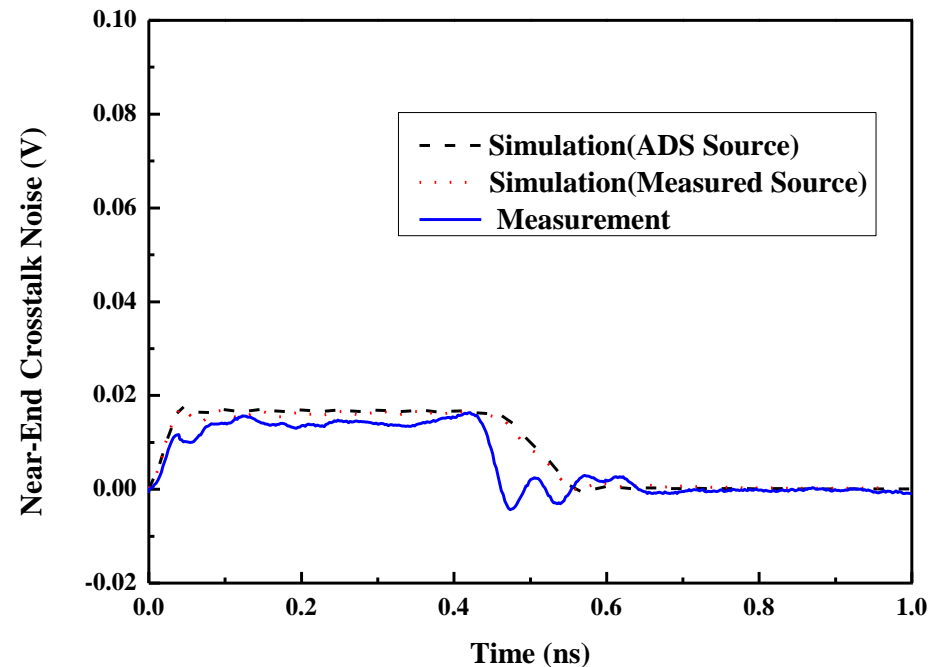


NEXT: $V_2(t)$

Coupled Microstrip Line

- Eye Diagram


- Simulation Setup

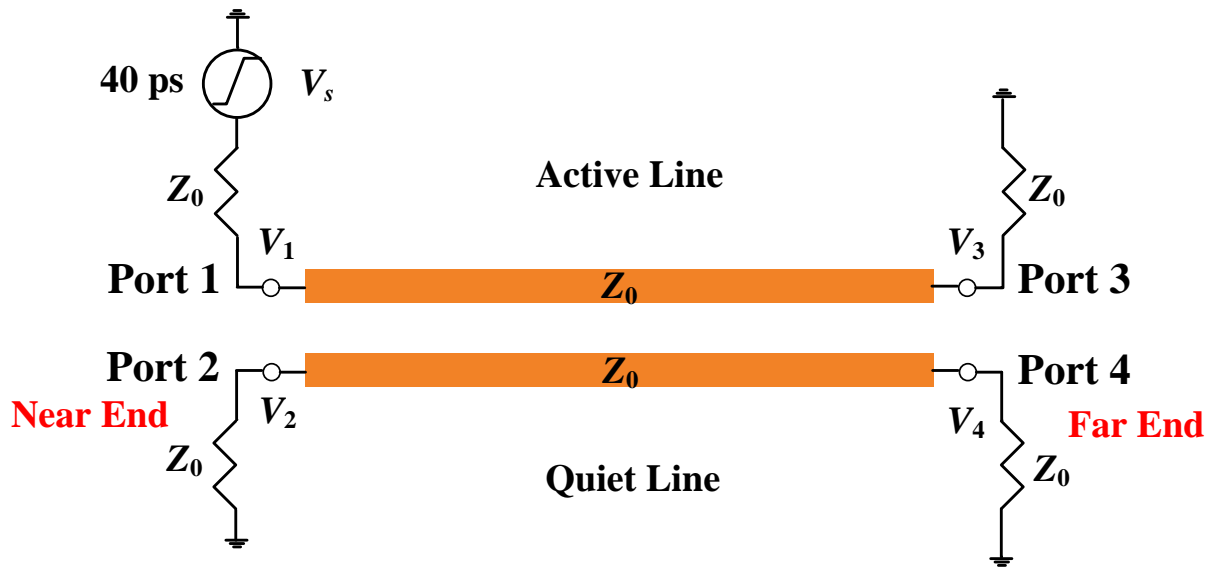- Source V_s : pseudo random bit sequence (PRBS)
 - Observation V_3




Coupled Microstrip Line

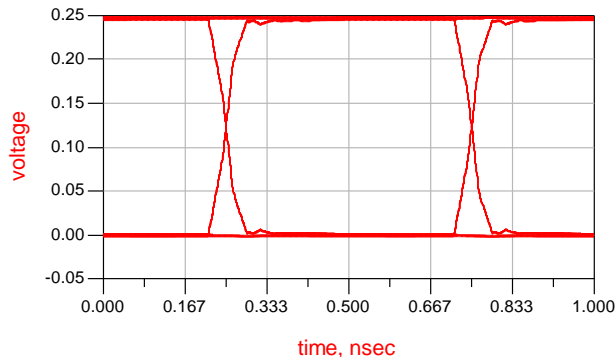
- Eye Diagram
 - Using Various Bit Rate and Rise Time (BR/10)




Bit rate=2 Gbps, $t_r=50$ ps

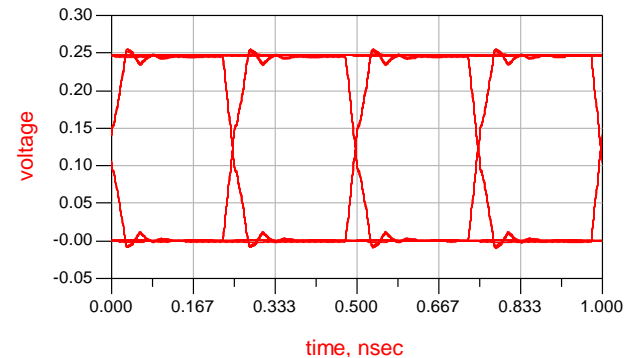

Bit rate=4 Gbps, $t_r=25$ ps

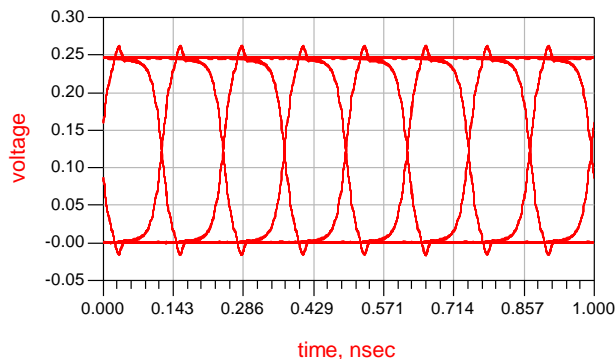

Bit rate=8 Gbps, $t_r=12.5$ ps

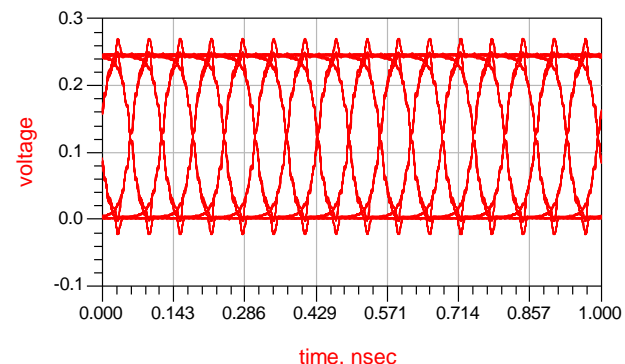

Bit rate=16 Gbps, $t_r=6.25$ ps

Coupled Microstrip Line

- Eye Diagram


- Eye Height, Width, and Jitter

| | Eye High (%) | Eye Width (%) | Jitter (%) |
|-------------------------------|--------------|---------------|------------|
| BR = 2 Gbps, $t_r = 50$ ps | 97.2 | 99.6 | 4.44 |
| BR = 4 Gbps, $t_r = 25$ ps | 95.2 | 99.6 | 4.44 |
| BR = 8 Gbps, $t_r = 12.5$ ps | 94 | 99.76 | 4.432 |
| BR = 16 Gbps, $t_r = 6.25$ ps | 79.6 | 99.2 | 13.36 |



Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Topology

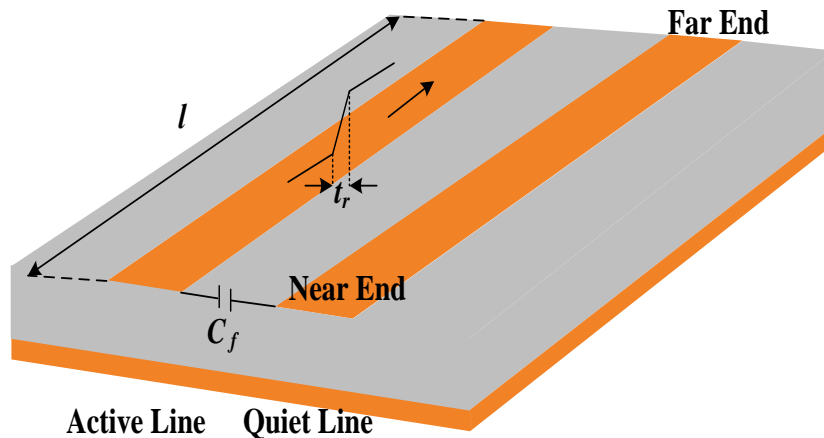
- FR4 Substrate with $\epsilon_r=4.4$ and $\tan\delta=0.02$



3-D view

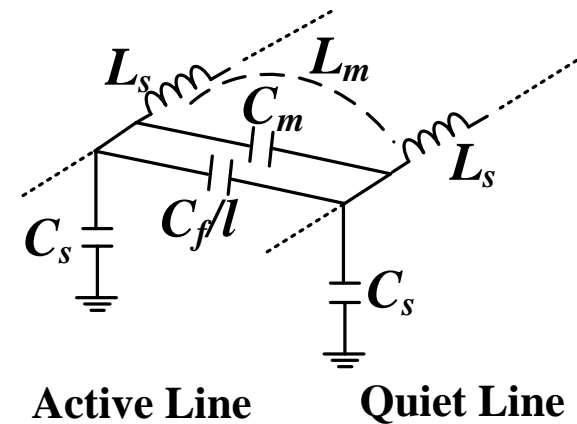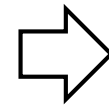

Equivalent circuit

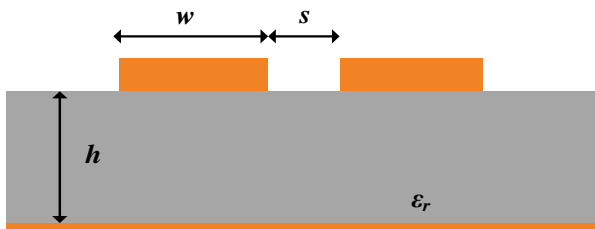


Cross-sectional view

| w (mm) | s (mm) | h (mm) | l (mm) |
|----------|----------|----------|----------|
| 1.42 | 0.7 | 0.8 | 40 |

Dimensions


Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Even- and Odd-Mode Equivalent Circuits

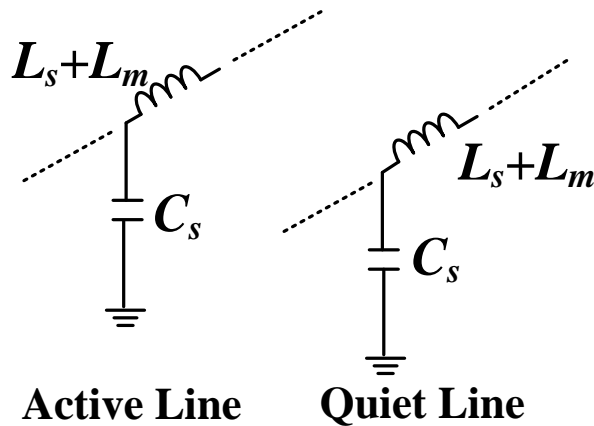

Even-mode equivalent circuit
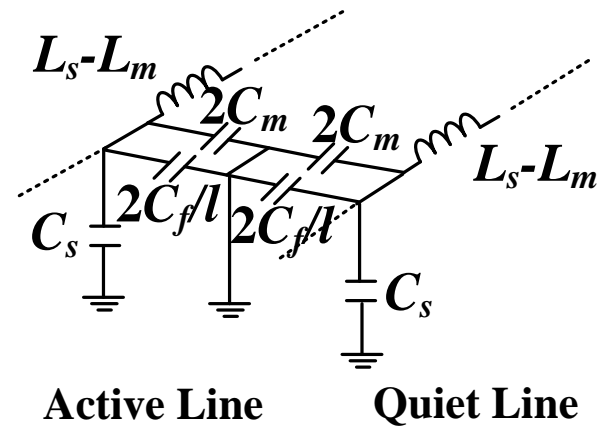
$$TD_{even} = l \sqrt{(L_s + L_m)(C_s)}$$



Odd-mode equivalent circuit

$$TD_{odd}^c = l \sqrt{(C_s + 2C_m + \frac{2C_f}{l})(L_s - L_m)}$$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Design Concept

- Make TD_{even} and TD_{odd} Equal through Adding the Front-End Decoupling Capacitor C_f

$$T_d = TD_{even} - TD_{odd} = TD_{odd}^c - TD_{odd}$$

$$T_d = l\sqrt{L_s - L_m} \left(\sqrt{C_s + 2C_m + \frac{2C_f}{l}} - \sqrt{C_s + 2C_m} \right)$$

TD_{even} : even - mode time delay with or without the front - end decoupling capacitor

TD_{odd} : odd - mode time delay without the front - end decoupling capacitor


TD_{odd}^c : odd - mode time delay with the front - end decoupling capacitor

T_d : time difference between the odd - mode and even - mode time delays


Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT

- Even-and Odd-mode Decomposition

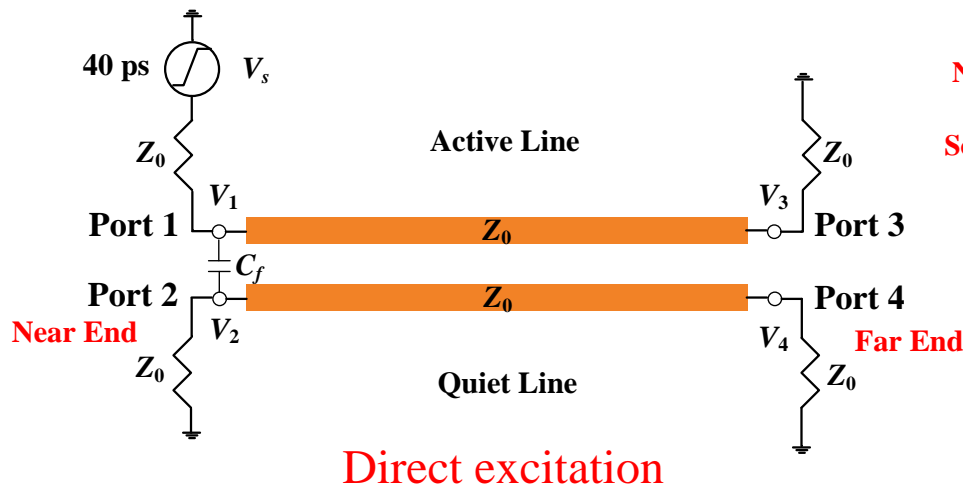

| T_d (ps) | C_f (pF) |
|------------|------------|
| 24.412 | 0.6 |

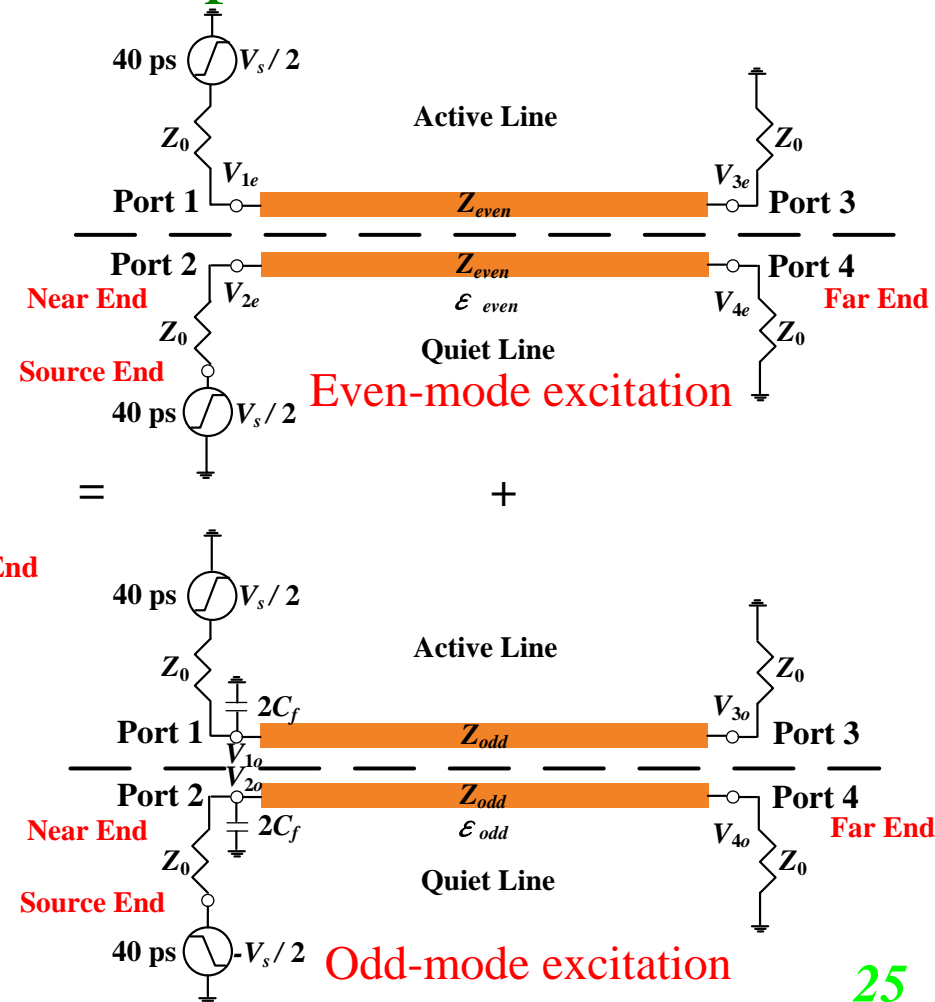


Coupled Microstrip Line Using Front-End Decoupling Capacitor


- FEXT and NEXT
 - Ideal Coupled Line

| TD_{even} (ps) | TD_{odd}^c (ps) | T_d (ps) |
|------------------|-------------------|------------|
| 253.614 | 253.614 | 0 |

| Far-end crosstalk noise (volt) | 0.027 |
|--------------------------------|-------|
|--------------------------------|-------|

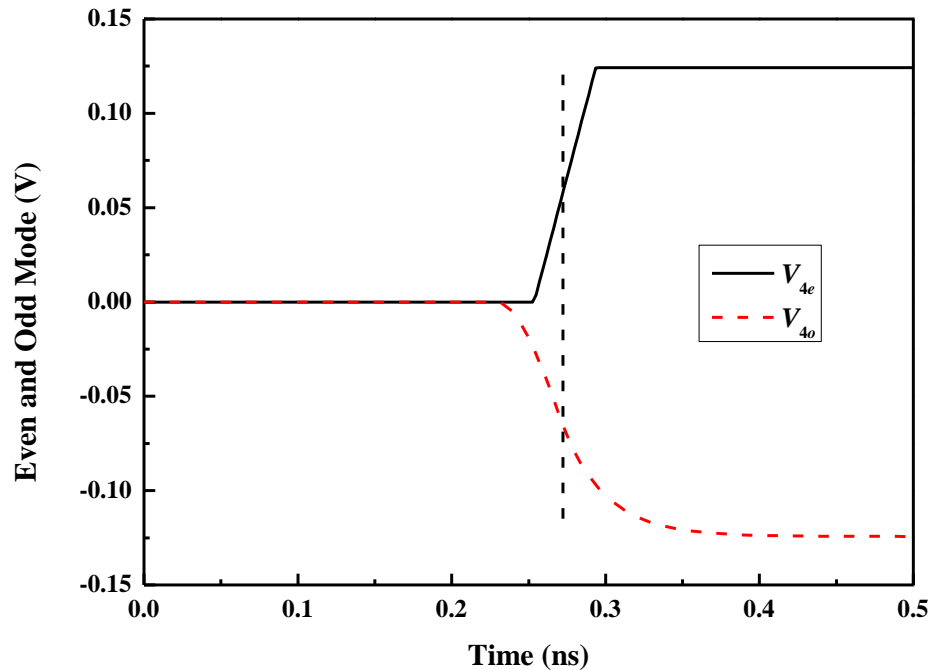


FEXT: $V_{4e}(t)$ and $V_{4o}(t)$

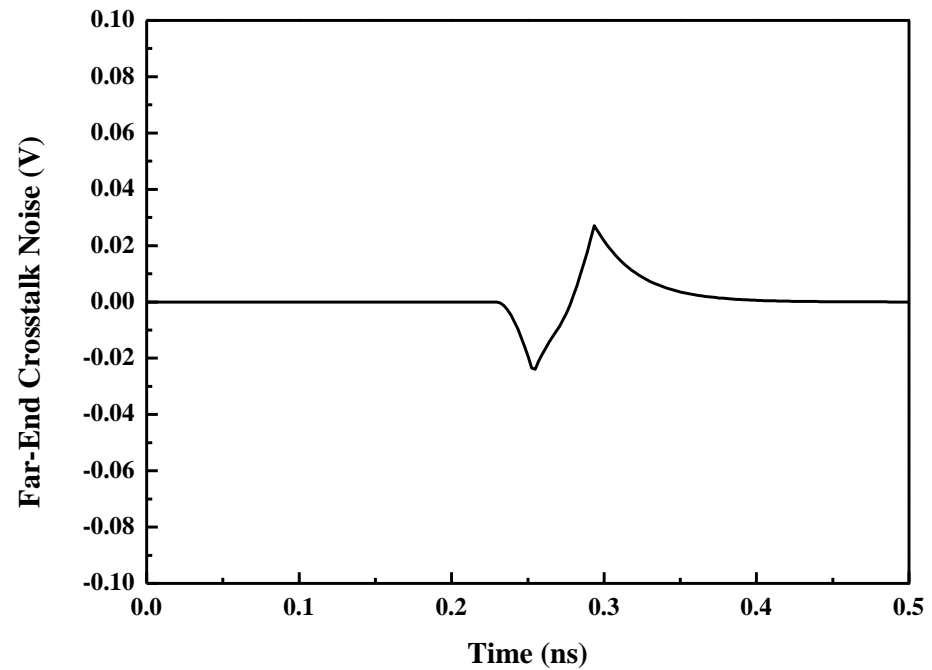

FEXT: $V_4(t)$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT
 - Ideal Coupled Line

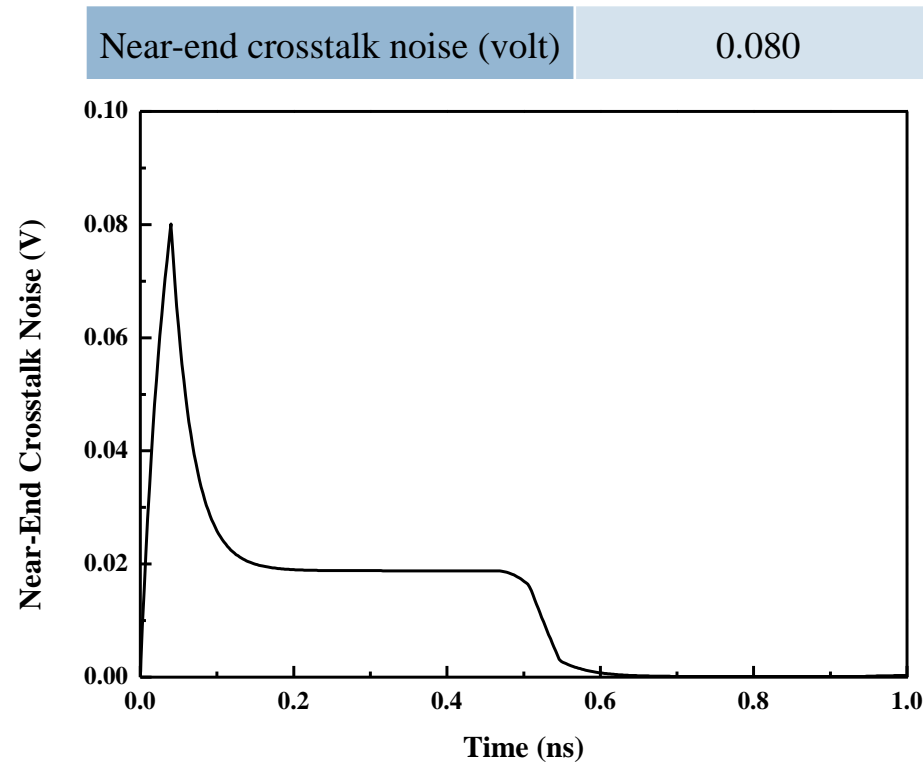


NEXT: $V_2(t)$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT

- Estimation Equations

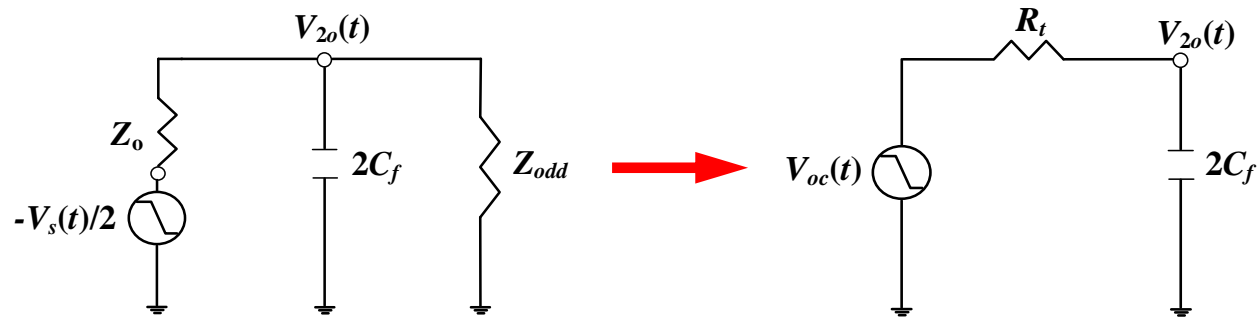- Peak of NEXT of the odd-mode excitation



$$V_s(t) = \frac{V_s}{t_r} [tu(t) - (t-t_r)u(t-t_r)]$$

$$V_{oc}(t) = V_{oc} [tu(t) - (t-t_r)u(t-t_r)]$$

$$V_{oc} = -\frac{V_s}{2t_r} \left(\frac{Z_{odd}}{Z_0 + Z_{odd}} \right) \quad R_t = \frac{Z_0 Z_{odd}}{Z_0 + Z_{odd}}$$

$$V_{2o}(t) = V_{oc} \tau [(e^{-t/\tau} - 1)u(t) - (e^{-(t-t_r)/\tau} - 1)u(t-t_r)] + V_{oc}(t)$$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT

- Estimation Equations

- Peak of NEXT occurs at $t=t_r$

$$V_2(t_r) = V_{2e}(t_r) + V_{2o}(t_r)$$

$$V_{2e}(t_r) = \frac{V_s}{2} \left(\frac{Z_{even}}{Z_{even} + Z_0} \right)$$

$$V_{2o}(t_r) = V_{oc} \tau (e^{-t_r/\tau} - 1) + V_{oc} t_r$$

$$V_2(t_r) = \frac{V_s}{2} \left(\frac{Z_{even}}{Z_{even} + Z_0} \right) + V_{oc} \tau (e^{-t_r/\tau} - 1) + V_{oc} t_r \quad \tau = 2R_t C_f$$

- Peak of FEXT occurs at $t=TD_{odd}+T_d+t_r$

$$V_4(t) = V_{4o}(t) + V_{4e}(t)$$

$$V_{4o}(t) = \left(\frac{2Z_0}{Z_0 + Z_{odd}} \right) V_{2o}(t - TD_{odd})$$

$$V_4(TD_{odd} + T_d + t_r) = \left(\frac{2Z_0}{Z_0 + Z_{odd}} \right) [V_{oc} \tau (e^{-(t_r+T_d)/\tau} - e^{-T_d/\tau}) + V_{oc} t_r] + V_{max}$$

Coupled Microstrip Line Using Front-End Decoupling Capacitor


- FEXT and NEXT

- Lossless Coupled Microstrip Line


| T_d (ps) | C_f (pF) |
|------------|------------|
| 20.412 | 0.5 |

| TD_{even} (ps) | TD_{odd}^c (ps) | T_d (ps) |
|------------------|-------------------|------------|
| 254.414 | 254.414 | 0 |

| Far-end crosstalk noise (volt) | 0.018 |
|--------------------------------|-------|
|--------------------------------|-------|

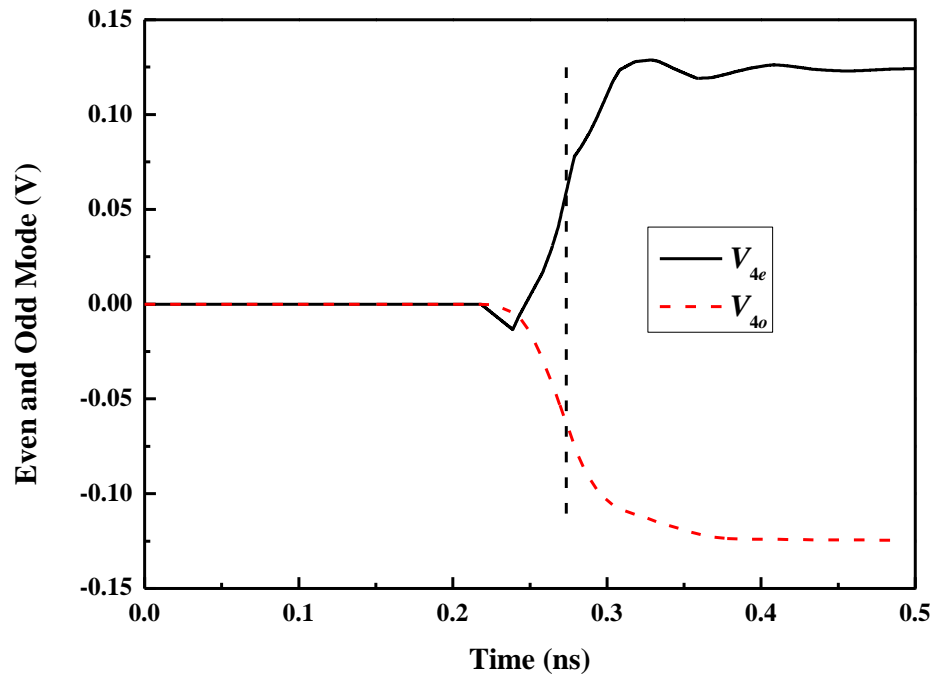

FEXT: $V_{4e}(t)$ and $V_{4o}(t)$

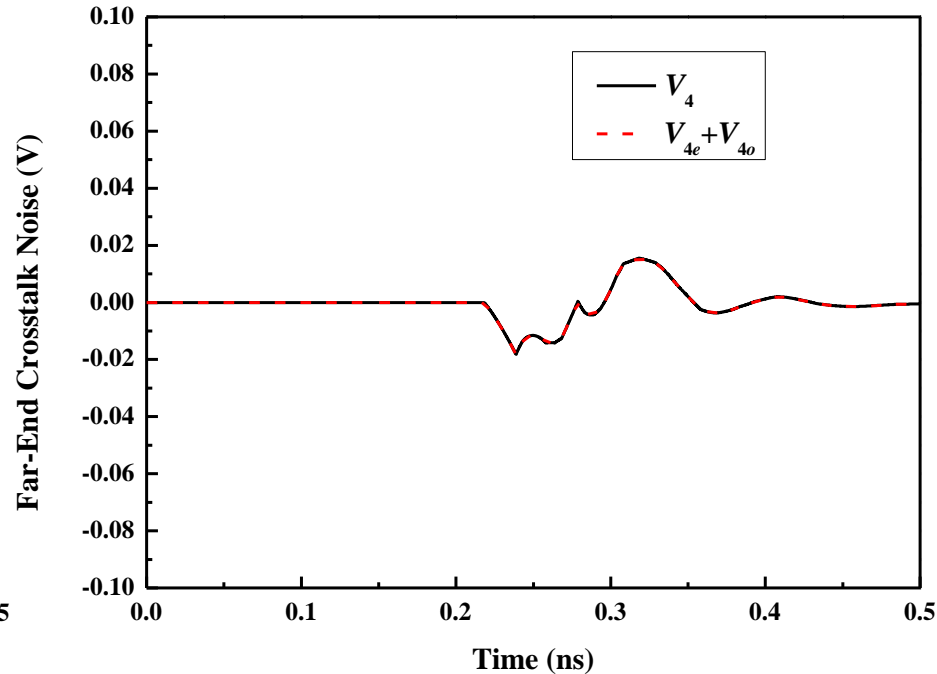


FEXT: $V_4(t)$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT
 - Lossless Coupled Microstrip Line

Near-end crosstalk noise (volt)

0.071

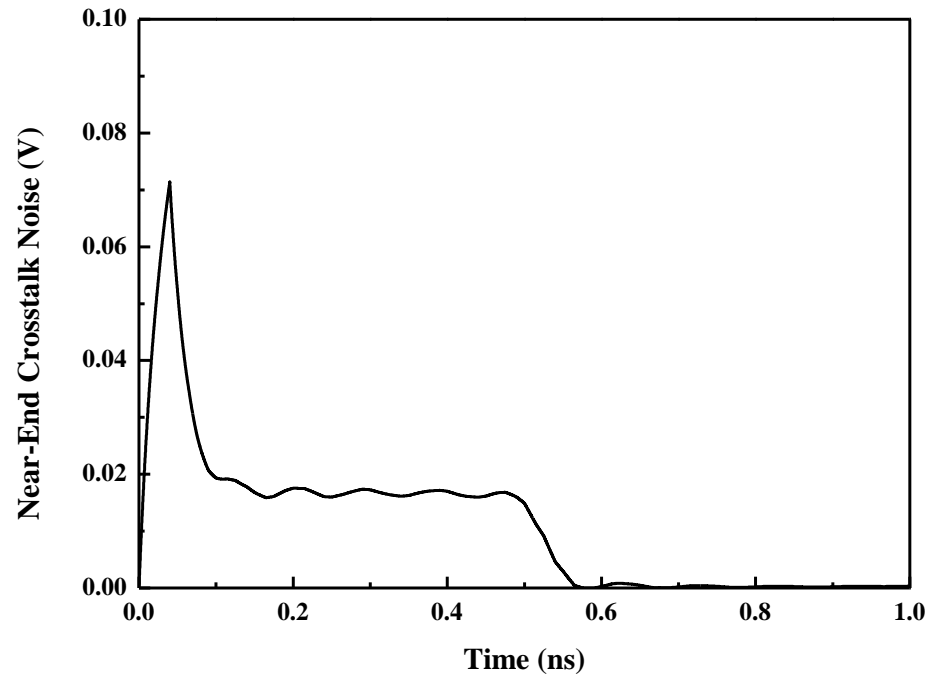

NEXT: $V_2(t)$


Coupled Microstrip Line Using Front-End Decoupling Capacitor

- FEXT and NEXT

- Lossy Coupled Microstrip Line


| T_d (ps) | C_f (pF) |
|------------|------------|
| 20.612 | 0.5 |

| TD_{even} (ps) | TD_{odd}^c (ps) | T_d (ps) |
|------------------|-------------------|------------|
| 258.814 | 258.814 | 0 |

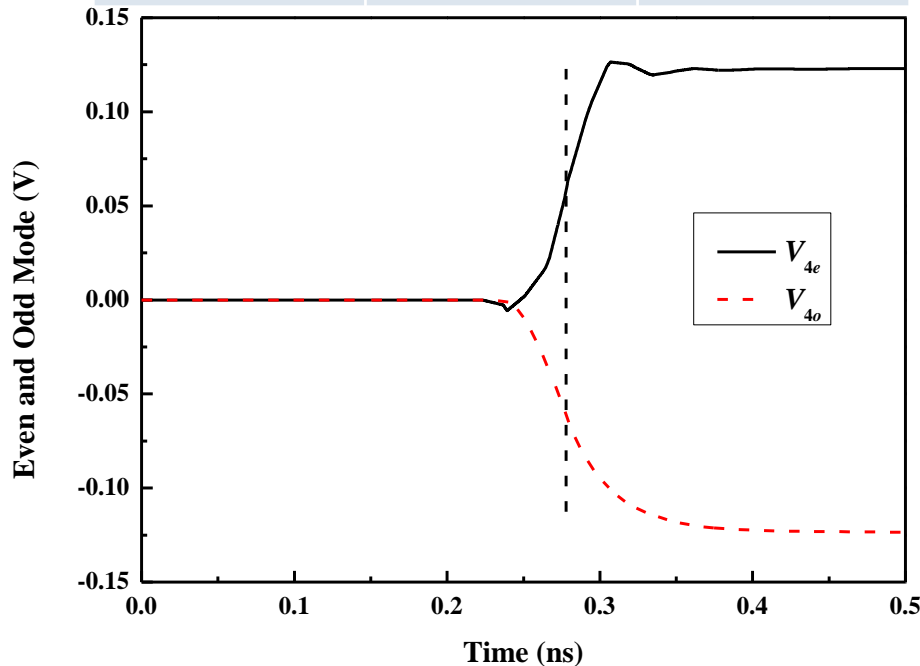

FEXT: $V_{4e}(t)$ and $V_{4o}(t)$


| Far-end crosstalk noise (volt) | Simulation | 0.0257 |
|--------------------------------|-------------|--------|
| | Measurement | 0.0268 |

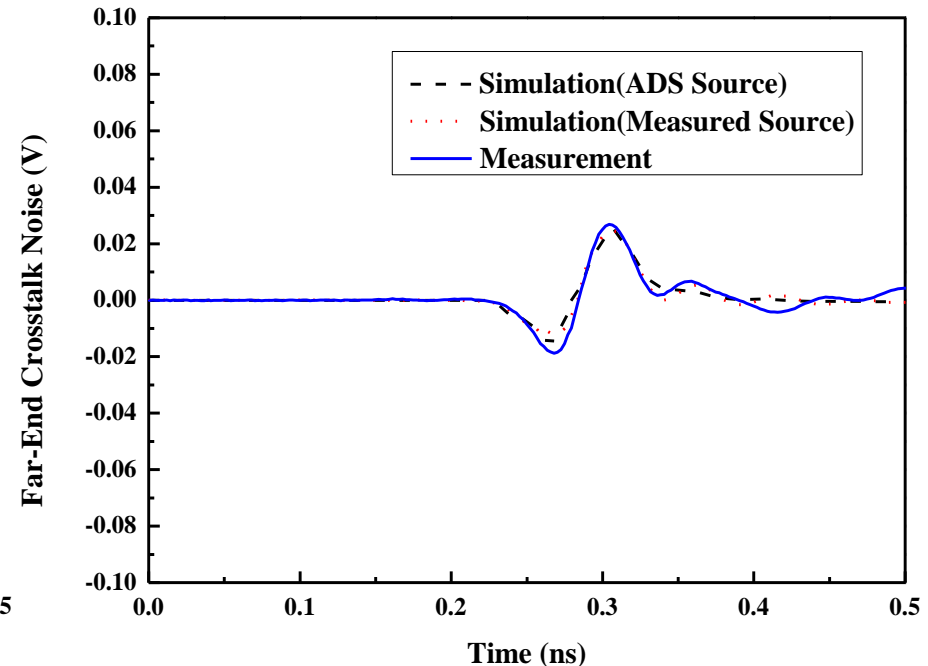


FEXT: $V_4(t)$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

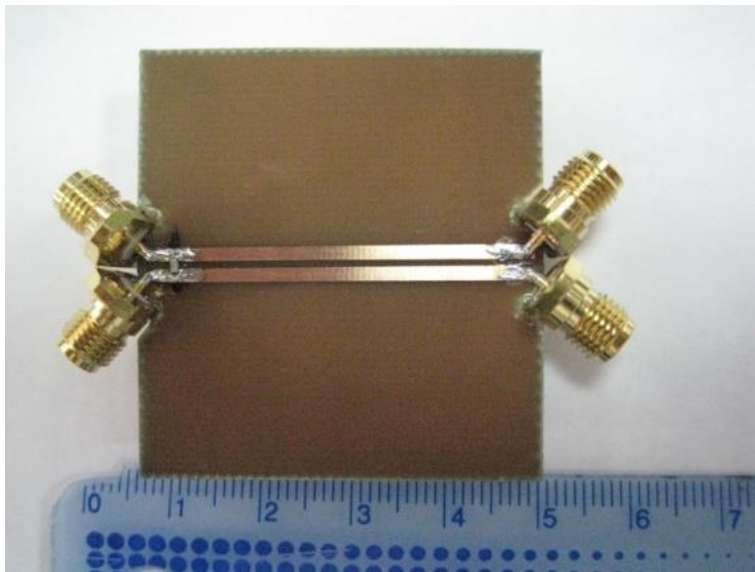- FEXT and NEXT
 - Lossy Coupled Microstrip Line



Real circuit

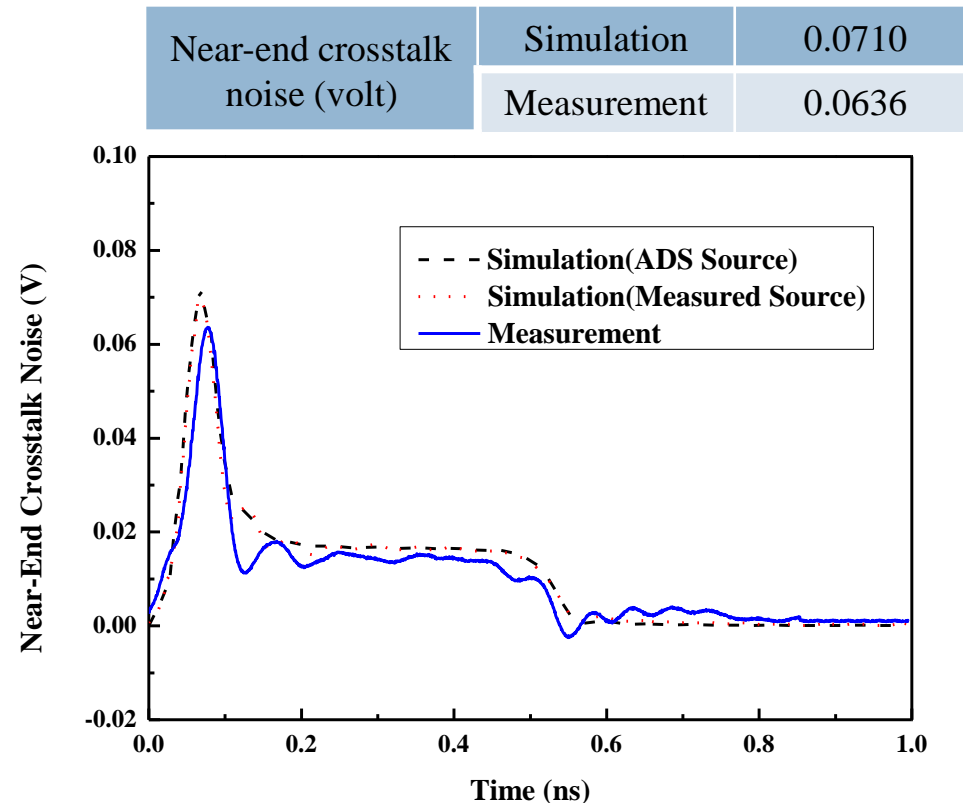


NEXT: $V_2(t)$

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Eye Diagram

- Simulation Setup

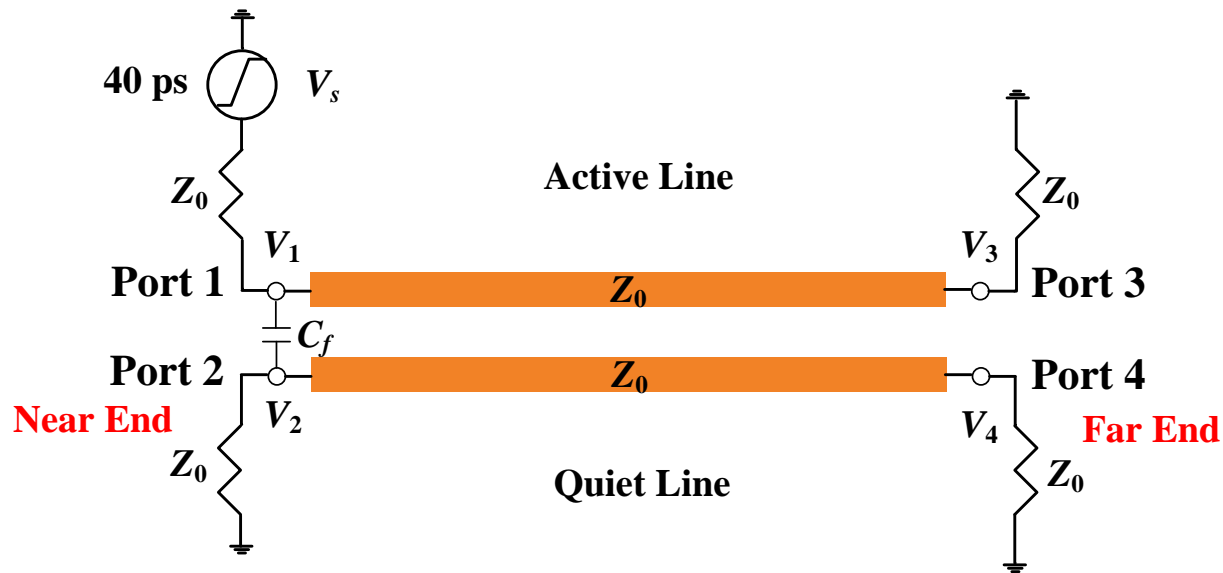
- Source V_s : pseudo random bit sequence (PRBS)
 - Observation V_3




Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Eye Diagram

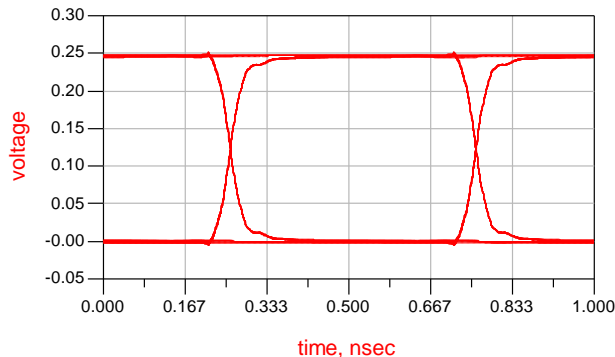
– Using Various Bit Rate and Rise Time (BR/10)




time, nsec
Bit rate=2 Gbps, $t_r=50$ ps

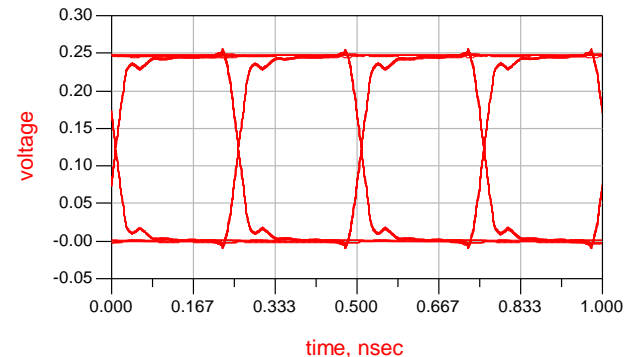

time, nsec
Bit rate=4 Gbps, $t_r=25$ ps

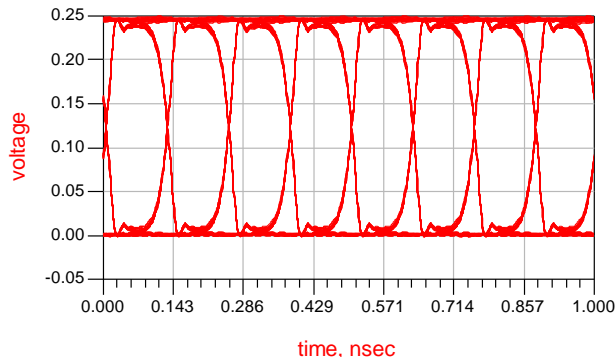

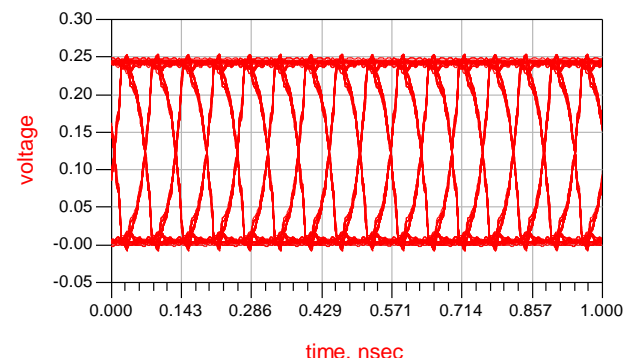time, nsec
Bit rate=8 Gbps, $t_r=12.5$ ps



time, nsec
Bit rate=16 Gbps, $t_r=6.25$ ps

Coupled Microstrip Line Using Front-End Decoupling Capacitor

- Eye Diagram


- Eye Height, Width, and Jitter

| | Eye High (%) | Eye Width (%) | Jitter (%) |
|-------------------------------|--------------|---------------|------------|
| BR = 2 Gbps, $t_r = 50$ ps | 97.2 | 99.6 | 4.44 |
| BR = 4 Gbps, $t_r = 25$ ps | 88.8 | 99.6 | 4.44 |
| BR = 8 Gbps, $t_r = 12.5$ ps | 86 | 99.2 | 8.88 |
| BR = 16 Gbps, $t_r = 6.25$ ps | 64.4 | 97.44 | 31.2 |


Coupled Microstrip Line Using Front-End Decoupling Capacitor

- S -Parameters

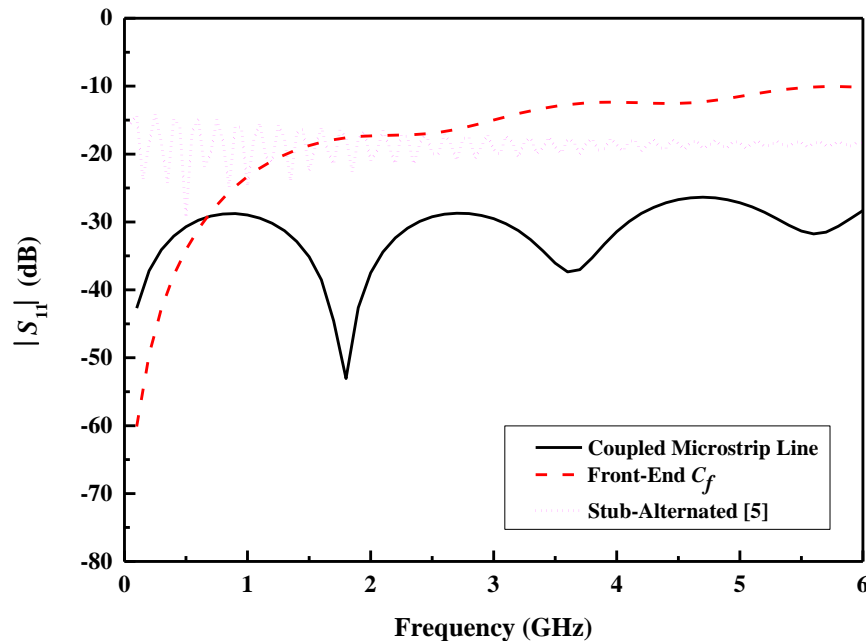- Reflection and Near-End Coupling Coefficients



Reflection coefficient

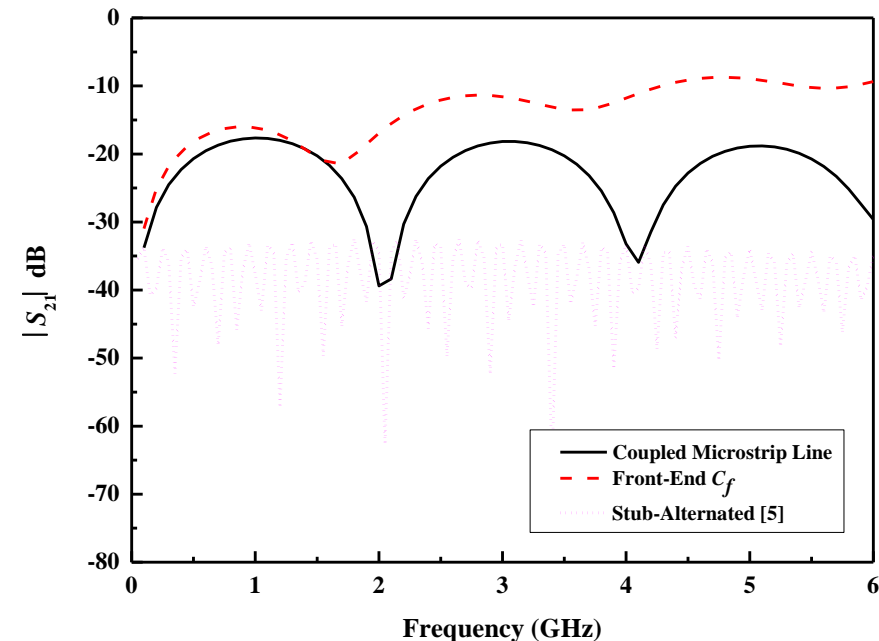


Near-end coupling coefficient


Coupled Microstrip Line Using Front-End Decoupling Capacitor

- S -Parameters

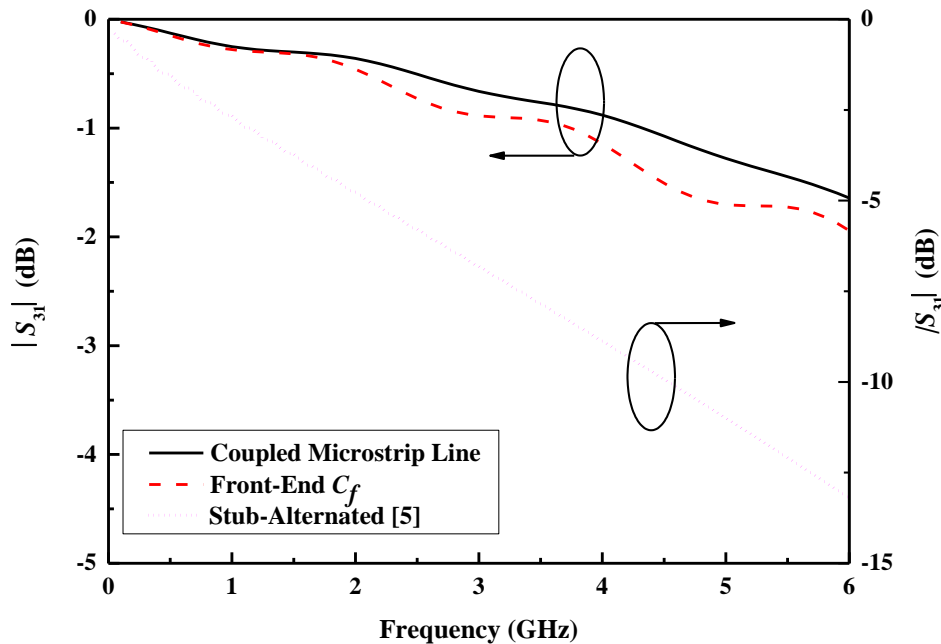– Transmission and Far-End Coupling Coefficients



Transmission coefficient

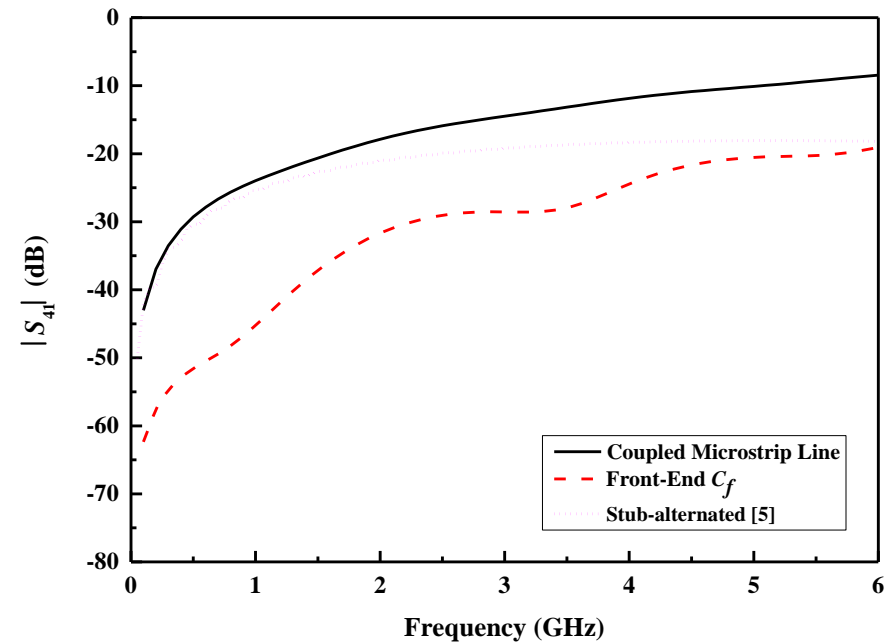


Far-end coupling coefficient

Coupled Microstrip Line Using Distributed Decoupling Capacitors

- FEXT and NEXT

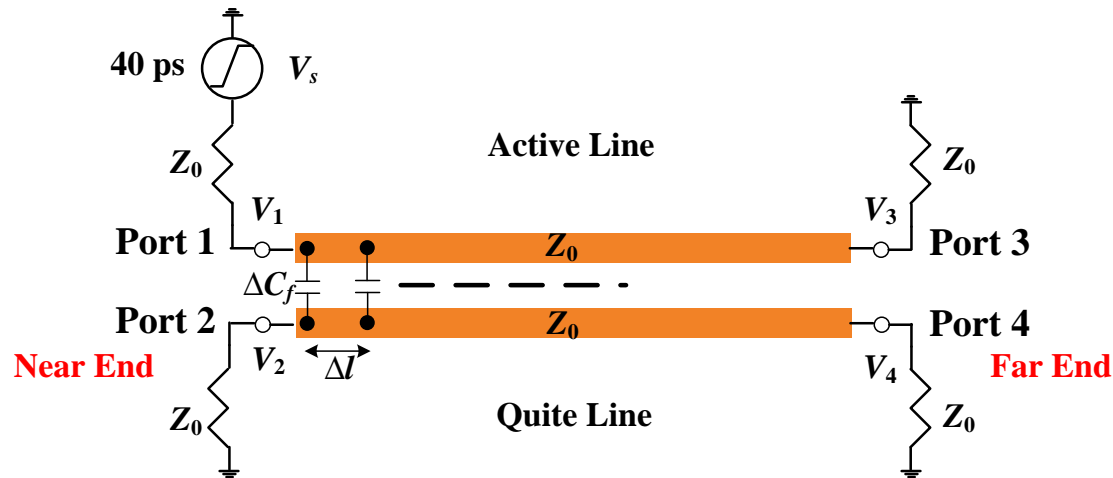– Lossy Coupled Microstrip Line $C_f = 0.5 \text{ pF}$



$$\lambda = \frac{3 \times 10^8}{f_{3\text{dB}}} \frac{1}{\sqrt{\epsilon_{\text{eff}}}}$$


$$f_{3\text{dB}} = \frac{0.35}{t_r}$$

| Δl (mm) | Number of distributed decoupling capacitor | Value of distributed decoupling capacitor (pF) |
|----------------------|--|--|
| 9.2 ($\lambda/2$) | 4 | 0.1250 |
| 4.6 ($\lambda/4$) | 8 | 0.0625 |
| 1.9 ($\lambda/10$) | 20 | 0.0250 |

Coupled Microstrip Line Using Distributed Decoupling Capacitors


- FEXT and NEXT
 - Lossy Coupled Microstrip Line

| | | |
|---------------------------------|--------------|-------|
| Near-end crosstalk noise (volt) | Lumped C_f | 0.071 |
| | $\lambda/10$ | 0.028 |

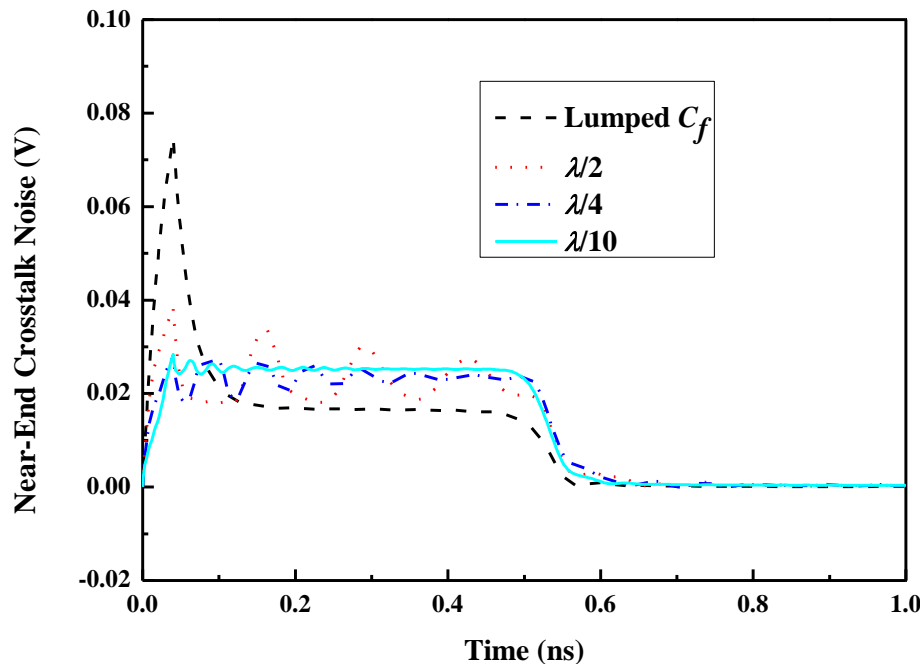

FEXT: $V_2(t)$

| | | |
|--------------------------------|--------------|--------|
| Far-end crosstalk noise (volt) | Lumped C_f | 0.0257 |
| | $\lambda/10$ | 0 |

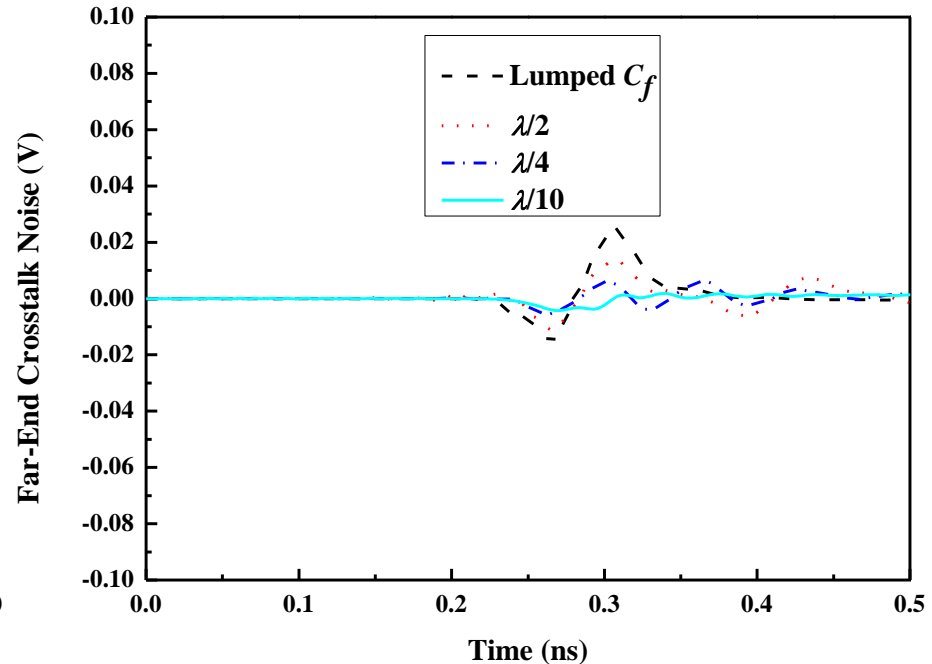


NEXT: $V_4(t)$


Coupled Microstrip Line Using Distributed Decoupling Capacitors

- *S*-Parameters

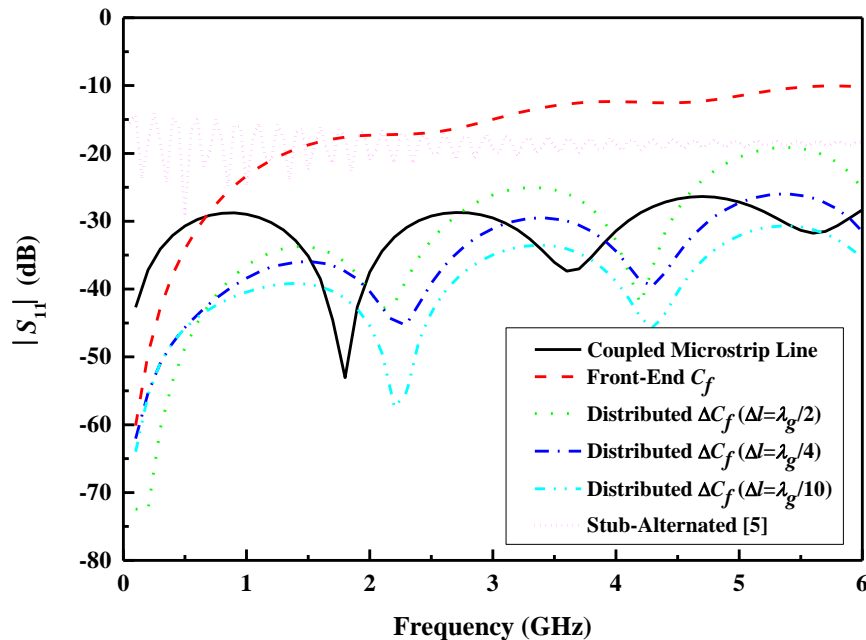- Reflection and Near-End Coupling Coefficients



Reflection coefficient

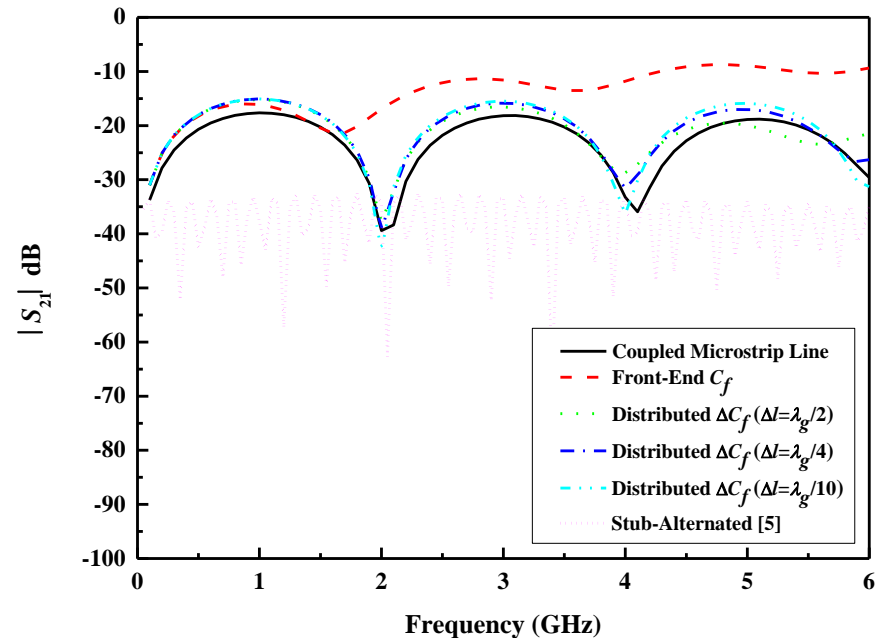


Near-end coupling coefficient


Coupled Microstrip Line Using Distributed Decoupling Capacitors

- S -Parameters

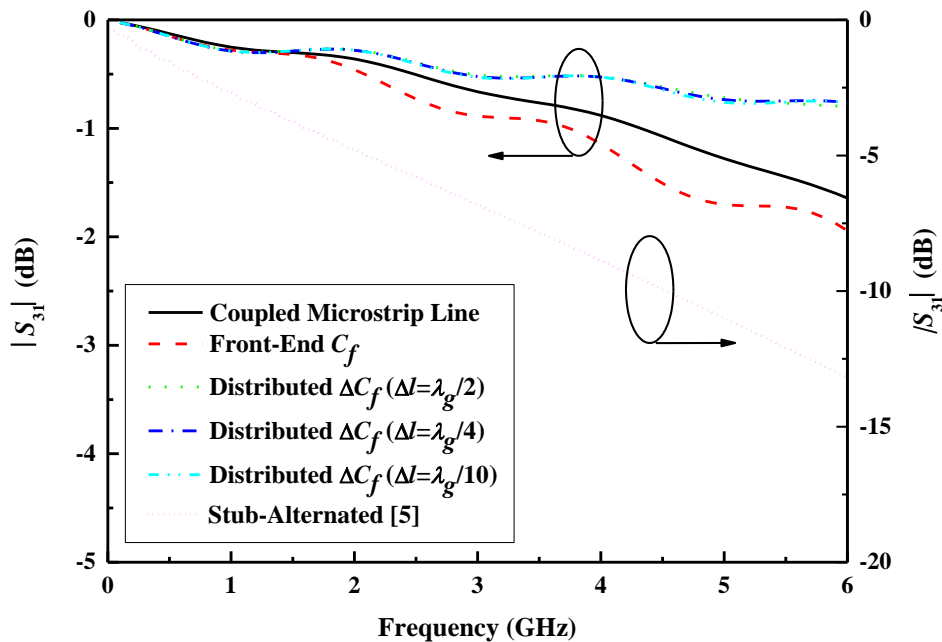– Transmission and Far-End Coupling Coefficients



Transmission coefficient

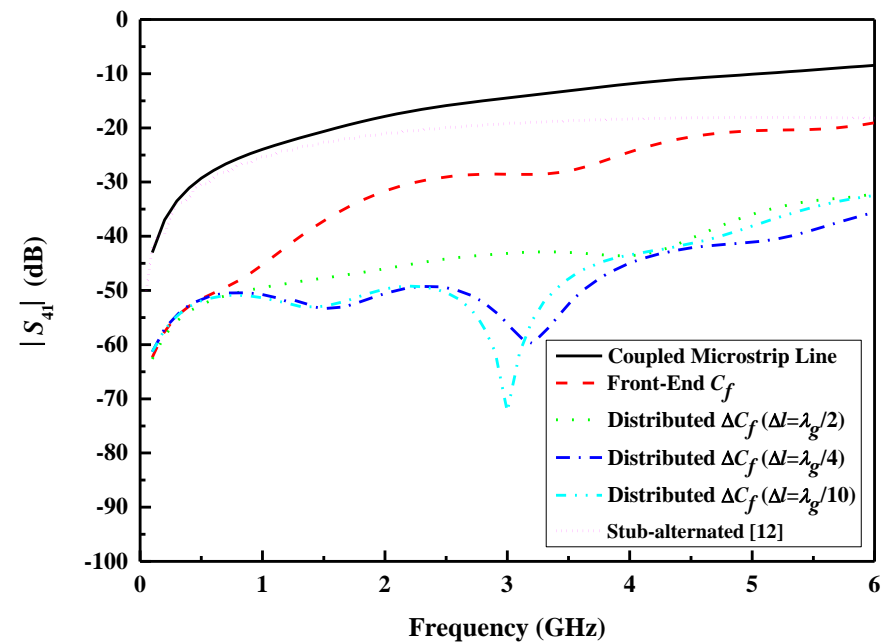


Far-end coupling coefficient

Conclusions

- FEXT and NEXT

| | FEXT (volt) | | NEXT (volt) | |
|------------------------|-------------|------------|-------------|------------|
| | Measurement | Simulation | Measurement | Simulation |
| Conventional | 0.0550 | 0.0630 | 0.0163 | 0.0180 |
| Front-end capacitor | 0.0268 | 0.0257 | 0.0636 | 0.0710 |
| Distributed capacitors | X | 0 | X | 0.0280 |

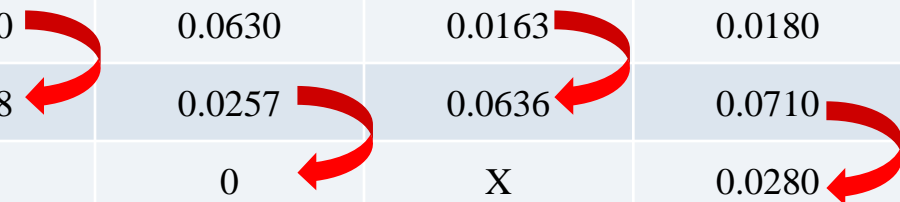

- Eye Diagram

- Performance Degraded Due to Adoption of Decoupling Capacitor

- S-Parameters

- Performance Restored While Using Distributed Capacitors