

Chapter 3

Crosstalk

National Taiwan University of
Science and Technology

Chun-Long Wang

Outline

- Mutual Inductance and Mutual Capacitance
- Inductance and Capacitance Matrix
- Field Simulators
- Crosstalk-Induced Noise
- Simulating Crosstalk Using Equivalent Circuit Models
- Crosstalk-Induced Flight Time and Signal Integrity Variations
- Crosstalk Trends
- Termination of Odd- and Even-Mode Transmission Line Pairs
- Minimization of Crosstalk
- Additional Examples

Introduction

- Influences of Crosstalk

- Disadvantages

- First, crosstalk will change the performance of impedance and propagation velocity, which will adversely affect system-level timings and the integrity of the signal.
 - Additionally, crosstalk will induce noise onto other lines, which may further degrade the signal integrity and reduce noise margins.

- Influence Factors

- Data patterns, line-to-line spacing, and switching rates.

Mutual Inductance and Mutual Capacitance

- Mutual Inductance

- Definition

- The coupling of current via the magnetic field is represented in the circuit model by a mutual inductance L_m .

- Mutual Inductance-Induced Noise

- The mutual inductance L_m will inject a voltage noise onto the victim proportional to the rate of change of the current on the driver line.
 - The magnitude of this noise is calculated as

$$V_{\text{noise}, L_m} = L_m \frac{dI_{\text{driver}}}{dt}$$

Mutual Inductance and Mutual Capacitance

- Mutual Capacitance

- Definition

- The coupling due to the electric field is represented in the circuit model by a mutual capacitor C_m .

- Mutual Capacitance-Induced Noise

- Mutual capacitance C_m will inject a current onto the victim line proportional to the rate in change of voltage on the driven line.
 - The magnitude of this noise is calculated as

$$I_{\text{noise}, C_m} = C_m \frac{dV_{\text{driver}}}{dt}$$

Inductance and Capacitance Matrix

- Introduction

- The inductance and capacitance matrices are known collectively as the *transmission line matrices*.

- Inductance Matrix

- Definition

- For an N -conductor system, the inductance matrix could be expressed as

$$\text{Inductance matrix} = \begin{bmatrix} L_{11} & L_{12} & \cdots & L_{1N} \\ L_{21} & L_{22} & & \\ \vdots & & \ddots & \\ L_{N1} & & & L_{NN} \end{bmatrix}$$

- where L_{NN} is the self-inductance of line N and L_{MN} is the mutual inductance between lines M and N .

Inductance and Capacitance Matrix

- Capacitance Matrix

- Definition

- For an N -conductor system, the capacitance matrix could be expressed as

$$\text{Capacitance matrix} = \begin{bmatrix} C_{11} & C_{12} & \cdots & C_{1N} \\ C_{21} & C_{22} & & \\ \vdots & & \ddots & \\ C_{N1} & & & C_{NN} \end{bmatrix}$$

- where C_{NN} is the total capacitance seen by line N , which consists of conductor N 's capacitance to ground plus all the mutual capacitance to other lines and C_{NM} = mutual capacitance between conductors N and M .

Inductance and Capacitance Matrix

- Capacitance Matrix

- Example 3.1 Two-Conductor TX Line Matrices


- The capacitance matrix is

$$\text{capacitance matrix} = \begin{bmatrix} C_{11} & C_{12} \\ C_{21} & C_{22} \end{bmatrix}$$

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} C_{11} & C_{12} \\ C_{21} & C_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- where $C_{11} = C_{1g} + C_m$ $C_{12} = C_{21} = -C_m$
- The inductance matrix is
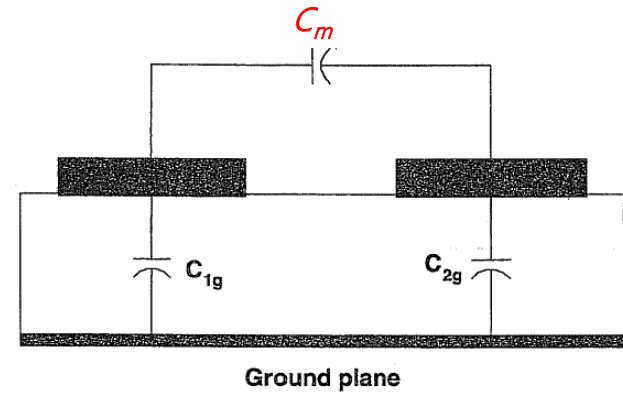
$$\text{inductance matrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{21} & L_{22} \end{bmatrix}$$



C_{11} is obtained by setting $V_2=0$, i.e. V_2 grounded

Field Simulators

- Categories

- Electrostatic (2D)

- *Advantage:*

- very easy to use and typically take a very short amount of time to complete the calculations.

- *Disadvantages:*

- simulate only relatively simple geometries.
 - They are based on static calculations of the electric field, and they usually do not calculate frequency-dependent effects such as internal inductance or skin effect resistance.
 - However, there are alternative methods of calculating effects such as frequency-dependent resistance and inductance.

Field Simulators

- Categories

- Full-Wave (3D)

- *Advantage:*

- They will simulate **complex three-dimensional geometries**, and they will predict **frequency-dependent** losses, internal inductance, dispersion, and most other electromagnetic phenomena, including radiation.

- *Disadvantages:*

- They are very **difficult to use**, and simulations typically **take hours or days** rather than seconds.
 - Additionally, the output is often in the form of ***S* parameters**, which are **not very useful** for interconnect simulations for digital applications.

Crosstalk-Induced Noise

- Categories

- Near-End Crosstalk (Backward Crosstalk)


- The near-end current could be expressed as the **summation** of the inductance-induced and capacitance-induced currents

$$I_{\text{near}} = I(L_m) + I_{\text{near}}(C_m)$$

- Far-End Crosstalk (Forward Crosstalk)




- The far-end current could be expressed as the **difference** of the inductance-induced and capacitance-induced currents
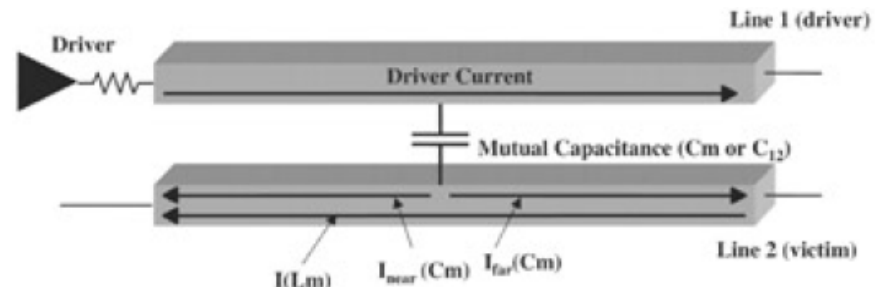
$$I_{\text{far}} = I_{\text{far}}(C_m) - I(L_m)$$



Crosstalk-Induced Noise

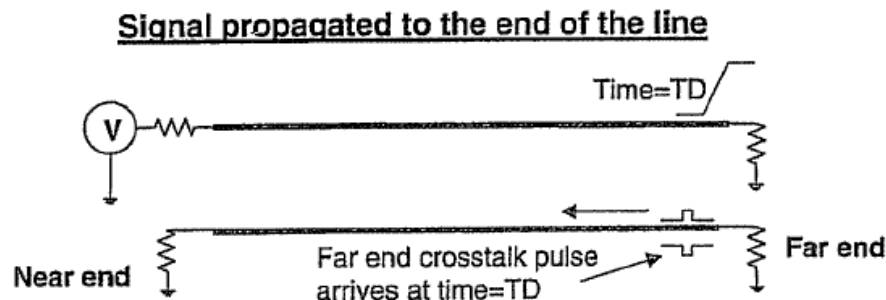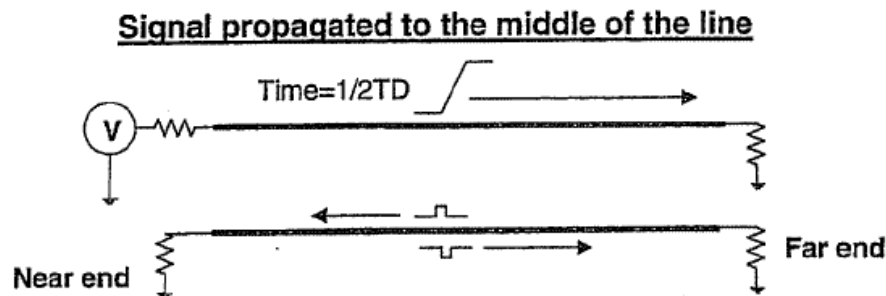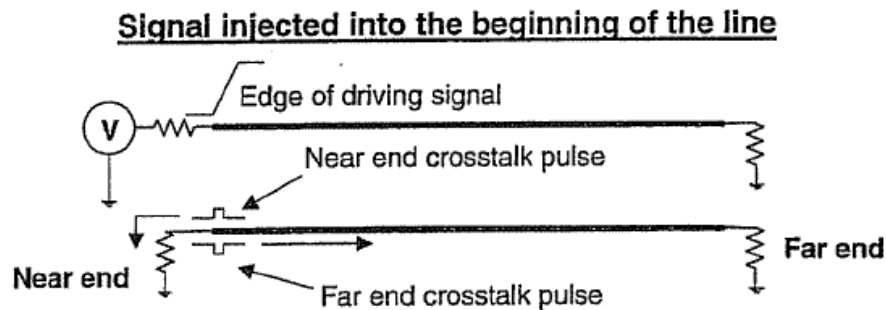- Graphical Representation
 - Near-End and Far-End Crosstalk













- The near-end crosstalk will begin at time $t=0$ and have a duration of $2TD$, or twice the electrical length of the line.
- Furthermore, the far-end crosstalk will occur at time $t=TD$ and have a duration approximately equal to the signal rise or fall time.
- The magnitude and shape of the crosstalk noise depend heavily on the amount of coupling and the termination.

Crosstalk-Induced Noise

- Matched Terminations
 - When $T_r < 2TD$

where X is the line length and L and C are the self-inductance and capacitance of the transmission line per unit length.

$$TD = X\sqrt{LC}$$

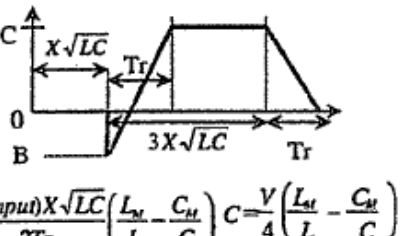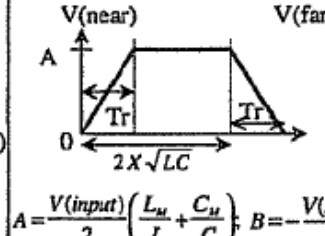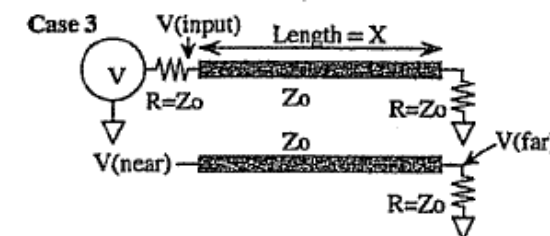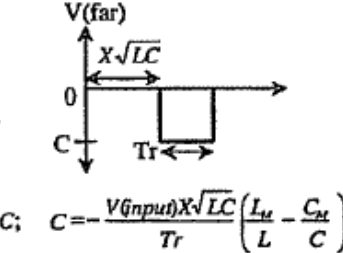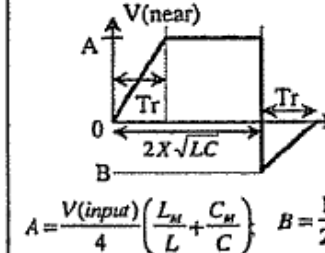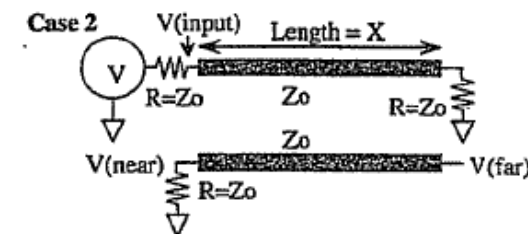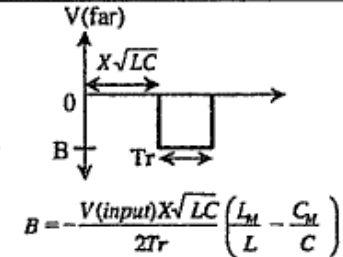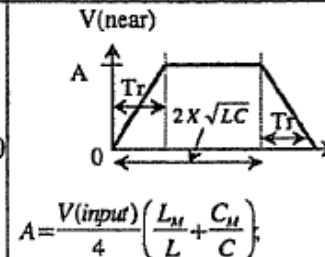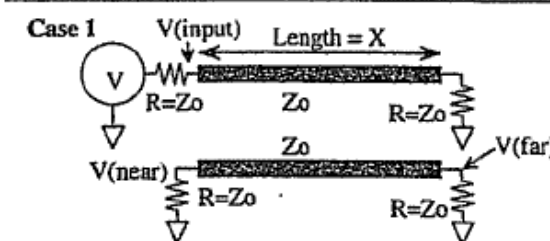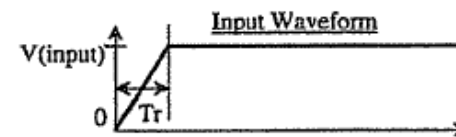

Crosstalk-Induced Noise

- Matched Terminations

- When $T_r < 2TD$ (Conti)

- The near-end magnitude is independent of length for the long-line case, while the far end always depends on rise time and length.

- When $T_r > 2TD$

- The near-end crosstalk will fail to achieve its maximum amplitude. To calculate the correct crosstalk voltages, simply multiply the near-end crosstalk by $2TD/T_r$.
 - The far-end crosstalk equations do not need to be adjusted.

Crosstalk-Induced Noise

- Mismatched Terminations

- Only Victim Line Mismatched

- Assume that the termination R in the victim line is not equal to the characteristic impedance of the victim transmission line, in this case the near- and far-end reflections must be added to the respective crosstalk voltages.

$$V_x = V_{\text{crosstalk}} \left(1 + \frac{R - Z_0}{R + Z_0} \right)$$

- where V_x is the crosstalk at the near or far end of the victim line adjusted for a nonperfect termination, R the impedance of the termination, Z_0 the characteristic impedance of the transmission line, and $V_{\text{crosstalk}}$ the value of perfect match.

Crosstalk-Induced Noise

- Conclusion

- For the Near-End Noise

- If the rise or fall time is short compared to the delay of the line, the near-end crosstalk noise is independent of the rise time.
 - If the rise or fall time is long compared to the delay of the line, the near-end crosstalk noise is dependent on the rise time.

- For the Far-End Noise


- The-far end crosstalk is always dependent on the rise or fall time.

Crosstalk-Induced Noise

- Examples

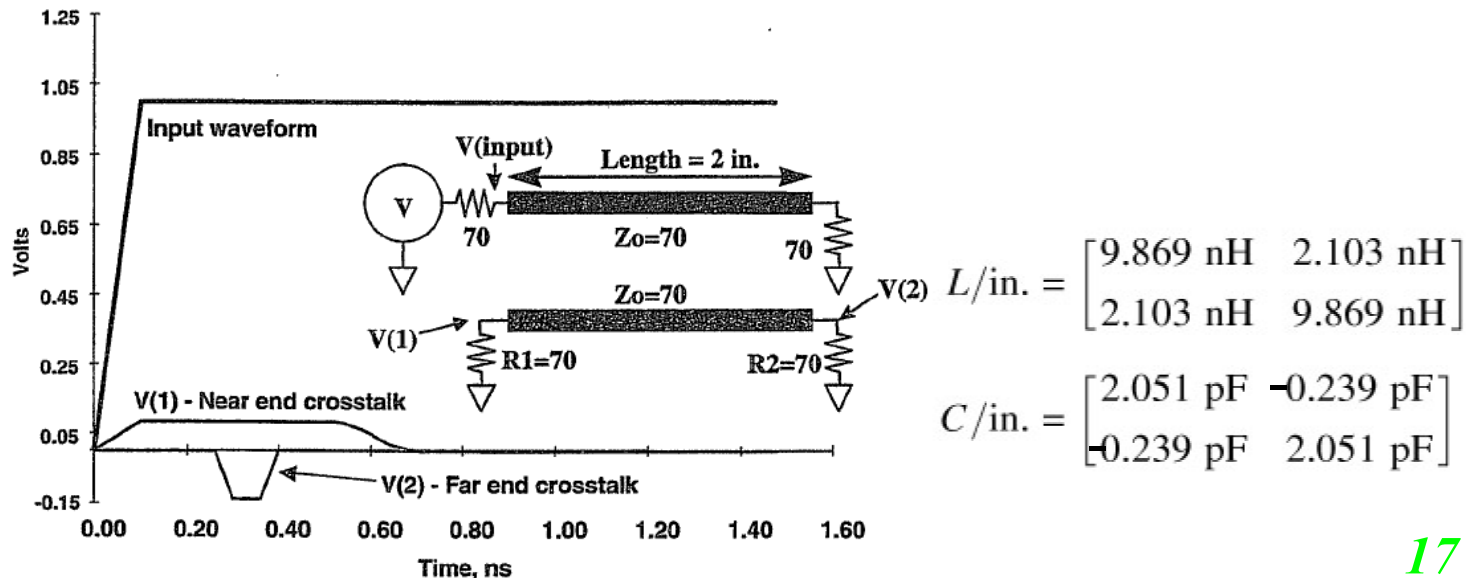- Example 3.2 Matched Terminations

- Assume $Z_0 \approx 70 \Omega$, the termination resistors = 70Ω , $V(\text{input}) = 1.0 \text{ V}$, $T_r = 100 \text{ ps}$, and $X = 2 \text{ in}$. Determine the near- and far-end crosstalk magnitudes assuming the following capacitance and inductance matrices:



Crosstalk-Induced Noise

- Examples

- Example 3.2 Matched Terminations (Conti)

- Using the equations described in case 1, we obtain


- For the near-end crosstalk:

$$V(1) = \frac{V(input)}{4} \left[\frac{L_M}{L} + \frac{C_M}{C} \right] = \frac{1}{4} \left(\frac{2.103 \text{ nH}}{9.869 \text{ nH}} + \frac{0.239 \text{ pF}}{2.051 \text{ pF}} \right) = 0.082 \text{ V}$$

- For the far-end crosstalk:

$$V(2) = -\frac{V(input)X\sqrt{LC}}{2T_r} \left[\frac{L_M}{L} - \frac{C_M}{C} \right]$$
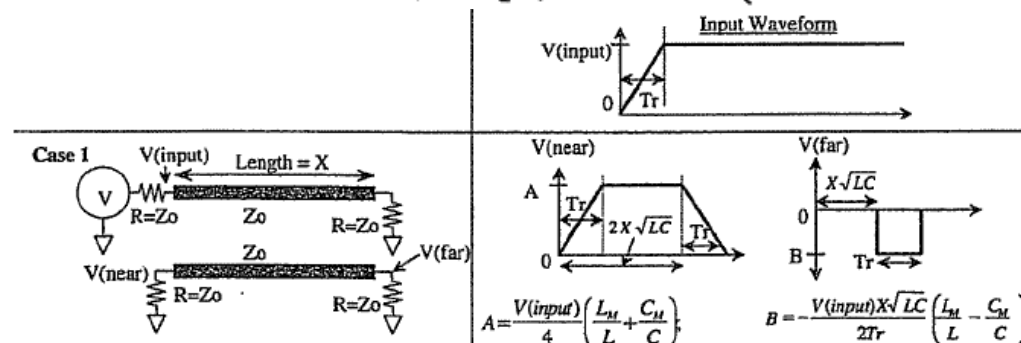
$$= \frac{1[2\sqrt{(9.869 \text{ nH})(2.051 \text{ pF})}]}{2(100 \text{ ps})} \left(\frac{2.103 \text{ nH}}{9.869 \text{ nH}} - \frac{0.239 \text{ pF}}{2.051 \text{ pF}} \right) = -0.137 \text{ V}$$



Crosstalk-Induced Noise

- Examples

- Example 3.3 Mismatched Victim Terminations

- If $R_1 = 45$ and $R_2 = 100 \Omega$, what are the **respective near- and far-end crosstalk voltages?**

- *Solution:*

$$Z_o = \sqrt{\frac{L_{11}}{C_{11}}} = \sqrt{\frac{9.869 \text{ nH}}{2.051 \text{ pF}}} = 69.4 \Omega$$

$$V(1) = V_{\text{crosstalk}} \left(1 + \frac{R - Z_o}{R + Z_o} \right) = 0.082 \left(1 + \frac{45 - 69.4}{45 + 69.4} \right) = 0.0645 \text{ V}$$

$$V(2) = V_{\text{crosstalk}} \left(1 + \frac{R - Z_o}{R + Z_o} \right) = -0.137 \left(1 + \frac{100 - 69.4}{100 + 69.4} \right) = -0.162 \text{ V}$$


Note: Near-end noise is modified by the reflection coefficient at the near end and far-end noise is modified by the reflection coefficient at the far end.

Simulating Crosstalk Using Equivalent Circuit Models

- Equivalent Circuit Model

- A Pair of Coupled Lines

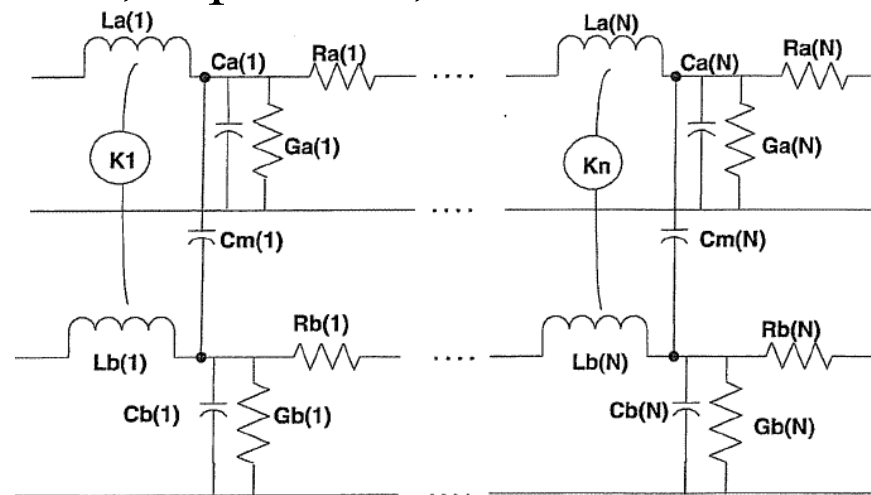- An N -segment equivalent circuit model of a pair of coupled lines as modeled in SPICE is depicted below, where N is the number of sections required such that the model will behave as a continuous transmission line and not as a series of lumped inductors, capacitors, and resistors.



Simulating Crosstalk Using Equivalent Circuit Models

- Equivalent Circuit Model

- A Pair of Coupled Lines

- The mutual inductance could be modeled as a coupling factor K :

$$K = \frac{L_{12}}{\sqrt{L_{11}L_{22}}}$$

- where L_{12} is the mutual inductance between lines 1 and 2, and L_{11} and L_{22} are the self-inductances of lines 1 and 2, respectively.

- Example 3.4 Creating a Coupled Line Model

- Assume that a pair of coupled transmission lines is 5 in. long and a digital signal with a rise time of 100 ps is to be simulated.

Capacitance matrix (per unit inch) = $\begin{bmatrix} 2 \text{ pF} & -0.1 \text{ pF} \\ -0.1 \text{ pF} & 2 \text{ pF} \end{bmatrix}$

Inductance matrix (per unit inch) = $\begin{bmatrix} 9 \text{ nH} & 0.7 \text{ nH} \\ 0.7 \text{ nH} & 9 \text{ nH} \end{bmatrix}$

Simulating Crosstalk Using Equivalent Circuit Models

- Equivalent Circuit Model

- Example 3.4 Creating a Coupled Line Model

- Calculate the characteristic impedance, the total propagation delay, the inductive coupling factor, the number of required segments, **the maximum delay per segment**, and the maximum L , R , C , G , C_m , and K values **for one segment**.

- *Solution:*

- **Characteristic impedance:** $Z_o = \sqrt{\frac{L_{11}}{C_{11}}} = \sqrt{\frac{9 \text{ nH}}{2 \text{ pF}}} = 67.09$

- **Total propagation delay:**

$$\text{TD} = \sqrt{L_{11}C_{11}} = \sqrt{(9 \text{ nH})(2 \text{ pF})} = 134 \text{ ps/in.} \rightarrow \text{5 in.} = 670 \text{ ps}$$

- **Inductive coupling factor:** $K = \frac{L_{12}}{\sqrt{L_{11}L_{22}}} = \frac{0.7 \text{ nH}}{9 \text{ nH}} = 0.078$

Simulating Crosstalk Using Equivalent Circuit Models


- Equivalent Circuit Model

- Example 3.4 Creating a Coupled Line Model

- Minimum number of segments:

$$N = \text{segments} = 10 \frac{X}{vT_r} = 10 \frac{(5 \text{ in.})(134 \text{ ps/in.})}{100 \text{ ps}} = 67$$

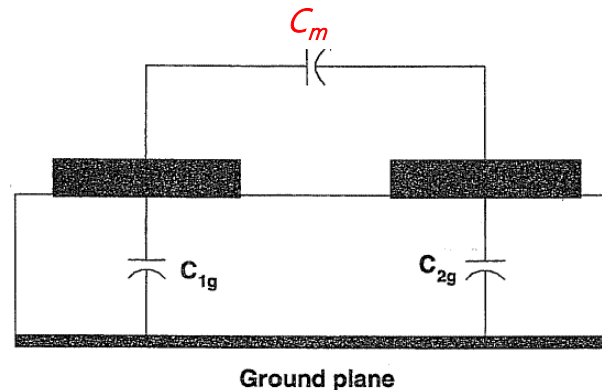- To calculate the inductance and capacitance per segment, the L , C , and C_m values must be multiplied by **5/67 (in./segment)**. Subsequently, $L(N) = 0.67 \text{ nH}$, $C_{1g}(N) = C_{11}(N) - C_m(N) = 0.1425 \text{ pF}$, and $C_m(N) = 0.0075 \text{ pF}$.



Crosstalk-Induced Flight Time and Signal Integrity Variations


- Effect of Switching Patterns on TX Line Performance

- Odd Mode

- Assume that $L_{11} = L_{22} = L_0$. Applying Kirchhoff's voltage law produces

$$V_1 = L_0 \frac{dI_1}{dt} + L_m \frac{dI_2}{dt}$$
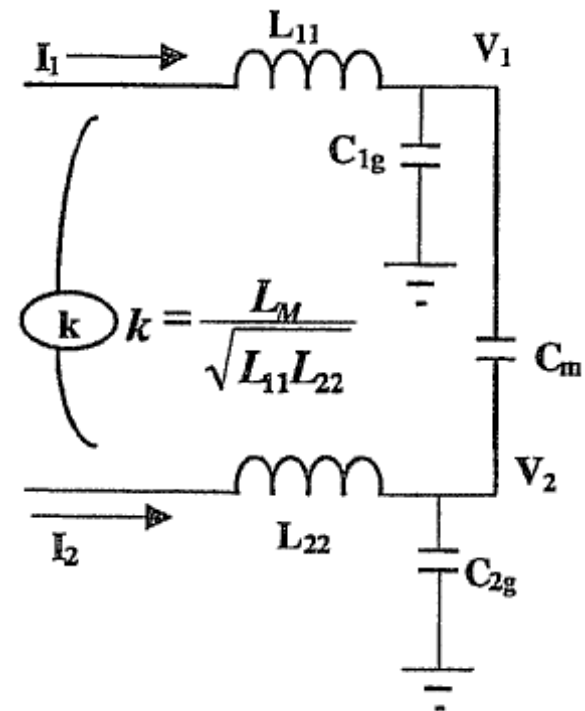
$$V_2 = L_0 \frac{dI_2}{dt} + L_m \frac{dI_1}{dt}$$



Crosstalk-Induced Flight Time and Signal Integrity Variations

- Effect of Switching Patterns on TX Line Performance

- Odd Mode

- Let $I_2 = -I_1$ and $V_2 = -V_1$, the equations become


$$V_1 = L_0 \frac{dI_1}{dt} + L_m \frac{d(-I_1)}{dt} = (L_0 - L_m) \frac{dI_1}{dt}$$

$$V_2 = L_0 \frac{dI_2}{dt} + L_m \frac{d(-I_2)}{dt} = (L_0 - L_m) \frac{dI_2}{dt}$$

- Therefore, the equivalent inductance **seen by line 1 propagating in odd mode** is

$$L_{\text{odd}} = L_{11} - L_m = L_{11} - L_{12}$$


The odd mode inductance is reduced.

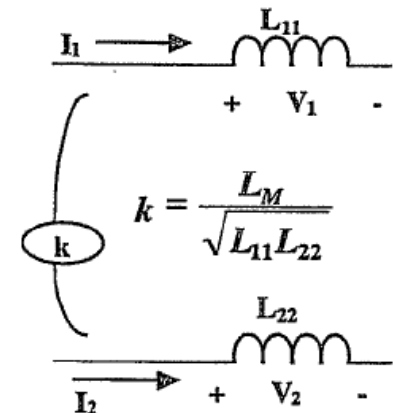

Crosstalk-Induced Flight Time and Signal Integrity Variations

• Effect of Switching Patterns on TX Line Performance

– Odd Mode

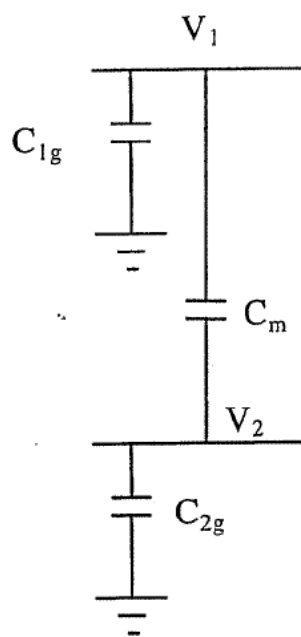

- Applying **Kirchhoff's current law** at nodes V_1 and V_2 yields (assume that $C_{1g}=C_{2g}=C_0$)

$$I_1 = C_0 \frac{dV_1}{dt} + C_m \frac{d(V_1 - V_2)}{dt} = (C_0 + C_m) \frac{dV_1}{dt} - C_m \frac{dV_2}{dt}$$

$$I_2 = C_0 \frac{dV_2}{dt} + C_m \frac{d(V_2 - V_1)}{dt} = (C_0 + C_m) \frac{dV_2}{dt} - C_m \frac{dV_1}{dt}$$

- Let $I_2 = -I_1$ and $V_2 = -V_1$ for odd-mode propagation yields

$$I_1 = C_0 \frac{dV_1}{dt} + C_m \frac{d(V_1 - (-V_1))}{dt} = (C_{1g} + 2C_m) \frac{dV_1}{dt}$$

$$I_2 = C_0 \frac{dV_2}{dt} + C_m \frac{d(V_2 - (-V_2))}{dt} = (C_{2g} + 2C_m) \frac{dV_2}{dt}$$

- Therefore, the equivalent capacitance **seen by trace 1 propagating in odd mode** is

$$C_{\text{odd}} = C_{1g} + 2C_m = C_{11} + C_m$$

The odd mode capacitance is increased.

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Effect of Switching Patterns on TX Line Performance

- Odd Mode

- Subsequently, the equivalent impedance and delay for a coupled pair of transmission lines propagating in an odd-mode pattern are

$$Z_{\text{odd}} = \sqrt{\frac{L_{\text{odd}}}{C_{\text{odd}}}} = \sqrt{\frac{L_{11} - L_{12}}{C_{11} + C_m}} \quad \downarrow$$
$$TD_{\text{odd}} = \sqrt{L_{\text{odd}} C_{\text{odd}}} = \sqrt{(L_{11} - L_{12})(C_{11} + C_m)}$$

- You could see that the odd mode characteristic impedance is reduced but the time delay is not obvious.

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Effect of Switching Patterns on TX Line Performance

- Even Mode

- For even-mode propagation, $I_1 = I_2$ and $V_1 = V_2$.

Thus, the coupled line equations become

$$\begin{aligned} V_1 &= L_0 \frac{dI_1}{dt} + L_m \frac{dI_2}{dt} \\ V_2 &= L_0 \frac{dI_2}{dt} + L_m \frac{dI_1}{dt} \end{aligned} \quad \rightarrow \quad \begin{cases} V_1 = L_0 \frac{dI_1}{dt} + L_m \frac{d(I_1)}{dt} = (L_0 + L_m) \frac{dI_1}{dt} \\ V_2 = L_0 \frac{dI_2}{dt} + L_m \frac{d(I_2)}{dt} = (L_0 + L_m) \frac{dI_2}{dt} \end{cases}$$

- Therefore, the equivalent inductance **seen by line 1 propagating in even mode** is

$$L_{\text{even}} = L_{11} + L_m$$

The even mode inductance is increased.

- Similarly, we have

$$\begin{aligned} I_1 &= C_0 \frac{dV_1}{dt} + C_m \frac{d(V_1 - V_2)}{dt} \\ I_2 &= C_0 \frac{dV_2}{dt} + C_m \frac{d(V_2 - V_1)}{dt} \end{aligned} \quad \rightarrow \quad \begin{cases} I_1 = C_0 \frac{dV_1}{dt} + C_m \frac{d(V_1 - V_1)}{dt} = (C_0) \frac{dV_1}{dt} \\ I_2 = C_0 \frac{dV_2}{dt} + C_m \frac{d(V_2 - V_2)}{dt} = (C_0) \frac{dV_2}{dt} \end{cases}$$

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Effect of Switching Patterns on TX Line Performance

- Even Mode

- Therefore, the equivalent capacitance **seen by trace 1 propagating in even mode** is

$$C_{\text{even}} = C_0 = C_{11} - C_m$$

The even mode capacitance is reduced.

- Subsequently, the **even-mode characteristic impedance and time delay** are


$$Z_{\text{even}} = \sqrt{\frac{L_{\text{even}}}{C_{\text{even}}}} = \sqrt{\frac{L_{11} + L_{12}}{C_{11} - C_m}} \quad \uparrow$$

$$TD_{\text{even}} = \sqrt{L_{\text{even}} C_{\text{even}}} = \sqrt{(L_{11} + L_{12})(C_{11} - C_m)}$$

- You could see that the **even mode impedance is increased** but the time delay is not obvious.


Crosstalk-Induced Flight Time and Signal Integrity Variations

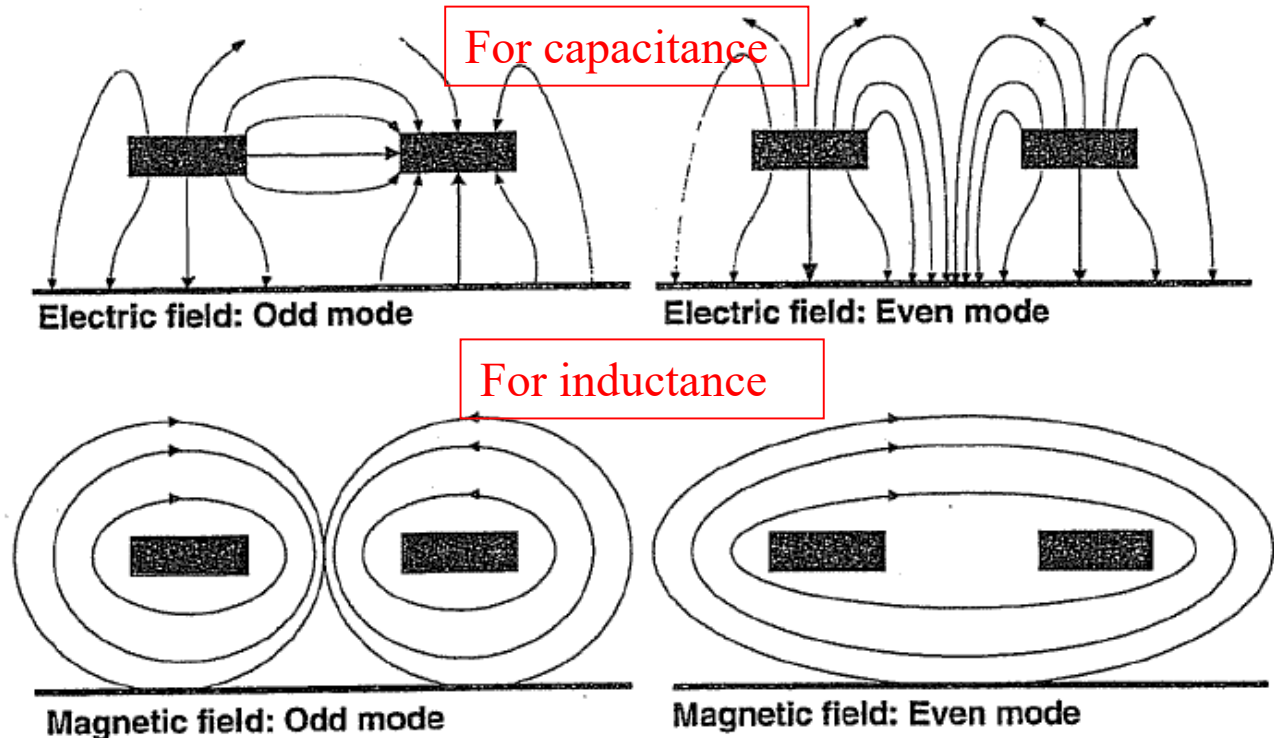- Effect of Switching Patterns on TX Line Performance
 - Field Patterns of Odd and Even Modes
 - Please think about the **variations of inductance and capacitance** using this figure.



Crosstalk-Induced Flight Time and Signal Integrity Variations

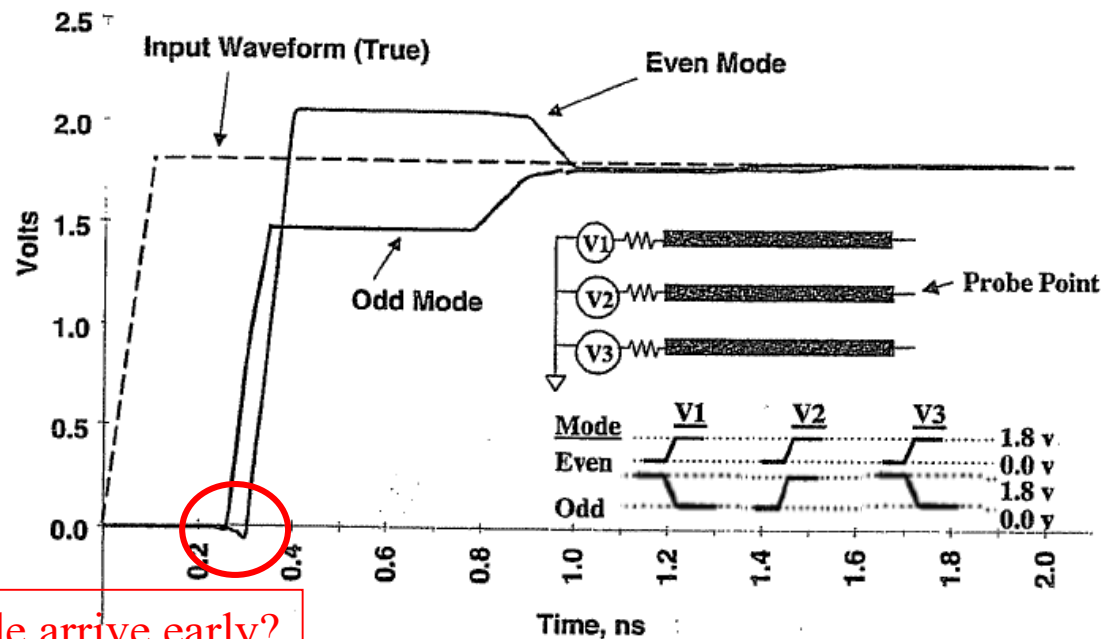- Effect of Switching Patterns on TX Line Performance
 - Effects of Switching Patterns
 - Odd Mode: $Z_S = Z_0 > Z_{odd}$, underdriven
 - Even Mode: $Z_S = Z_0 < Z_{even}$, overdriven



Why does odd-mode arrive early?

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Effect of Switching Patterns on TX Line Performance

- Conclusions


- Odd-mode impedance will always be lower than the single-line case.
- Even-mode impedance will always be higher than the single-line case.
- The signal pattern influence on the time delay for odd- and even-mode are not obvious.
- Crosstalk will induce velocity variations in a microstrip.
- However, crosstalk will not induce velocity variations in a stripline.

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Simulating Traces in a Multiconductor System Using a Single-Line Equivalent Circuit
 - All Signals in Phase
 - Let the target be line 2, the equivalent impedance and time delay per unit length **seen by line 2** can be calculated as

$$Z_{2,\text{eff}} = \sqrt{\frac{L_{22} + L_{12} + L_{23}}{C_{22} - C_{12} - C_{23}}}$$
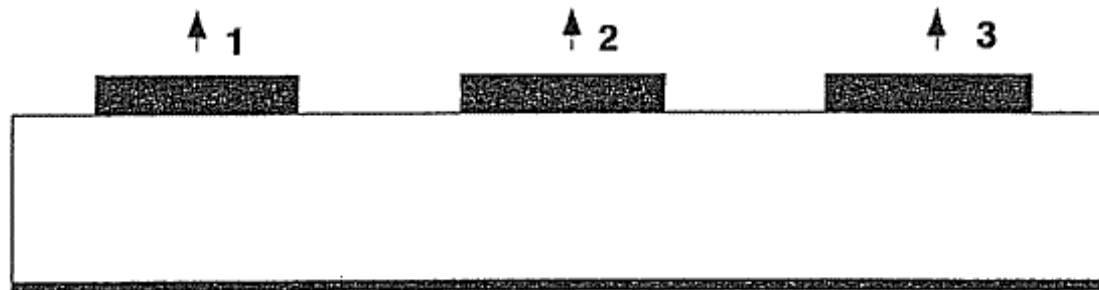
$$\text{TD}_{2,\text{eff}} = \sqrt{(L_{22} + L_{12} + L_{23})(C_{22} - C_{12} - C_{23})}$$




Ground plane

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Simulating Traces in a Multiconductor System Using a Single-Line Equivalent Circuit

– One Signal Out of Phase with Other Signals

- For equivalent capacitance of line 2:

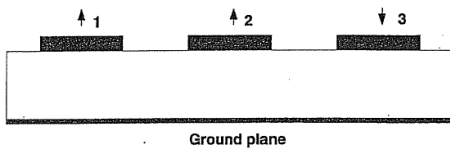

- Even-mode capacitance of conductor 2 with 1 = $C_{22} - C_{12}$
- Odd-mode capacitance of conductor 2 with 3 = $C_{22} + C_{23}$
- Equivalent capacitance of conductor 2 = $C_{22} - C_{12} + C_{23}$

- For equivalent inductance of line 2:

- Even-mode inductance of conductor 2 with 1 = $L_{22} + L_{12}$
- Odd-mode inductance of conductor 2 with 3 = $L_{22} - L_{23}$
- Equivalent inductance of conductor 2 = $L_{22} + L_{12} - L_{23}$

- The equivalent impedance and time delay are

$$Z_{2,\text{eff}} = \sqrt{\frac{L_{22} + L_{12} - L_{23}}{C_{22} - C_{12} + C_{23}}} \quad \text{TD}_{2,\text{eff}} = \sqrt{(L_{22} + L_{12} - L_{23})(C_{22} - C_{12} + C_{23})} \quad 34$$

Crosstalk-Induced Flight Time and Signal Integrity Variations

- Simulating Traces in a Multiconductor System Using a Single-Line Equivalent Circuit

– Conclusion

- When estimating the effect of crosstalk in a system, **the nearest neighbors** have **the greatest effect**. The effects of the other lines fall off exponentially.
- The SLEM method **should be used early** in the design stage to quickly get a handle on the effect of crosstalk. **Fully coupled simulations** should always be performed on the final design.
- **Common mode (all bits in phase)** and **differential mode (target bit out of phase)** will produce the **worst-case** impedance and velocity variations.
- **The accuracy** of a three-line SLEM model falls off when the **edge-to-edge spacing/height** (above the ground plane) ratio is **less than 1**.


Crosstalk Trends

- Different Perspectives
 - From Impedance

Better
electromagnetic
field confining

- Lower-impedance lines are usually achieved either by widening the trace width or using a thinner dielectric. Thus, Lower-impedance traces will tend to exhibit less crosstalk-induced impedance variation than will high-impedance traces for a given dielectric constant.

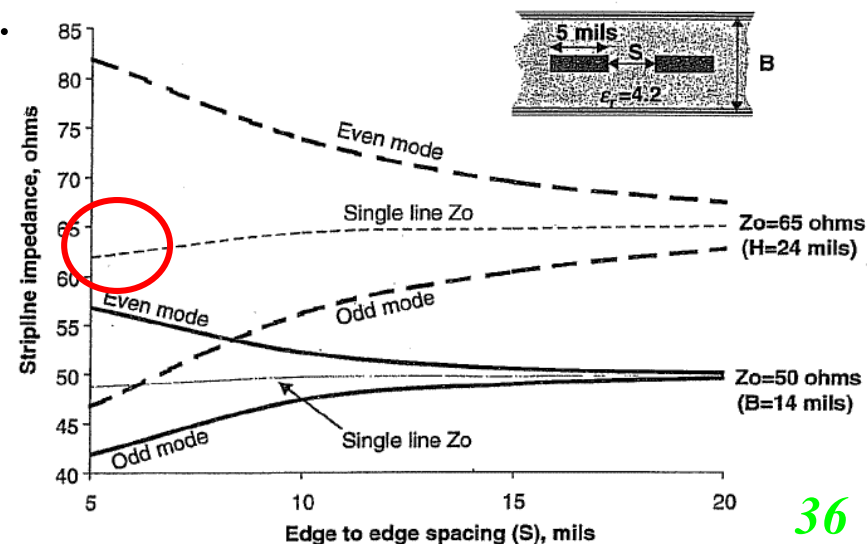For a single line Z_0 , it will start to increase the self-capacitance of the single line while the edge-to-edge spacing is small, thus, reducing the characteristic impedance, although the adjacent line is not excited.





Crosstalk Trends

- Different Perspectives

- From Mutual Inductance and Capacitance

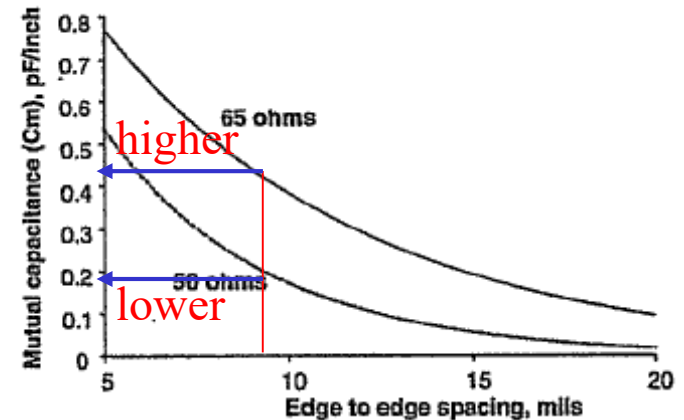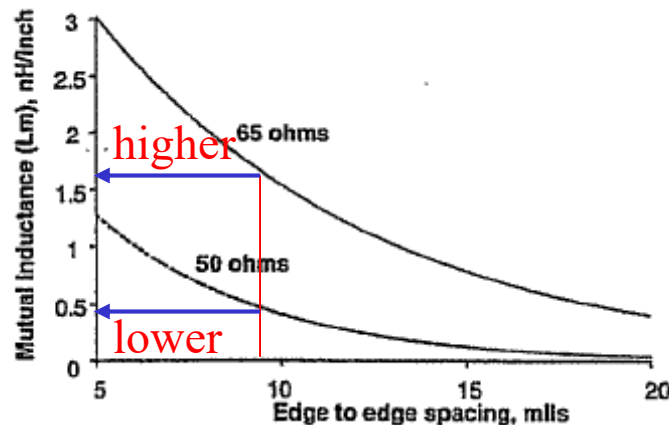- Note that the mutual **parasitics drop off exponentially** with **spacing**.
 - The mutual inductance and capacitance for lower-impedance lines **are smaller** than those for higher-impedance lines.



Crosstalk Trends

- Conclusion

- Points to Remember


- For a given dielectric constant, low-impedance line will produce less impedance variations from cross-talk.
 - The impedance of a single line on a board is influenced by the proximity of other traces even when they are not being actively driven.
 - Mutual parasitics fall off exponentially with trace-to-trace spacing.

Termination of Odd- and Even-Mode Transmission Line Pairs

- Pi-Termination Network


- Even Mode

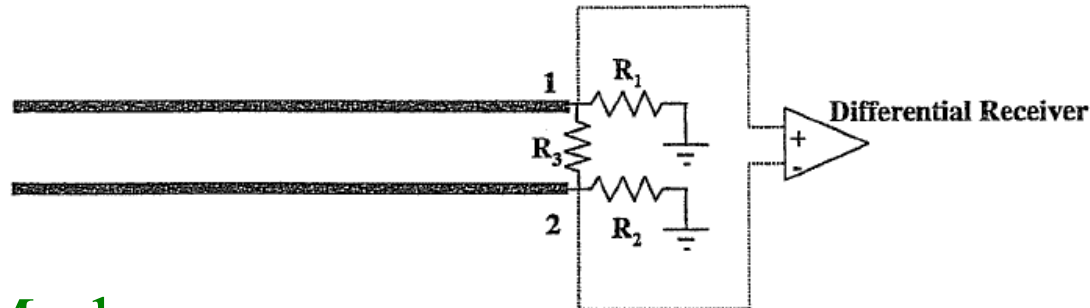- Since $V_1 = V_2 = V_e$, we obtain $R_1 = R_2 = Z_{\text{even}}$



- Odd Mode

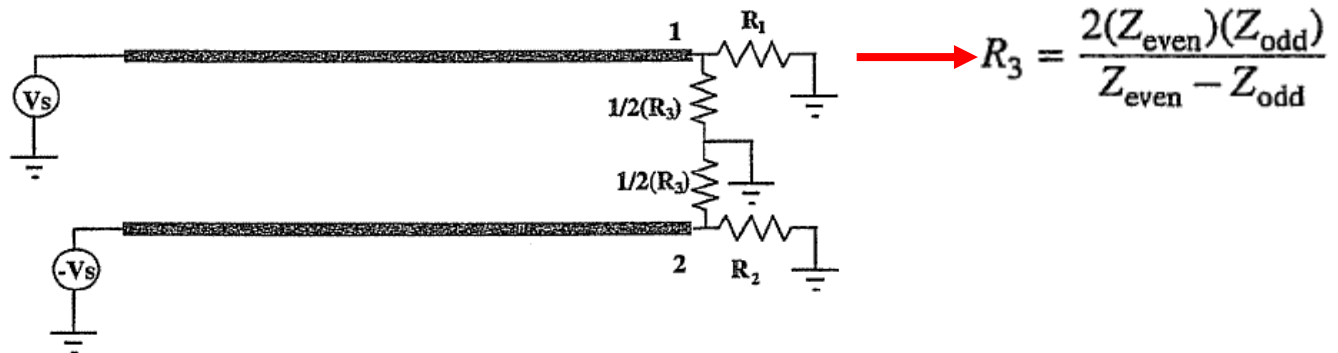- Since $V_1 = -V_2 = V_o$, we obtain $Z_{\text{odd}} = (1/2 R_3) // R_1$




Termination of Odd- and Even-Mode Transmission Line Pairs

- T-Termination Network

- Odd Mode

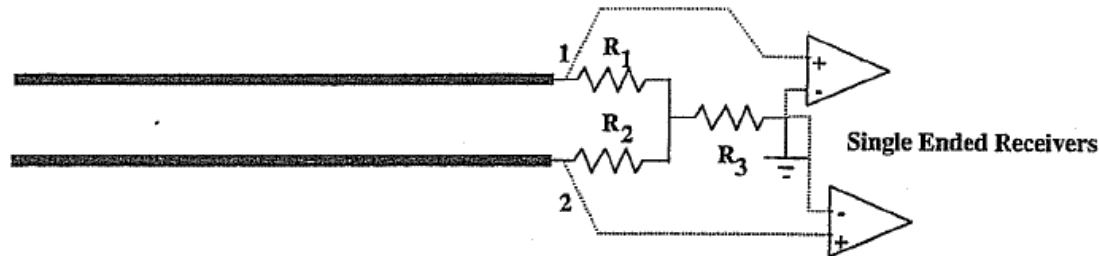
- Since $V_1 = -V_2 = V_0$, we obtain $R_1 = R_2 = Z_{\text{odd}}$



- Even Mode

- Since $V_1 = V_2 = V_e$, we obtain $Z_{\text{even}} = R_1 + 2R_3$
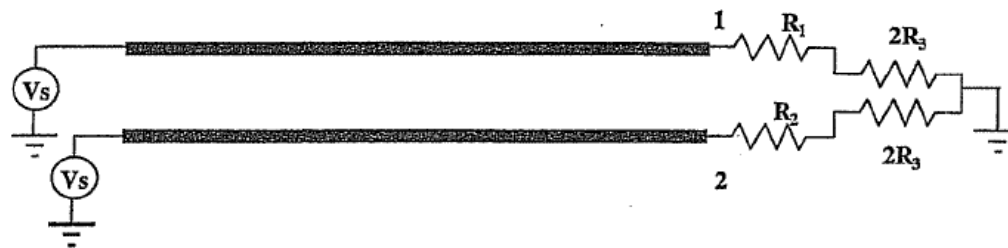
$$\longrightarrow R_3 = \frac{1}{2}(Z_{\text{even}} - Z_{\text{odd}})$$



Minimization of Crosstalk

- Rule of Thumb

- 1. **Widen the spacing S** between the lines as much as routing restrictions will allow.
- 2. Design the transmission line so that **the conductor is as close to the ground plane** as possible (i.e., **minimize H**) while achieving the target impedance of the design. This will couple the transmission line **tightly to** the ground plane and less to adjacent signals.
- 3. **Use differential routing techniques for critical nets**, such as the system clock if system design allows.



Minimization of Crosstalk


- Rule of Thumb (Conti)

- 4. If there is significant coupling between signals on different layers (such as layers $M3$ and $M4$), route them orthogonal to each other.
- 5. If possible, route the signals on a stripline layer or as an embedded microstrip to eliminate velocity variations.
- 6. Minimize parallel run lengths between signals. Route with short parallel sections and minimize long coupled sections between nets.
- 7. Place the components on the board to minimize congestion of traces.
- 8. Use slower edge rates. This, however, should be done with extreme caution. There are several negative consequences associated with using slow edge rates.

Additional Examples

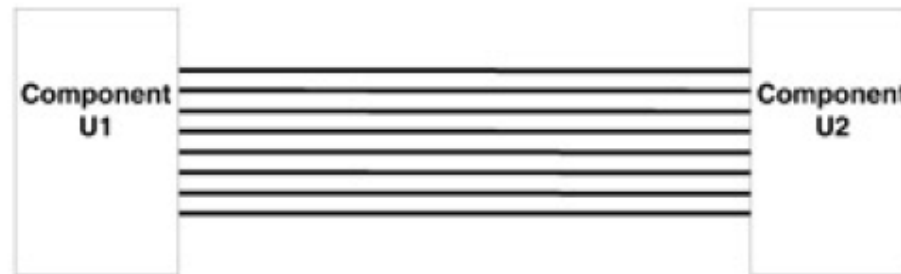- Problem


- Assume that two components, U_1 and U_2 , need to communicate with each other via an 8-bitwide high-speed digital bus.



- The components are mounted on a standard four-layer motherboard with the stackup shown below. The driving buffers on component U_1 have an impedance of $30\ \Omega$ and a swing of 0 to 2 V.

Additional Examples

- Problem

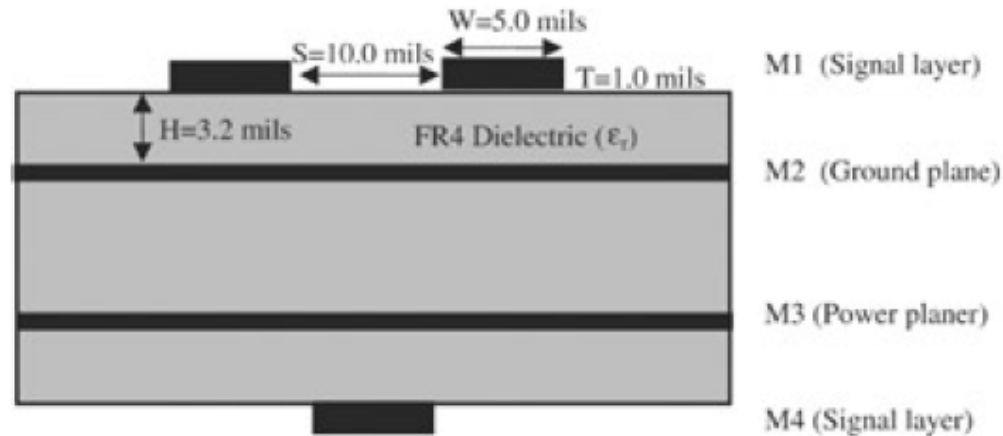

- The traces on the printed circuit board (PCB) are required to be **5 in. long** with center-to-center spacing of 15 mils and **impedance 50Ω** (ignoring crosstalk).
- The **relative dielectric constant** of the board (ϵ_r) is 4.0.

Additional Examples

- Problem

- The transmission line parasitics are
 - mutual inductance = 0.54 nH/in.
 - mutual capacitance = 0.079 pF/in.
 - self-inductance = 7.13 nH/in. (from the Chapter 2, additional example)
 - self-capacitance = 2.85 pF/in. (from the Chapter 2, additional example)

- Goals


- 1. Determine the maximum impedance variation.
- 2. Determine the maximum velocity difference.
- 3. Assuming that the input buffers at component U_2 will switch at 1.0 V, determine if the buffer will false trigger due to crosstalk effects.

Additional Examples

- Determining the Maximum Crosstalk-Induced Impedance and Velocity Swing

- The patterns that produce the **worst-case crosstalk** effects will always be **either common mode or differential mode**.

- Common-Mode Propagation

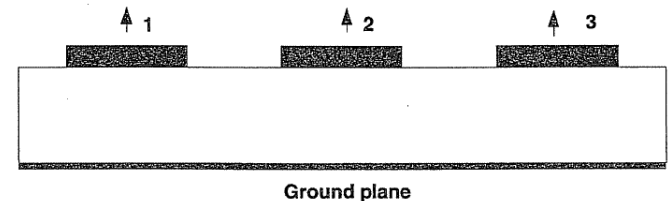

- For calculation of equivalent capacitance:
 - Even-mode capacitance of conductors 2 and 1 = $C_{22} - C_{12}$
 - Even-mode capacitance of conductors 2 and 3 = $C_{22} - C_{23}$
 - Equivalent capacitance of conductor 2 = $C_{22} - C_{12} - C_{23}$
- For calculation of equivalent inductance:
 - Even-mode inductance of conductors 2 and 1 = $L_{22} + L_{12}$
 - Even-mode inductance of conductors 2 and 3 = $L_{22} + L_{23}$
 - Equivalent inductance of conductor 2 = $L_{22} + L_{12} + L_{23}$

Additional Examples

- Determining the Maximum Crosstalk-Induced Impedance and Velocity Swing
 - Common-Mode Propagation (Conti)
 - Therefore, the characteristic impedance and time delay are


$$\begin{aligned} Z_{2,\text{common}} &= \sqrt{\frac{L_{22} + L_{12} + L_{23}}{C_{22} - C_{12} - C_{23}}} \\ &= \sqrt{\frac{7.13 \text{ nH} + 0.54 \text{ nH} + 0.54 \text{ nH}}{2.85 \text{ pF} - 0.079 \text{ pF} - 0.079 \text{ pF}}} = 55.26 \Omega \end{aligned}$$

$$\begin{aligned} \text{TD}_{2,\text{common}} &= \sqrt{(L_{22} + L_{12} + L_{23})(C_{22} - C_{12} - C_{23})} \\ &= \sqrt{(7.13 \text{ nH} + 0.54 \text{ nH} + 0.54 \text{ nH})(2.85 \text{ pF} - 0.079 \text{ pF} - 0.079 \text{ pF})} \\ &= 148.6 \text{ pF/in.} \end{aligned}$$

Additional Examples

- Determining the Maximum Crosstalk-Induced Impedance and Velocity Swing

- Differential-Mode Propagation

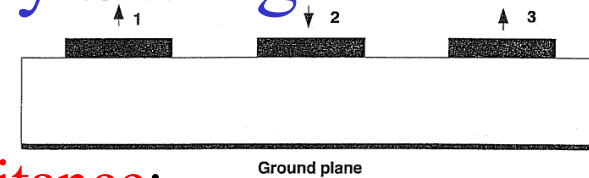

- For calculation of equivalent capacitance:

- Odd-mode capacitance of conductors 2 and 1 = $C_{22} + C_{12}$
- Odd-mode capacitance of conductors 2 and 3 = $C_{22} + C_{23}$
- Equivalent capacitance of conductor 2 = $C_{22} + C_{12} + C_{23}$

- For calculation of equivalent inductance:

- Odd-mode inductance of conductors 2 and 1 = $L_{22} - L_{12}$
- Odd-mode inductance of conductors 2 and 3 = $L_{22} - L_{23}$
- Equivalent inductance of conductor 2 = $L_{22} - L_{12} - L_{23}$

Additional Examples

- Determining the Maximum Crosstalk-Induced Impedance and Velocity Swing
 - Differential-Mode Propagation (Conti)

- Therefore, the characteristic impedance and time delay are

$$Z_{2,\text{differential}} = \sqrt{\frac{L_{22} - L_{12} - L_{23}}{C_{22} + C_{12} + C_{23}}}$$

$$= \sqrt{\frac{7.13 \text{ nH} - 0.54 \text{ nH} - 0.54 \text{ nH}}{2.85 \text{ pF} + 0.079 \text{ pF} + 0.079 \text{ pF}}} = 44.8 \Omega$$

$$\text{TD}_{2,\text{differential}}$$

$$= \sqrt{(L_{22} - L_{12} - L_{23})(C_{22} + C_{12} + C_{23})}$$

$$= \sqrt{(7.13 \text{ nH} - 0.54 \text{ nH} - 0.54 \text{ nH})(2.85 \text{ pF} + 0.079 \text{ pF} + 0.079 \text{ pF})}$$

$$= 135 \text{ ps/in.}$$


- The velocity and impedance variations due to crosstalk are as follows:

$$44.8 \Omega < Z_o < 55.26 \Omega$$

$$135 \text{ ps/in.} < \text{TD} < 148.6 \text{ ps/in.}$$

Additional Examples

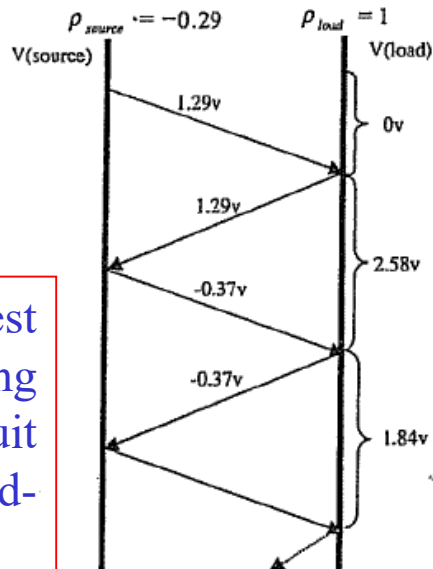- Determining if Crosstalk Will Induce False Triggers
 - Since the most ringing will occur when the driver impedance is low and the transmission line impedance is high (overdriven), *common mode propagation* is chosen.




$$V_{\text{initial}} = V_S \frac{Z_0}{R_S + Z_0} = (2) \left(\frac{55}{30 + 55} \right) = 1.29$$

$$\rho_{\text{source}} = \frac{R_S - Z_0}{R_S + Z_0} = \frac{30 - 55}{30 + 55} = -0.29$$

$$\rho_{\text{load}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\infty - 55}{\infty + 55} = 1$$

No false triggers since the voltage is greater than $V_{\text{TH}} = 1\text{V}$.

Worst case waveform at U2

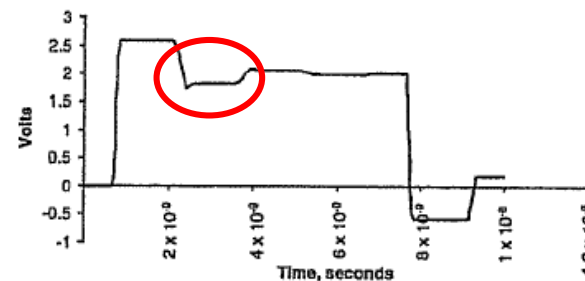

What about the lowest level of the receiving signal while the circuit is operating in odd-mode propagation?