

# Microwave Circuits and Sub-Systems

## A2M17MOS

### Wide-Band Amplifier Design

**Přemysl Hudec**  
**CTU Prague, Faculty of Electrical Engineering**

**hudecp@fel.cvut.cz**

version 2014




# Contents

- General considerations
- Analytical solutions
- Recommended LC structures
- Recommended distributed MCs
- Wide-band amplifier design
- Gain equalization
- Balanced amplifiers
- Amplifiers with resistive matching
- Feedback amplifiers
- Distributed amplifiers

# Narrow-Band Impedance Matching

- Design of narrow-band matching circuits → relatively simple
- Ideal impedance matching at 1 frequency can be reached:  $|\Gamma_{in}| \rightarrow 0$   $RL \rightarrow \infty$
- Solution exists always
- Numerous solutions exist
- Solutions can be calculated using direct design formulas
- Applicable for frequency bands  $B \leq 10\% \cdot f_0$
- The 10% frequency band comply with many communication applications
- But wider frequency bands are also required

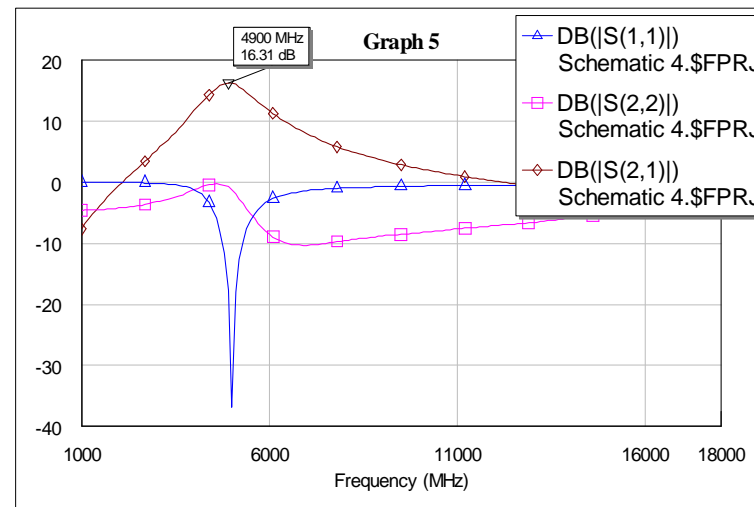

# Wide-Band Impedance Matching

- Substantially more complicated
- Ideal matching  $|\Gamma_{in}(j\omega)| \rightarrow 0$  can never be reached in the whole frequency band
- Ideal matching can be reached only at separate and distanced frequencies


- **Attainable condition:**

$$|\Gamma_{in}(j\omega)| \leq \text{const.} = |\Gamma_{\max}|$$


- In the frequency band

$$B = \Delta\omega = \omega_b - \omega_a$$


- $\Gamma_{in}$  passes through 0 at distanced frequencies
- In many cases – does not pass through 0 at all

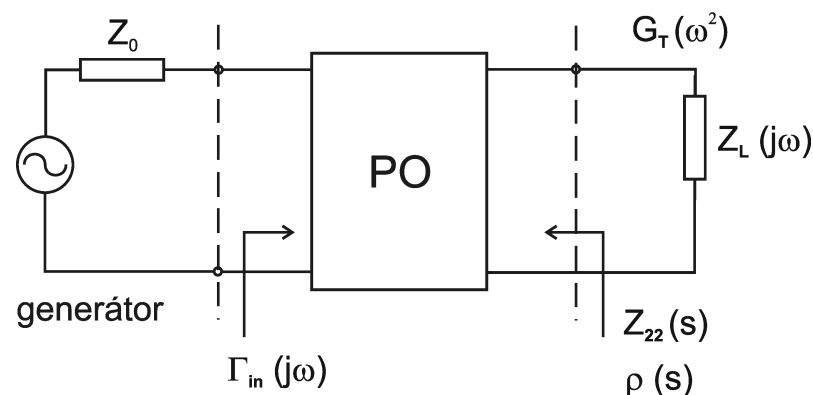

Graph 1: Amplitude of S11 [-] - frequency [GHz]


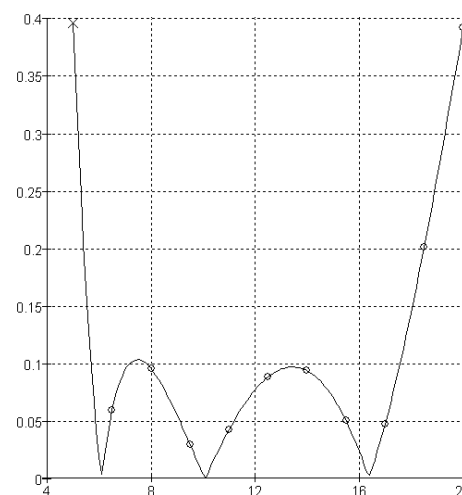


Graph 2: Polar S11 [-]

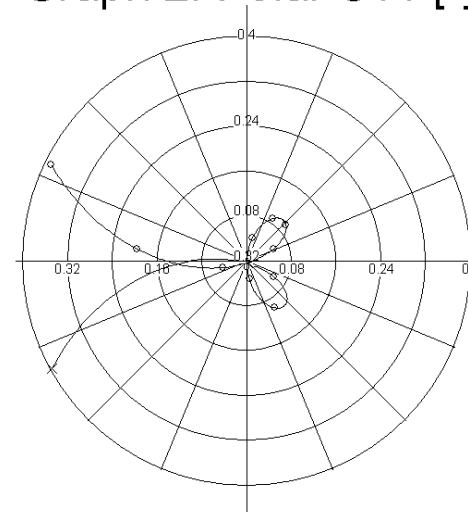

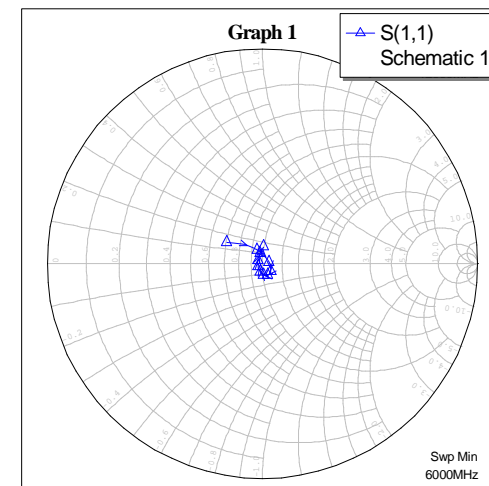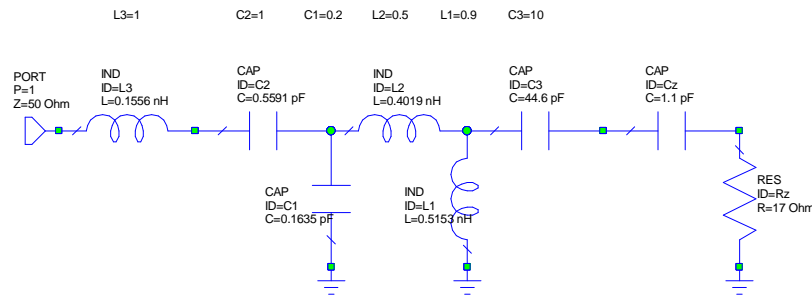
# Wide-Band Impedance Matching

- Simple and direct solutions exist only rarely
- For the given requirements → **NO solution can exist**
- Solutions are based on **approximations and iterations** nearly always
- **CAD optimization** is recommended
- Numerous different approaches exist
- **Analytical solutions** → based on analog filter design
- **Iteration solutions** → based on optimization of the recommended wideband structures



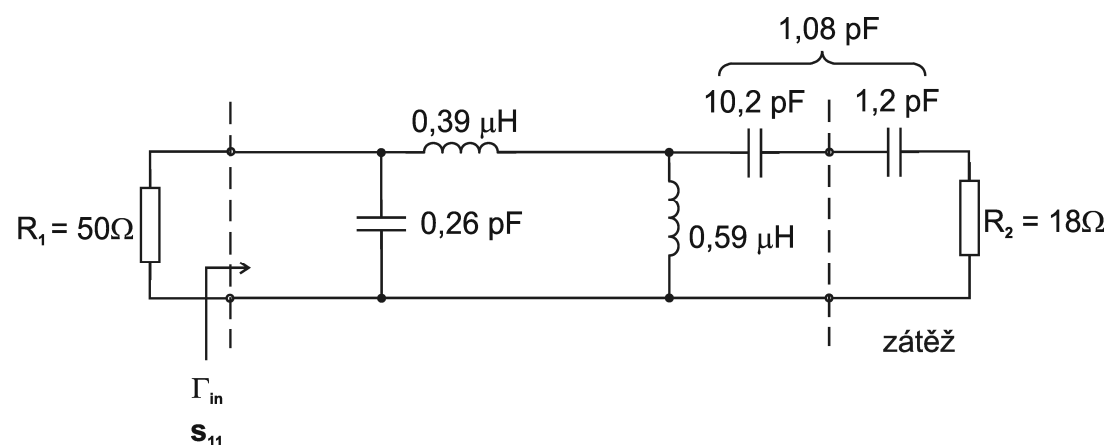
# Analytical Solutions

- Based on the **filter synthesis process**
- Filters with **different impedances at both ports** can be designed
- The filter synthesis process leads to **LC structures**
- The LC structures must be converted to structures practically realizable at microwave frequencies (real LC, microstrip lines, ...) – the conversion is never ideal (B drops by 50% usually)
- During the design process, several **approximations** must be used
- Many different approaches can be found
- Wideband MC synthesizers are available as part of the RF CAD programs usually
- More details e.g. in: „Aktivní mikrovlnné obvody“, skriptum ČVUT.



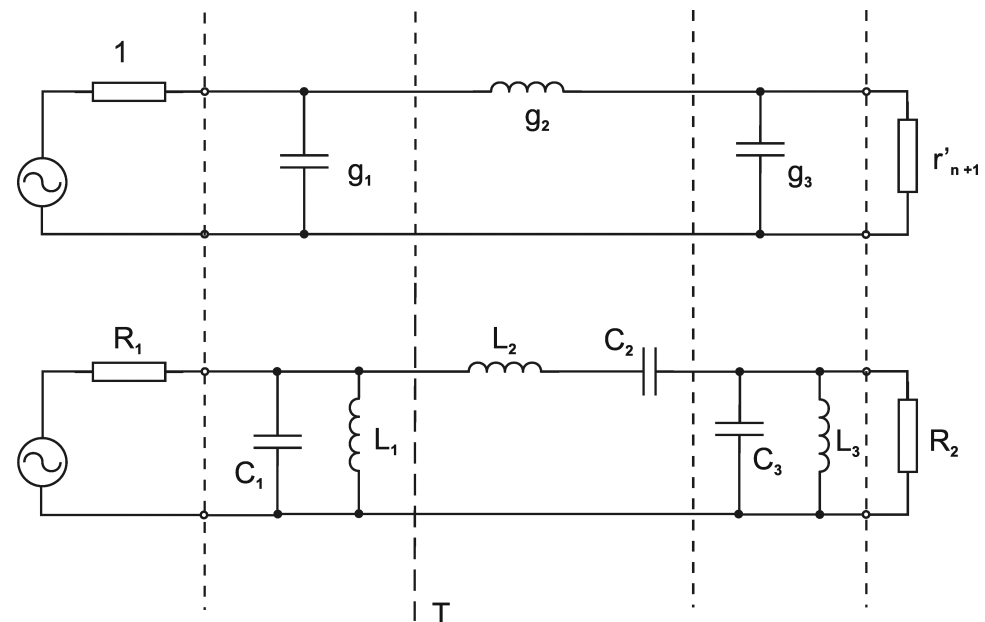
# Example of Analytical Design Method

- Wide-band MCs = filters with **maximum impedance transformation**
- One of possible solutions with very good results
- Based on standard analog filter synthesis:
  - Normalized **low-pass filter prototype** based on the required  $\Gamma_{\max}$  value
  - **Thebyshev or Butterworth transfer-function approximations**
  - Conversion of the low-pass prototype to the band-pass filter
- Example: Individual task No.5.
- The synthesized filters show different load impedances  $R_1$  and  $R_2$  at both ends
- The filter is able to perform the  $N=R_2/R_1$  **impedance transformation**



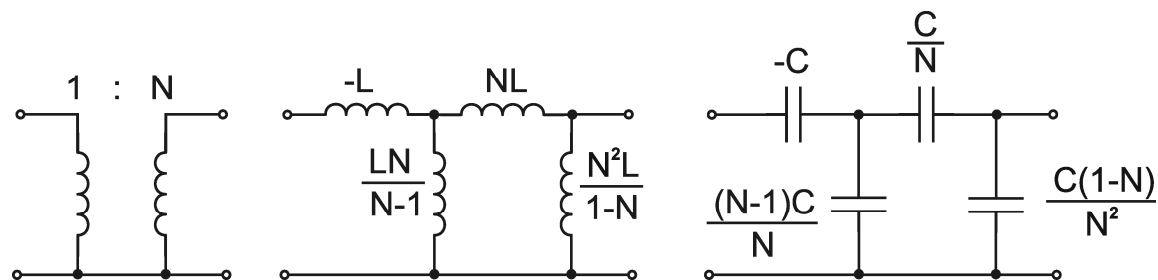
# Additional Impedance Transformation

- In order to raise the  $N=R_2/R_1$  ratio, an **additional impedance transformer** can be connected to the filter structure
- The standard transformer can be realized by equivalent L or C circuits




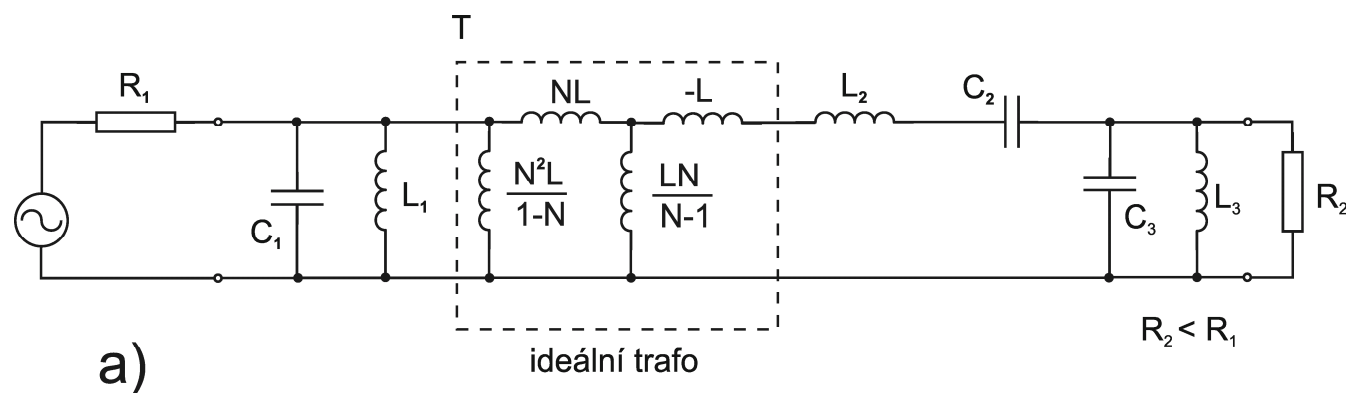
- Values of the side L, C elements are negative and can be absorbed in the filter structure







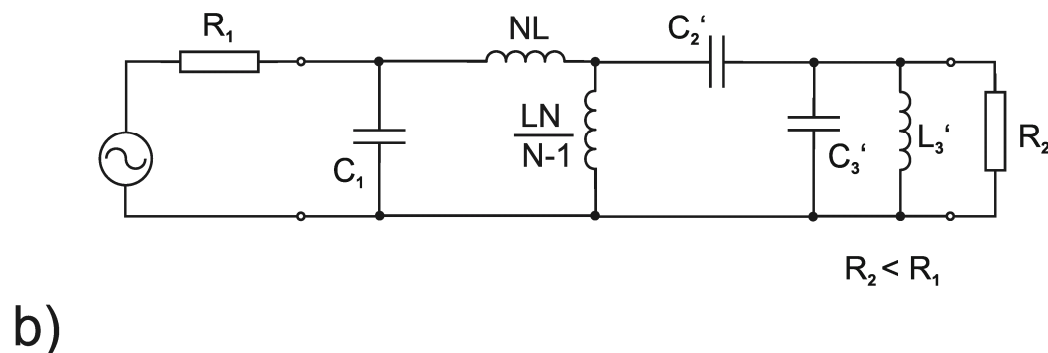
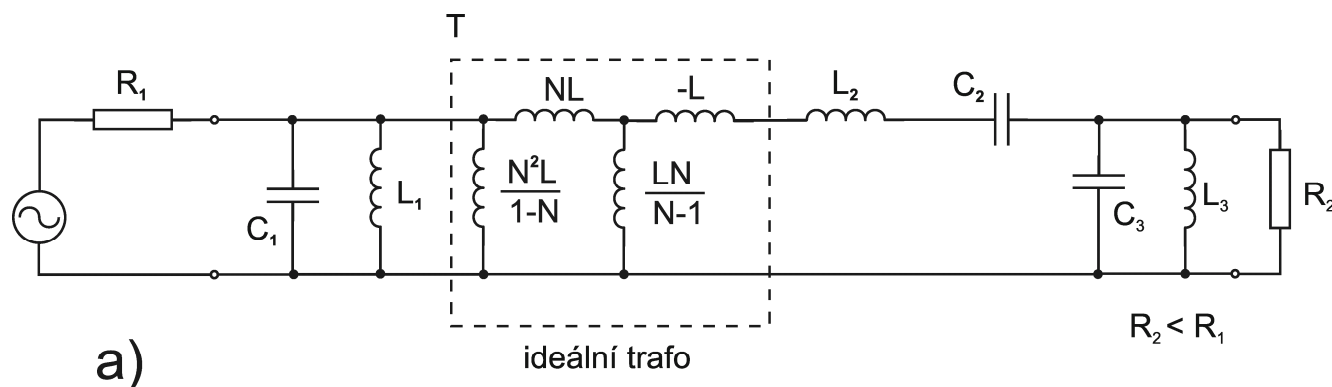
# Resulting Wide-Band MC

- The negative equivalent circuit values can be **canceled out** by the neighboring positive filter elements
- These conditions lead to L and N values (2 equations with 2 unknowns)
- The resulting MC provides the **maximum available impedance transformation**
- Or for the fixed transformation ratio → **the maximum frequency band-width**







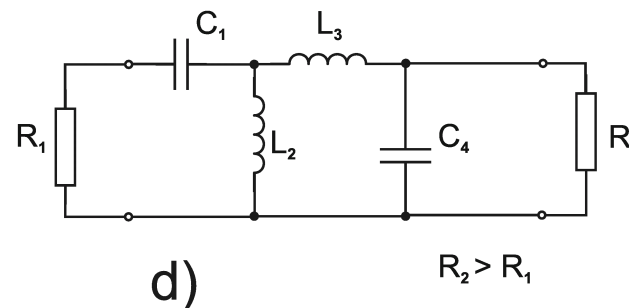
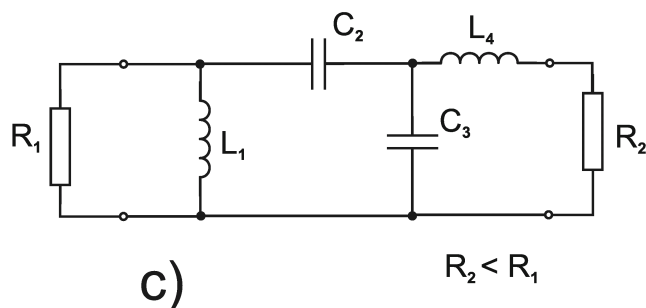
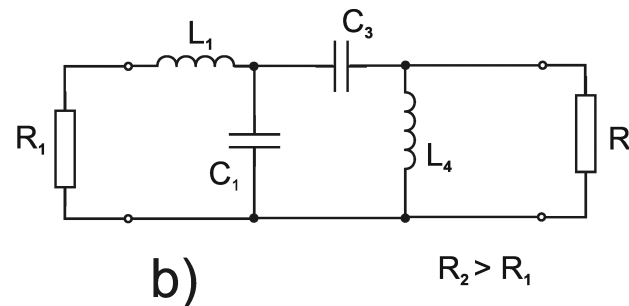
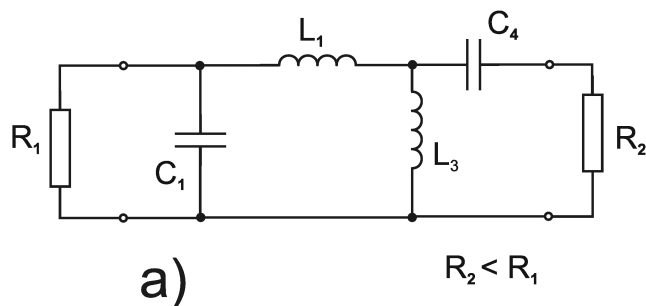
# Recommended Structures n=2

- Recommended structures based on the **2-nd order filter**
- Structures a) and c) provide the **down-transformation  $R_2 < R_1$**  (e.g. from 50Ω to 15Ω)
- Structures b) and d) provide the **up-transformation  $R_2 > R_1$**  (e.g. from 50Ω to 250Ω)
- Values of the LC elements can be calculated or obtained by the CAD optimization



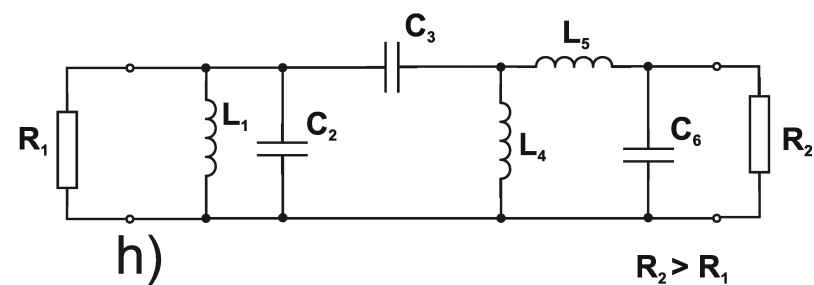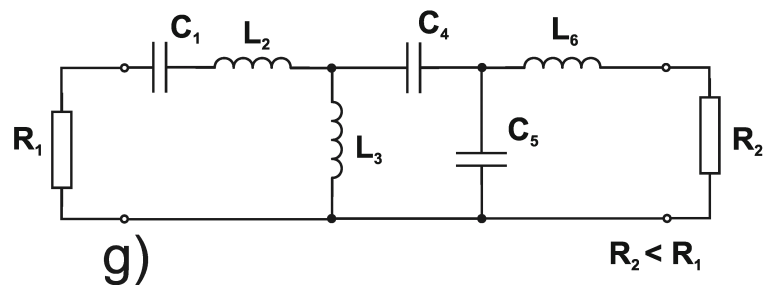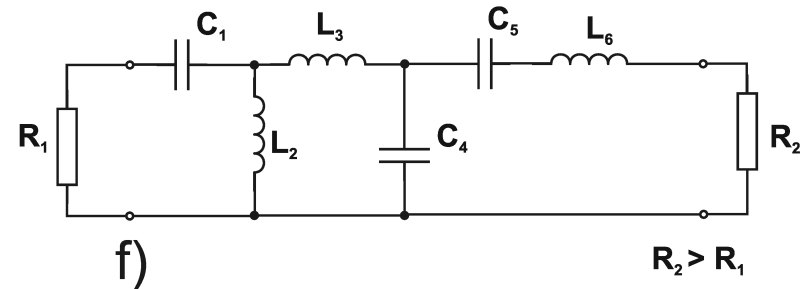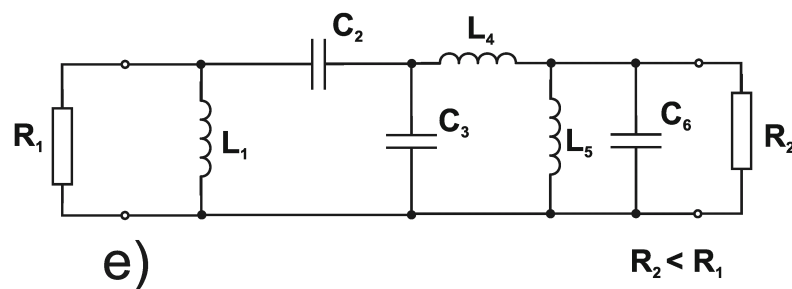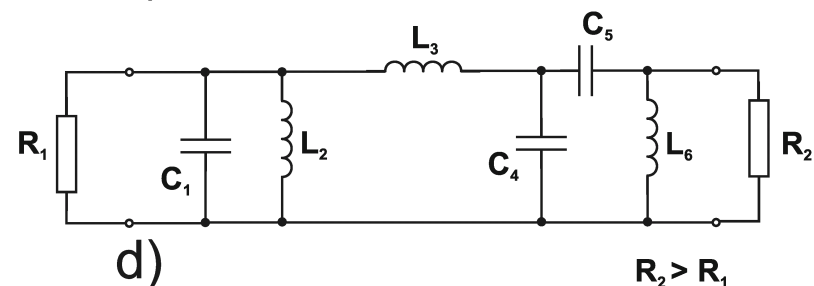
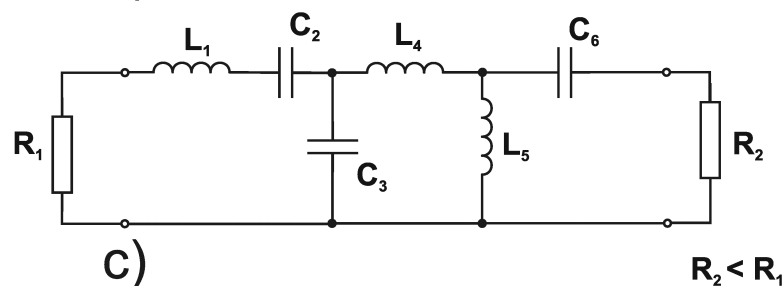
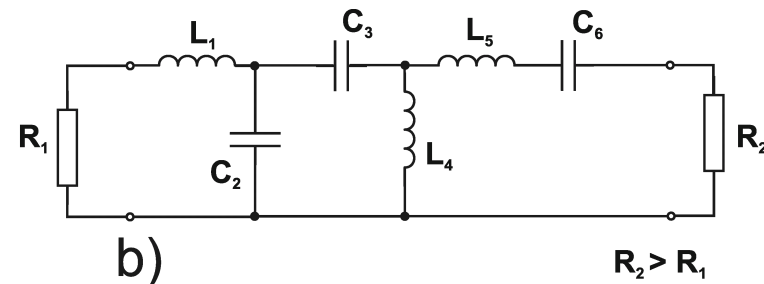
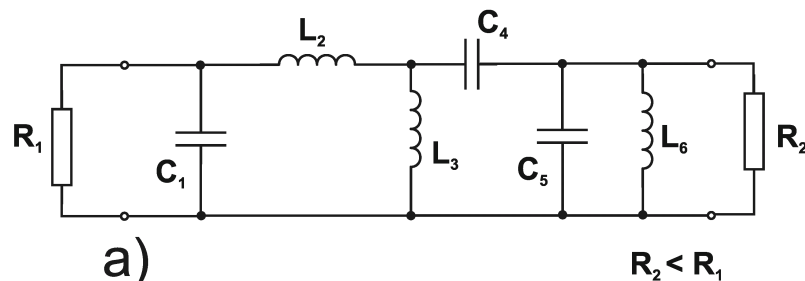
# Recommended Structures $n=3$

- Recommended structures based on the **3-rd order filter**


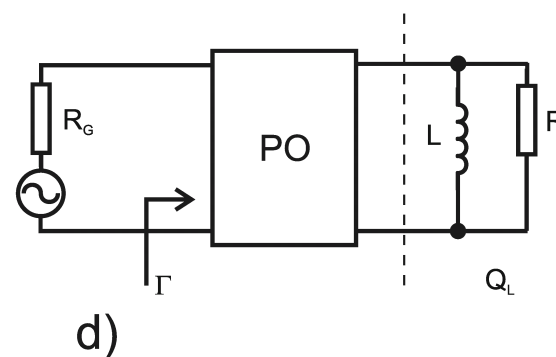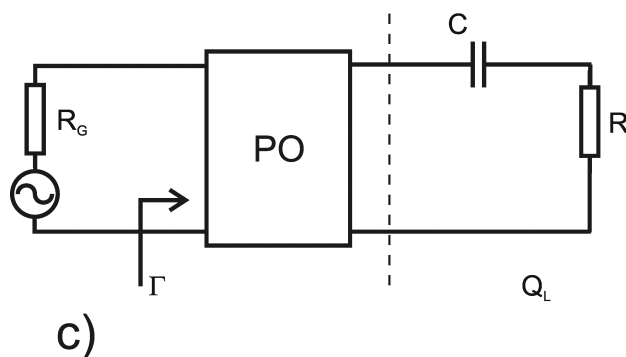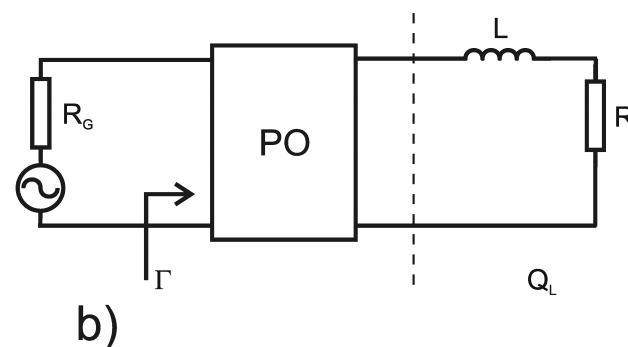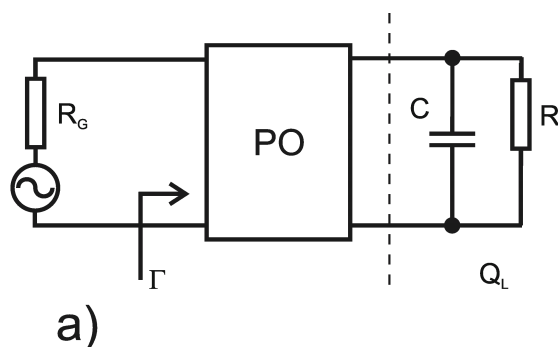
# Problems


- Usually, only one of impedances of the wide-band MC is real (e.g.  $R_1=Z_0=50\Omega$ )
- The latter impedance is generally complex
- **RLC approximation can be used for modeling the complex load**
- If lucky, the reactance part of the load can be **absorbed into the matching filter**
- Often used wide-band load equivalent circuits




# Example

- The input of the microwave transistor can be modeled as a **series combination of the  $18\Omega$  resistance and  $1,2\text{pF}$  capacitance**
- Structure  $n=2$  and down-converting MC can be chosen
- Using design formulas, the  $C_1$ ,  $L_2$ ,  $L_3$  and  $C_4$  values can be calculated  $\rightarrow C_4=1,08\text{pF}$
- This capacitance can be realized by the series combination of the  $C_L=1,2\text{pF}$  load capacitance and  $C_{\text{ext}}=10,2\text{pF}$  external filter capacitance
- Formulas used

$$C_4 = \frac{C_{\text{ext}} C_L}{C_{\text{ext}} + C_L} \quad C_{\text{ext}} = \frac{C_4 C_L}{C_L - C_4}$$

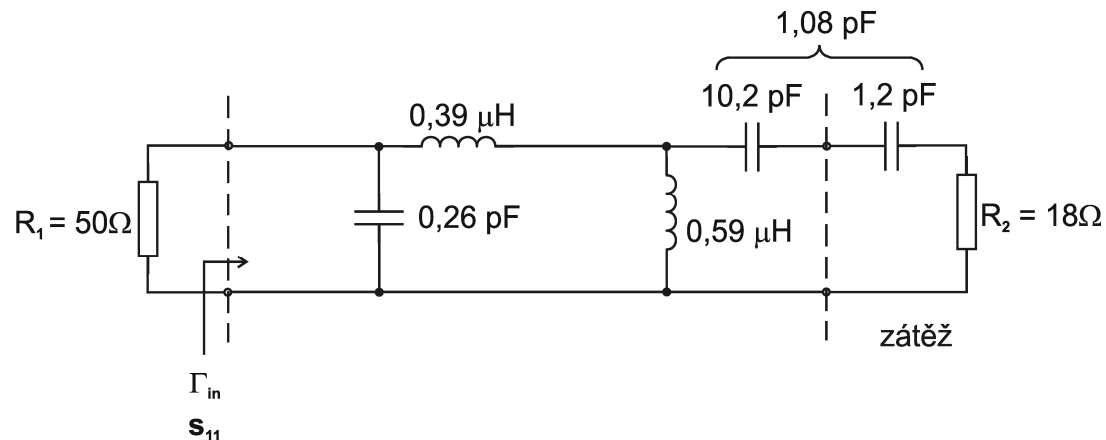


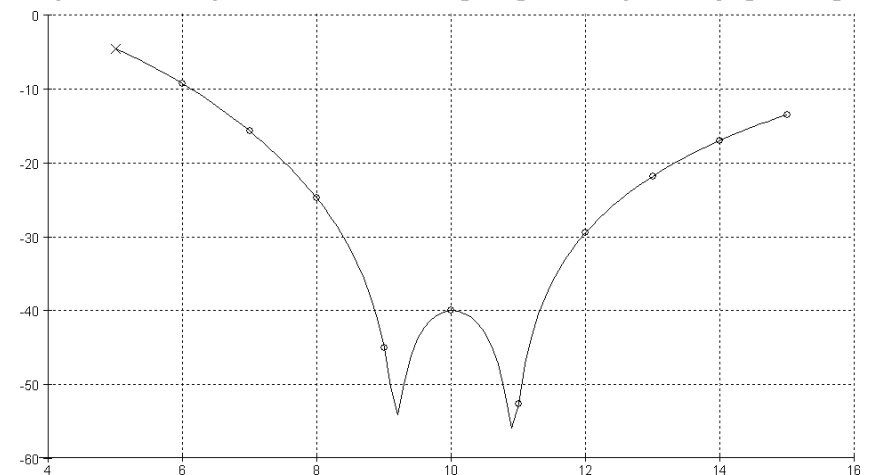Graph 1: Amplitude of S11 [dB] - frequency [GHz]




# Problems

- If  $C_4 \geq C_L \rightarrow$  ideal absorption cannot be reached
- It is recommended to neglect the  $C_{ext}$  and optimize the circuit using the CAD tool
- **Lumped LC matching circuits** are applicable at low frequencies (<1GHz) or inside MMICs
- Parasitic properties of real LC elements must be taken into account
- At higher frequencies, **distributed** (transmission line based) **solutions** must be used
- The lumped $\rightarrow$ distributed conversion can be performed
- But any lumped $\rightarrow$ distributed conversion **narrows B substantially** ( $B_{distributed} \approx 0,5 B_{lumped}$ )
- Direct synthesis of wide-band distributed MCs is advantageous

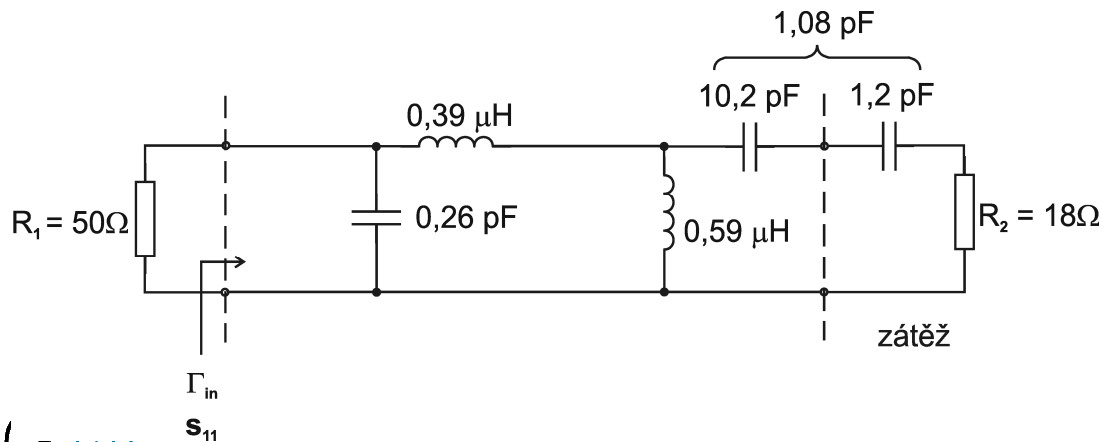


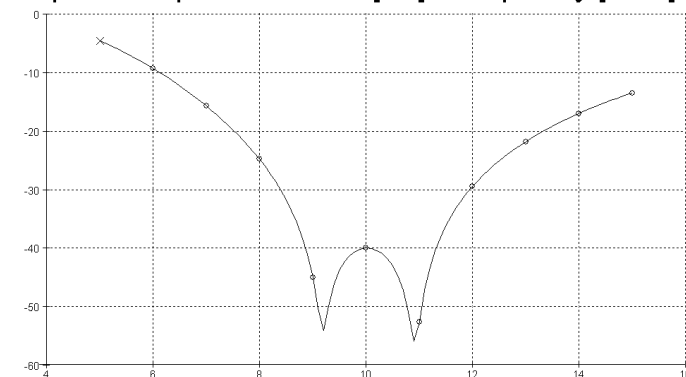Graph 1: Amplitude of S11 [dB] - frequency [GHz]




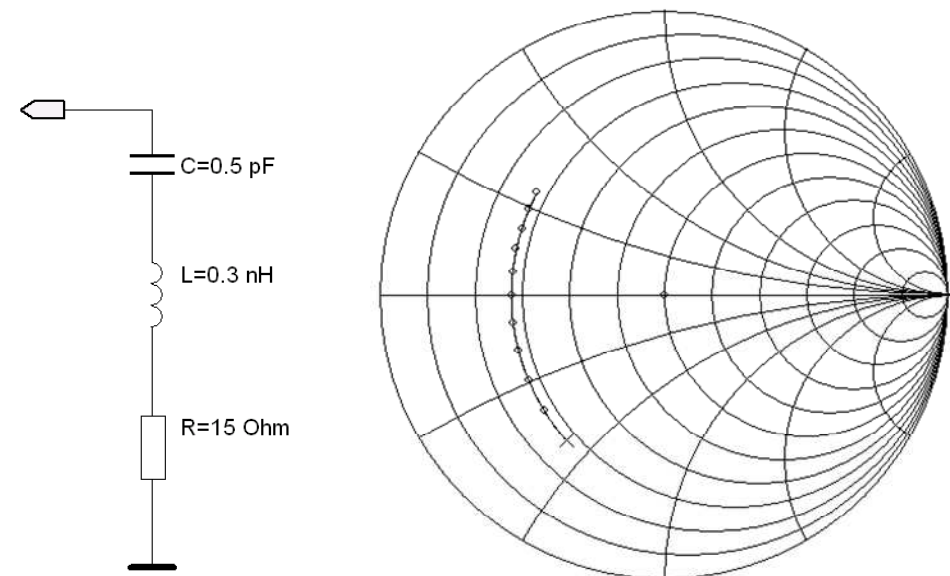
# Recommended Distributed MC – Step No.1

- Direct synthesis of a wide-band distributed MC – can be performed by an **iterative process**
- Based on the calculated or measured  $\Gamma_L(j\omega)$  frequency plot
- The MC can be synthesized in several relatively simple steps supported by a suitable CAD tool
- Recommended for octave band-width requirements
- Individual task No.5
- Example: RLC load 8-18GHz
- **Step No. 1:**
- Center of the  $\Gamma_L(j\omega)$  plot @13GHz should be transformed to the  $X=0$  axis by using a section of the transmission line


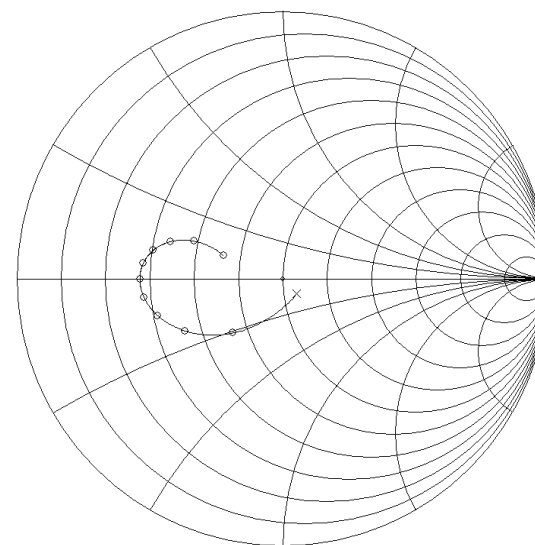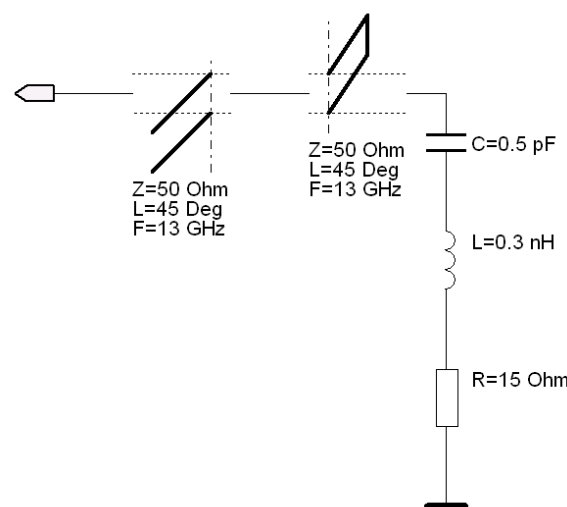
# Recommended Distributed MC – Step No. 2

- Add parallel connection of 2 stubs:
  - $\lambda/8$  long open stub
  - $\lambda/8$  long short stub
- Open/short stubs enable to **curl ends of the initial  $\Gamma_L(j\omega)$  frequency plot**
- The area of the  $\Gamma_L(j\omega)$  gets smaller, but still at a wrong position in the Smith chart





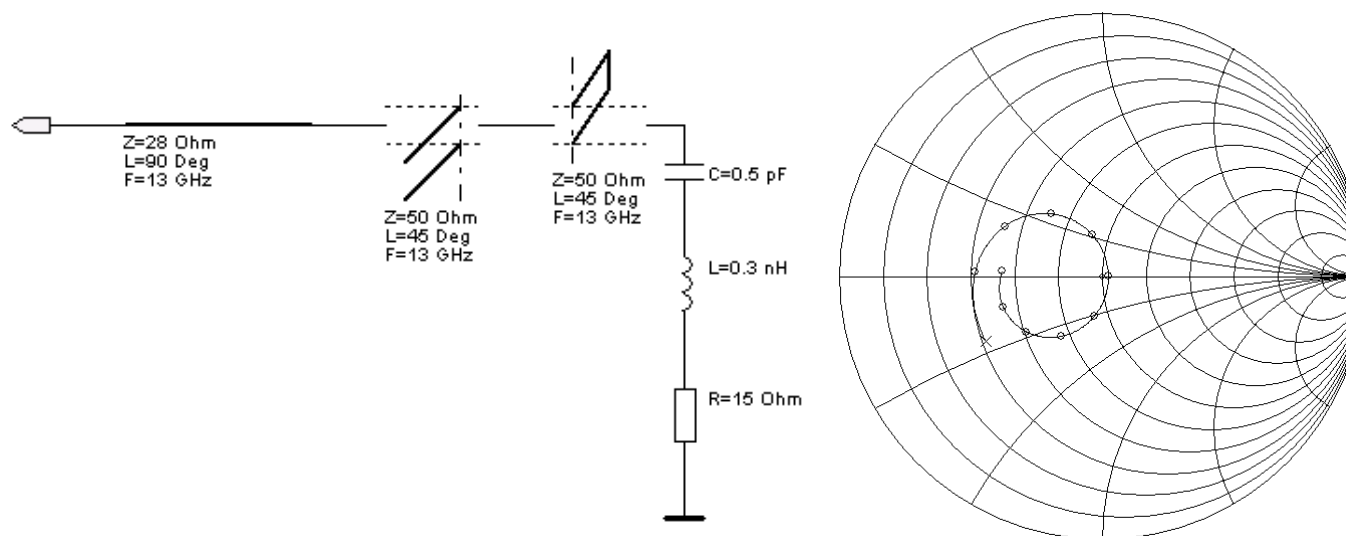
# Recommended Distributed MC – Step No. 3




- In order to shift the  $\Gamma(j\omega)$  frequency plot closer to the Smith chart center, it is advantageous to use the  **$\lambda/4$  impedance transformer**
- Using the  $\lambda/4$  long microstrip line with impedance  $Z_1$ , it is possible to transform the  $Z_x$  impedance to the  $Z_0$  impedance:  

$$Z_1 = \sqrt{Z_x Z_0} = \sqrt{15.50} = 27,4\Omega$$
- The  $\lambda/4$  transformer enables to shift the curled  $\Gamma(j\omega)$  frequency plot to the surroundings of the Smith chart center


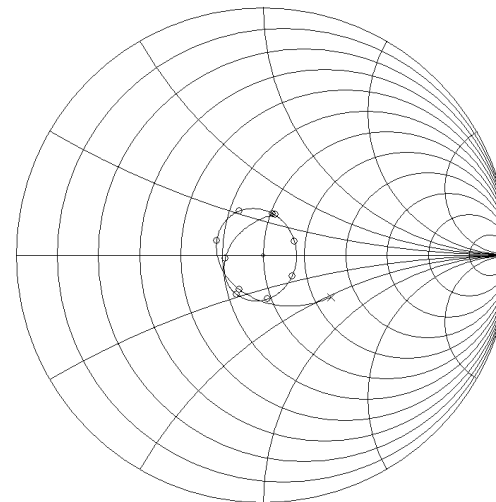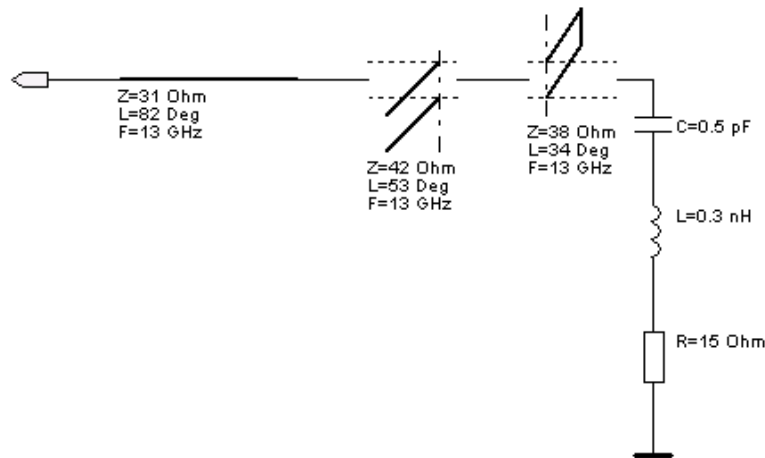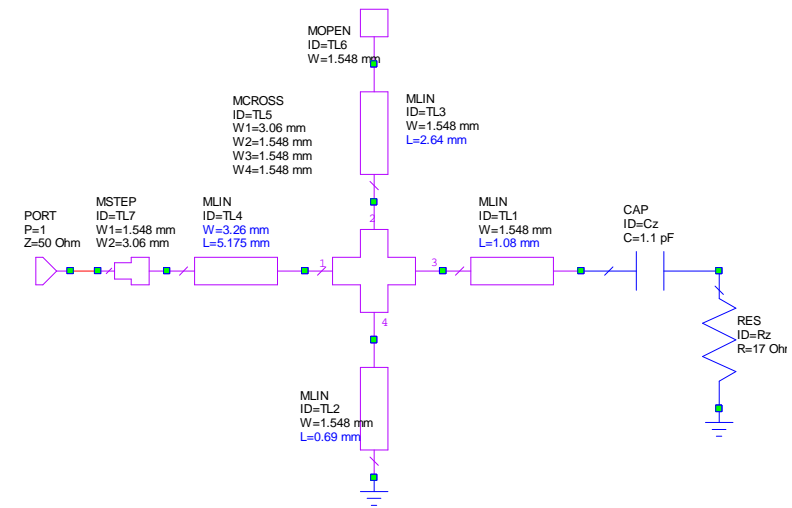
# Recommended Distributed MC – Step No. 4

- **Final CAD optimization:**
  - Fine tuning of all transmission line sections
  - Add models of discontinuities (MCROSS, MTEE, MSTEP, ...)
- The resulting MC is:
  - Wideband
  - Shows a directly realizable microstrip structure
- Example: RCL load 8-18 GHz  $\rightarrow \Gamma_{in}(j\omega) \leq 0,3$




# Wide-Band Amplifier Design

- Wide-band amplifiers with loss-less MCs (LC, microstrip, coplanar waveguide, ...)
- Typically wideband **LNAs or power amplifiers**
- In the B-wide frequency band only **compromise impedance matching can be reached**



$$|\Gamma_{in}(j\omega)| \leq \text{const.} \leq \Gamma_{in\max} \quad |\Gamma_{out}(j\omega)| \leq \text{const.} \leq \Gamma_{out\max}$$

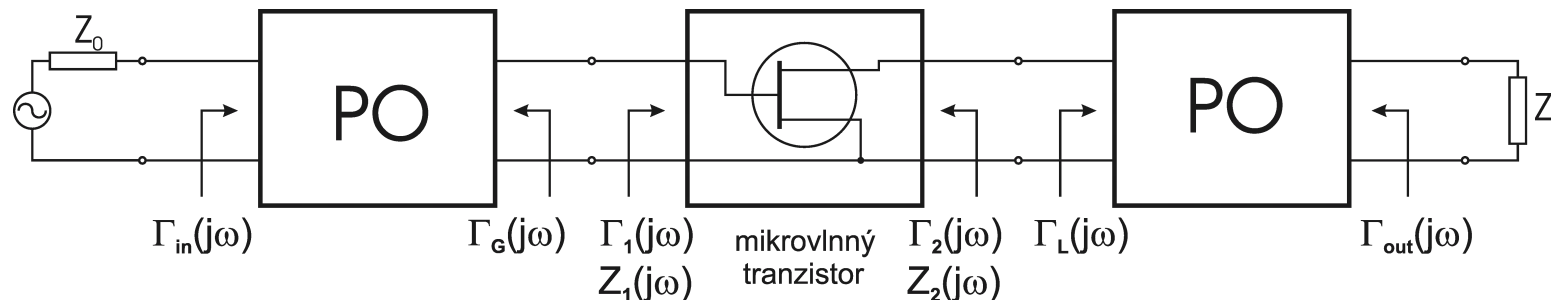- All design procedures are based on **numerous approximations**, CAD optimization is necessary
- For the given requirements → **NO solution can exist**
- Besides the MC design → **gain equalization** must also be treated
- Wideband **biasing circuits** are necessary
- Substantially more complicated than the narrow-band amplifier design


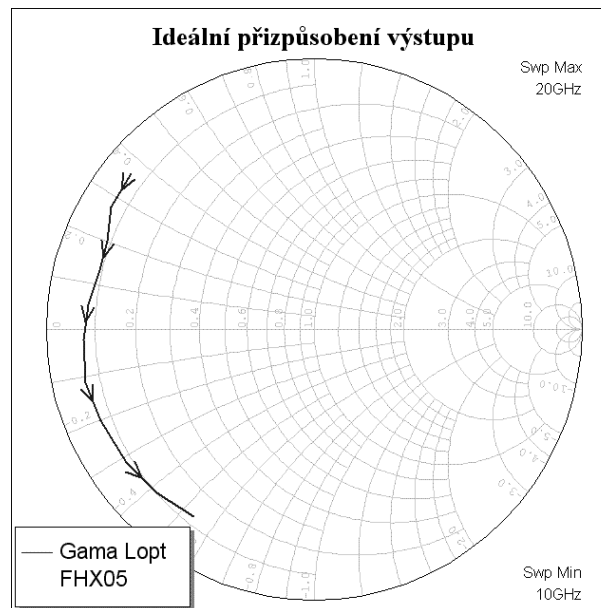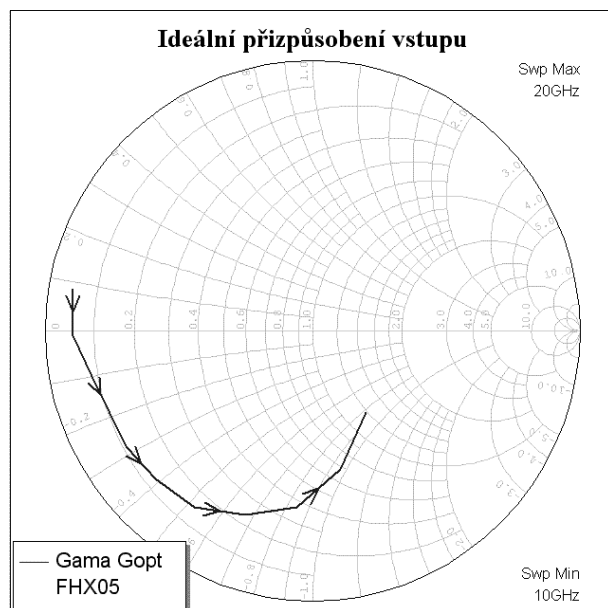
# Wide-Band Amplifier Design


- **AWR-MO:**  $\Gamma_{Gopt} = GM1$      $\Gamma_{Lopt} = GM2$



- Frequency plots of  $\Gamma_{Gopt}$  and  $\Gamma_{Lopt}$  run **counter-clockwise**
- Frequency plot of ANY matching circuit run clockwise
- Ideal impedance matching can be reached only at 1 frequency, or at several discrete and distant frequencies
- It is NOT possible to design wide-band amplifiers with ideal impedance matching


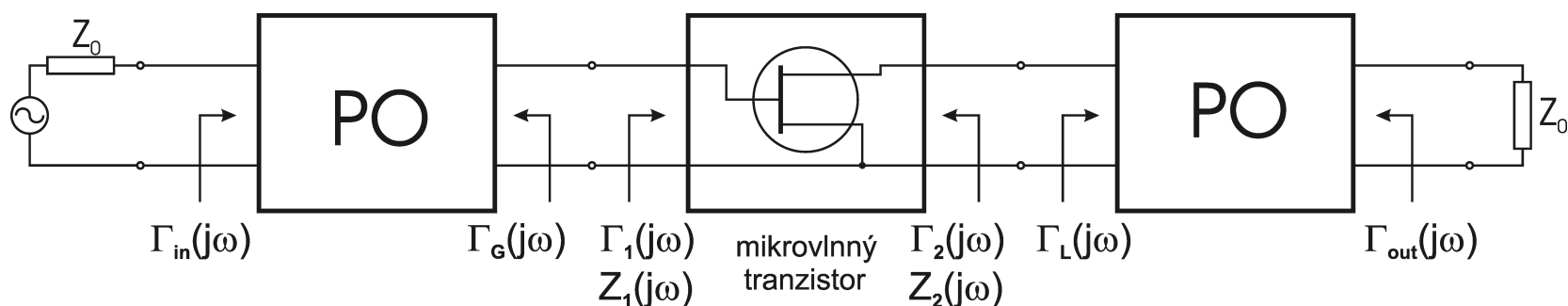
# Wide-Band Amplifier Design

- The problem is enhanced by the fact, that **both input and output MCs must be designed:**
  - The MC<sub>1</sub> transforms Z<sub>0</sub> to  $\Gamma_1(j\omega)$  but  $\Gamma_1(j\omega) = f(\Gamma_L) = s_{11}(j\omega) + \frac{s_{12}(j\omega)s_{21}(j\omega)\Gamma_L(j\omega)}{1 - s_{22}(j\omega)\Gamma_L(j\omega)}$
  - The MC<sub>2</sub> transforms Z<sub>0</sub> to  $\Gamma_2(j\omega)$  but  $\Gamma_2(j\omega) = f(\Gamma_G) = s_{22}(j\omega) + \frac{s_{12}(j\omega)s_{21}(j\omega)\Gamma_G(j\omega)}{1 - s_{11}(j\omega)\Gamma_G(j\omega)}$
- MC<sub>1</sub> and MC<sub>2</sub> must be solved simultaneously → CAD optimization
- Multiple iterations must be performed



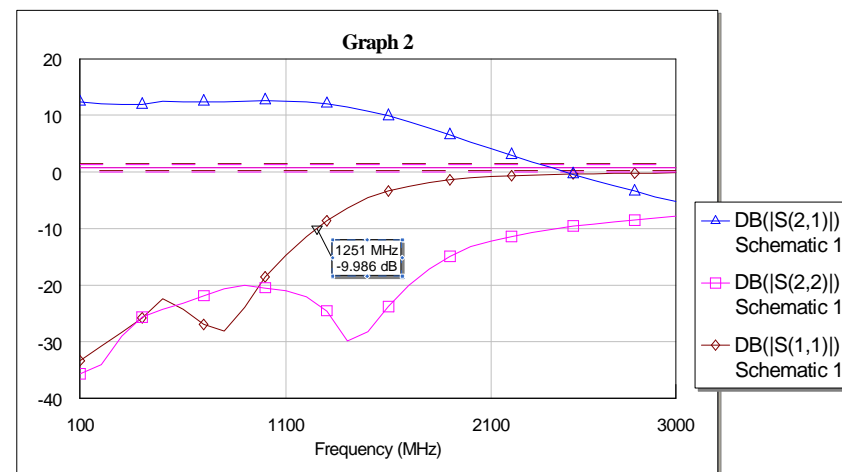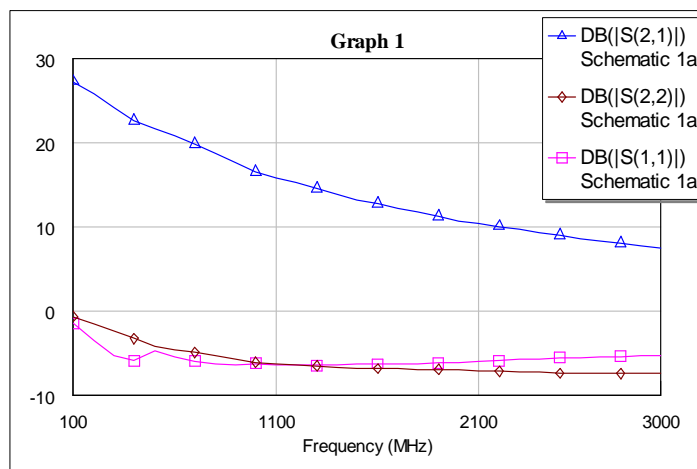
# Gain Equalization

- Transistor gain (available, power) **decreases -6dB/oct**
- Wide-band amplifiers → **constant gain** is required usually
- The drop in gain must be equalized → possible solutions:
  - **Higher reflections**  $\Gamma_{in}(j\omega)$  and  $\Gamma_{out}(j\omega)$  at lower frequencies
  - Passive **equalizing structures** (frequency dependent attenuators)
  - Special **feedback structures** (cannot be used in case of LNAs and PAs)
- Easier in the balanced structures


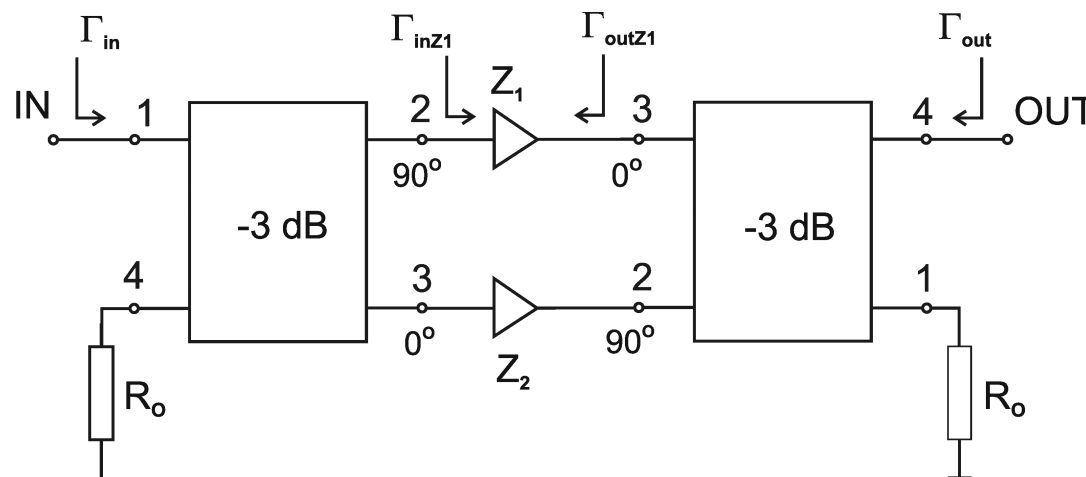
# Balanced Amplifiers

- More complex amplifier structure
- Employs 2 identical amplifying stages **operated in parallel**
- Input signal is divided 1:1 by the **90° power divider**
- Quadrature divider or Wilkinson divider with additional  $\lambda/4$  transmission line can be used
- Dividing loss  $L_d = 3dB + L_a$
- Amplified signals are **summed in-phase** with an identical and symmetrically connected 90° power splitter/combiner




- **Gain**  $G_{resdB} = G_{ZdB} - 2L_{adB} \cong G_{zdB}$
- **Output power**  $P_{resdBm} = P_{ZdBm} + 3dB - L_{adB}$

- **Input reflections**  $\Gamma_{in} = \frac{1}{2}(\Gamma_{inZ1}e^{2j\pi/2} + \Gamma_{inZ2}e^{2j0}) = \frac{1}{2}(-\Gamma_{inZ1} + \Gamma_{inZ2})$

- **Output reflections**  $\Gamma_{out} = \frac{1}{2}(\Gamma_{outZ1}e^{-2j0} + \Gamma_{outZ2}e^{-2j\pi/2}) = \frac{1}{2}(\Gamma_{outZ1} - \Gamma_{outZ2})$

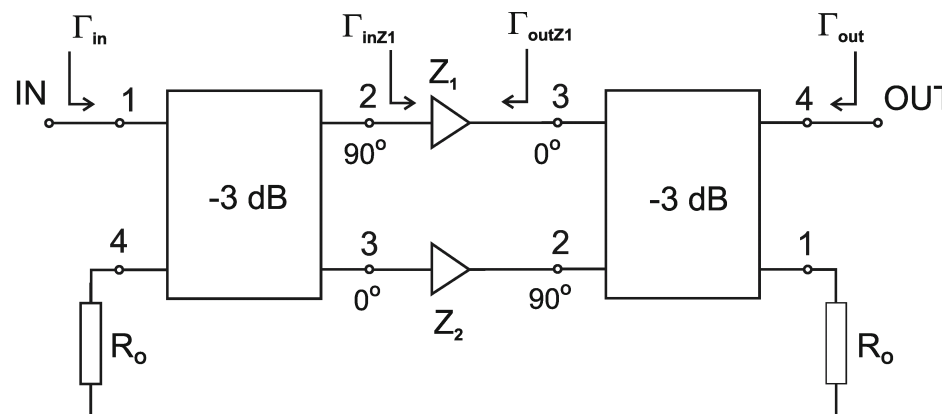- If  $\Gamma_{inZ1} = \Gamma_{inZ2}$  and  $\Gamma_{outZ1} = \Gamma_{outZ2}$ , **input and output reflections can be very small**
- The structure enable reduction of reflections even in case of LNAs or other highly reflecting amplifiers






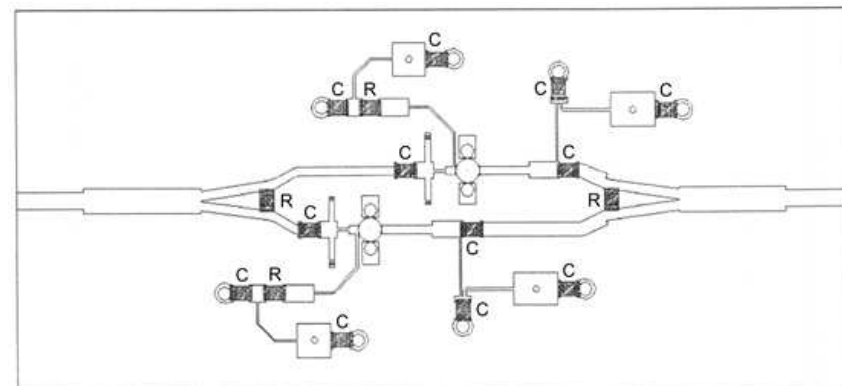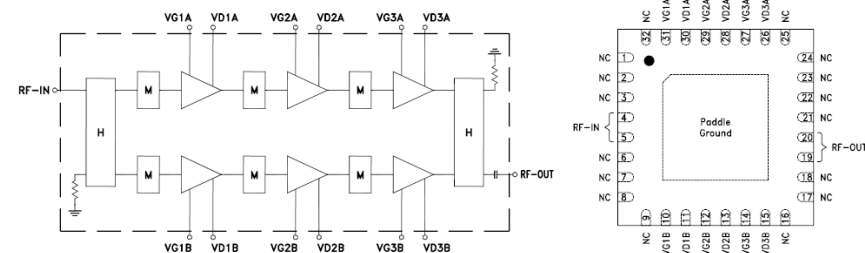
# AVM-273HP+




- **Disadvantages:**

- ### Simplified Schematic and Pad Description


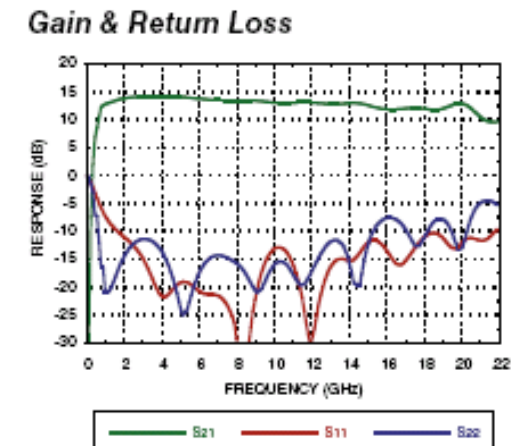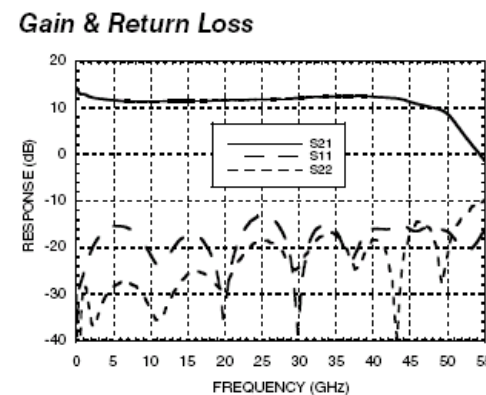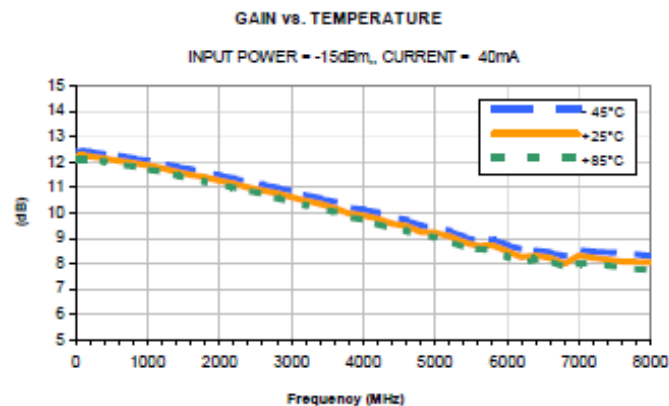
# Ultra-Wideband Amplifiers


- Standard wide-band impedance matching provides approx. 1-2 octaves bandwidth
- Even wider amplifiers are required (DC-8GHz, 1 – 20GHz, DC- 35GHz, ...)
- For these purposes, special matching techniques must be used:
  - Lossy impedance matching
  - Feedback structures
  - Distributed structures
- Available parameters:
  - Wide bandwidth
  - Flat gain, fair input and output reflections, typ.  $RL \geq 10\text{dB}$
  - But often – higher F


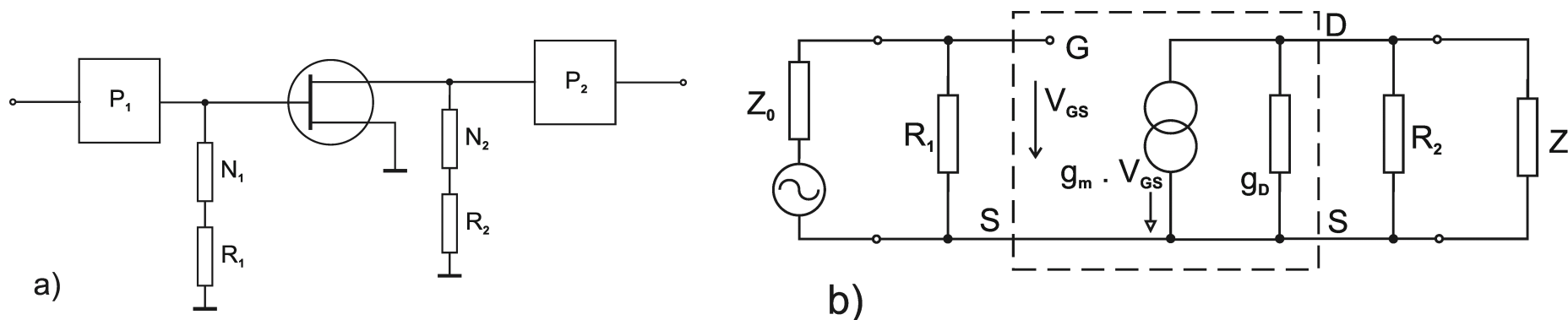
# Amplifiers with Resistive Matching


- Employ  $R_1$  and  $R_2$  **resistors in the input and output matching circuits**
- The  $N_1$  and  $N_2$  frequency dependant components (L usually) reduce influences of  $R_1$  and  $R_2$  at higher frequencies → contribute to **gain equalization**
- Additional simple matching circuits  $P_1$  and  $P_2$  improve wide-band impedance matching
- Amplifiers of this type are designed by CAD optimization
- The initial  $R_1$  and  $R_2$  values and gain can be calculated from the LF model:

$$R_1 \cong Z_0 = \frac{1}{G_0} \quad R_2 \cong \frac{1}{G_0 - g_D} \quad G \cong \left( \frac{g_m}{2G_0} \right)^2$$



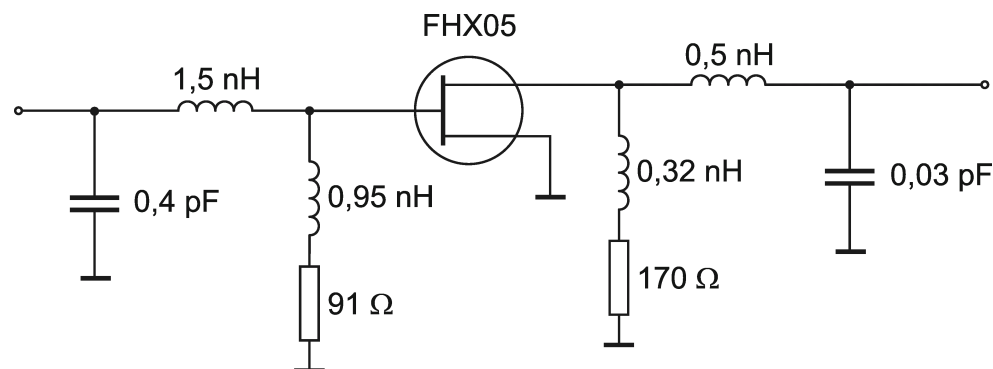
# Properties - Example

- **Properties** of amplifiers with resistive matching:
  - Simple structure
  - Low frequency is limited only by the blocking capacitors used
  - But high noise figure, low output power and PAE, strong dependence of  $G$  on  $g_m$
- **Example:**
  - Design DC – 6 GHz, HEMT, AWR optimization
  - $G=6,2\text{dB}$  @ 1GHz,  $G=8,9\text{dB}$  @ 6GHz
  - $RL_{in} \geq 10\text{dB}$ ,  $RL_{out} \geq 10\text{dB}$  @ DC – 6GHz




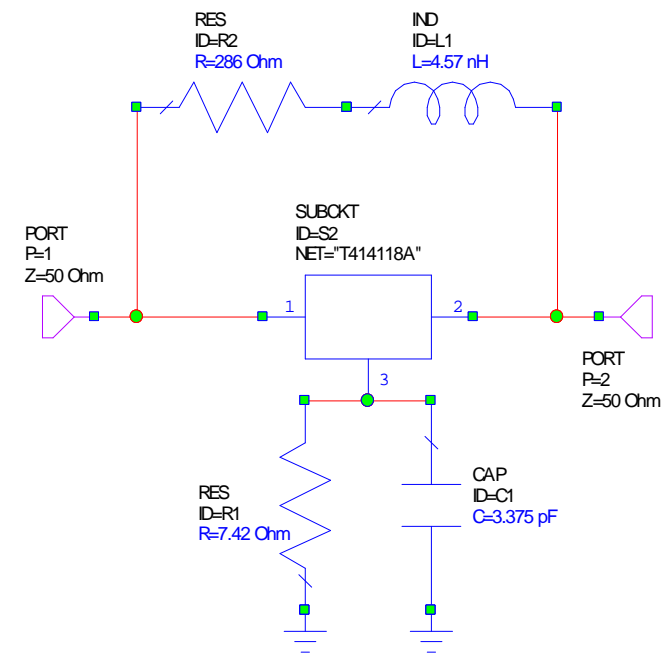
# Feedback Amplifiers

- Employ **resistive feedback with additional frequency dependent components**
  - Series feedback → BJT
  - Parallel feedback → FET
  - Combination of both → BJT
- Additional frequency dependent components are used for **gain equalization**
- Feedback structures:
  - Ensure wide-band input and output matching
  - Ensure flat gain
  - Improve stability
  - But raise F
  - MMIC – the most frequent amplifier type
- Design → CAD optimization


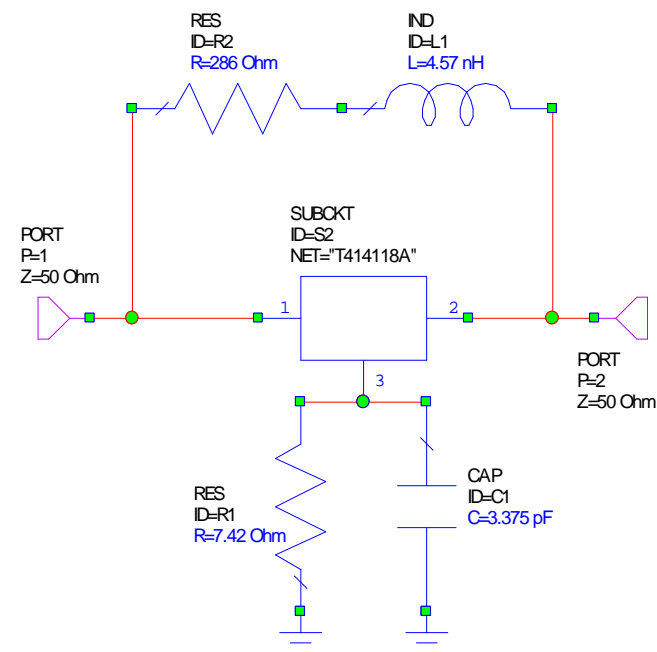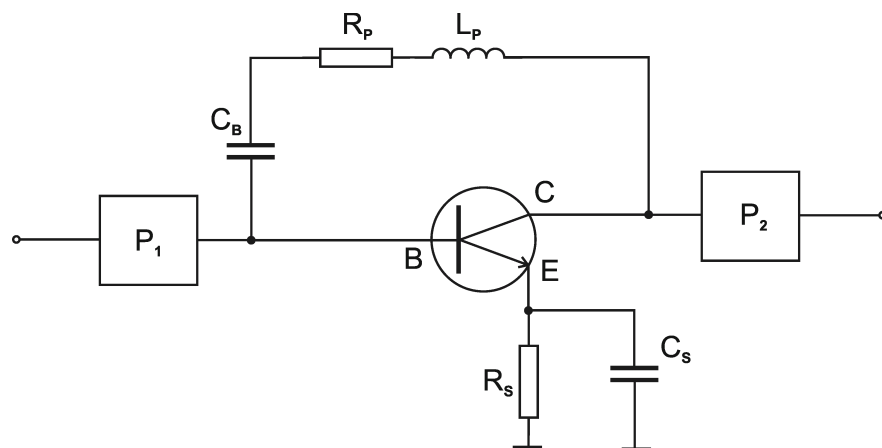
# Feedback Amplifiers - BJT

- BJT → both **series and parallel negative resistive feedbacks used**
- $C_s$  parallel to  $R_s$  reduces influence of the series feedback at higher frequencies
- $L_p$  in series with  $R_p$  reduces influence of the parallel feedback at higher frequencies
- $P_1, P_2$  → simple additional matching circuits – optional
- Common values:
  - $R_s=10\Omega$
  - $R_p=250\Omega$
- Upper frequency → HBT MMIC DC-8GHz





# Feedback Amplifiers - FET

- FETs → **only parallel feedback used**
- Initial values for the CAD optimization can be derived from the LF model

$$R_p \approx \frac{g_m - g_d}{G_0(G_0 + g_d)} \quad G \approx \left( \frac{G_0 - g_m}{G_0 + g_D} \right)^2$$

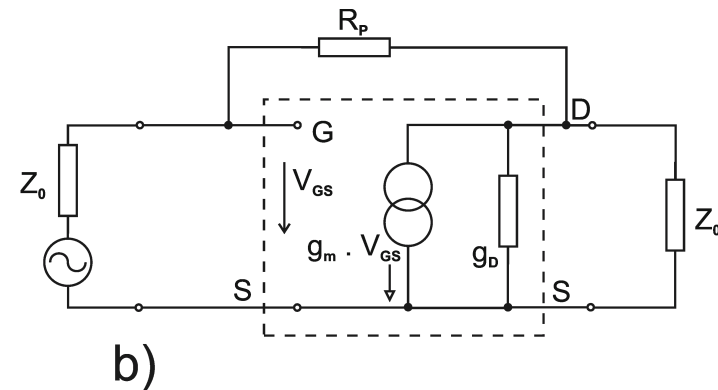
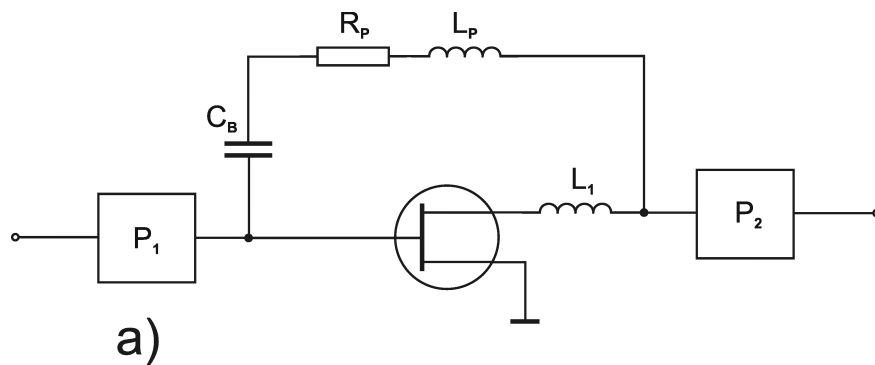
- Common values:  $g_d = 0,0025$   $g_m = 0,007$  lead to  $R_p = 150 \, \Omega$   $G = 6,9 \, dB$



# Example 1

- Several Mini-Circuits wide-band MMIC amplifiers:






Type	band B [GHz]	gain G [dB]	$P_{-1dB}$ [dBm]	F [dB]	$V_N$ [V]	$I_N$ [mA]
ERA-1	DC ÷ 8	11,4	11,7	5,3	3,6	40
ERA-2	DC ÷ 6	15,2	12,8	4,7	3,6	40
ERA-3	DC ÷ 3	21,3	12,1	3,8	3,5	35
ERA-4	DC ÷ 4	13,5	17,0	5,5	5,0	65
ERA-5	DC ÷ 4	18,6	18,4	4,5	4,9	65
ERA-6	DC ÷ 4	11,4	18,5	8,4	5,5	70

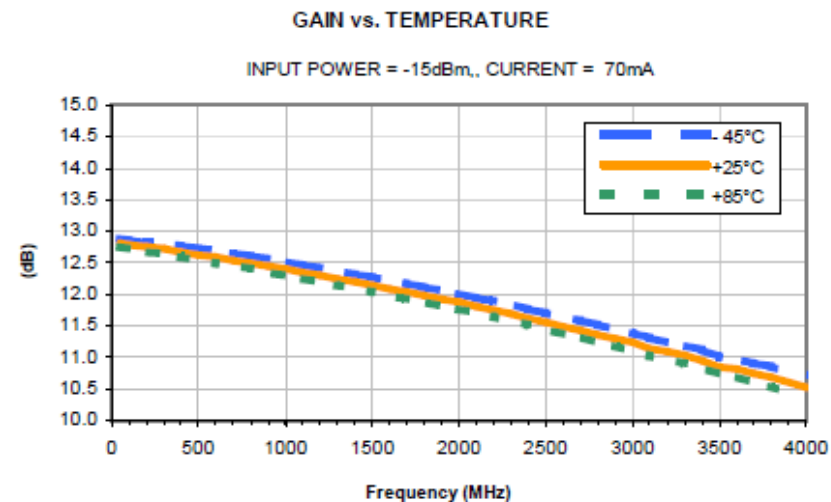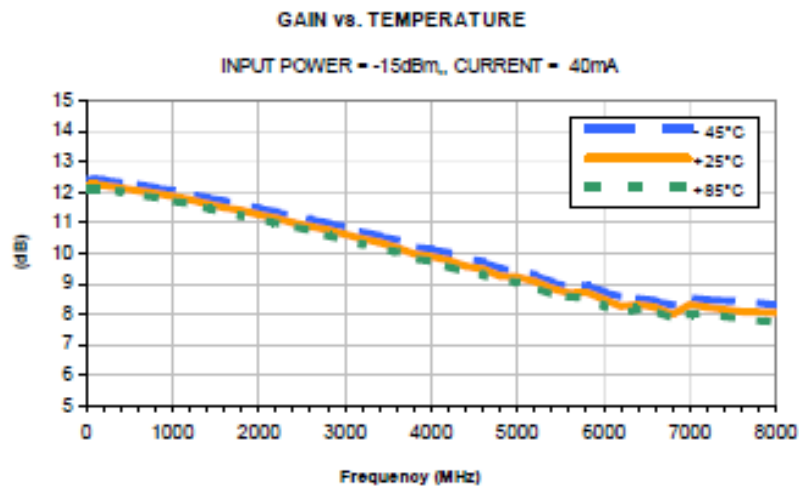



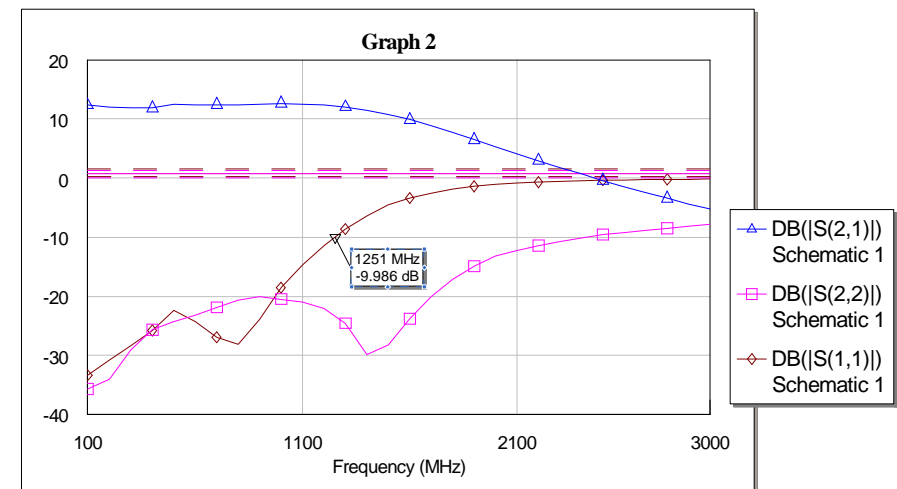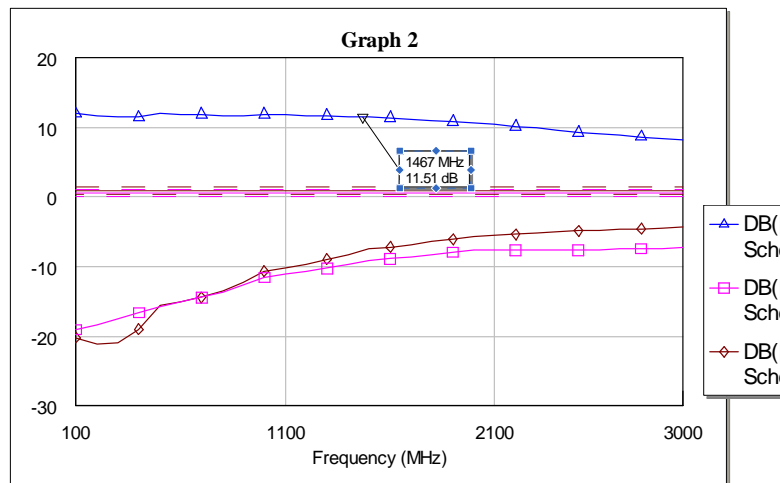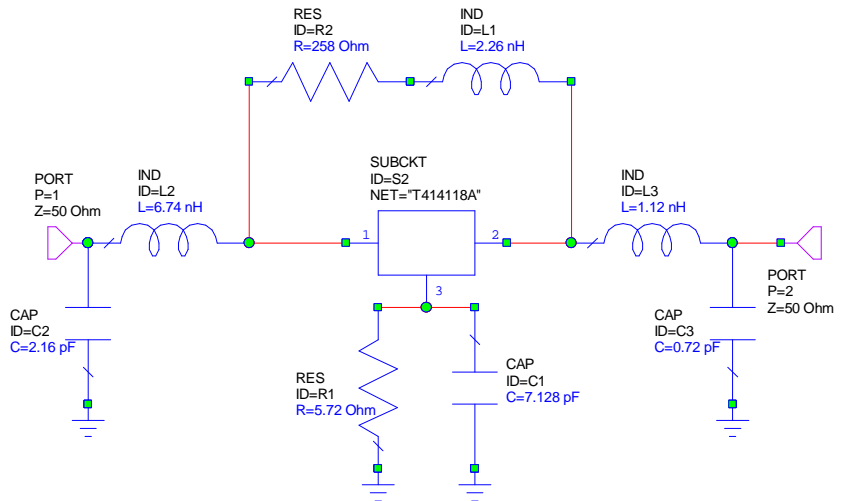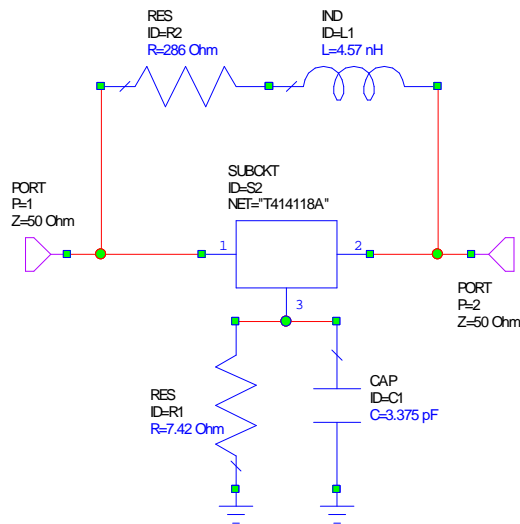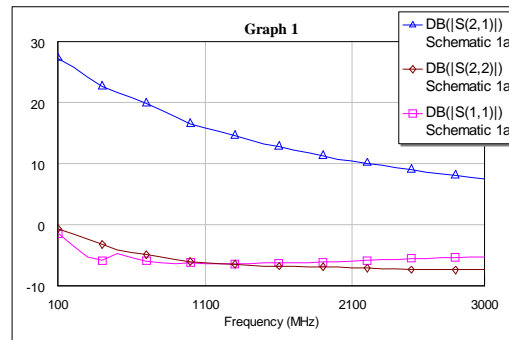
# Example 2

- Individual task No.6
- BJT AT-41411, 8V/10mA




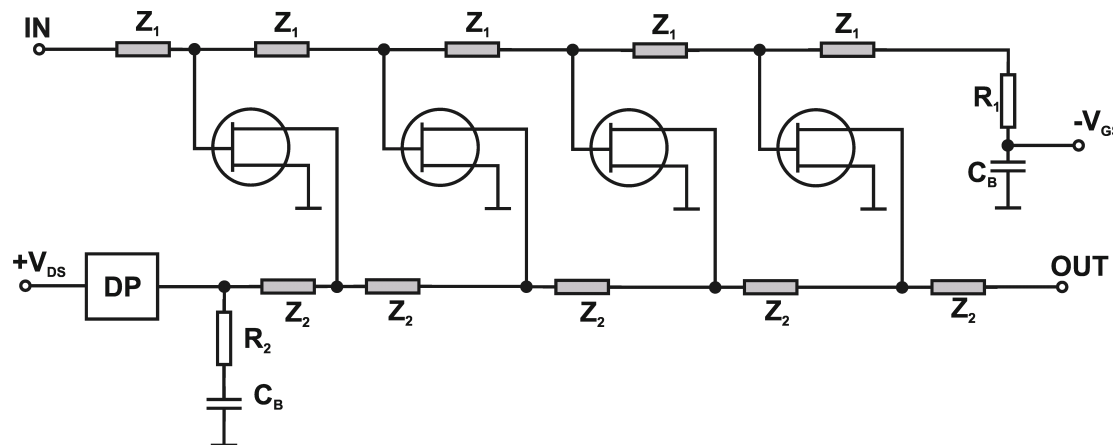
# Distributed Amplifiers

- Truly **wide-band components/structures**:
  - Ideal resistors
  - Matched transmission lines
- Distributed amplifiers employ wideband capabilities of the **matched transmission lines**
- The **input transmission line** distributes the input RF power to FETs
- The rest of the input wave is absorbed in the  $R_1$  termination
- The **output transmission line** collects in phase the amplified RF powers from the FET outputs



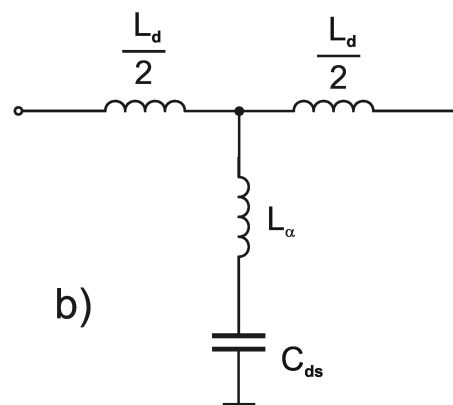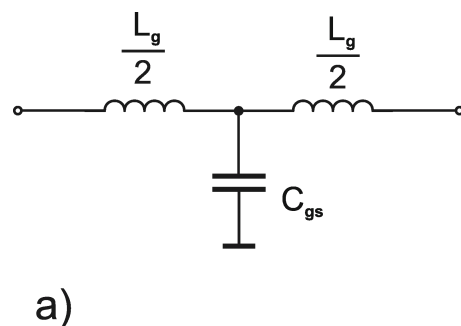
# Artificial Transmission Lines

- Extremely wide-band amplifiers → can be obtained by realizing **artificial transmission lines and by incorporating FET parasitic reactances into them:**
  - Artificial transmission lines are formed by the equivalent **LC structures**
  - The input transmission line is formed by a cascade of external series inductances  $L_g/2$  and FET **input parasitic capacitances  $C_{gs}$**
  - The output transmission line is formed by a cascade of external series inductances  $L_d/2$  and FET **output parasitic capacitances  $C_{ds}$**
- Problem:**  $C_{gs} \gg C_{ds}$ , while impedances  $Z_{in} = Z_{out} = Z_0 = 50\Omega$  and phase velocities in both transmission lines must be the same
- Solution:** Compensating inductance  $L_\alpha$



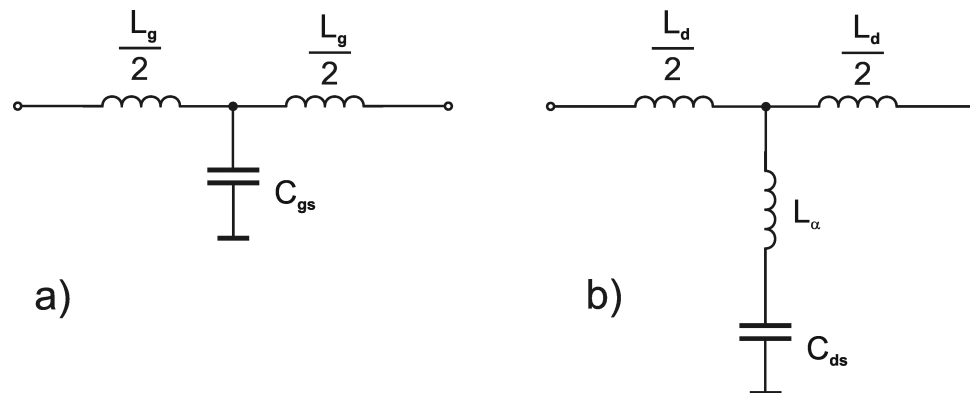
# Artificial Transmission Lines

- Artificial transmission lines:
  - Enable realization of the distributed amplifiers (DAs)
  - Are not ideal transmission lines → only equivalent circuits
  - Behave like **low-pass filters and limit the DA upper frequency**  $f_m = \frac{1}{\pi\sqrt{LC}}$
- DA gain:
  - Depends upon number of FET sections  $G = \frac{n^2 g_m^2 Z_0^2}{4}$
  - The formula considers the loss-less transmission lines
  - In practice – both lines are lossy, input power drops alongside the cascade
- Practical No. of FET sections → **4 - 5**


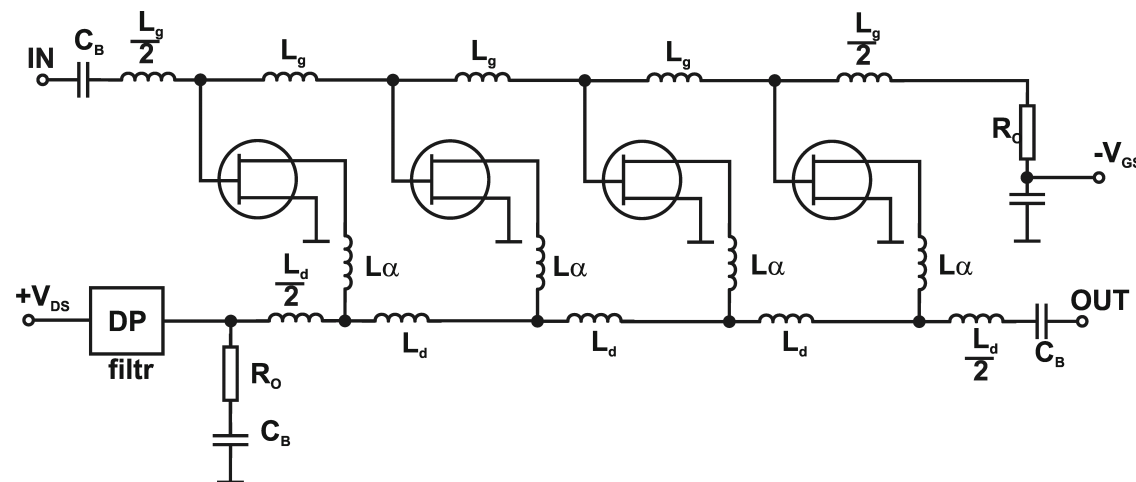
# Practical DA Circuit


- Practical DA circuit:
  - Four FET sections
  - **External inductances**  $L_g$ ,  $L_\alpha$ ,  $L_d$  → their parasitic capacitances limit the DA upper frequency
  - **Gate biasing** (zero current) – through the  $R_0$  termination
  - **Drain biasing** (high current) – through the low-pass filter
  - The LP filter limits the lower operating frequency
- Realization → MMIC (with external powering circuits)





# Example

- HITTITE ([www.hittite.com](http://www.hittite.com)) :
  - Amplifiers – Wideband (Distributed)
  - Tens of models, also LNAs and PAs
  - Frequency ranges: DC-20GHz, 2-22 GHz, DC-35GHz, 0,5-65 GHz
  - Usually chips - but also in the LP5 package (DC-20GHz)

Gain & Return Loss

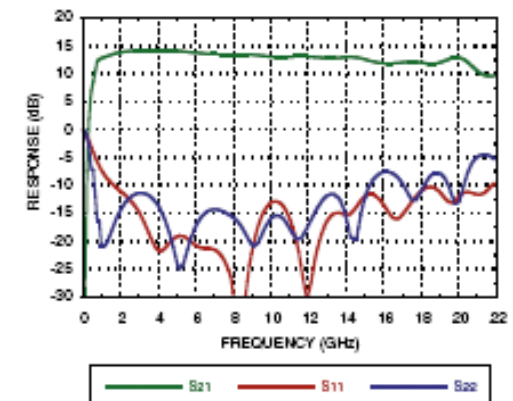

Gain & Return Loss

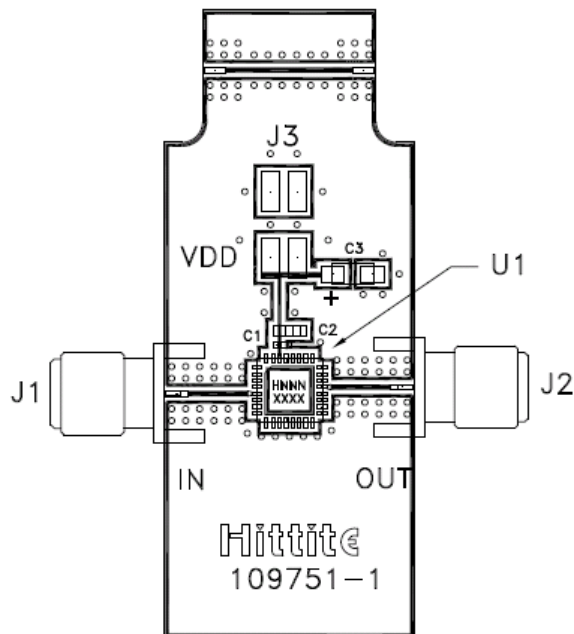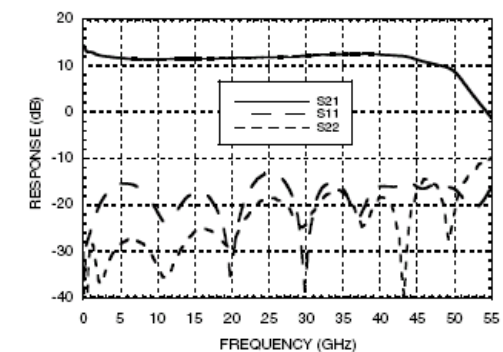

Assembly Diagram

