

Chapter 11

Millimeter-Wave Flip-Chip Transitions

National Taiwan University of
Science and Technology


Chun-Long Wang

Outline

- Introduction
- Conventional Flip-chip Transition
- Resonant Flip-chip Transition
- Inductive Compensation Flip-chip Transition
- Locally Matching Flip-chip Transition
- On Chip Design and Measurement Correction
- Conclusions

Introduction

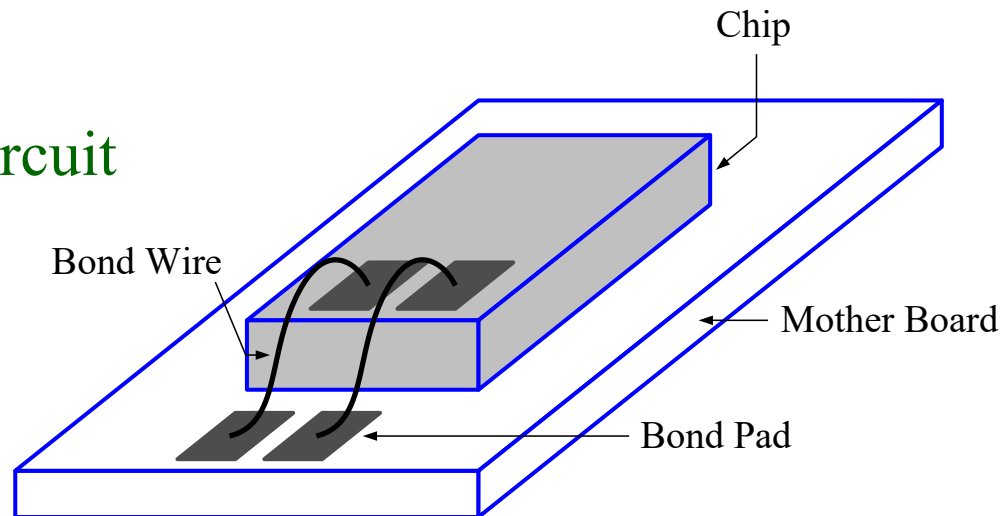- Bonding Wire → Inductive
 - Multiple Bonding Wires [1]
 - Ribbon Wire [1]-[2]
 - Up to 40 GHz
 - Capacitive Matching Circuit [3]-[4]
 - Sacrifice of chip areas
 - Requirement of precise fabrication



[1] J. Y. Kim et al., IEEE APMC'00, pp. 1265-1268.

[2] A. Sutono et al., IEEE Advanced Packaging-24, pp. 595-603, 2001.

[3] U. Goebel, IEEE EPEP'94, pp. 182-185.

[4] T. P. Budka, IEEE MTT-49, pp. 715-718, 2001.

Introduction

- Why Flip-chip over Bonding Wire
 - Short and Stable Electrical Interconnection [5]
 - Lower insertion loss
 - Good Power Distribution Fidelity [6]
 - Good Heat Sinking Ability [7]
 - Good Surface Wave Immunity [8]
 - Available Fabrication in Millimeter-wave Frequencies [9]

[5] T. Krems et al., IEEE MTT-S'96, pp. 247-250.

[6] H. Hashemi et al., IEEE EPEP'96, pp. 24-26.


[7] E. Wolf, Proc. Semiconductor Packaging Symposium, 2000.

[8] T. Krems et al., IEEE MTT-S'97, pp. 987-990.

[9] Y. Arai et al., IEEE MTT-45, pp. 2261-2266, 1997.

Introduction

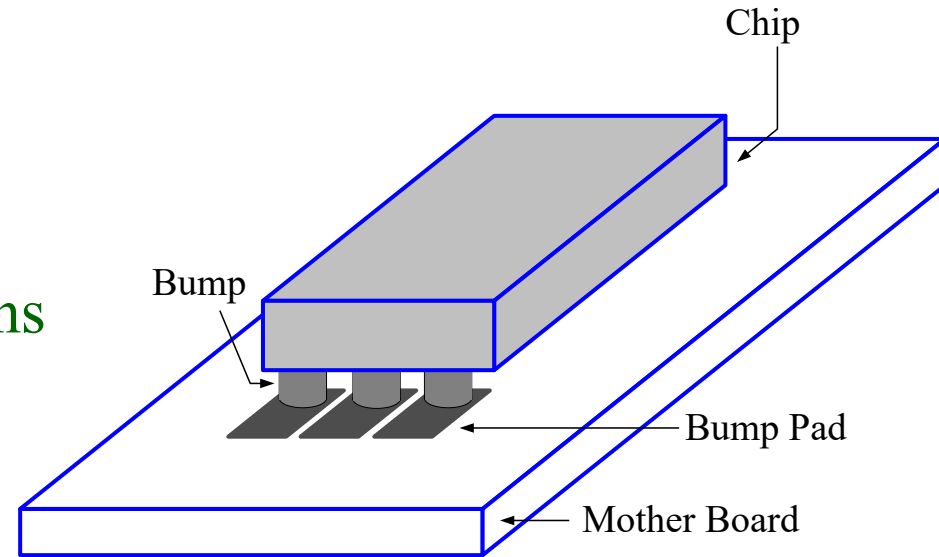- Flip-chip → Capacitive
 - Geometry of the Bumps
 - e.g. Bump pad and height [10]
 - Bump cross section [11]
 - Structure of the Transitions
 - e.g. Staggered structure [12]
 - Resonant structure [13]
 - Impedance Matching
 - e.g. Compensated structure [11]
 - Locally matching structure [14]



- [10] W. Heinrich et al., IEEE MTT-S'98, p. 1083.
- [11] A. Jentzsch et al., IEEE MTT-S'99, pp. 637-640.
- [12] H. H. M. Ghouz et al., IEEE MTT-44, p. 2550, 1996.
- [13] C. L. Wang et al., IEEE MTT-S'99, pp. 1423-1426.
- [14] C. L. Wang et al., IEEE MTT-S'02, pp. 1397-1400.




Introduction

- Various Structure Achievement
 - Two Resonant Designs
 - Control of the large return loss region
 - Optimization up to millimeter-wave frequencies
 - Inductive Compensation Design
 - A systematic design rule for implementing the inductive circuit
 - Locally Matching Technique
 - Enhancement of the frequencies above millimeter-wave
 - On Real Chip Design
 - Consideration of the conductor thickness.
 - A procedure for acquiring the correct return loss level

Conventional Flip-chip Transition

- Configuration

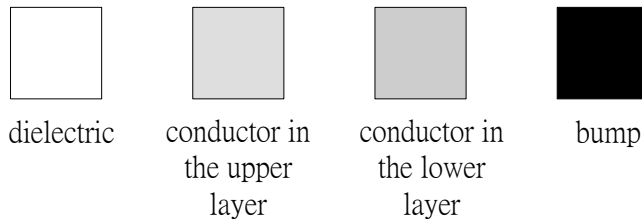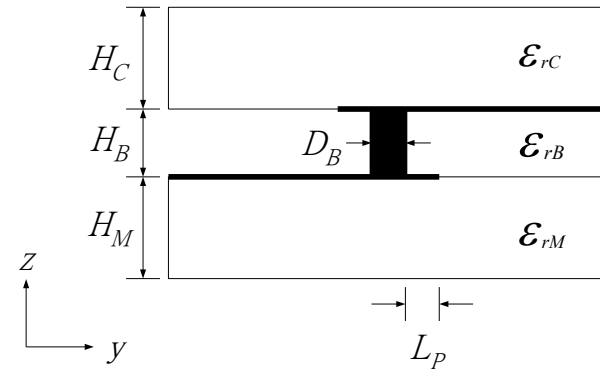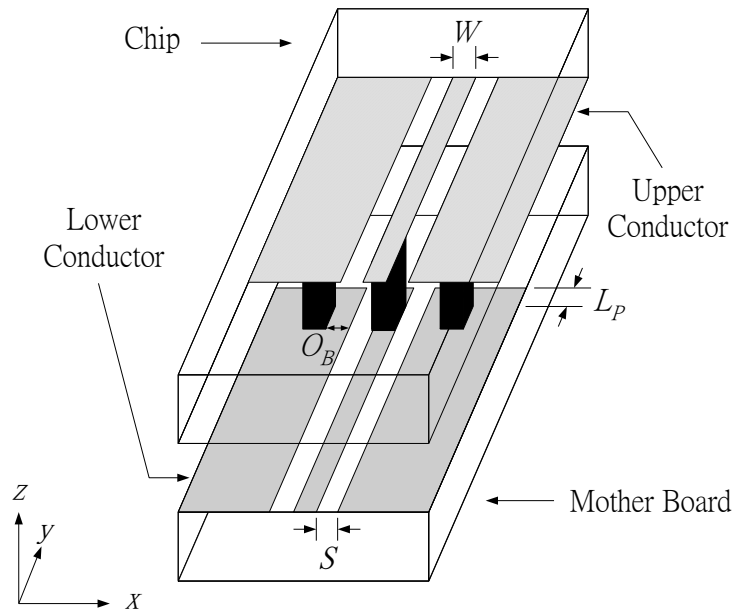
- Use Rectangular Bump Cross Section [10]



$$H_C=H_M=0.36\text{mm}, W=S=0.12\text{mm}, H_B=D_B=0.12\text{mm}, L_P=O_B=0\text{mm}, \epsilon_{rM}=12.9, \epsilon_{rB}=1, \epsilon_{rC}=12.9.$$


Conventional Flip-chip Transition

- Comparison between Different Methods

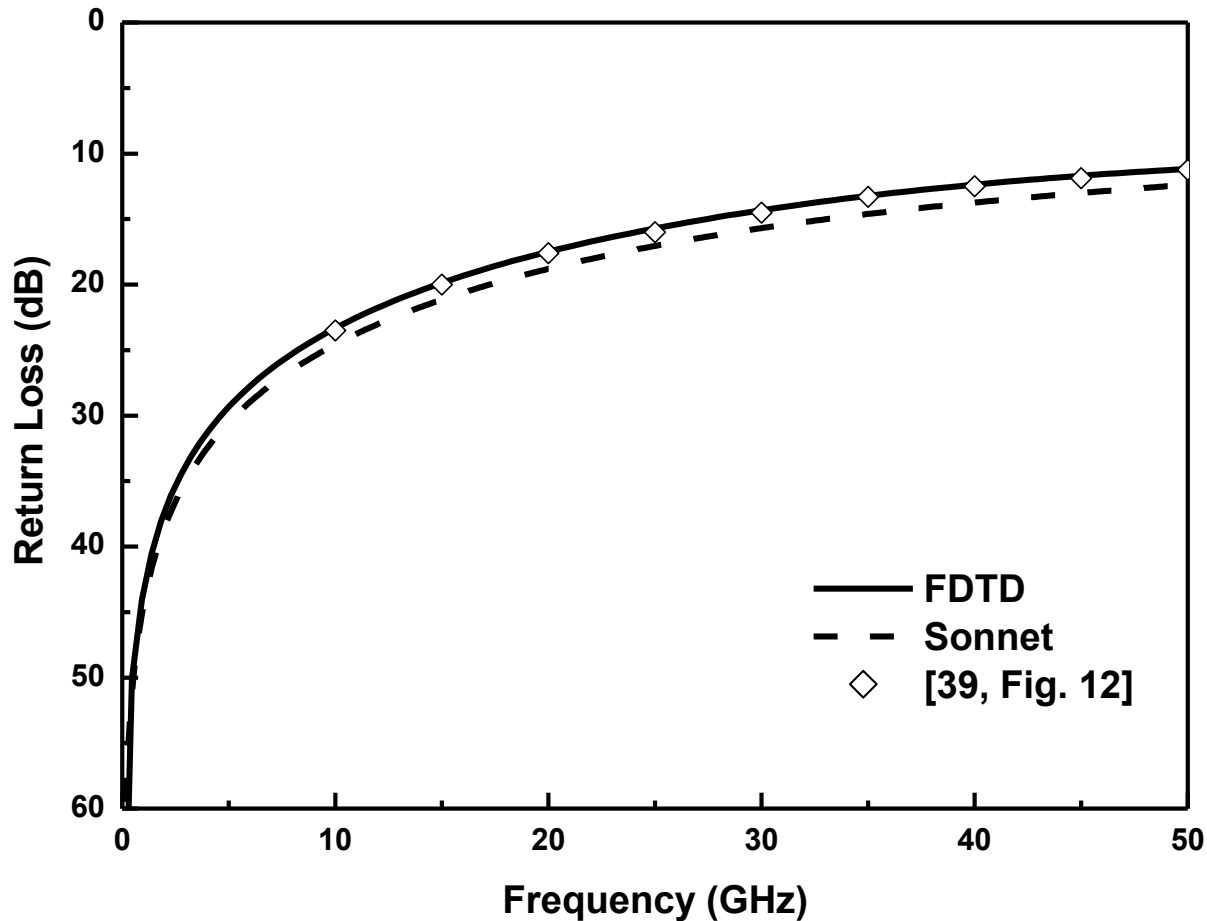


Conventional Flip-chip Transition

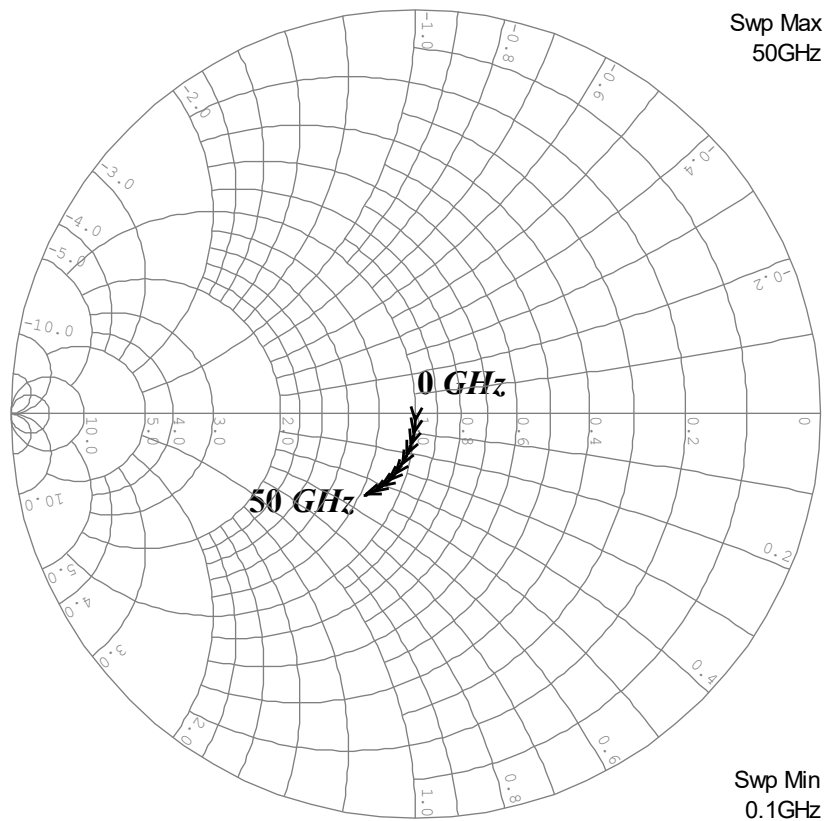- S_{11} Plotted on the Admittance Smith Chart



Conventional Flip-chip Transition

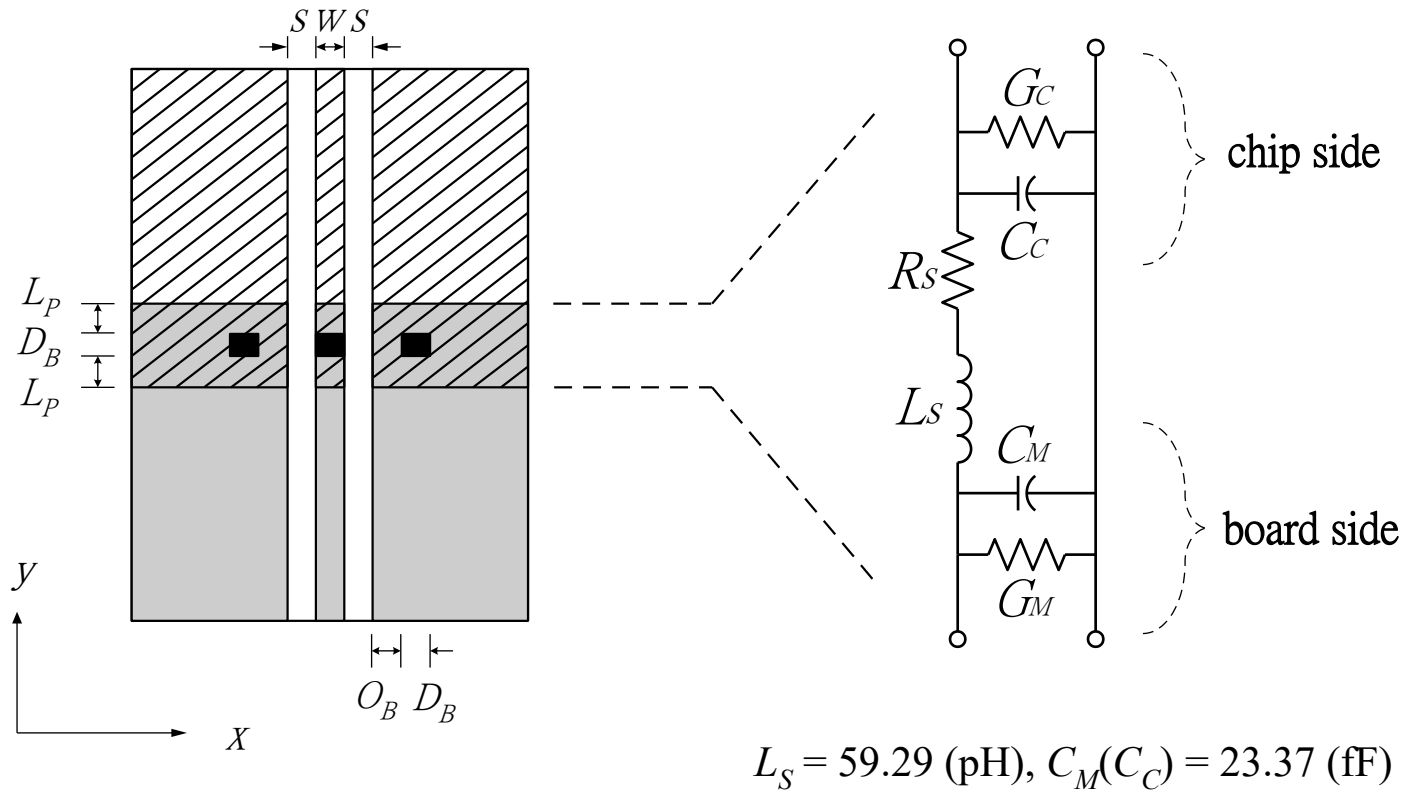
- Equivalent Circuit Model [12]
 - Extracted Using ABCD Matrix by Least Square Method



Conventional Flip-chip Transition

- Return Loss of Equivalent Circuit Model [11]


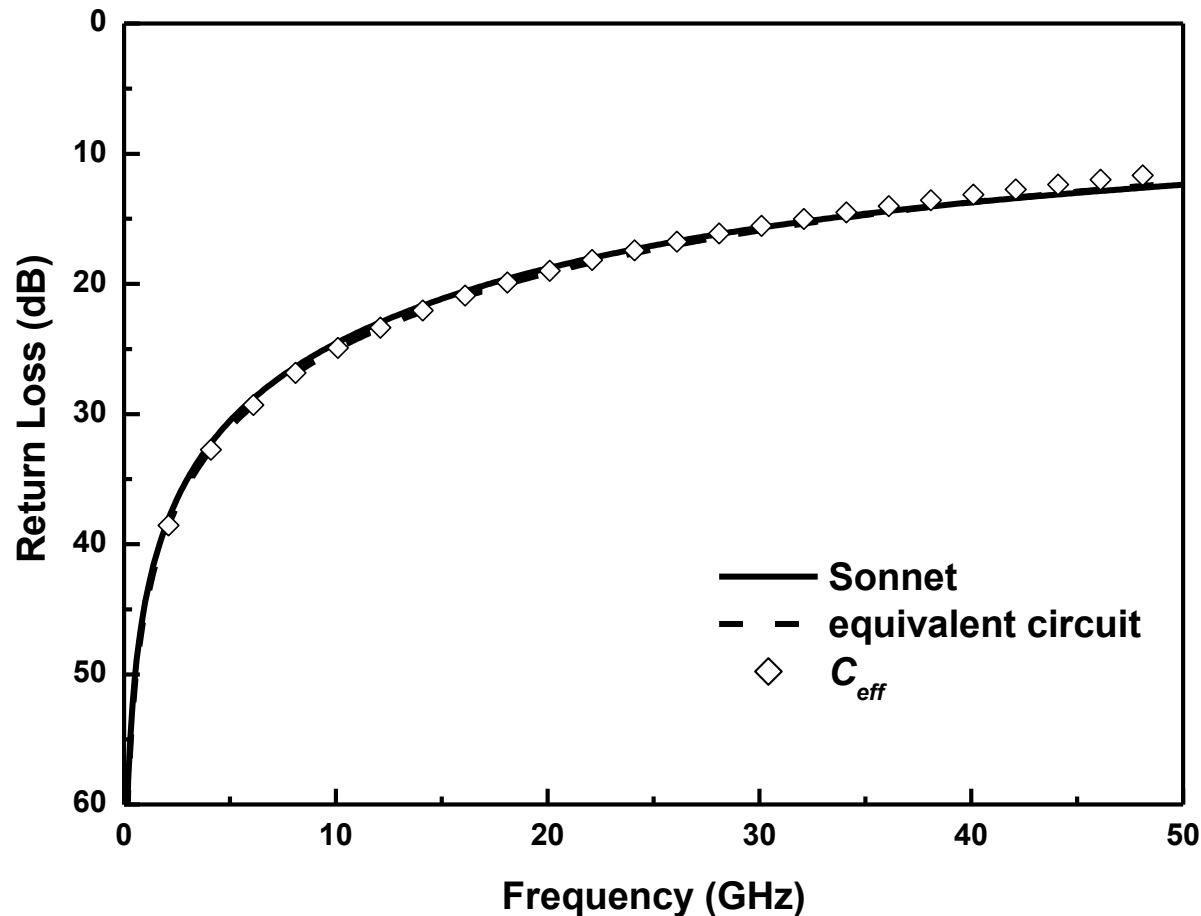
$$C_{eff} = (C_M + C_C) - \frac{L_S}{Z_0^2} = 29.11 \text{ (fF)}$$



Conventional Flip-chip Transition

- The Influence of Bump Diameter D_B on L_S and $C_M(C_C)$

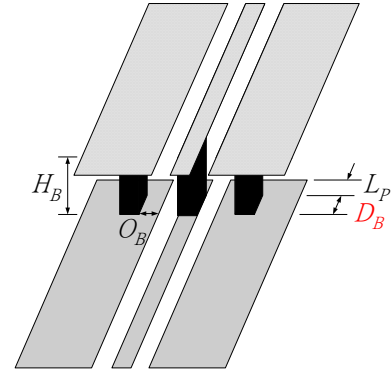
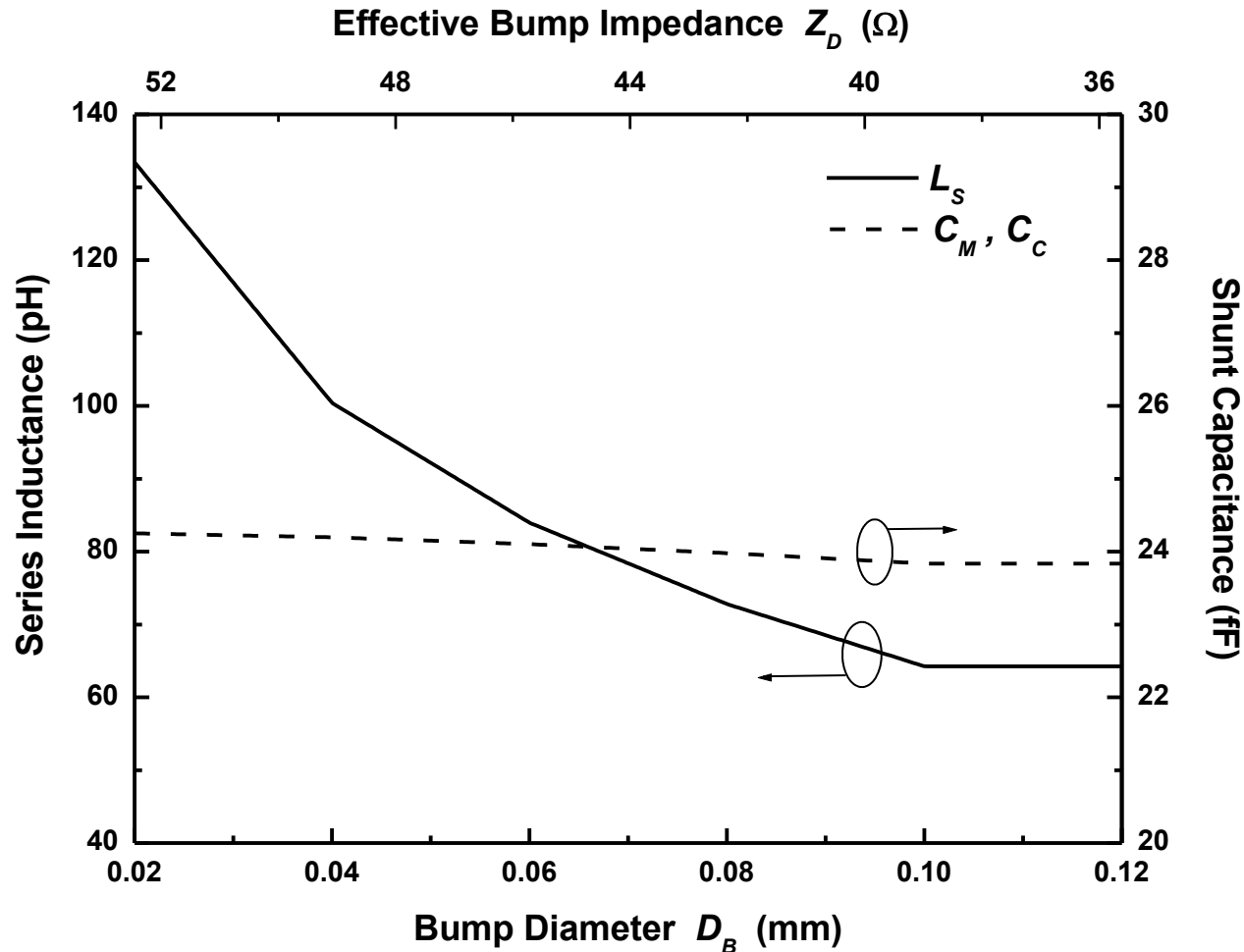
– $H_B=0.12\text{mm}$, $L_P=O_B=0\text{mm}$ $Z_D = \sqrt{L_S / (C_M + C_C)}$



Conventional Flip-chip Transition

- The Influence of Bump Height H_B on L_S and $C_M(C_C)$

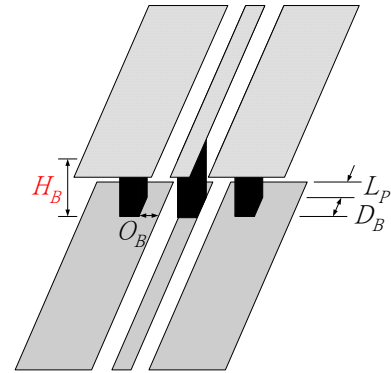
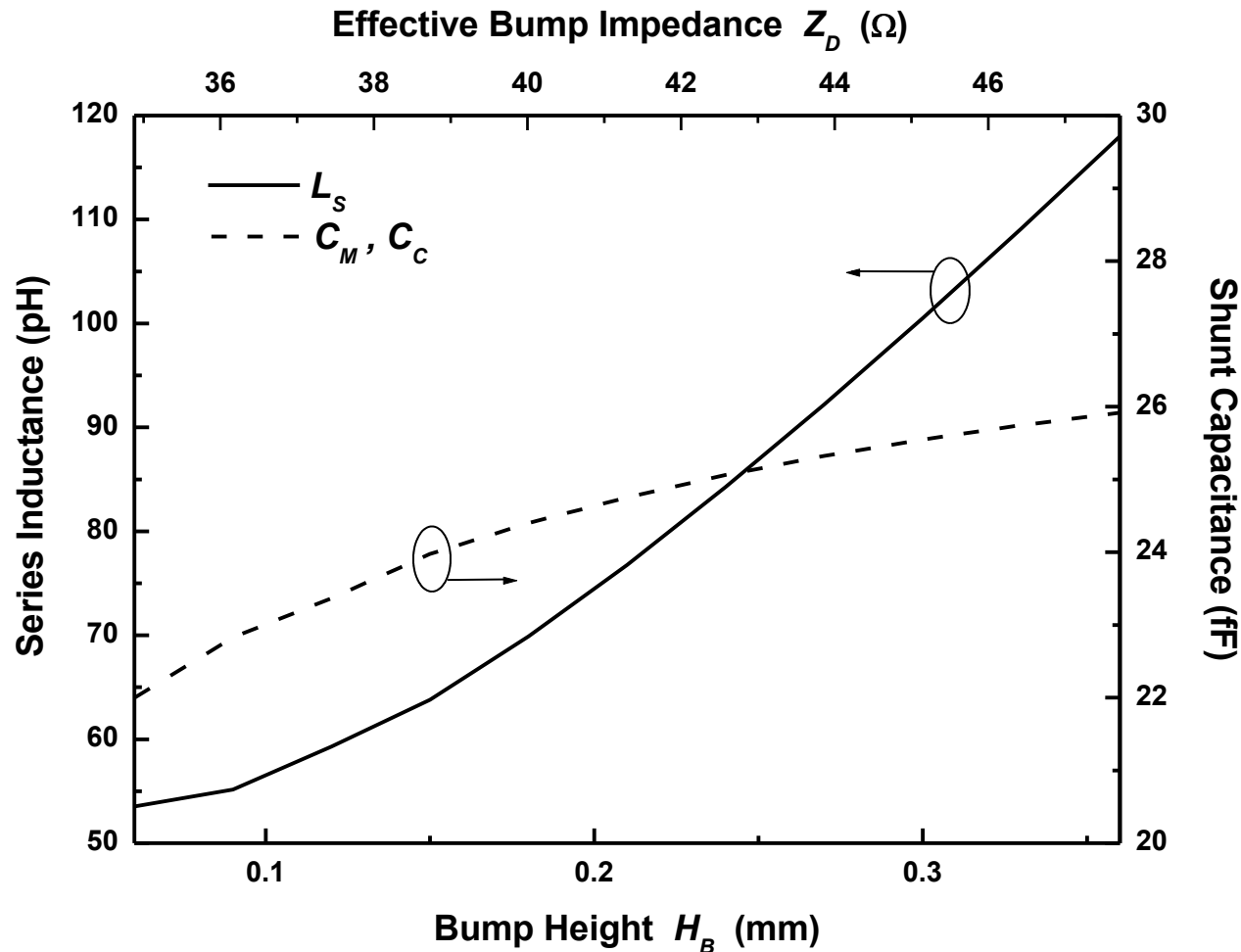
– $D_B=0.12\text{mm}$, $L_P=O_B=0\text{mm}$



Conventional Flip-chip Transition

- The Influence of Bump Pad Length L_P on L_S and $C_M(C_C)$

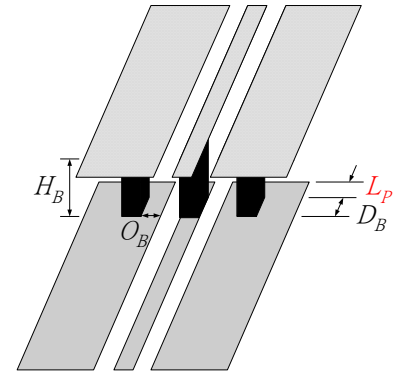
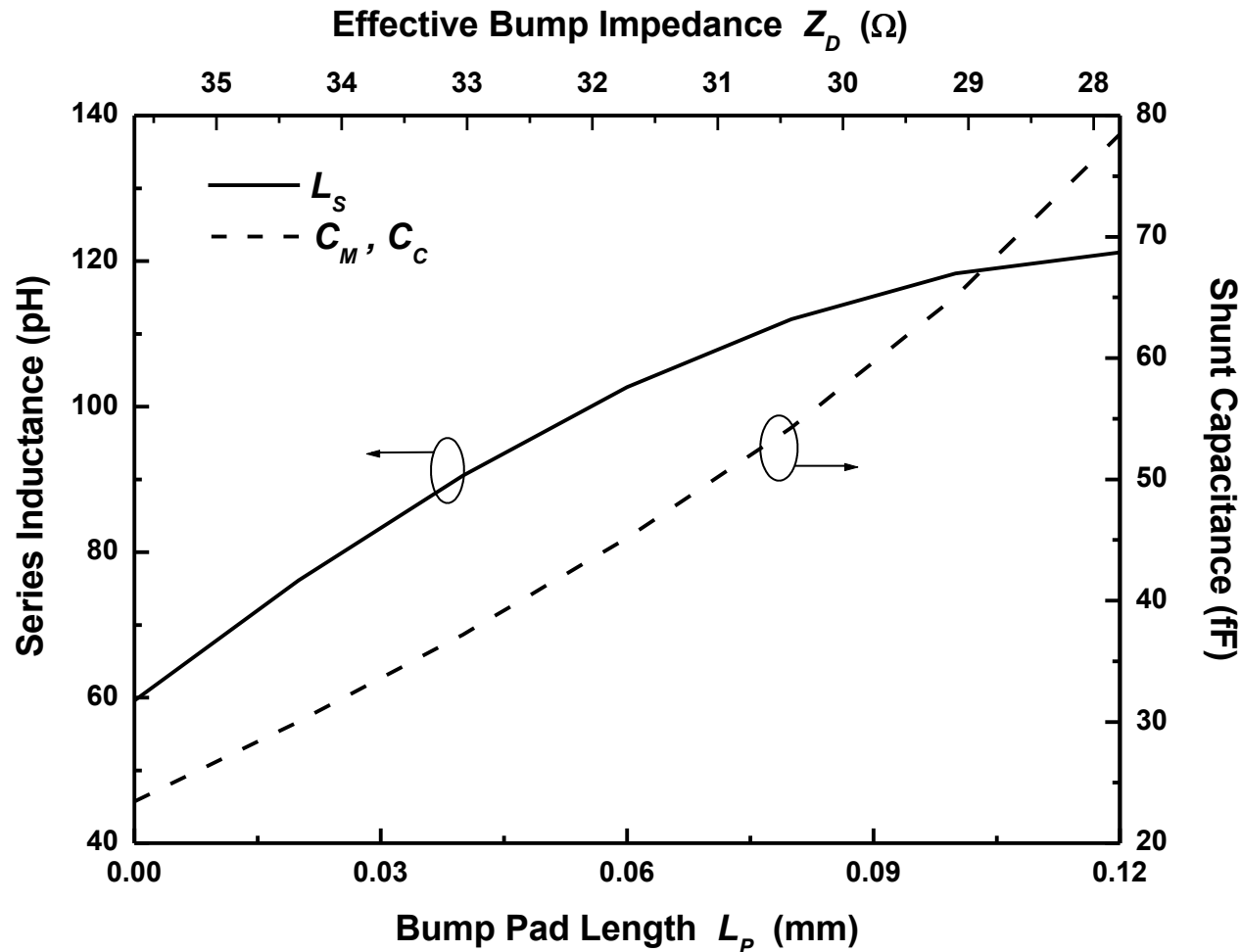
– $H_B = D_B = 0.12\text{mm}$, $O_B = 0\text{mm}$



Conventional Flip-chip Transition

- The Influence of Bump Offset O_B on L_S and $C_M(C_C)$

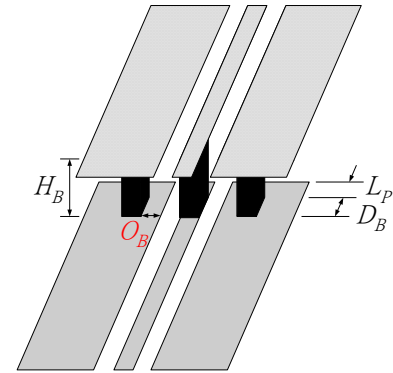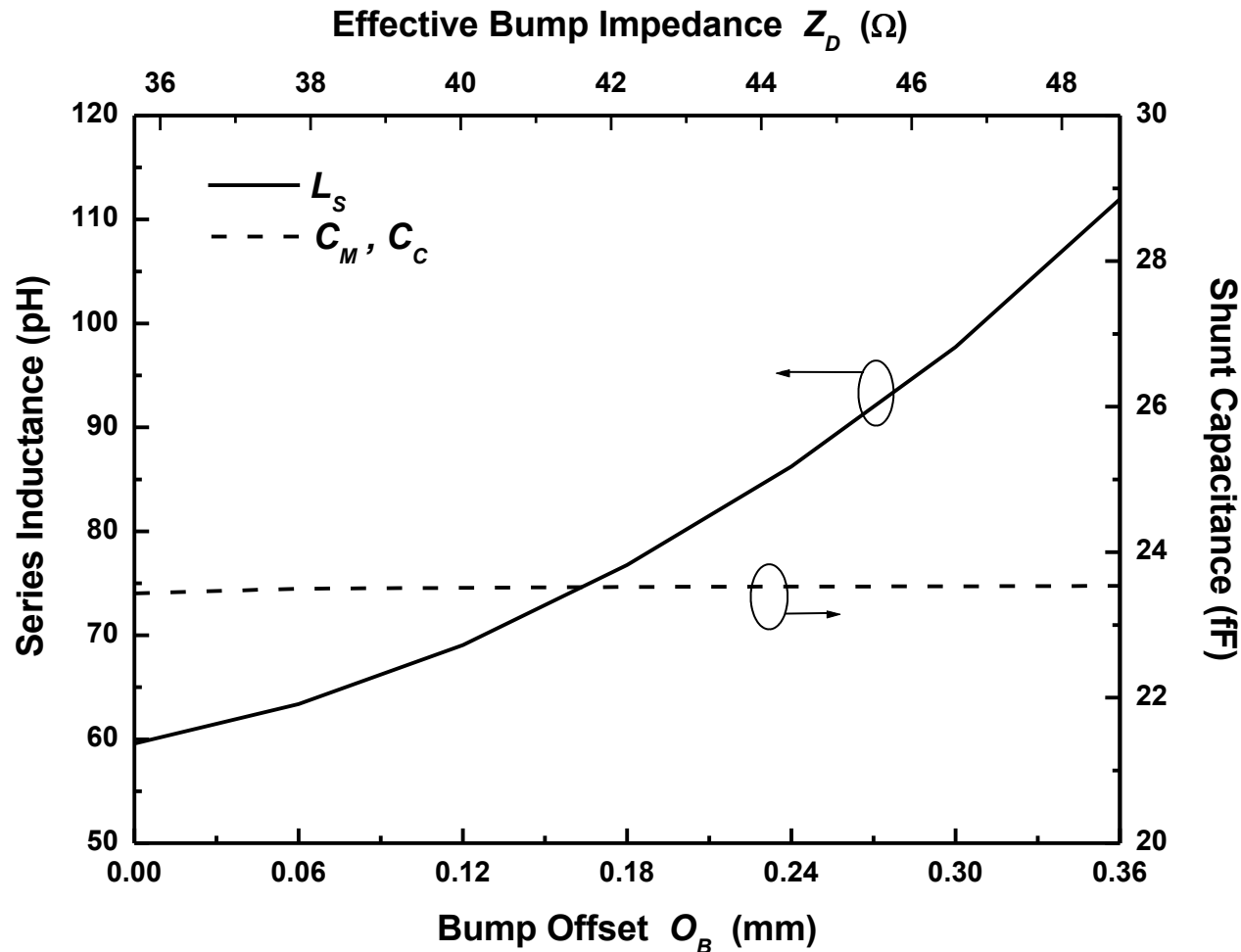– $H_B = D_B = 0.12\text{mm}$, $L_P = 0\text{mm}$




Conventional Flip-chip Transition

- Summary
 - Three methods are in a good agreement.
 - The equivalent circuit resembles a low pass prototype
 - The conventional flip-chip possesses a capacitive effect
 - Ways to lower down the capacitive effect:
 - Reduce the Bump Diameter
 - Lengthen the Bump Height
 - Minimize the Bump Pad Length
 - Maximize the Bump Offset

Resonant Flip-chip Transition

- Single Resonance Design
 - Simulated via FDTD
 - Control of Resonant Length ($L_{stg} * 2 + D_B$)
 - Sacrifice of Chip Areas

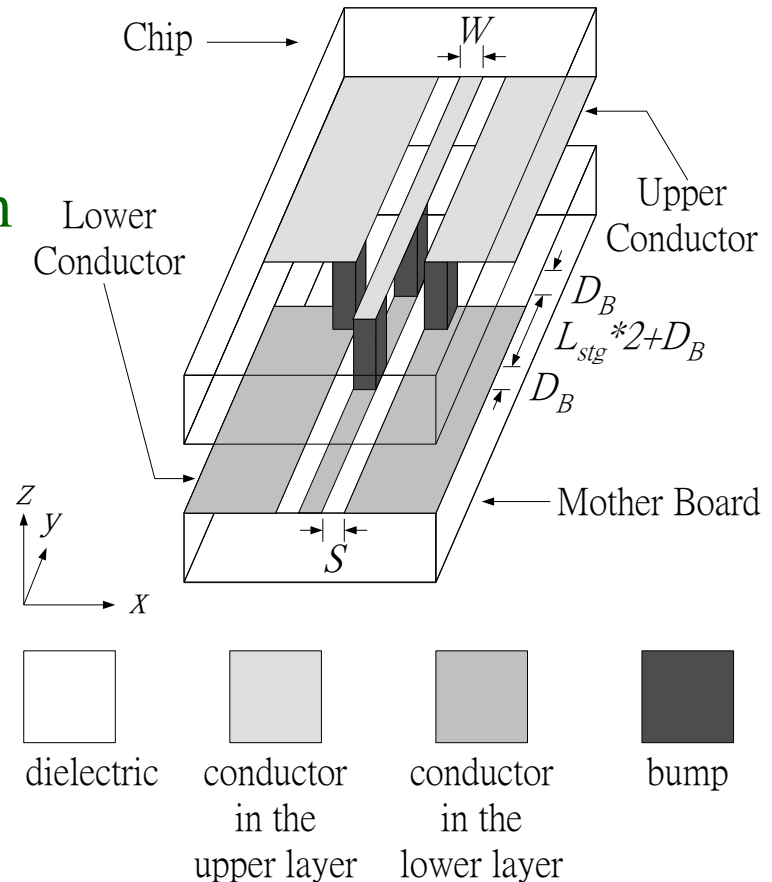
$W=S=D_B=0.12\text{mm}$, other parameters are the same as conventional



Resonant Flip-chip Transition

- Return Loss


	f_0 (GHz)	20dB BW (%)
$L_{stg}=0.24$ mm	68.21	26.17
$L_{stg}=0.48$ mm	38.91	17.65
$L_{stg}=0.96$ mm	22.89	18.67

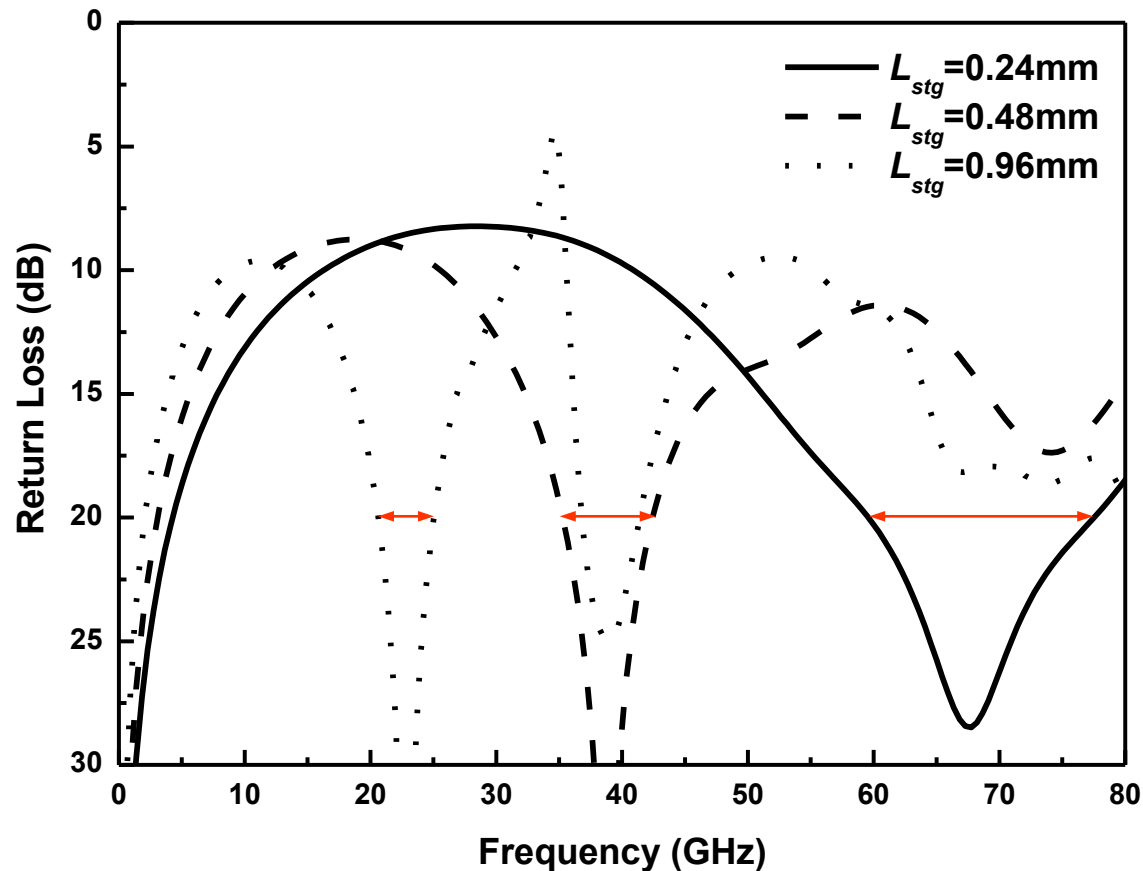

Resonant Flip-chip Transition

- Design Chart

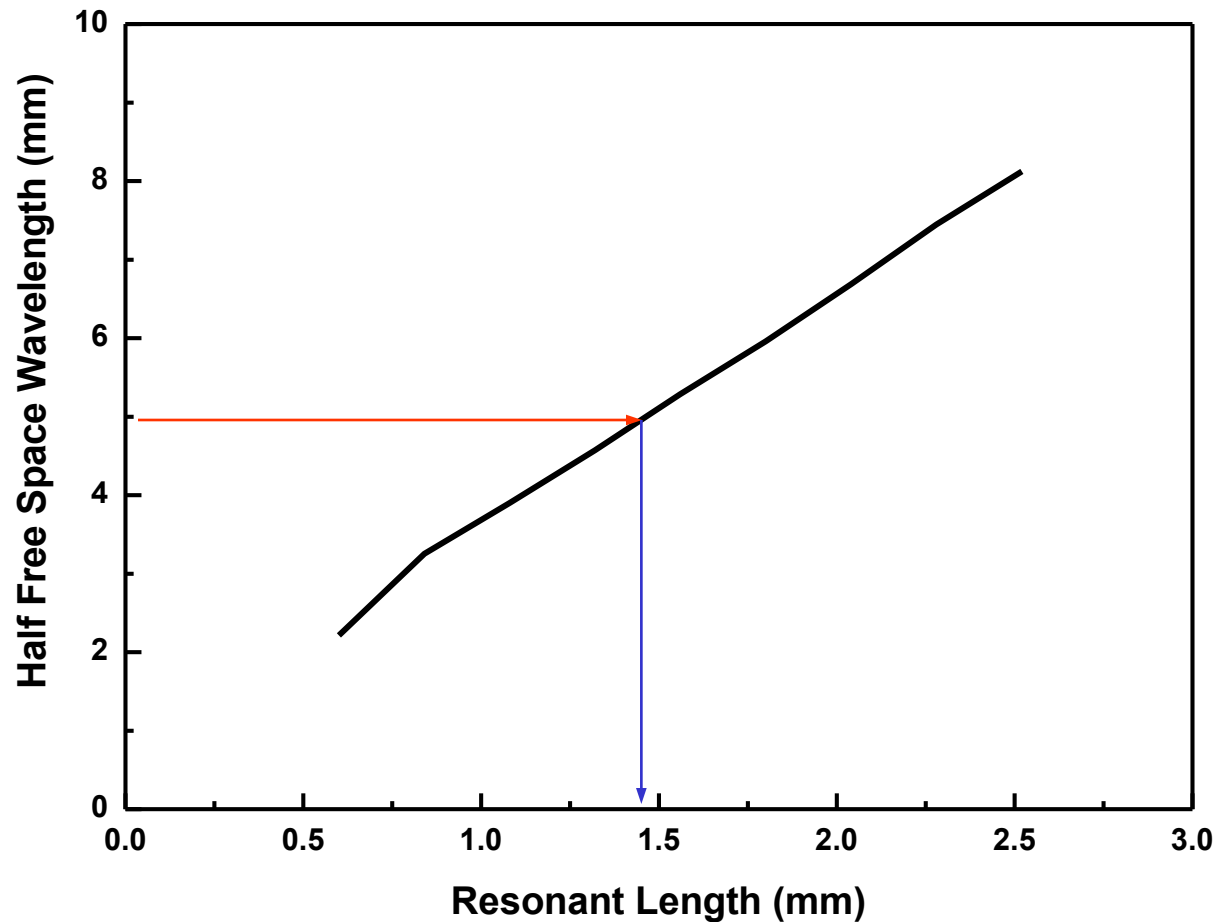
- $\lambda_0/2$ versus Resonance Length ($L_{stg} * 2 + D_B$)



Resonant Flip-chip Transition


- Insertion Loss

	IL at f_0 (dB)	IL in 20dB BW (dB)
$L_{stg}=0.24$ mm	0.81	<1.46
$L_{stg}=0.48$ mm	0.30	<0.47
$L_{stg}=0.96$ mm	0.02	<0.06

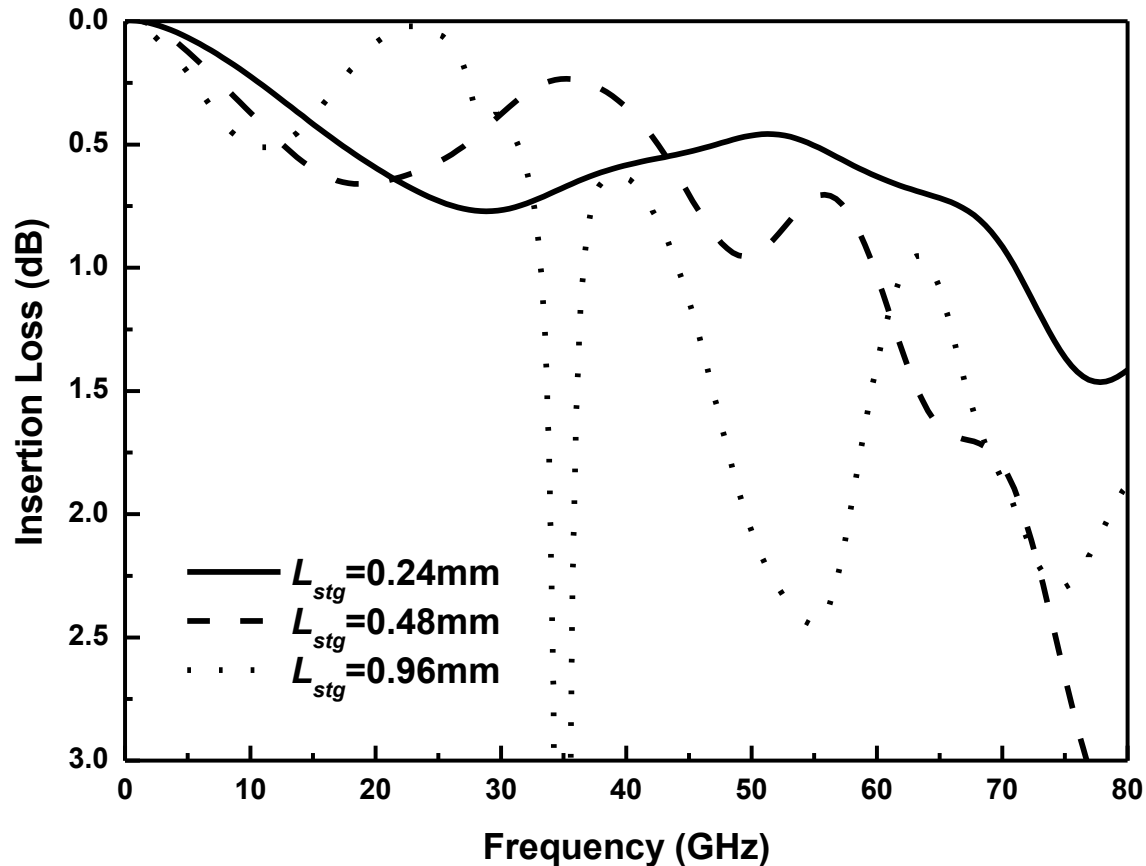

Resonant Flip-chip Transition

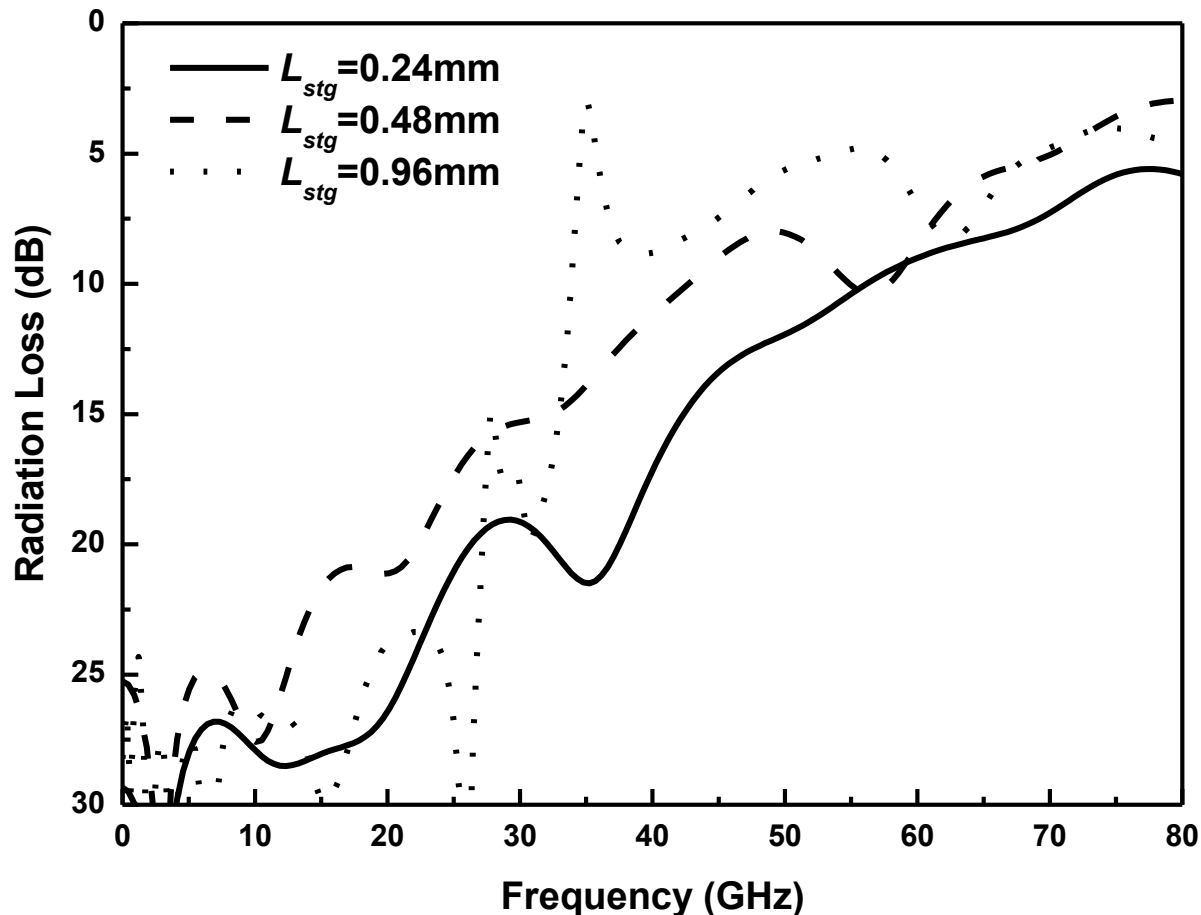
- Radiation Loss
 - Severe above Millimeter-wave Frequencies



Resonant Flip-chip Transition


- Discrete Equivalent Circuit
 - Simulated by Sonnet and Extracted via LSM

C_{M1} (fF)	L_1 (pH)	C_{C1} (fF)	Z_1 (Ω)	ϵ_{eff1}	C_{C2} (fF)	L_2 (pH)
21.01	48.04	14.42	40.07	7.70	22.83	65.17

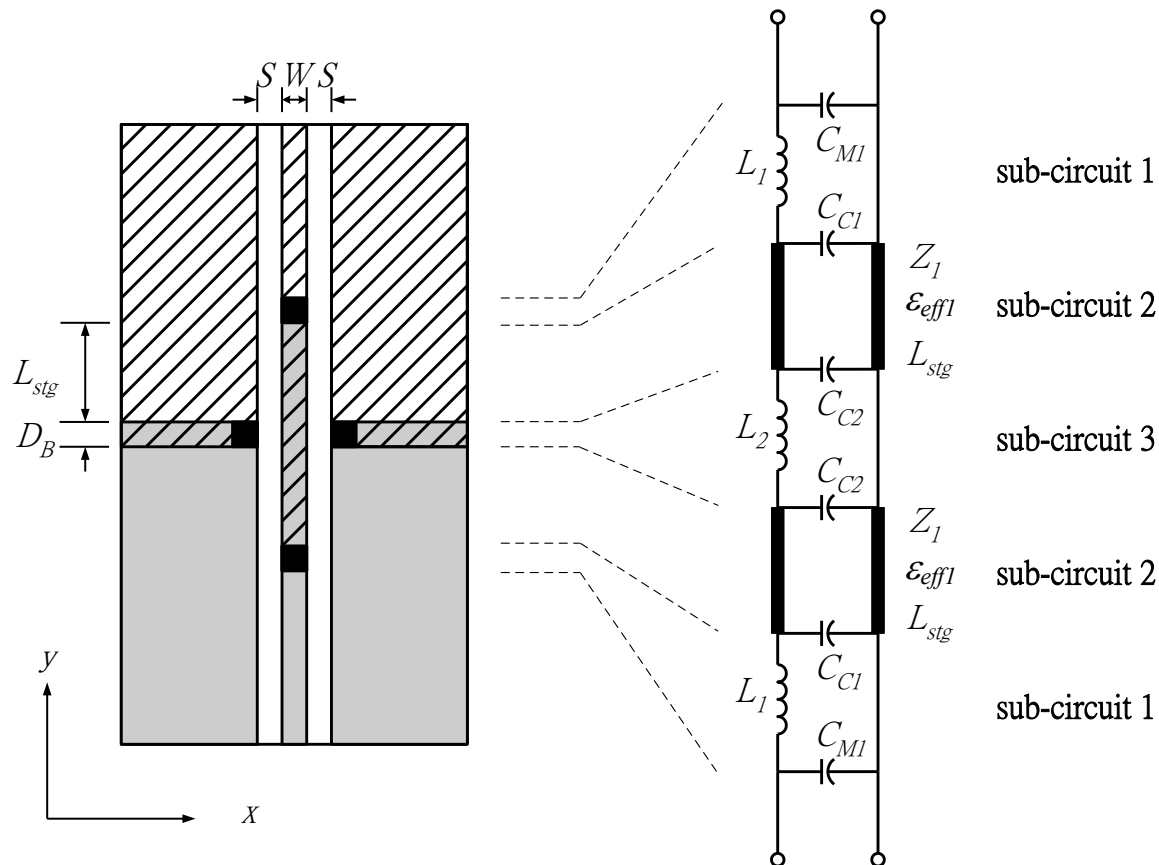


Resonant Flip-chip Transition

- Comparison for $L_{stg}=0.24\text{mm}$

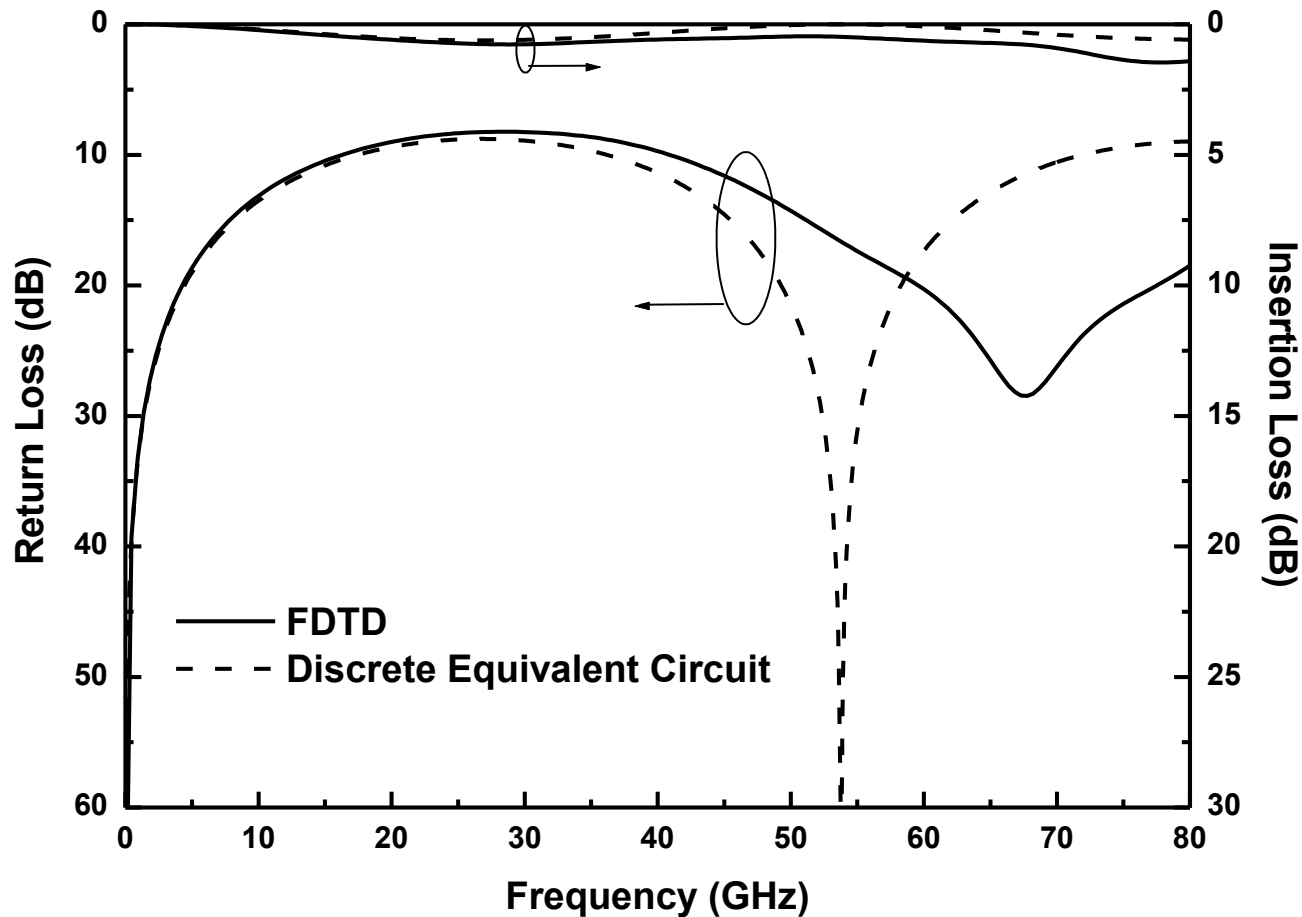


Resonant Flip-chip Transition

- Comparison for $L_{stg}=0.48\text{mm}$

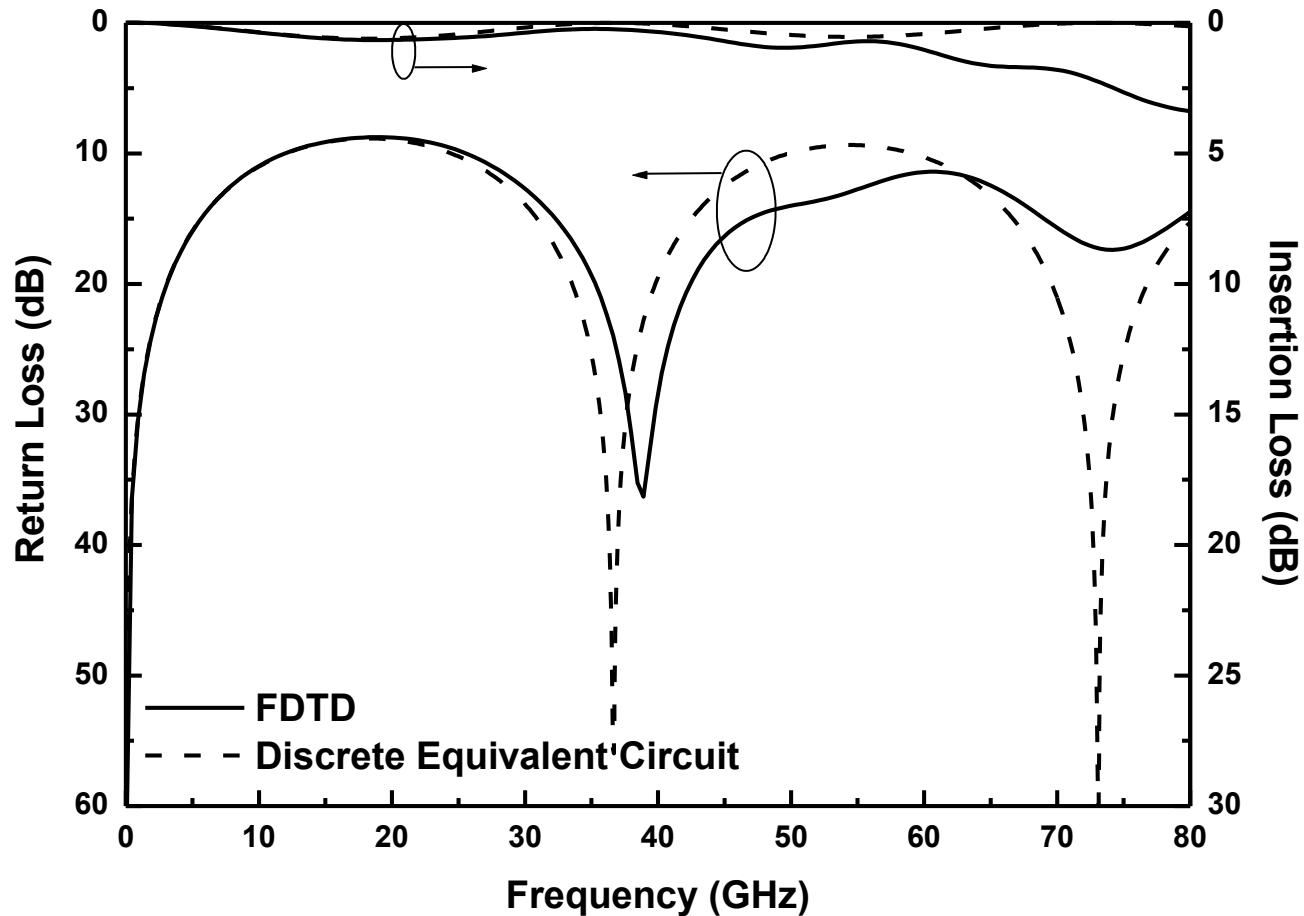

Resonant Flip-chip Transition


- Comparison for $L_{stg}=0.96\text{mm}$

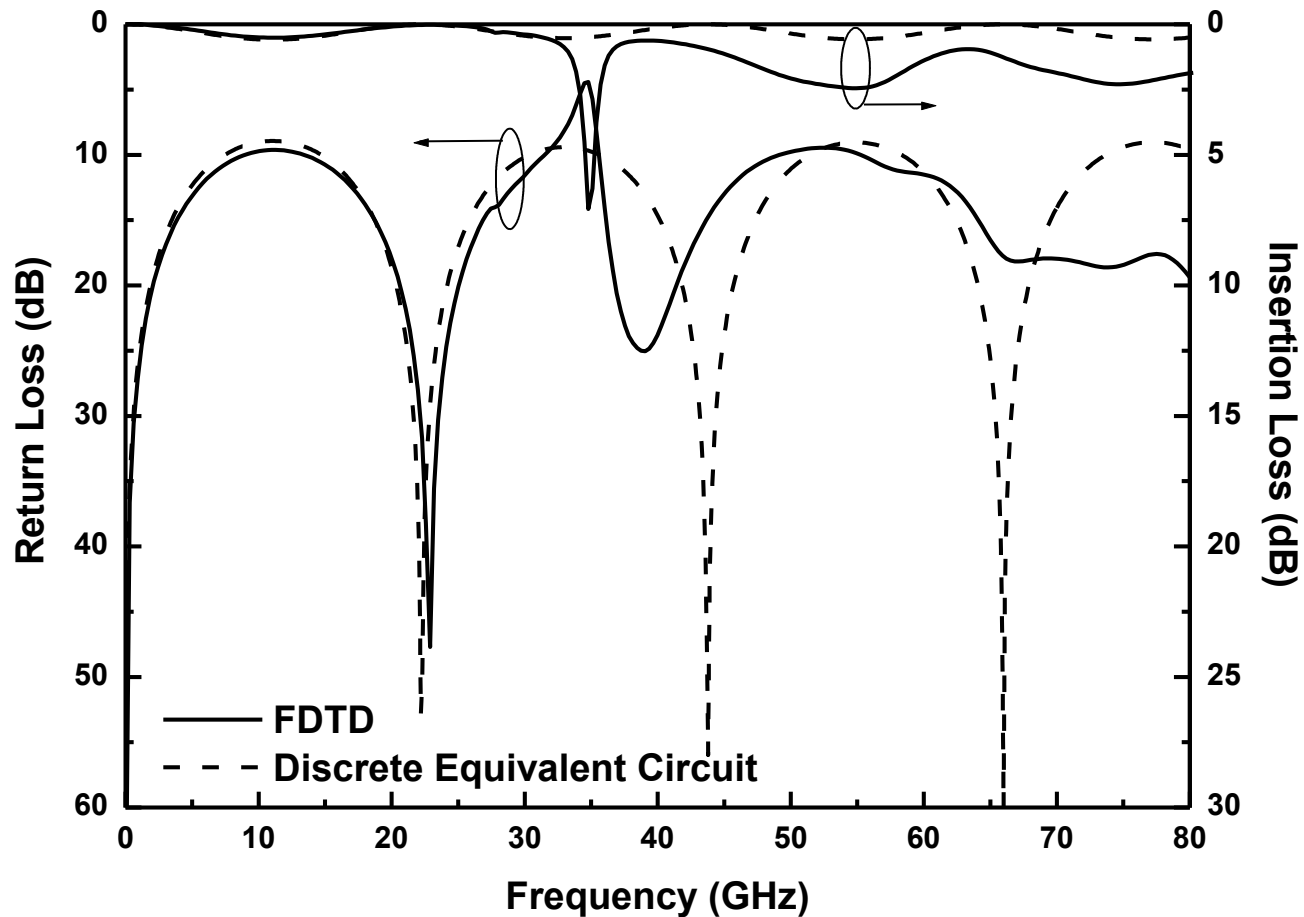

Resonant Flip-chip Transition

- Optimum Results


	$L_{stg}=0.24$ mm	$L_{stg}=0.48$ mm	$L_{stg}=0.96$ mm
Z_l (Ω)	67.50	59.10	56.60
20dB Bound (GHz)	45.50	36.30	34.30

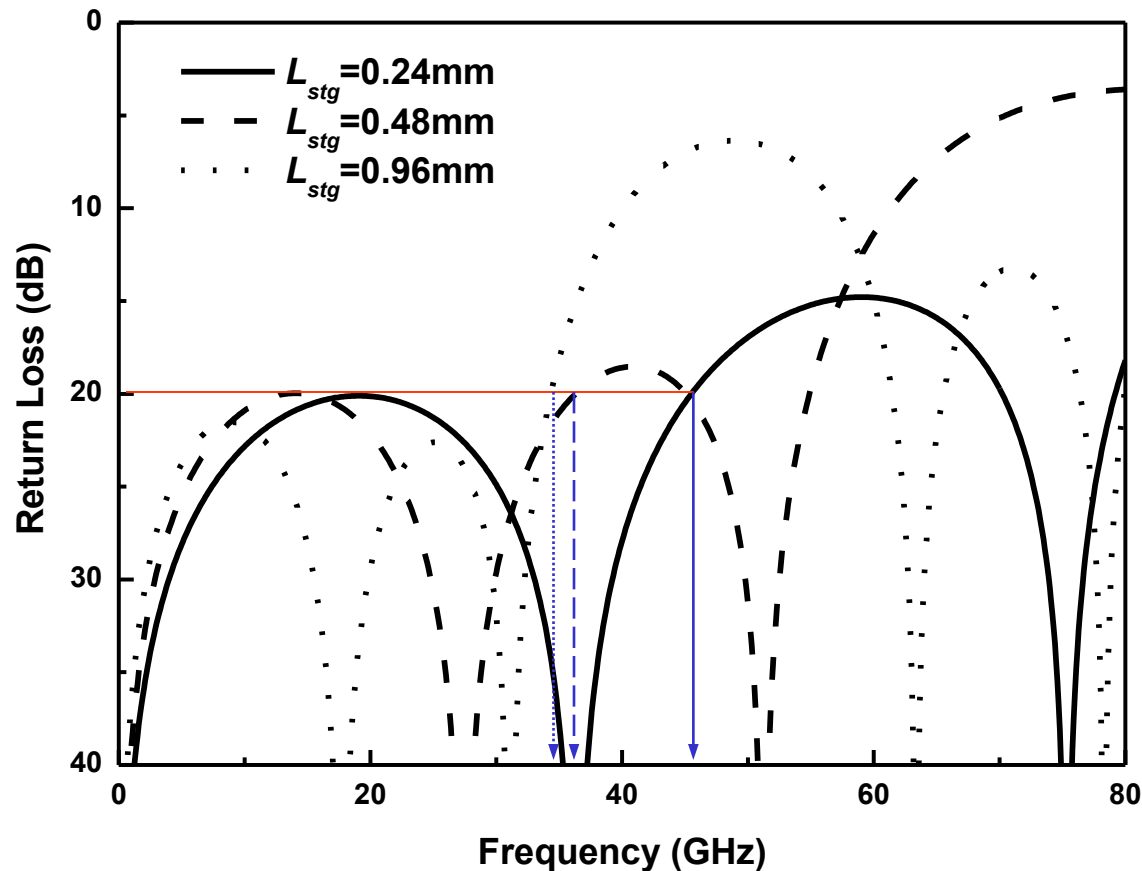

Resonant Flip-chip Transition

- Transformer Design
 - Simulated via FDTD
 - Impedance Transformer Idea
 - Sacrifice of Chip Areas
 - Better Field Confinement

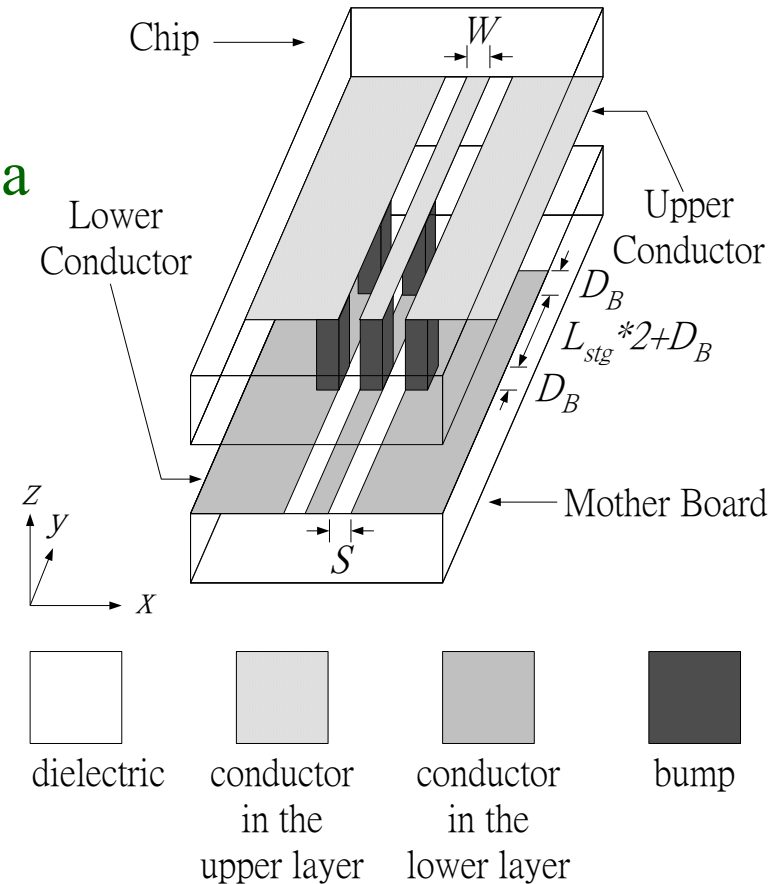$W=S=D_B=0.12\text{mm}$, other parameters are the same as conventional




Resonant Flip-chip Transition

- Return Loss

- 20 dB Bandwidth: 11.5%


	f_0 (GHz)
$L_{stg}=0.24$ mm	55.54
$L_{stg}=0.48$ mm	36.32
$L_{stg}=0.96$ mm	21.67

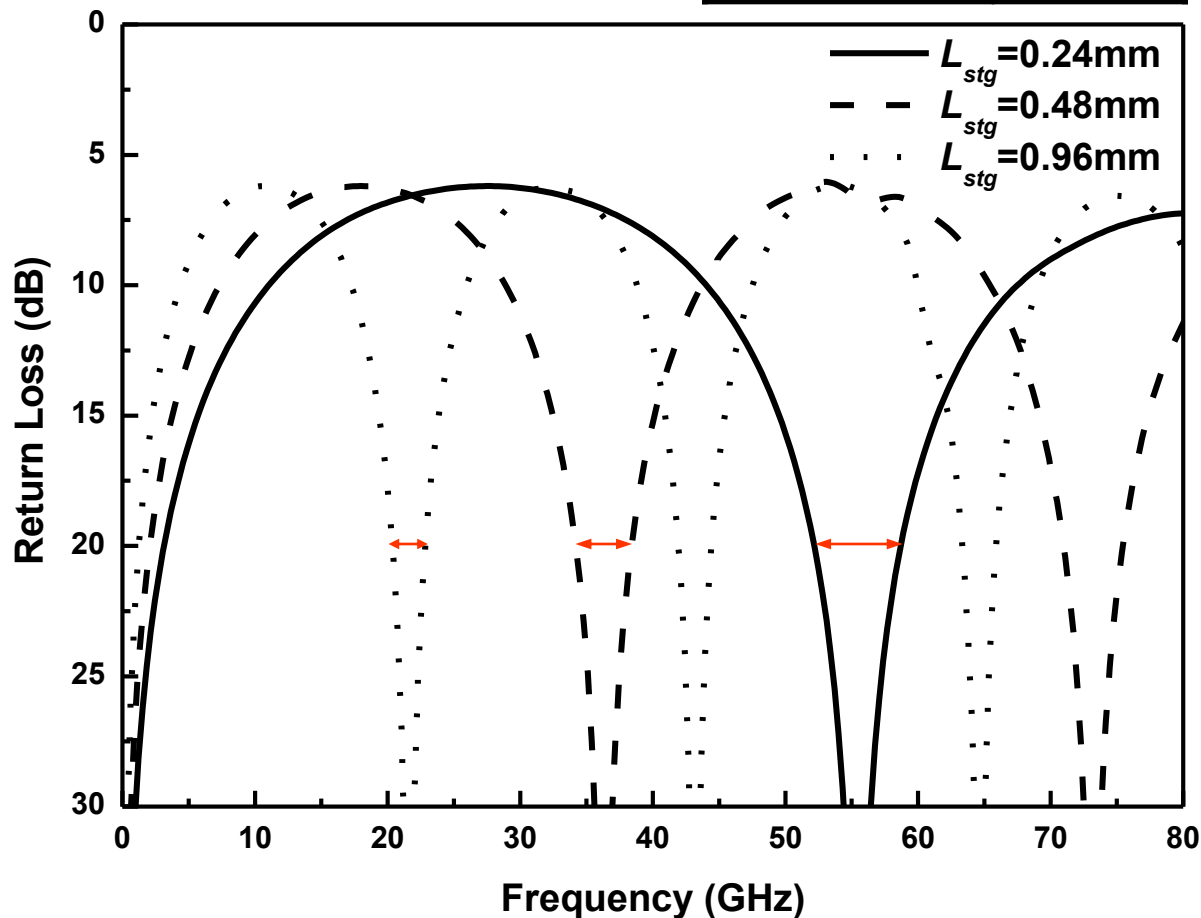

Resonant Flip-chip Transition


- Design Chart

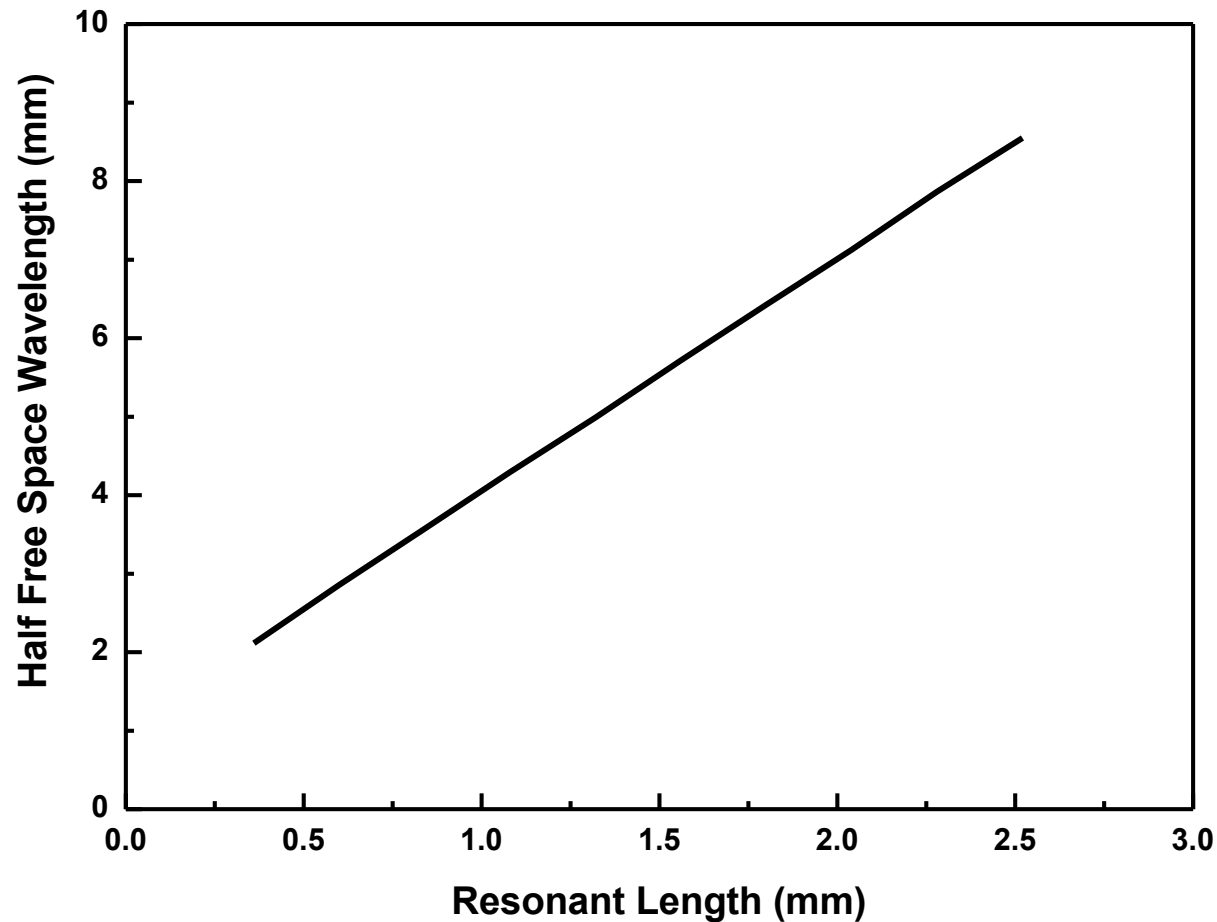- $\lambda_0/2$ versus Resonance Length ($L_{stg} * 2 + D_B$)




Resonant Flip-chip Transition

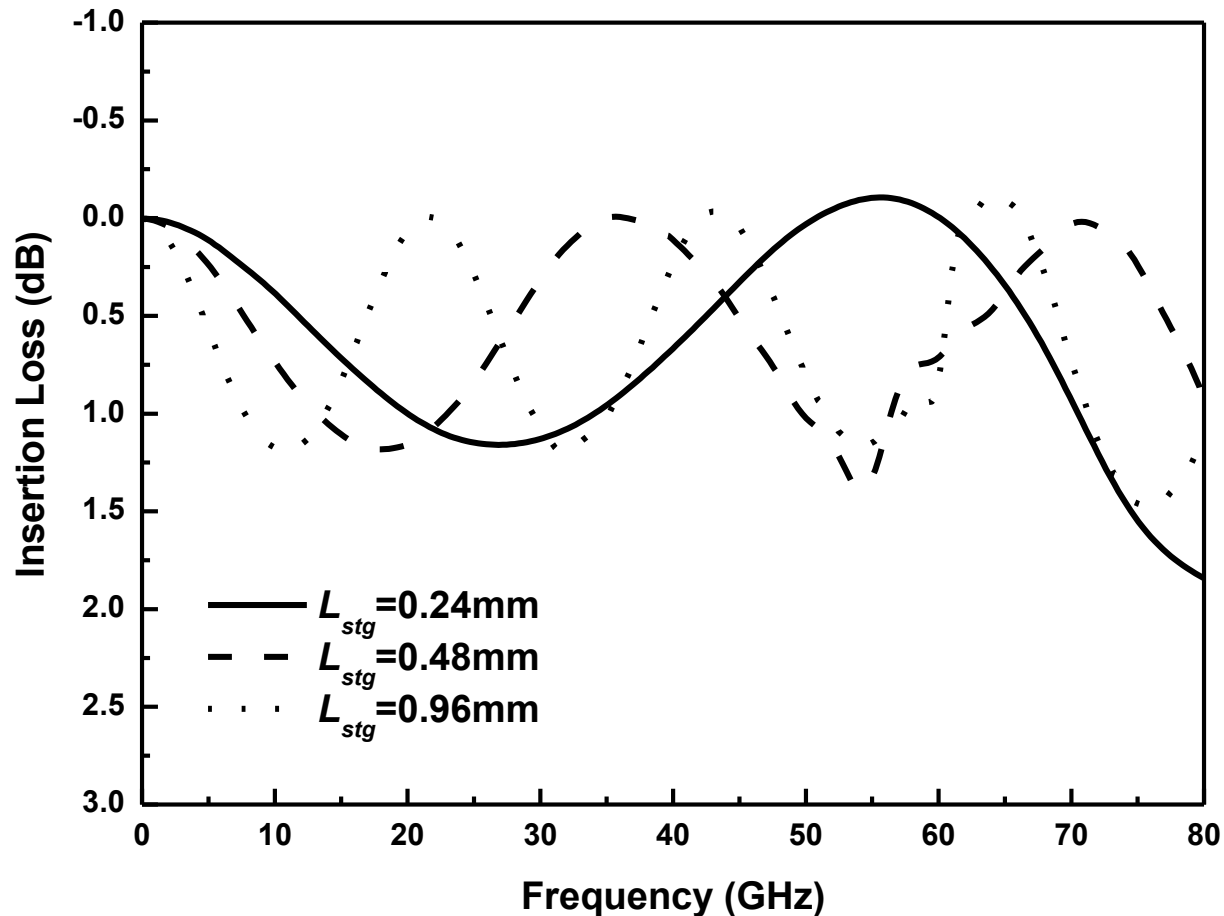- Insertion Loss
 - IL in 20 dB Bandwidth > 0.05 dB



Resonant Flip-chip Transition


- Radiation Loss
 - Severe above 60 GHz

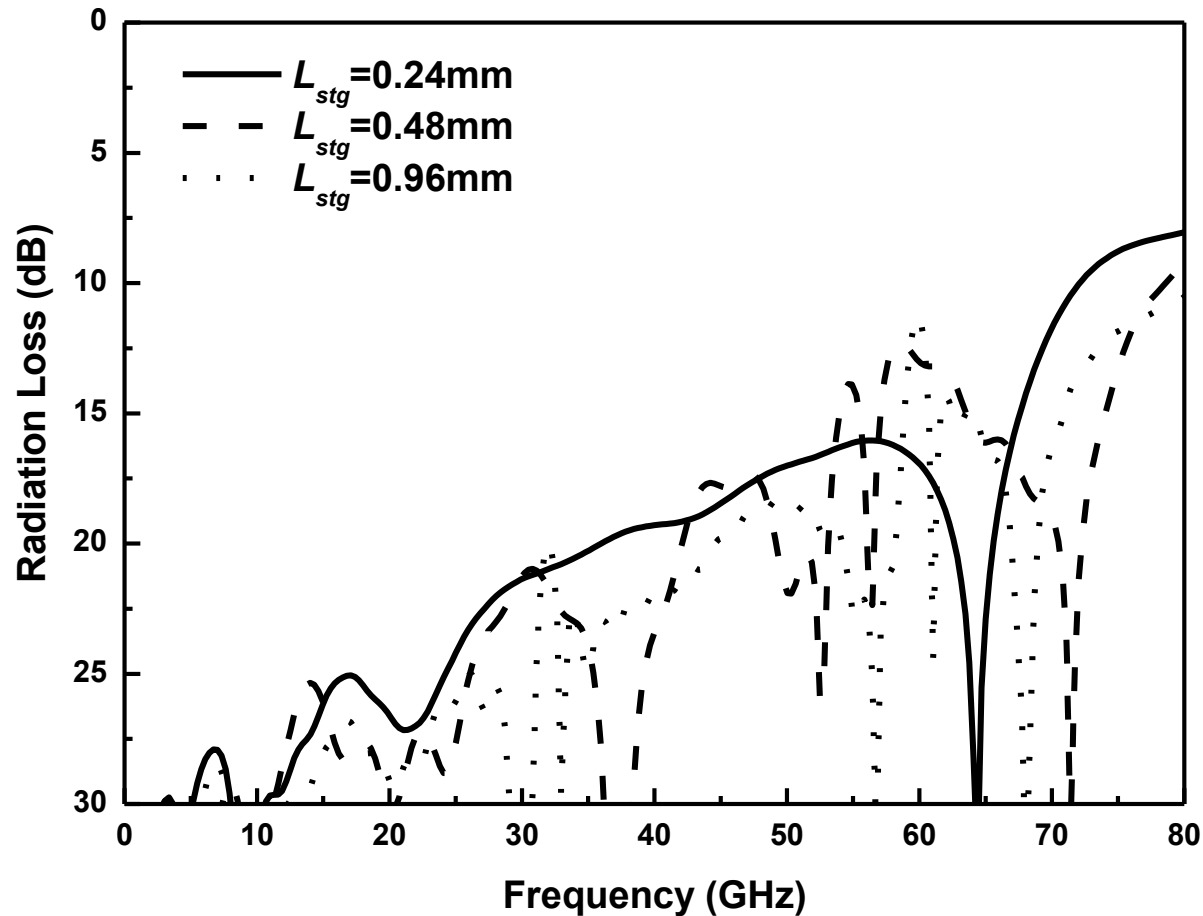

Resonant Flip-chip Transition


- Discrete Equivalent Circuit
 - Simulated by Sonnet and Extracted via LSM

C_{M3} (fF)	L_3 (pH)	C_{C3} (fF)	Z_2 (Ω)	ϵ_{eff2}
23.05	41.42	18.32	37.78	8.45

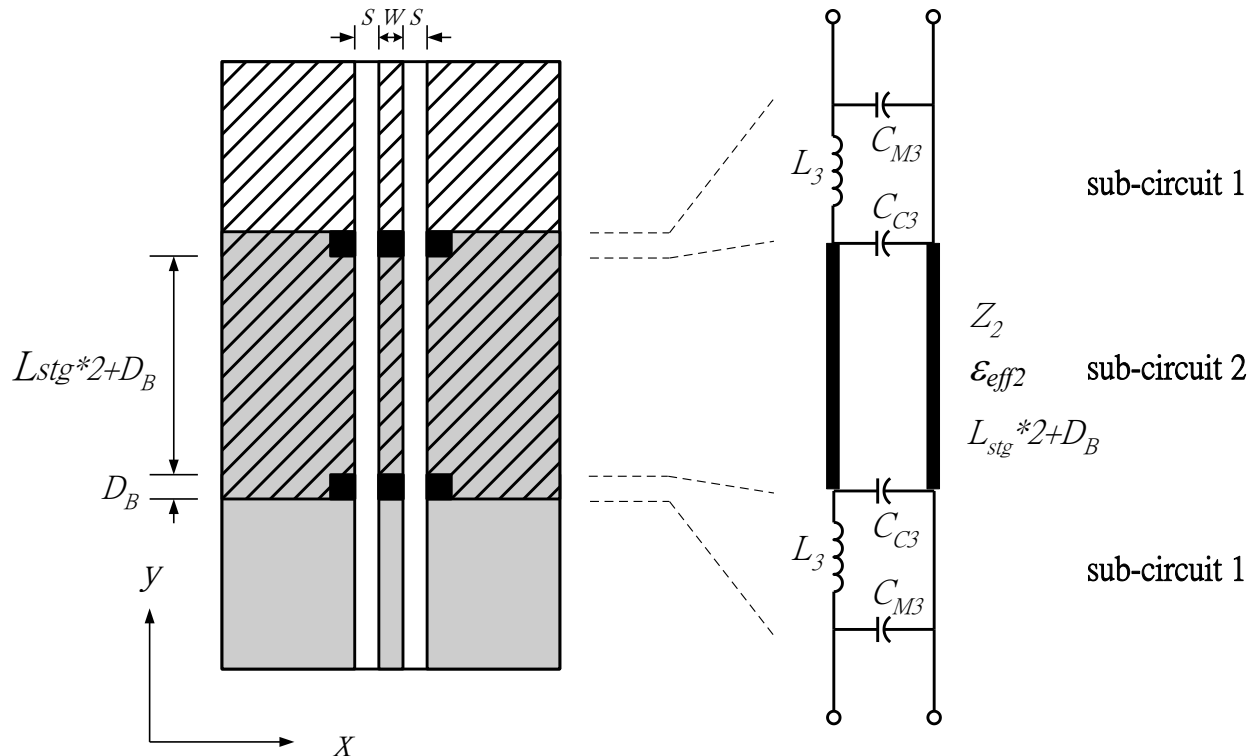


Resonant Flip-chip Transition

- Comparison for $L_{stg}=0.24\text{mm}$

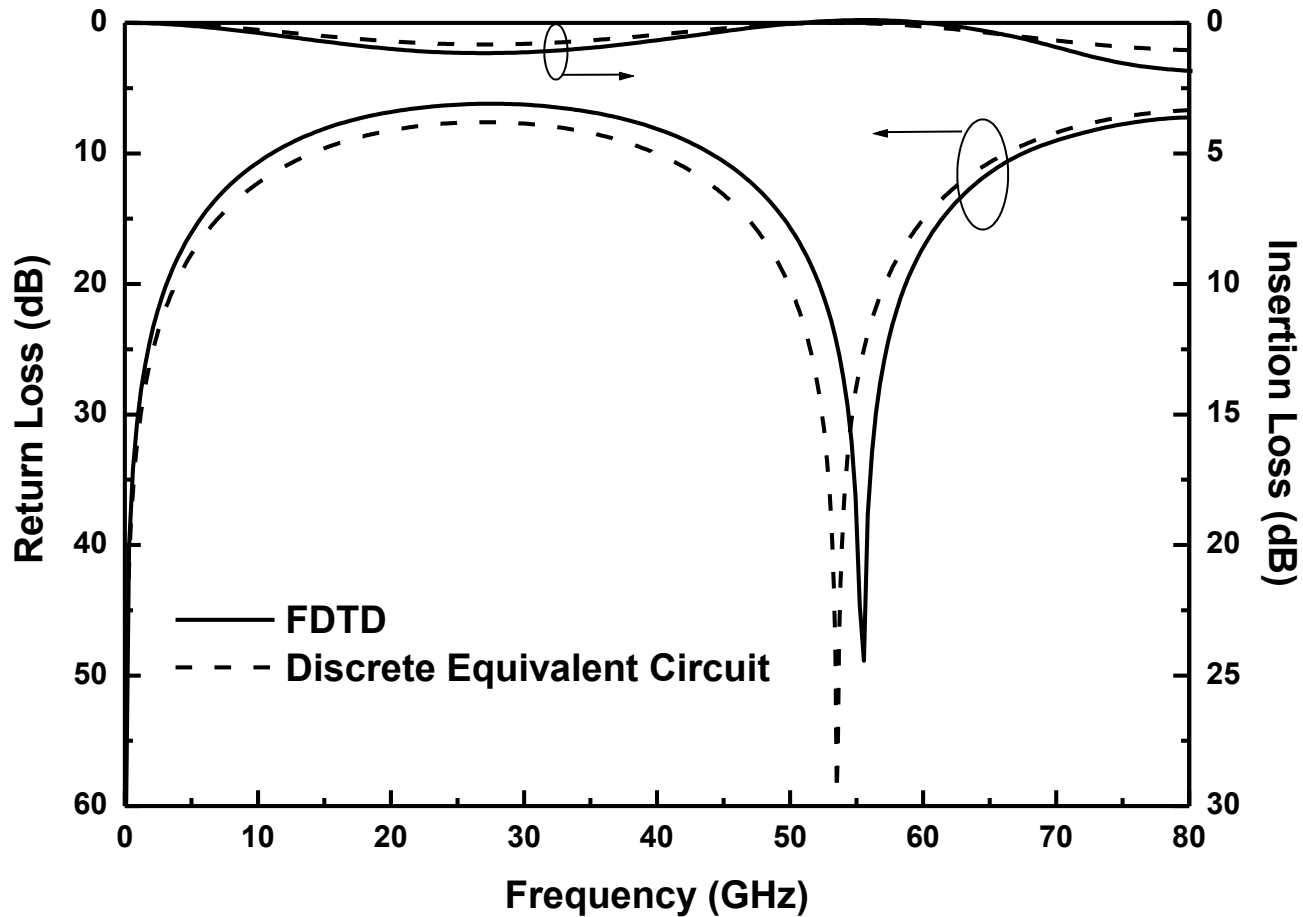


Resonant Flip-chip Transition

- Comparison for $L_{stg}=0.48\text{mm}$

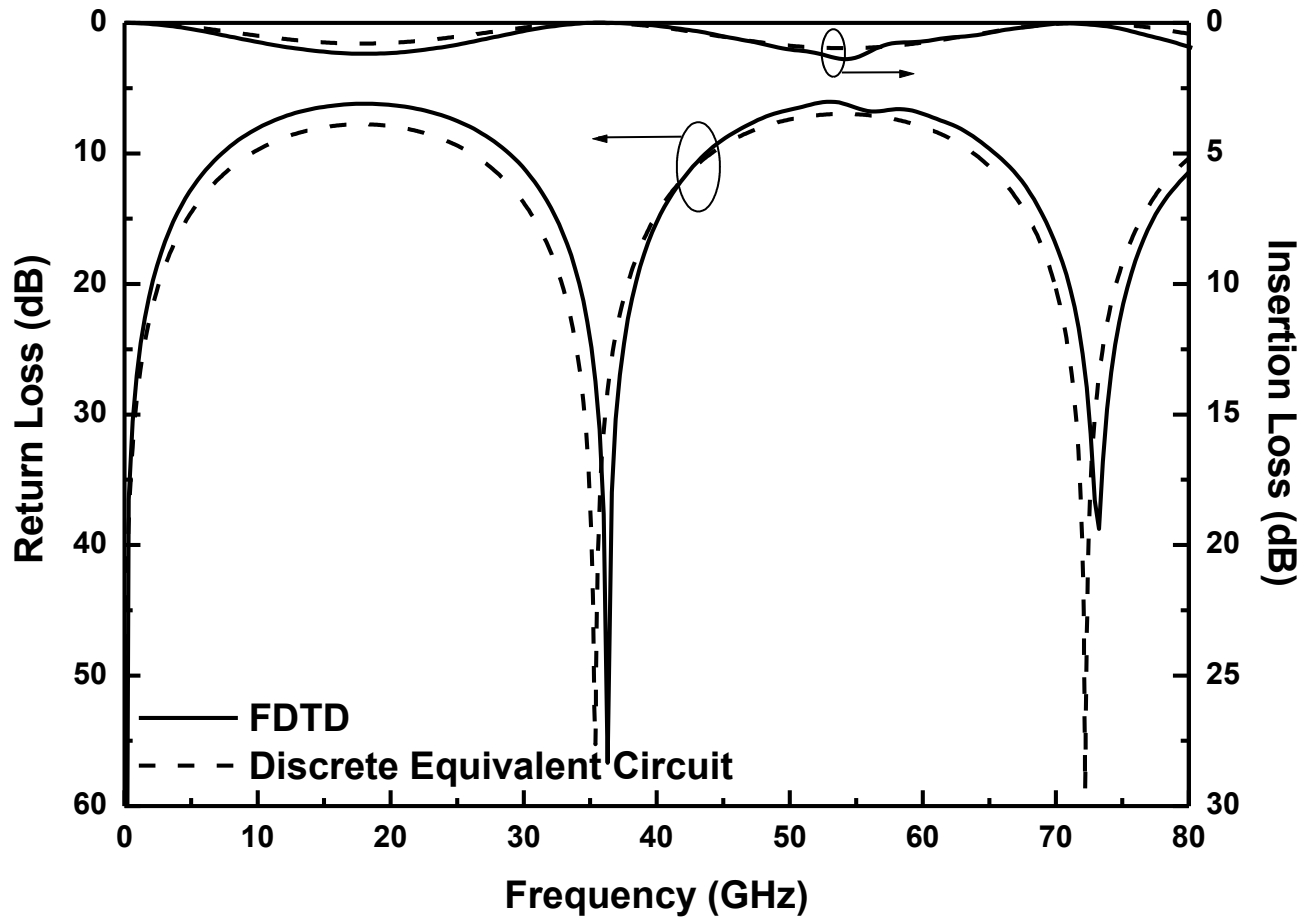

Resonant Flip-chip Transition


- Comparison for $L_{stg}=0.96\text{mm}$

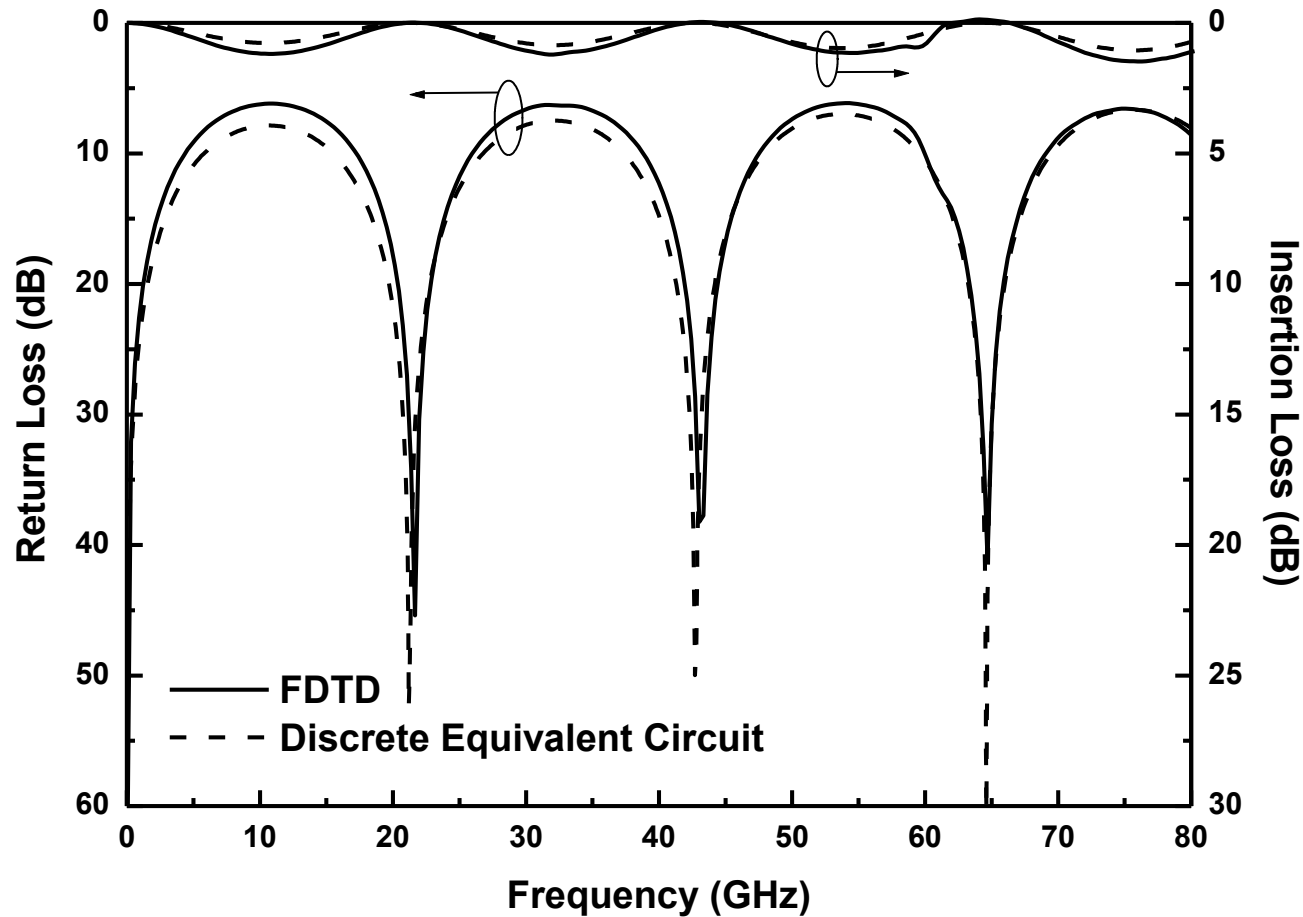

Resonant Flip-chip Transition

- Optimum Results

	$L_{stg}=0.12$ mm	$L_{stg}=0.24$ mm	$L_{stg}=0.48$ mm	$L_{stg}=0.96$ mm
Z_l (Ω)	96.80	58.00	55.60	53.50
20dB Bound (GHz)	49.60	33.40	25.30	18.20

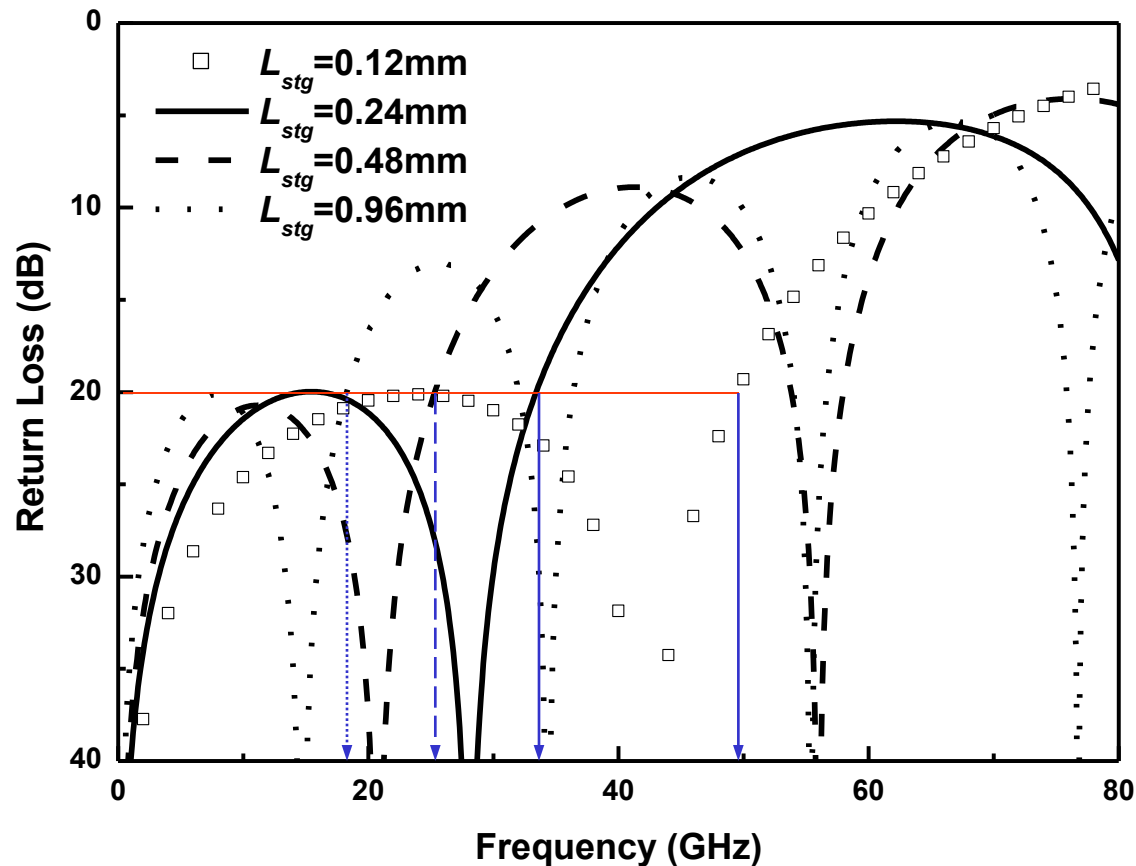

Resonant Flip-chip Transition

- Summary

- Single Resonance Design

- 20 dB Bandwidth: 17.5 ~ 26 %
 - Insertion Loss in 20 dB BW: 1.5 dB
 - Optimum Design

	$L_{stg}=0.24$ mm	$L_{stg}=0.48$ mm	$L_{stg}=0.96$ mm
20dB Bound (GHz)	45.50	36.30	34.30



- Transformer Design

- 20 dB Bandwidth: 11.5 %
 - Insertion Loss in 20 dB BW: 0.05 dB
 - Optimum Design

	$L_{stg}=0.12$ mm	$L_{stg}=0.24$ mm	$L_{stg}=0.48$ mm	$L_{stg}=0.96$ mm
20dB Bound (GHz)	49.60	33.40	25.30	18.20

Inductive Compensation Flip-chip Transition

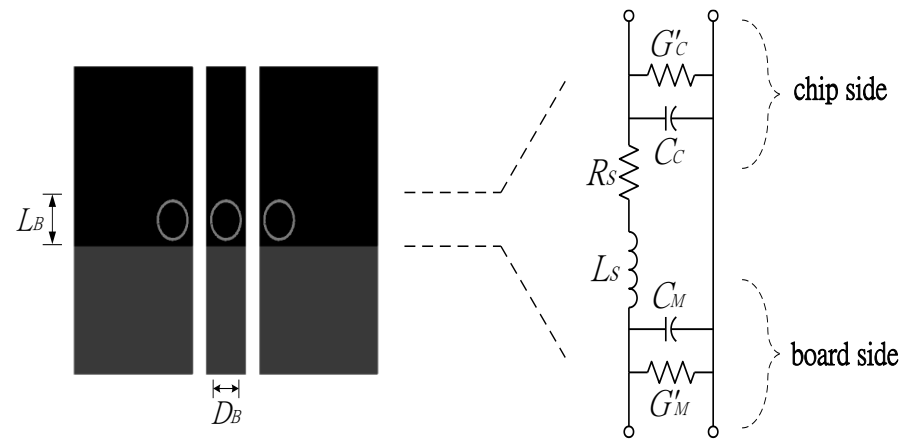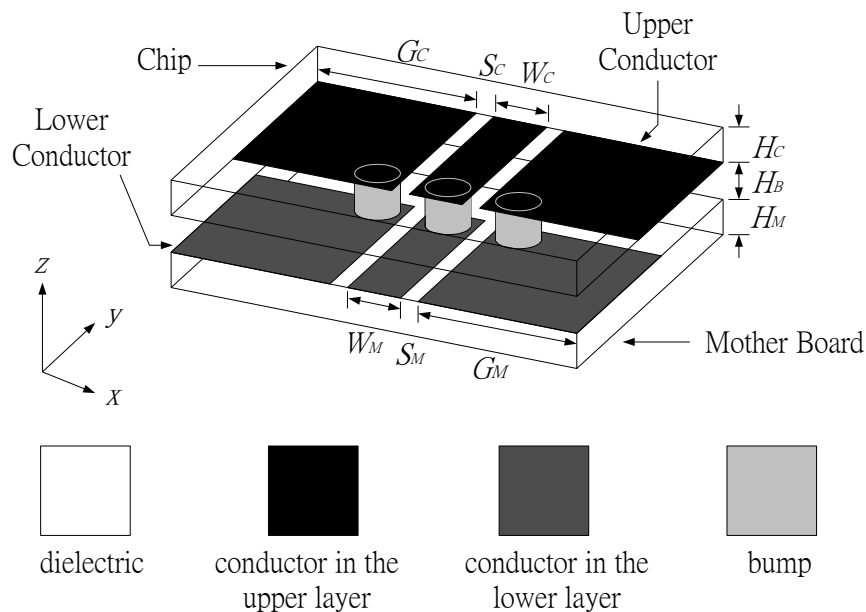- Structure Parameters
 - Introduce an Inductive Element to Compensate the Capacitive Effect




$$L_S = 68.67 \text{ pH}, C_M = C_C = 34.91 \text{ fF}$$

$$W_C = W_M = 200 \mu\text{m}, S_C = S_M = 70 \mu\text{m}, G_C = G_M = 600 \mu\text{m}, H_C = H_B = H_M = 127 \mu\text{m}, \epsilon_r = 10.2.$$


Inductive Compensation Flip-chip Transition

- Lumped Element Compensation


Low pass filter
of order $N=3$

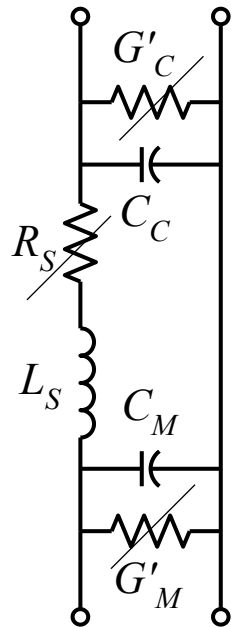

Approximation procedures

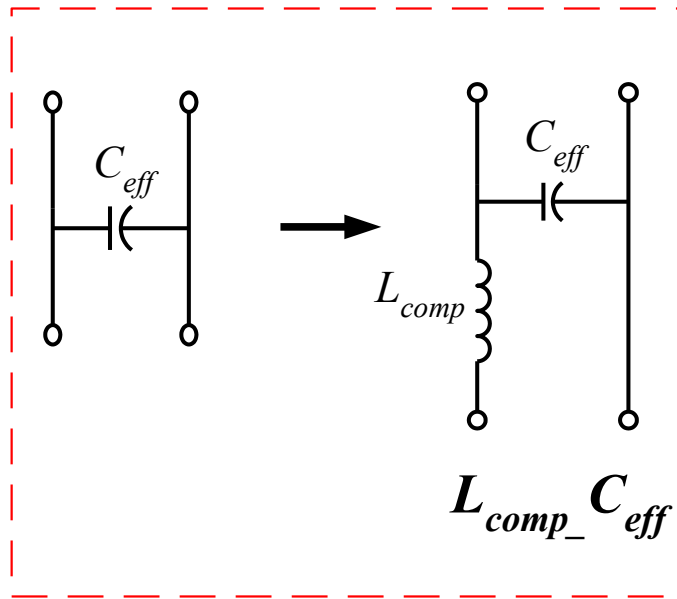

Low pass filter
of order $N=4$

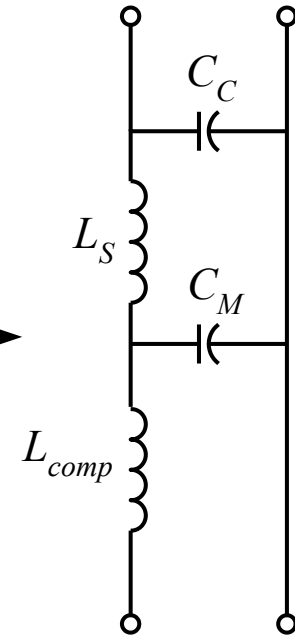

$$C_{eff} = C_M + C_C - L_S / Z_0^2$$

$$= 41.8 \text{ fF}$$


$$L_{comp} = C_{eff} * Z_0^2$$

$$= 104.5 \text{ pH}$$

**Inductor
compensation**


Inductive Compensation Flip-chip Transition

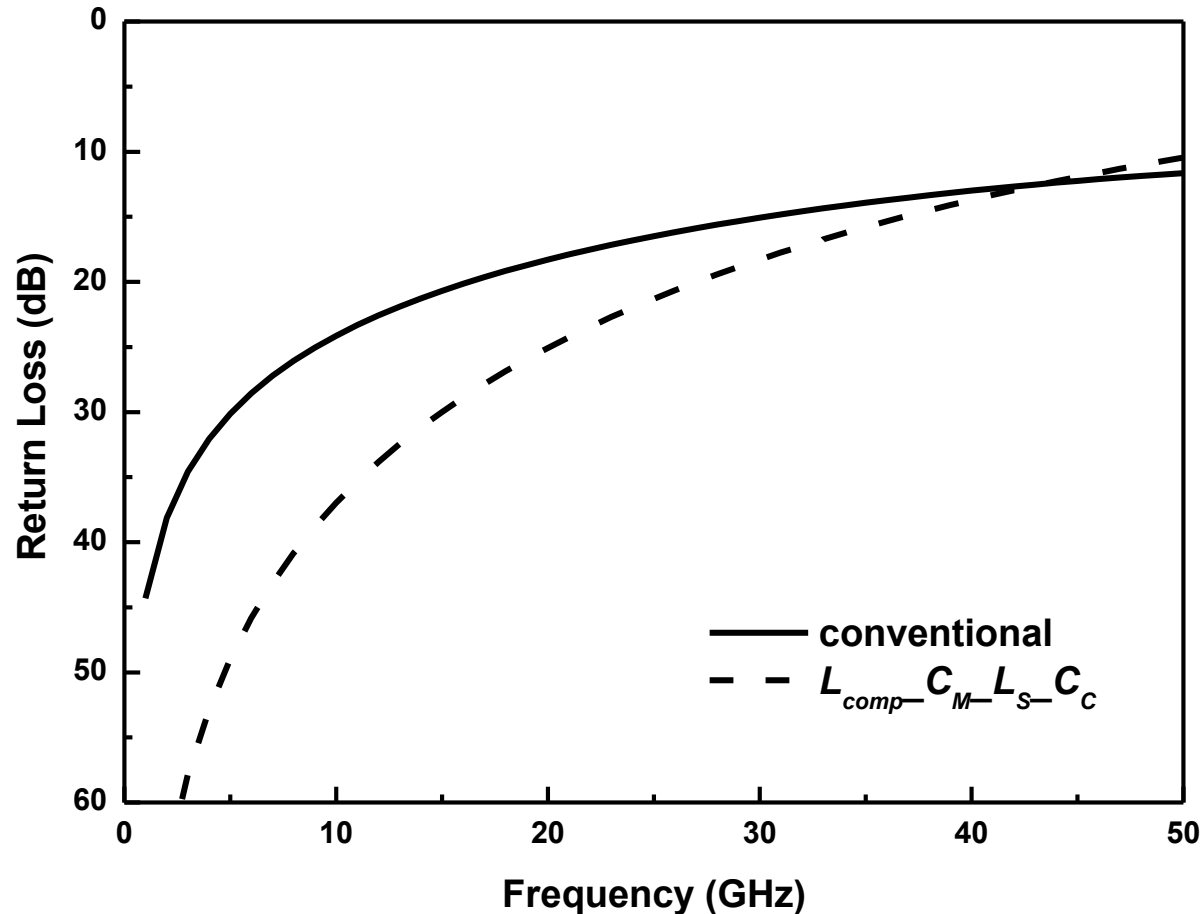- Comparison between Inductance Compensation and Conventional Transition



Inductive Compensation Flip-chip Transition

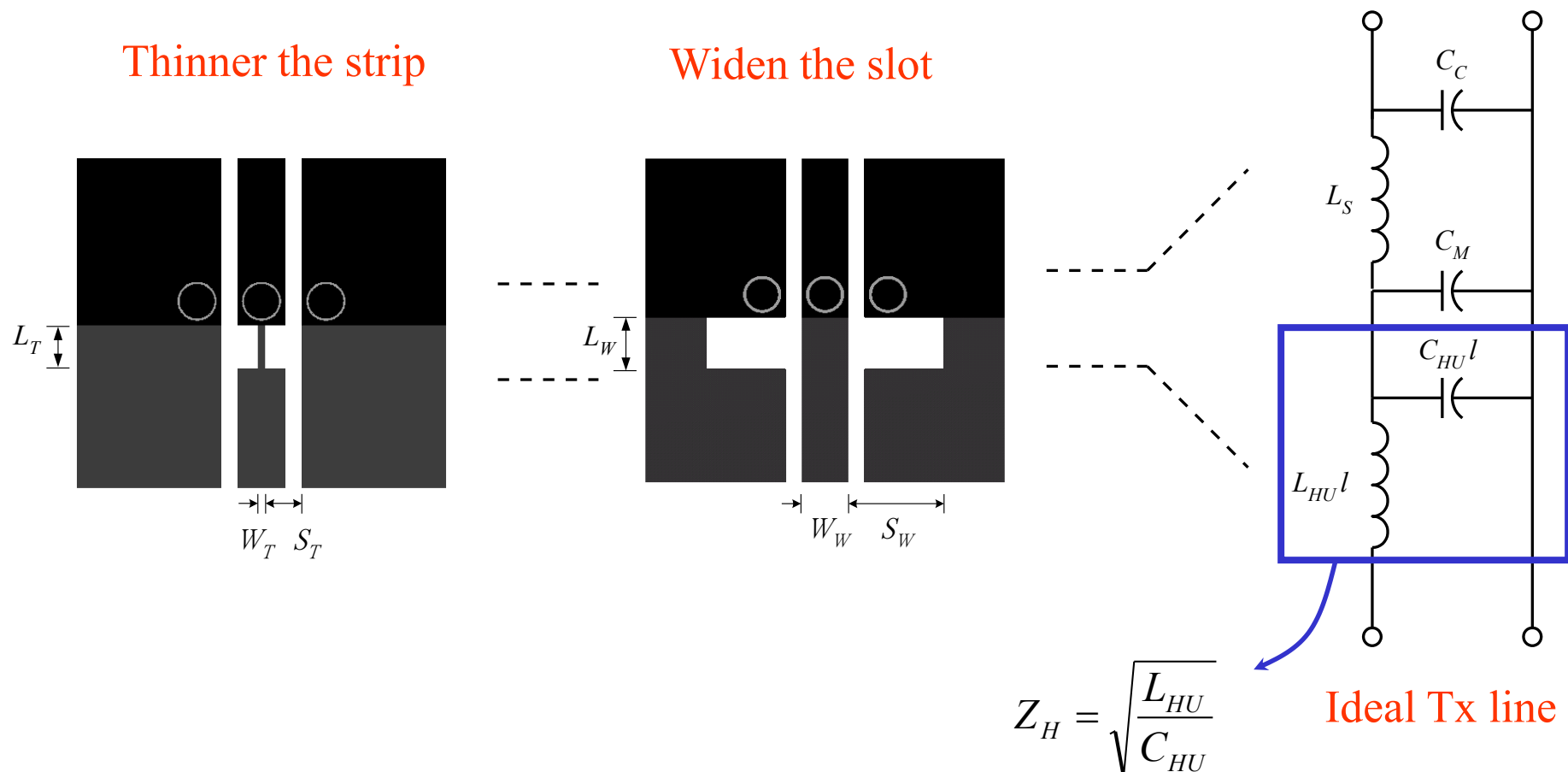- High Impedance Transmission Line Compensation [11]



Inductive Compensation Flip-chip Transition

- High Impedance Transmission Line Compensation
 - Matching Condition

$$\sqrt{\frac{L_{HU}l}{C_{HU}l + C_{eff}}} = Z_0 \quad \rightarrow \quad l = \left(\frac{\omega_H}{\beta_H}\right) \left(\frac{Z_H Z_0^2 C_{eff}}{Z_H^2 - Z_0^2}\right)$$

• $Z_H = 100\Omega$


$\beta l _{30\text{GHz}}(^{\circ})$	$W_T (\mu\text{m})$	$S_T (\mu\text{m})$	$L_T (\mu\text{m})$	$W_W (\mu\text{m})$	$S_W (\mu\text{m})$	$L_W (\mu\text{m})$
15.048	30	155	185	200	410	230

• $Z_H = 76\Omega$

$\beta l _{30\text{GHz}}(^{\circ})$	$W_T (\mu\text{m})$	$S_T (\mu\text{m})$	$L_T (\mu\text{m})$	$W_W (\mu\text{m})$	$S_W (\mu\text{m})$	$L_W (\mu\text{m})$
25.554	30	130	315	200	240	340


Inductive Compensation Flip-chip Transition

- $Z_H = 100\Omega$

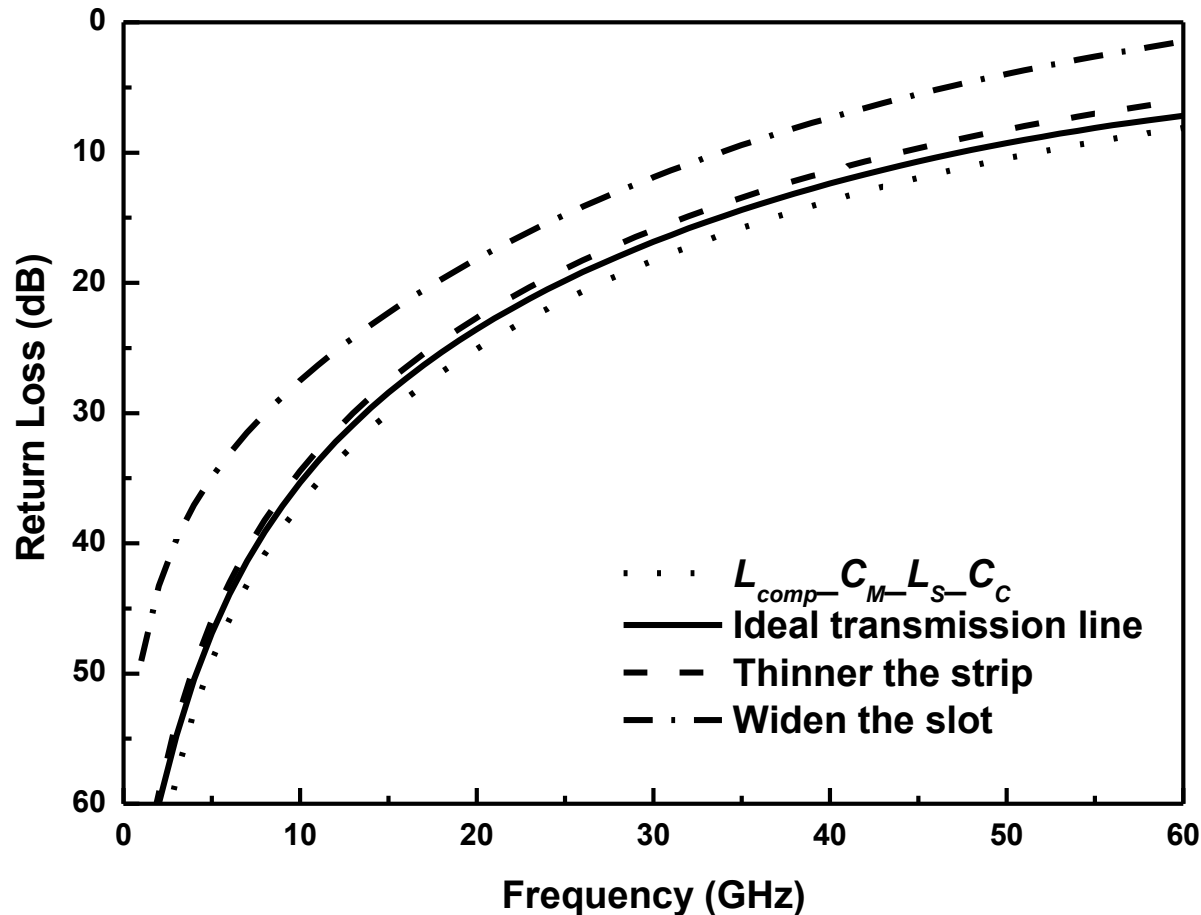


Inductive Compensation Flip-chip Transition

- $Z_H = 76\Omega$

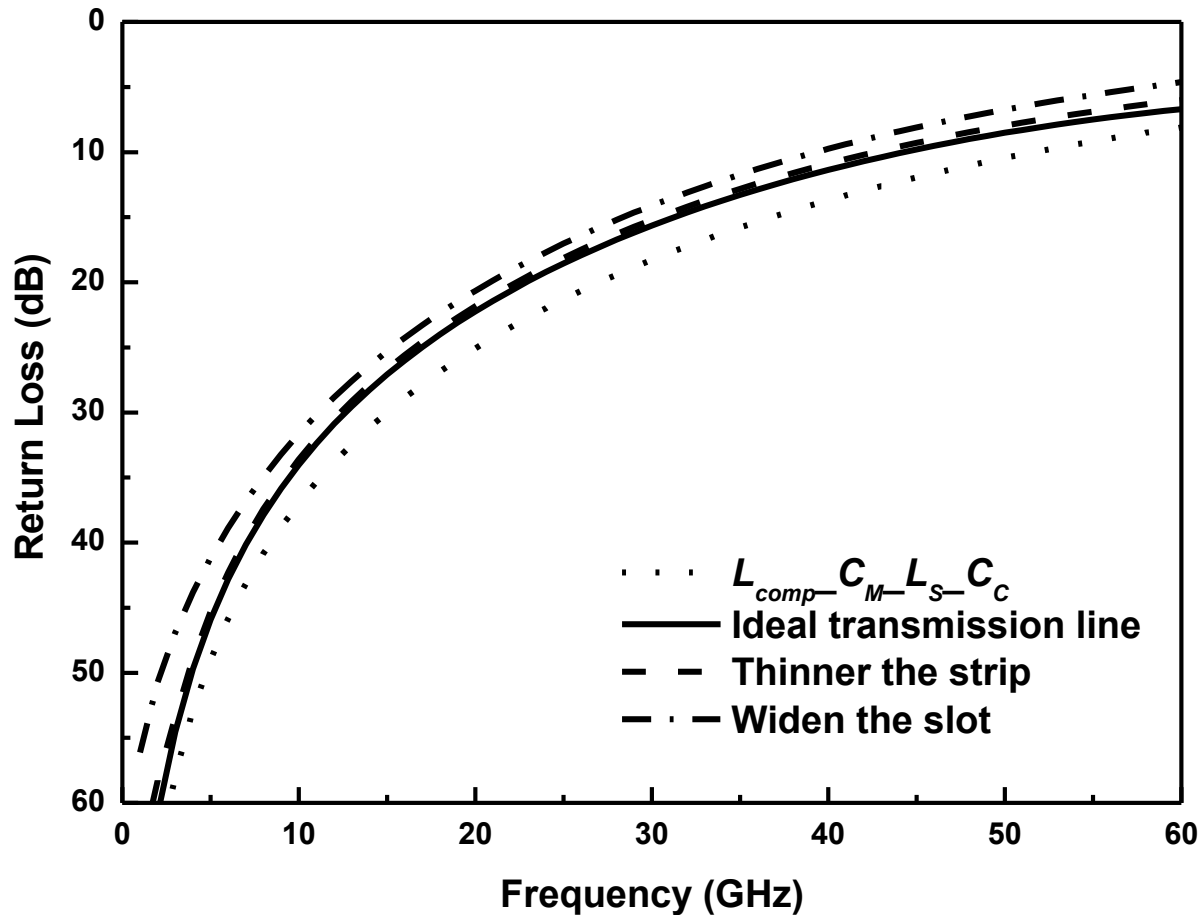

Inductive Compensation Flip-chip Transition

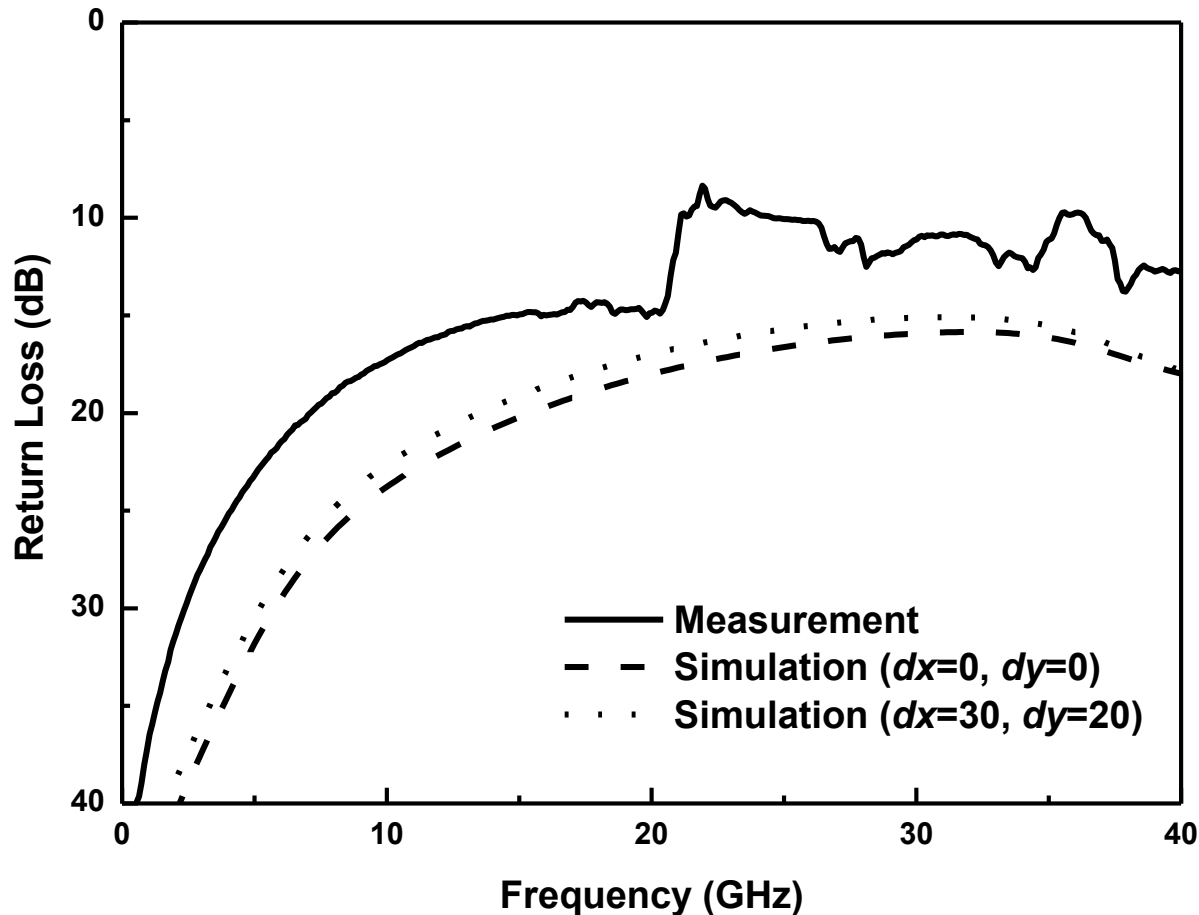- Comparison between Simulation and Measurement




Inductive Compensation Flip-chip Transition

- Summary
 - Lumped Inductance
 - This can well compensate the capacitive effect at low frequencies
 - Ideal High Impedance Transmission Line
 - Higher impedance results in smaller length
 - Higher impedance can better represent the inductance
 - High Impedance Compensation
 - Thin strip has little discontinuity effect than wide slot
 - The Best Choice is to Adopt
 - higher impedance implemented with thin strip
 - Experiment
 - Return Loss is better than 15dB up to 20 GHz

Locally Matching Flip-chip Transition

- Ground Retreat on Mother Board [15]

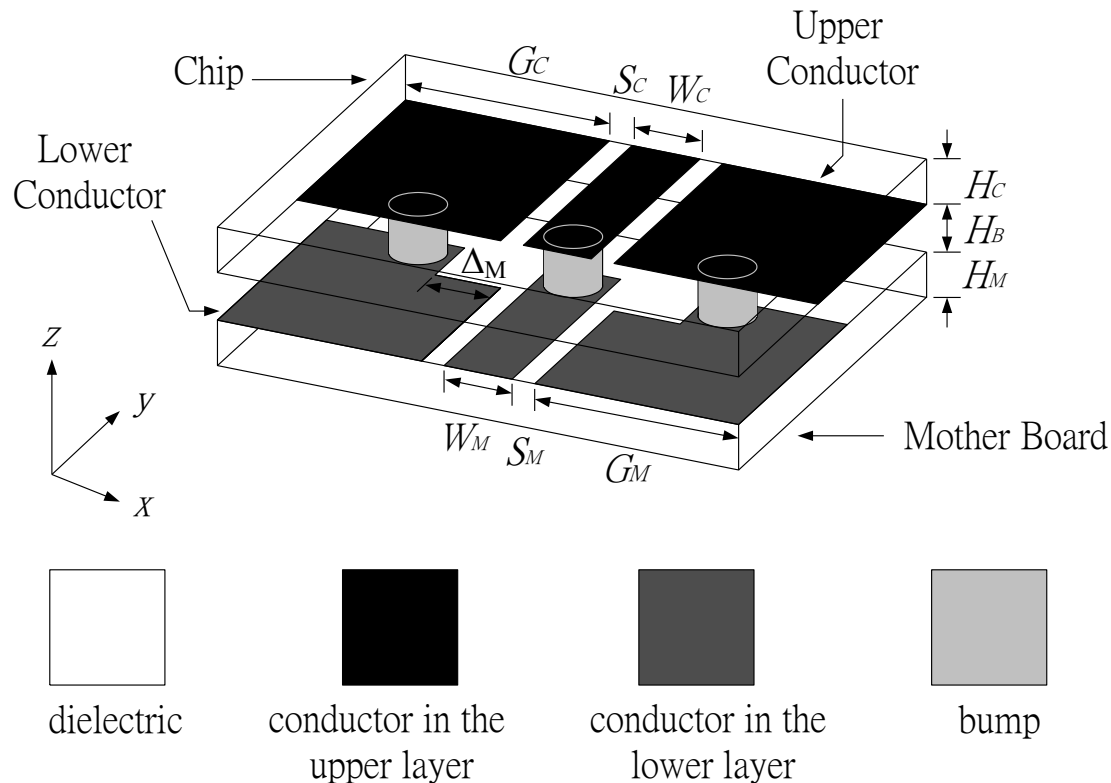
– Make $Z_D = \sqrt{L_S / (C_M + C_C)}$ Close to 50Ω



$$W_C = W_M = 200 \mu\text{m}, S_C = S_M = 70 \mu\text{m}, G_C = G_M = 600 \mu\text{m}, H_C = H_B = H_M = 127 \mu\text{m}, \epsilon_r = 10.2.$$


Locally Matching Flip-chip Transition

- Return Loss

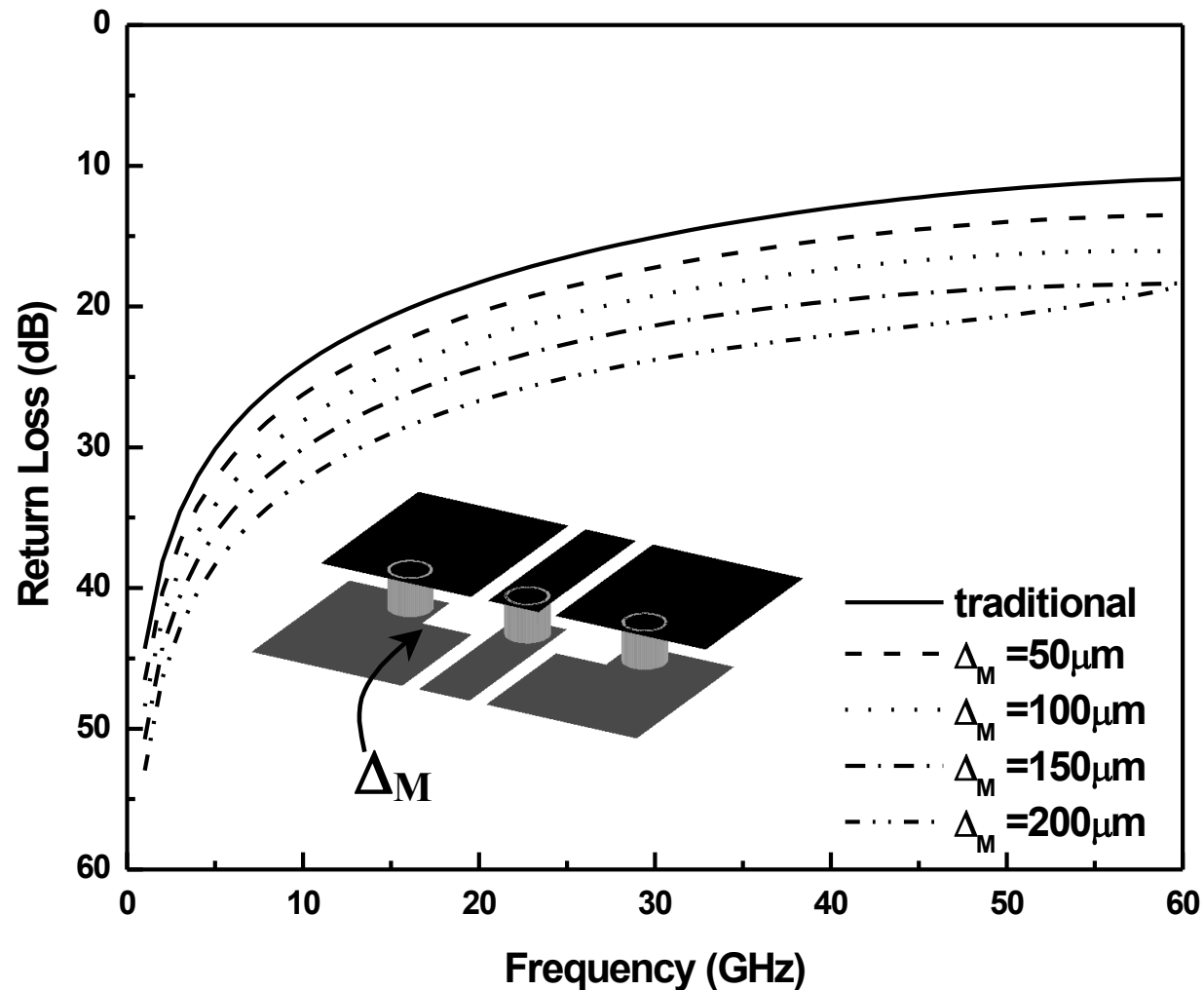


Locally Matching Flip-chip Transition

- Equivalent Circuit Values versus Δ_M

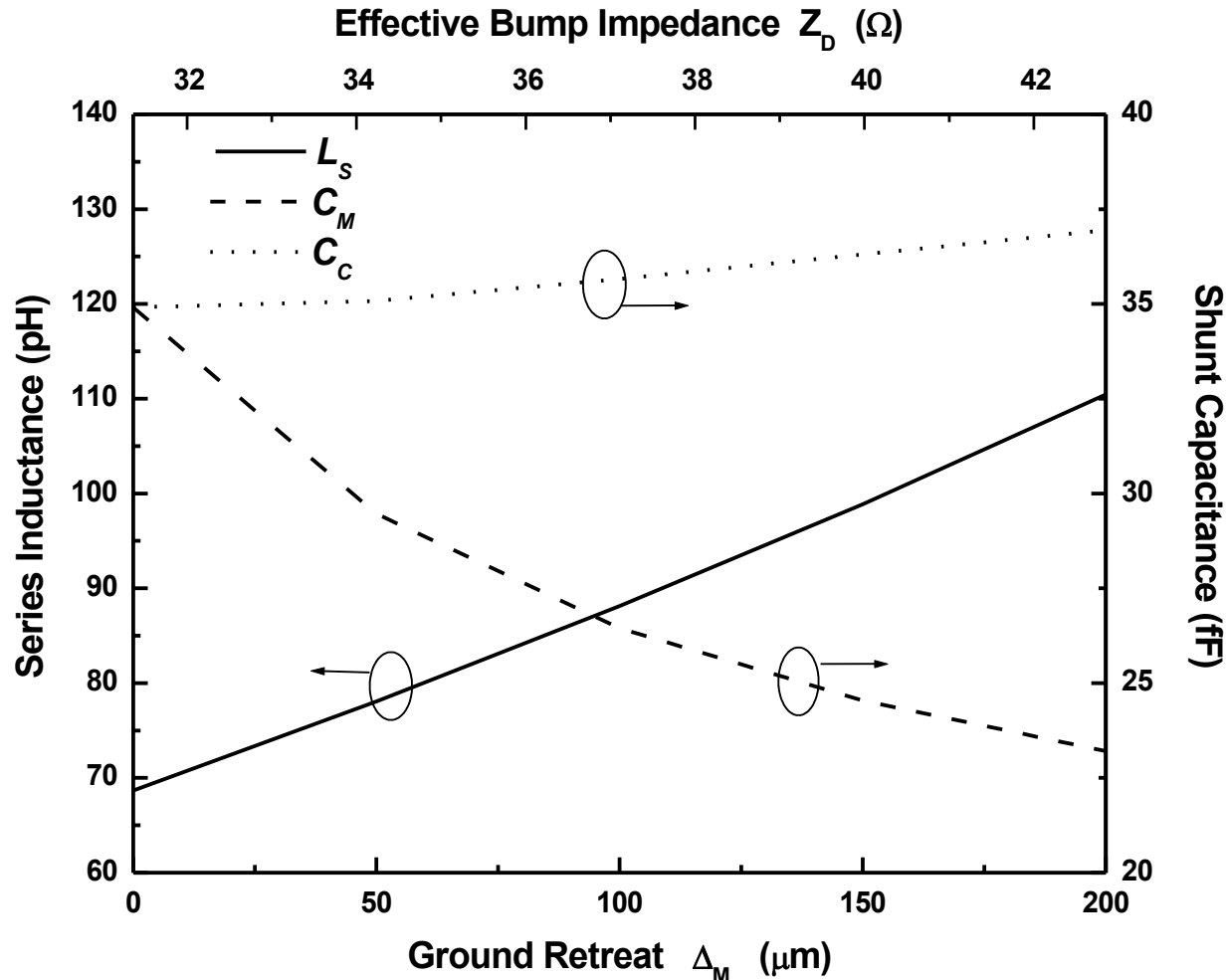

Locally Matching Flip-chip Transition

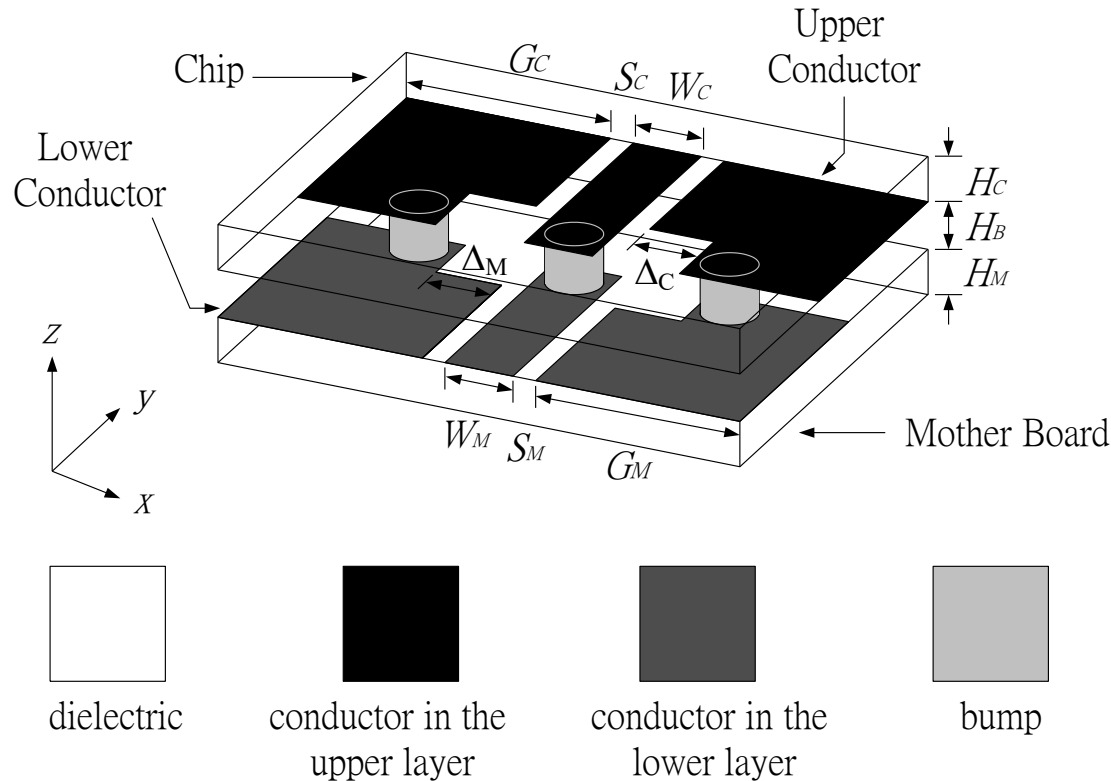
- Ground Retreats Both on Mother Board and Chip



$$W_C=W_M=200\mu\text{m}, S_C=S_M=70\mu\text{m}, G_C=G_M=600\mu\text{m}, H_C=H_B=H_M=127\mu\text{m}, \epsilon_r=10.2.$$


Locally Matching Flip-chip Transition

- Return Loss

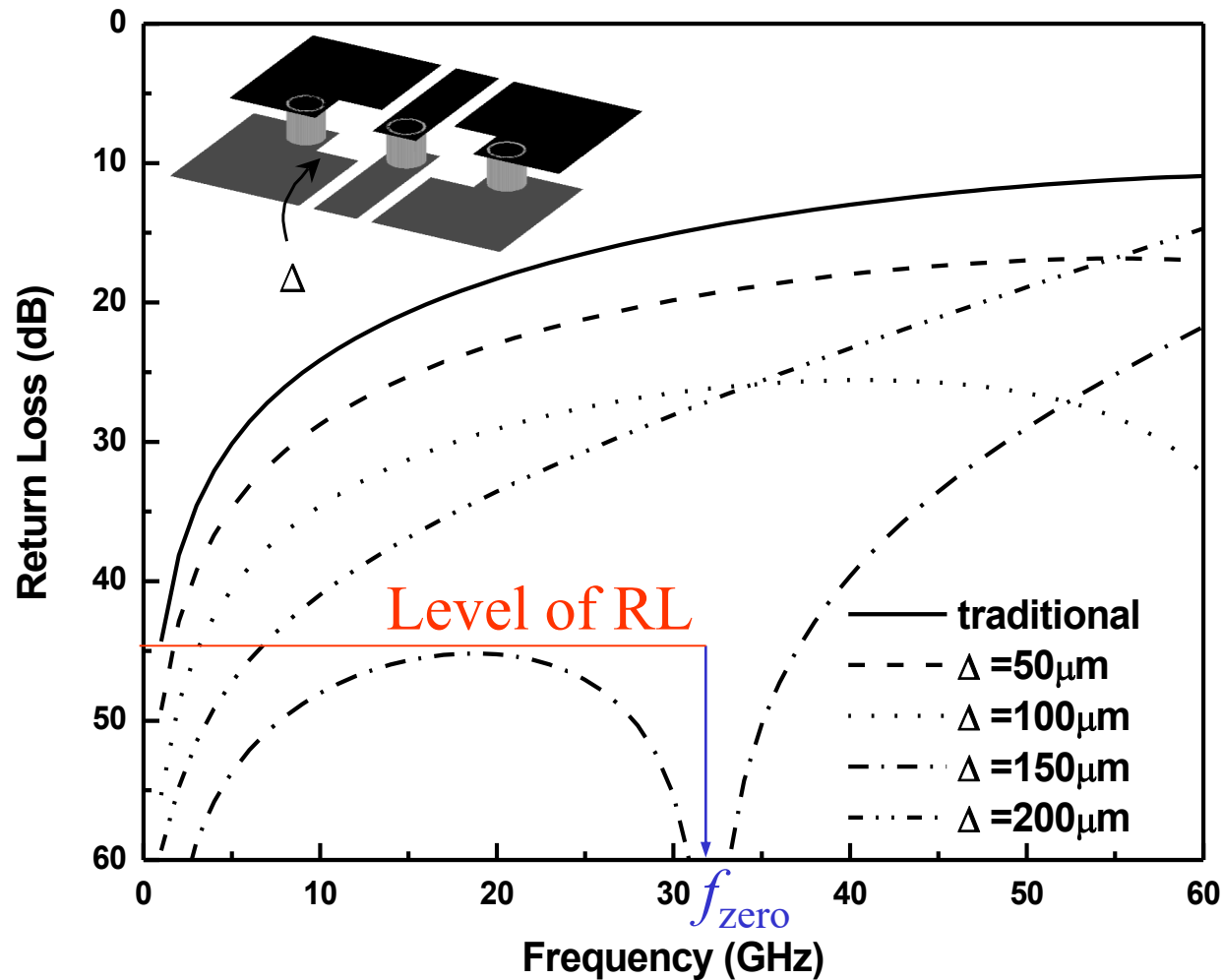


Locally Matching Flip-chip Transition

- Equivalent Circuit Values versus Δ_M

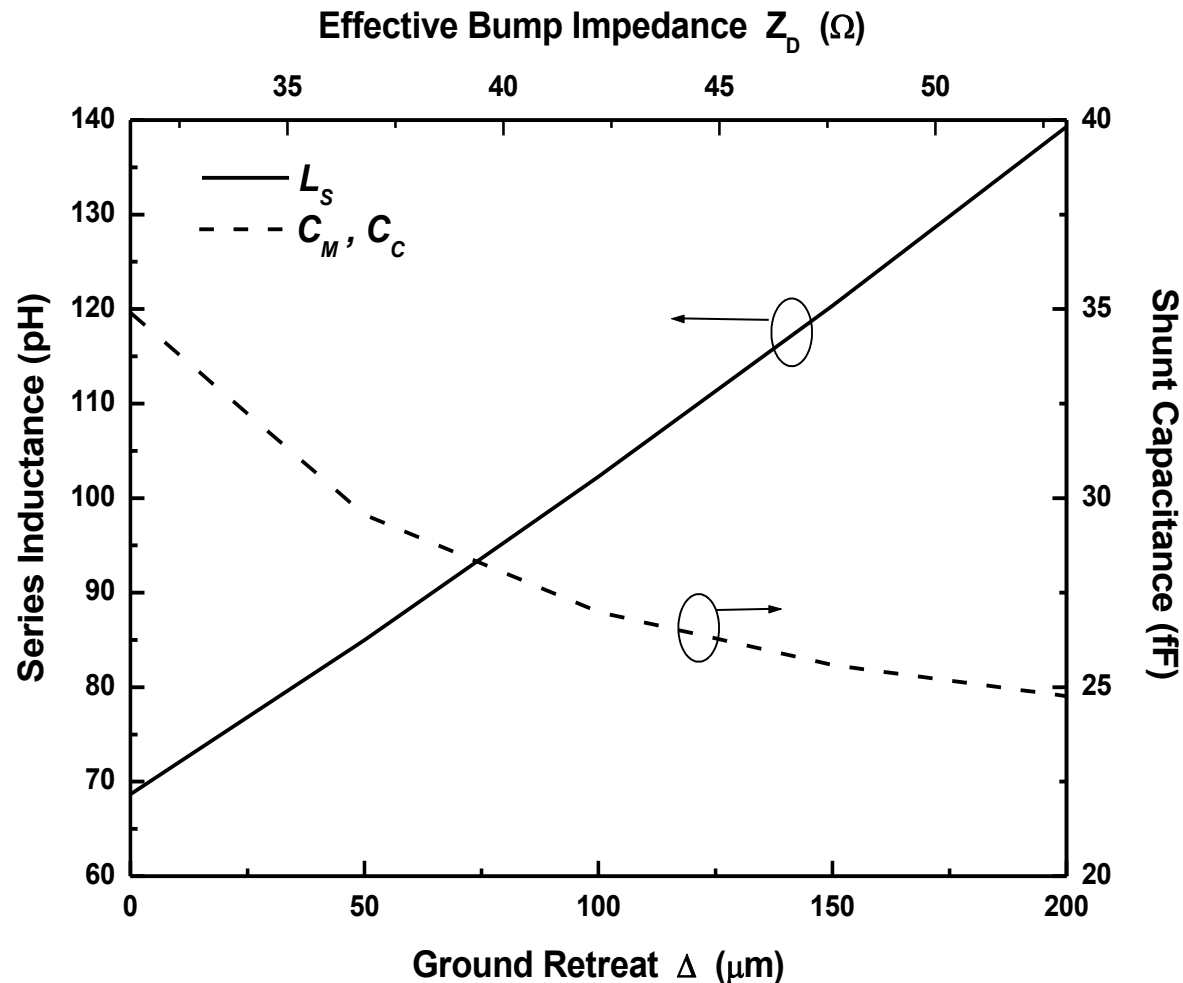


Locally Matching Flip-chip Transition

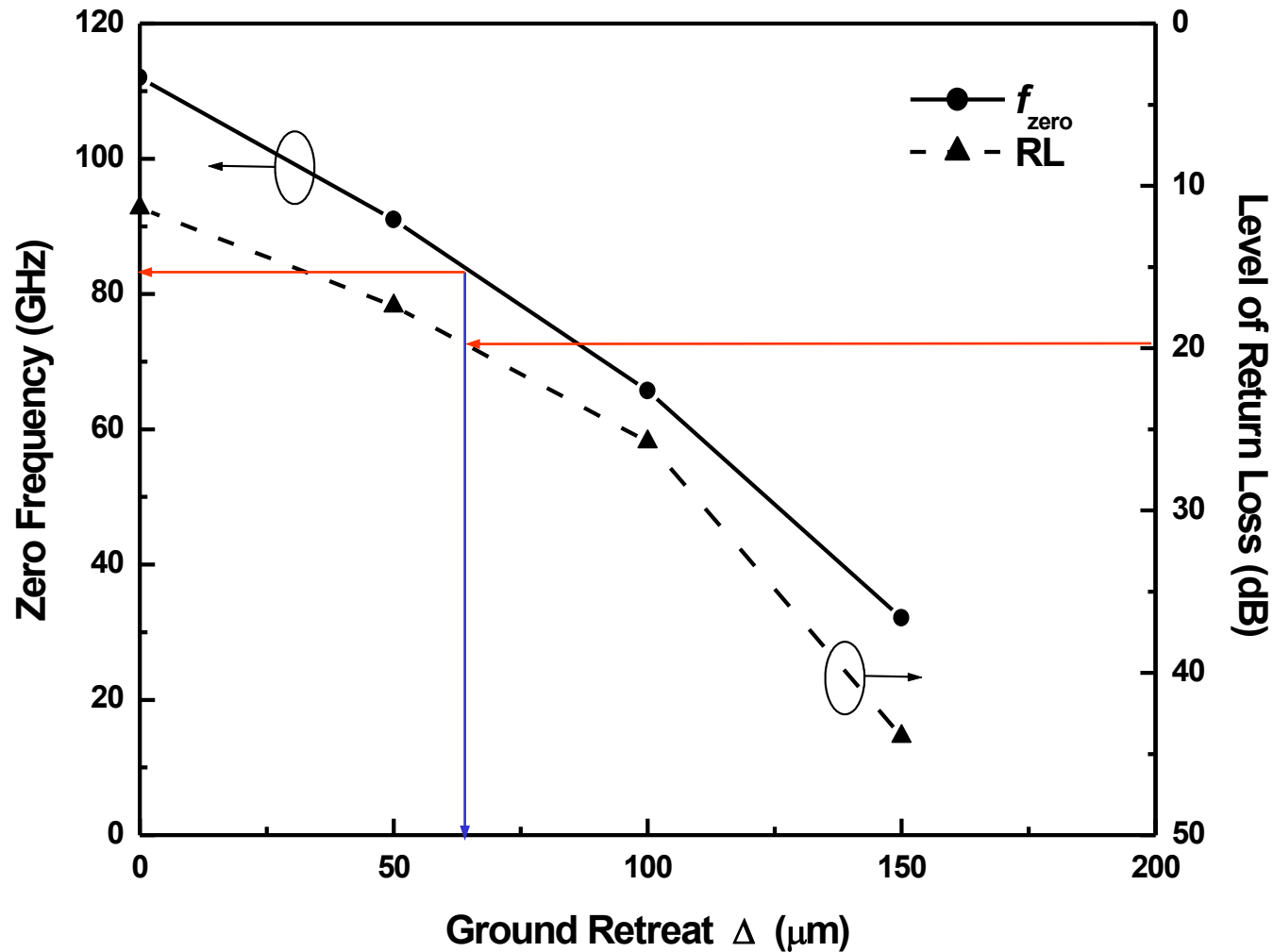- Design Chart $f_{zero} = \frac{1}{2\pi} \sqrt{\frac{1}{L_S C_C^2} (2C_C - \frac{L_S}{Z_o^2})}$




Locally Matching Flip-chip Transition

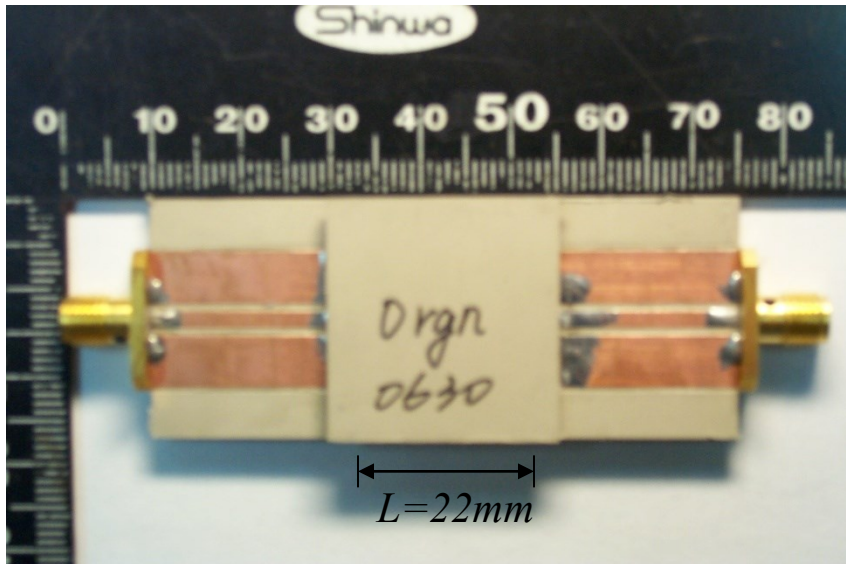- 10 times Scaled up Circuit
 - Fabricated on RT/Duroid6010 of $\epsilon_r=10.2$, and Measured with TRL Calibration.



Top view of the whole circuit

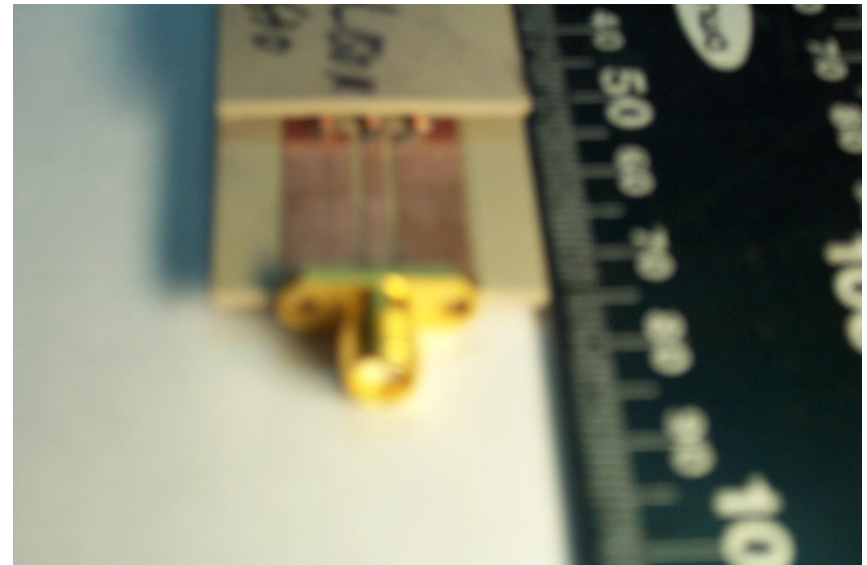


Local view of the bump area

Many thanks to Mr. Shih-Chieh Yen and Shih-Je Yang for helps on the fabrication.

Many thanks to Mr. Wen-Hua Tu for the suggestions in the measurement.

Locally Matching Flip-chip Transition

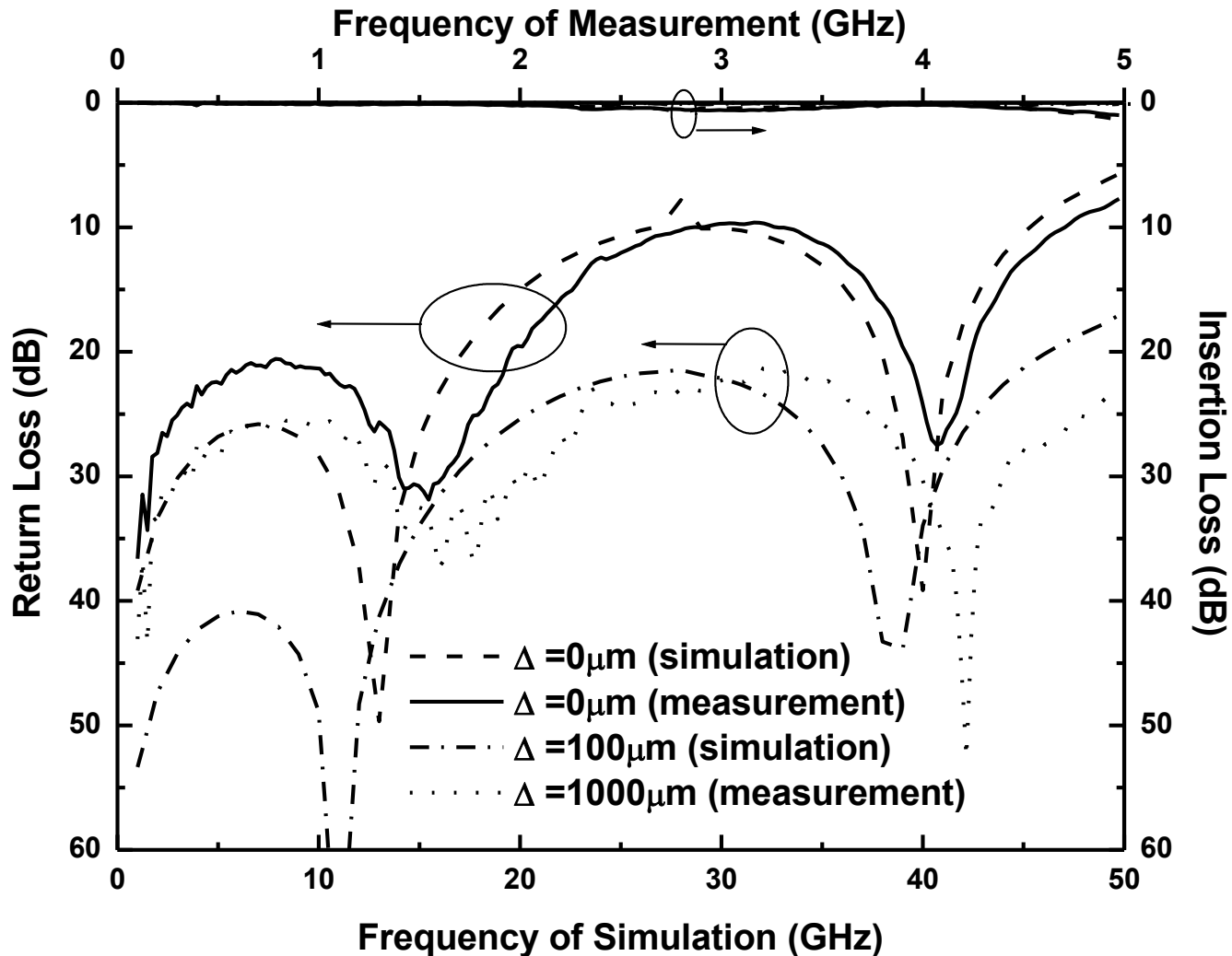- Comparison between Simulation and Measurement



Locally Matching Flip-chip Transition

- Summary

- Ground Retreat on Mother Board


- The response of return loss does not change severely with Δ_M
 - The performance is still restricted by C_C on the chip side

- Ground Retreats on Mother Board and Chip

- This structure exhibits good transition when Δ is chosen well to match the impedance.
 - The area occupied is in the transverse direction of propagation and the frequency band is wide.
 - A design graph built with four simulated points can be used to design the return loss level validated up to the resonant frequency.
 - Measurement results of the ten-times scaled up circuit show good agreement with the simulation results.

On Chip Design and Measurement Correction

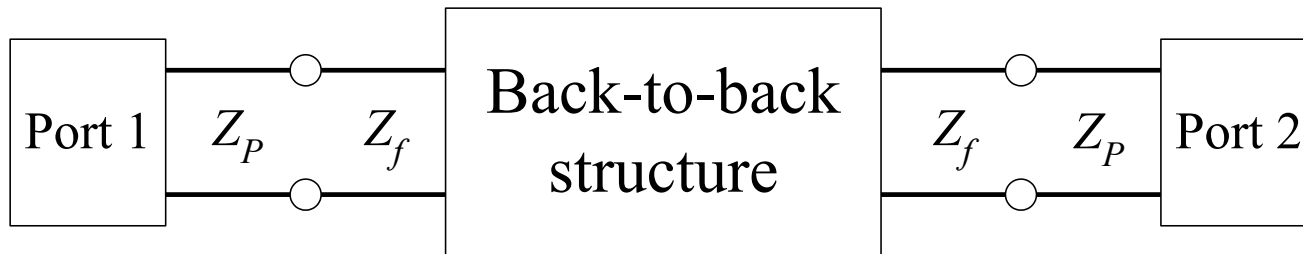- Design Consideration
 - Simulated with Zero Conductor Thickness
 - $Z'_f = Z'_p = 52\Omega$
 - Measured with Real Conductor Thickness
 - $Z_f = Z_p = 50\Omega$




Z_f : characteristic impedance of feed line

Z_p : characteristic impedance of port


Many thanks to Airwave Inc. for fabricating the real flip-chip circuits, and Mr. Kun-You Lin and Ping-Yu Chen for doing the on wafer measurements.

On Chip Design and Measurement Correction

- Chip Photo

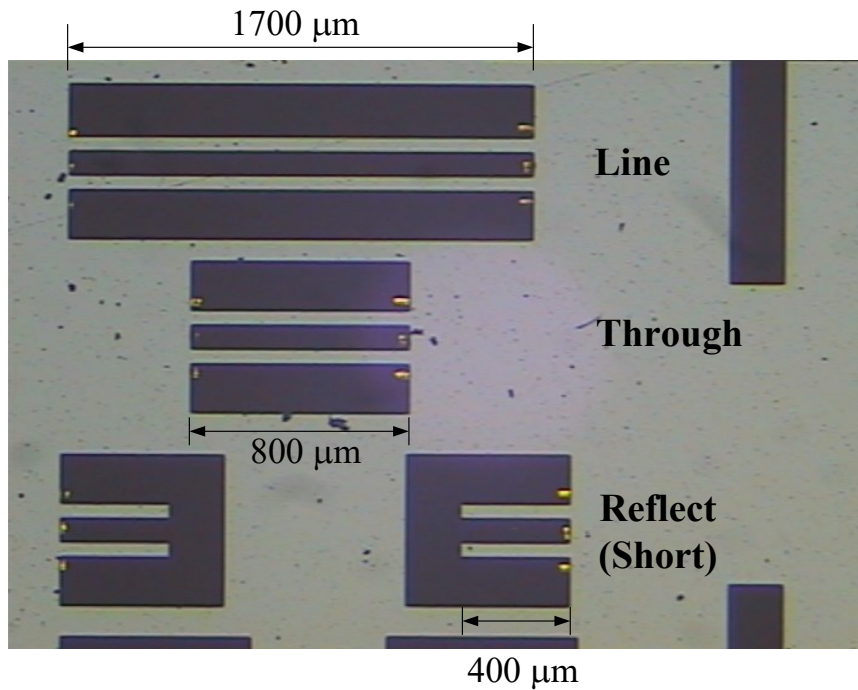

TRL Calibration Kit

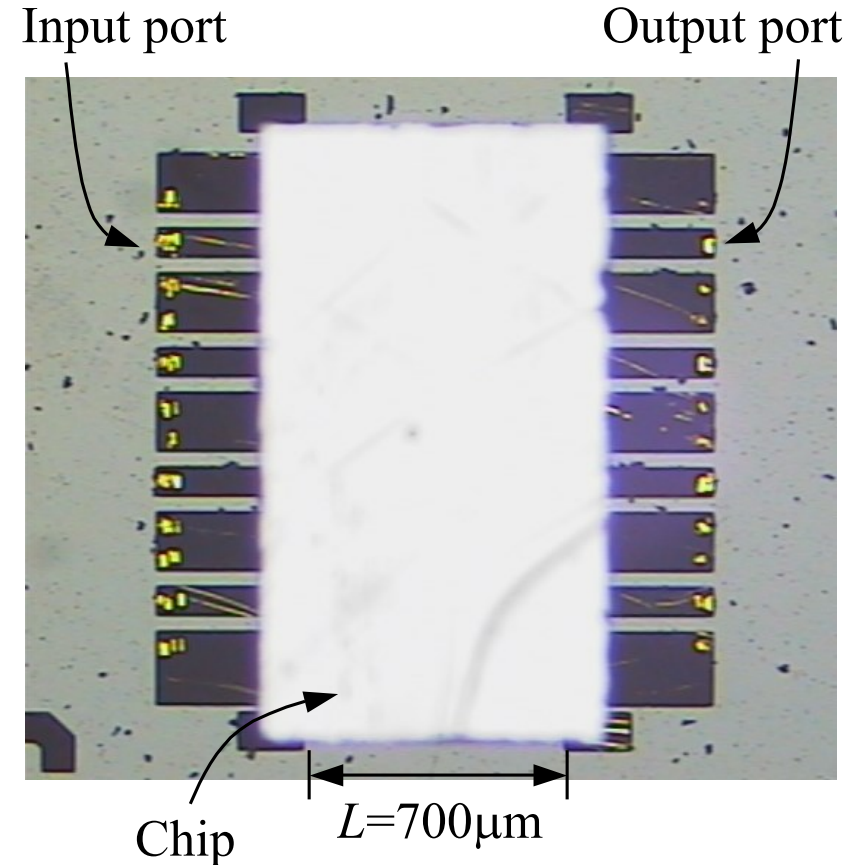


Back to Back Circuit

Bump: $H_B=35\ \mu\text{m}$, $D_B=80\ \mu\text{m}$

Mother Board (GCPW): $H_M=381\ \mu\text{m}$, $\epsilon_r=9.9$, **Chip (CPW):** $H_C=635\ \mu\text{m}$, $\epsilon_r=12.9$

On Chip Design and Measurement Correction

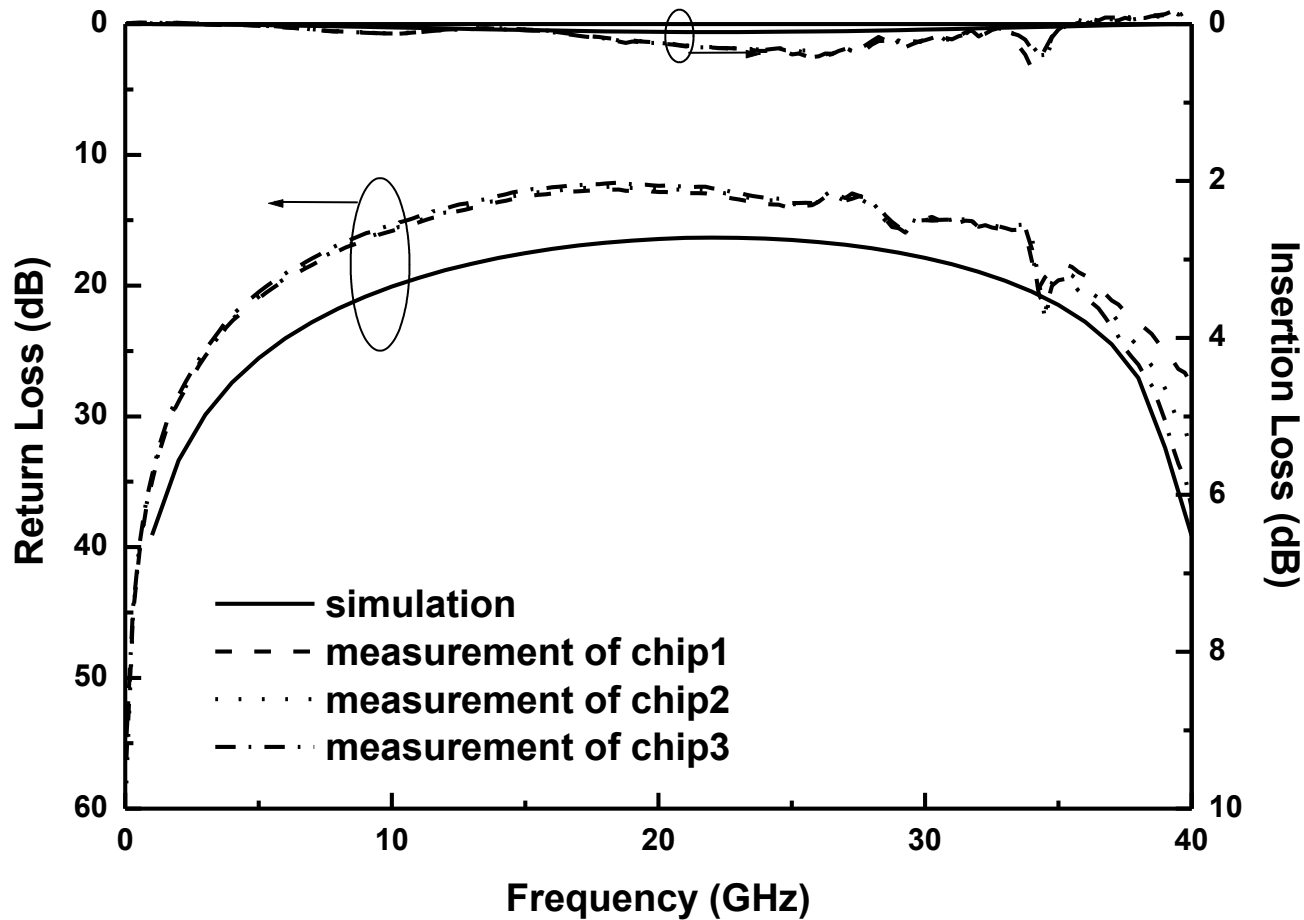
- Ground Retreat on Mother Board Only — $\Delta_M=50\mu\text{m}$
 - Measured Based on $Z_f=Z_p=50\Omega$




Mother Board: $W_M=100\mu\text{m}$, $S_M=50\mu\text{m}$, $G_M=200\mu\text{m}$. **Chip:** $W_C=100\mu\text{m}$, $S_C=50\mu\text{m}$, $G_C=200\mu\text{m}$.

On Chip Design and Measurement Correction

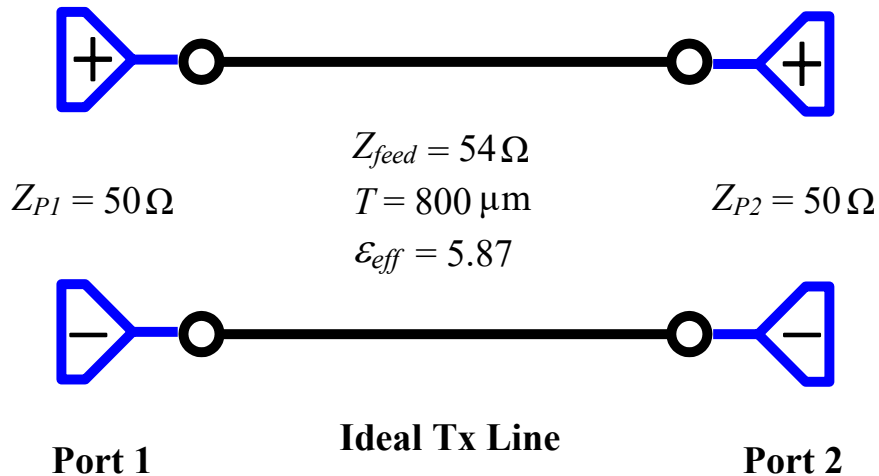- Circuit for Acquiring the Correct Feedline Impedance
 - Z_f is Estimated to be $54\ \Omega$




Equivalent Circuit

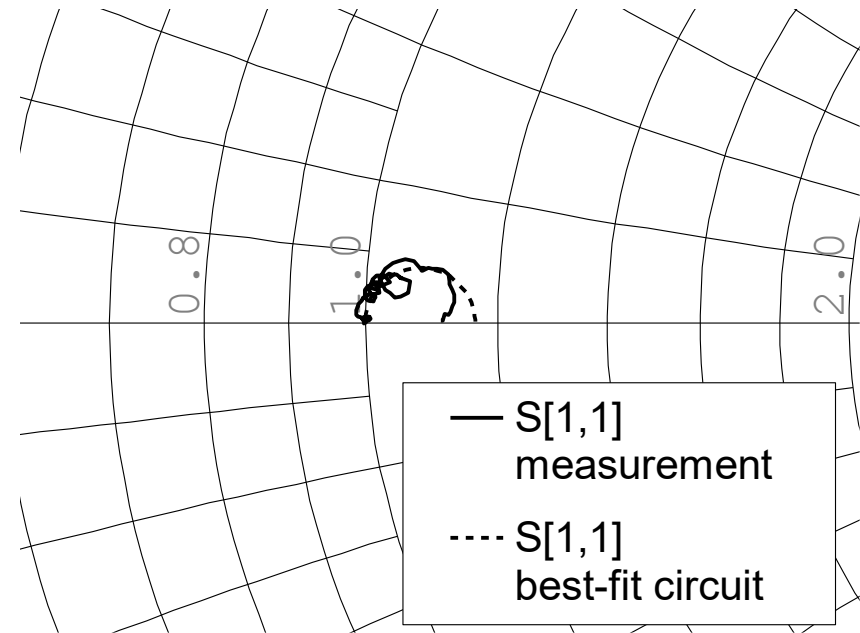

Comparison Result


On Chip Design and Measurement Correction

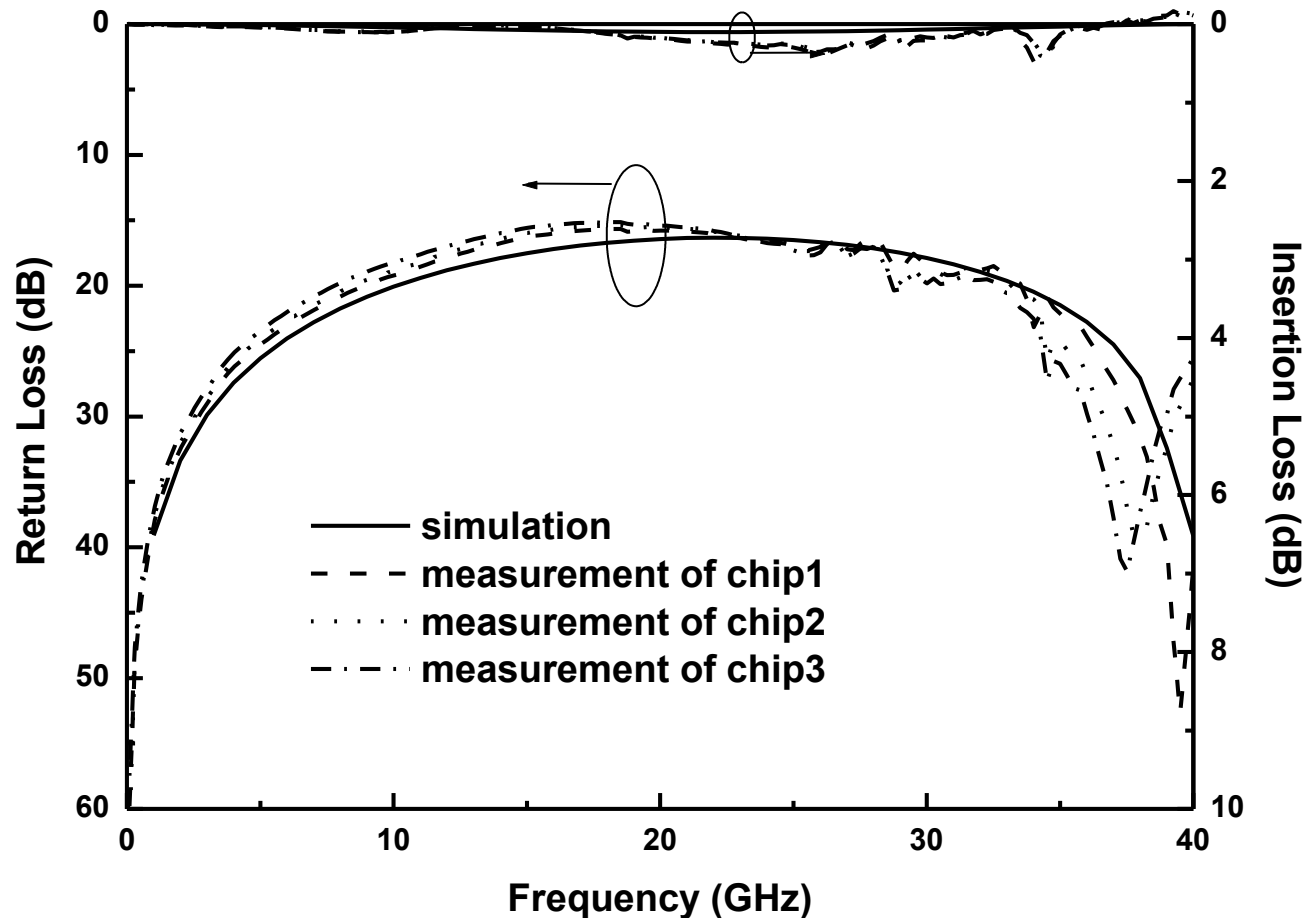- Ground Retreat on Mother Board Only — $\Delta_M = 50\mu\text{m}$
 - Measured Based on $Z_f = Z_p = 54\Omega$



On Chip Design and Measurement Correction

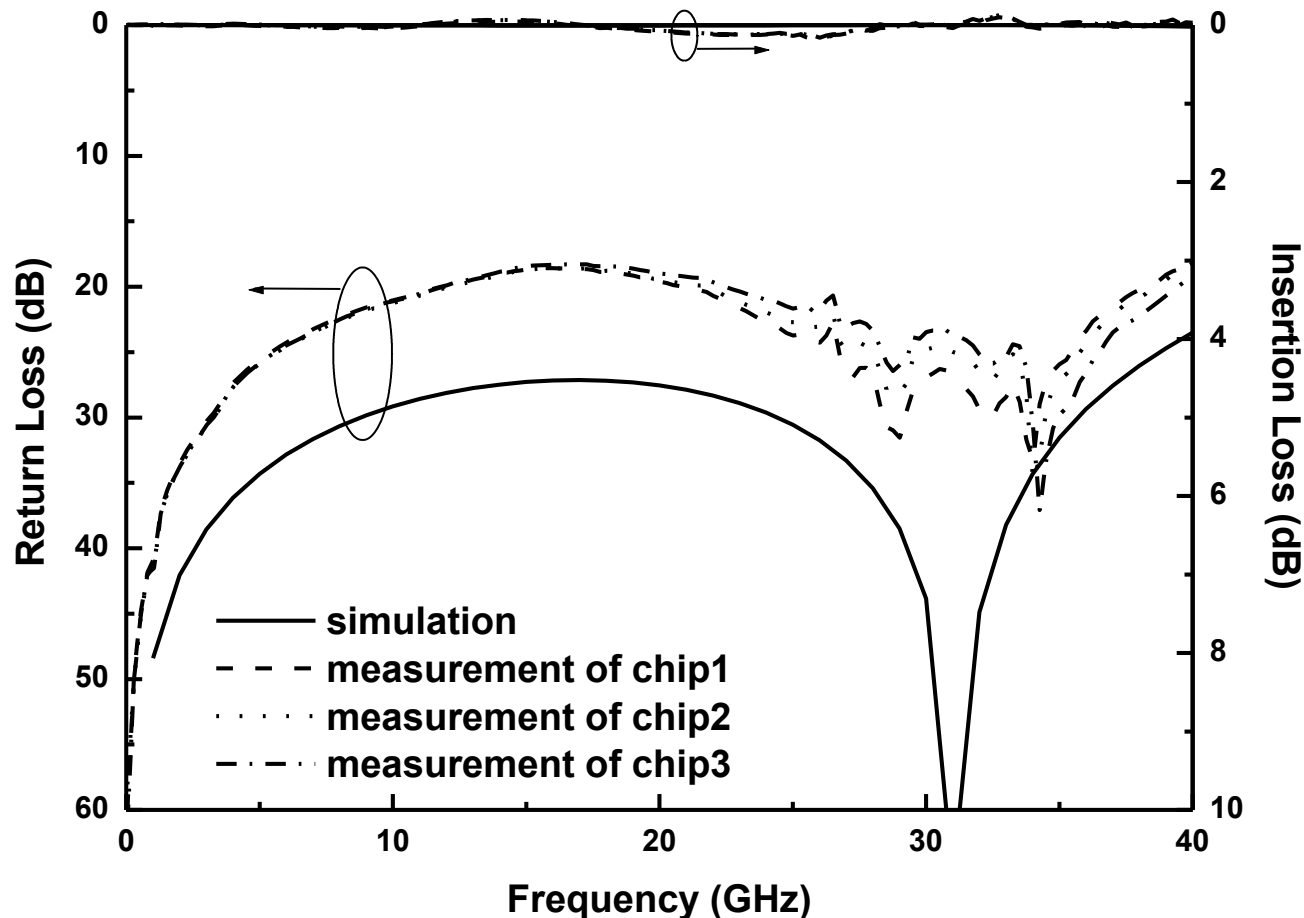
- Ground Retreat on Both Sides — $\Delta_M=75\mu\text{m}$, $\Delta_C=50\mu\text{m}$
 - Measured Based on $Z_f=Z_p=50\Omega$



Mother Board: $W_M=100\mu\text{m}$, $S_M=55\mu\text{m}$, $G_M=295\mu\text{m}$. **Chip:** $W_C=100\mu\text{m}$, $S_C=80\mu\text{m}$, $G_C=270\mu\text{m}$.

On Chip Design and Measurement Correction

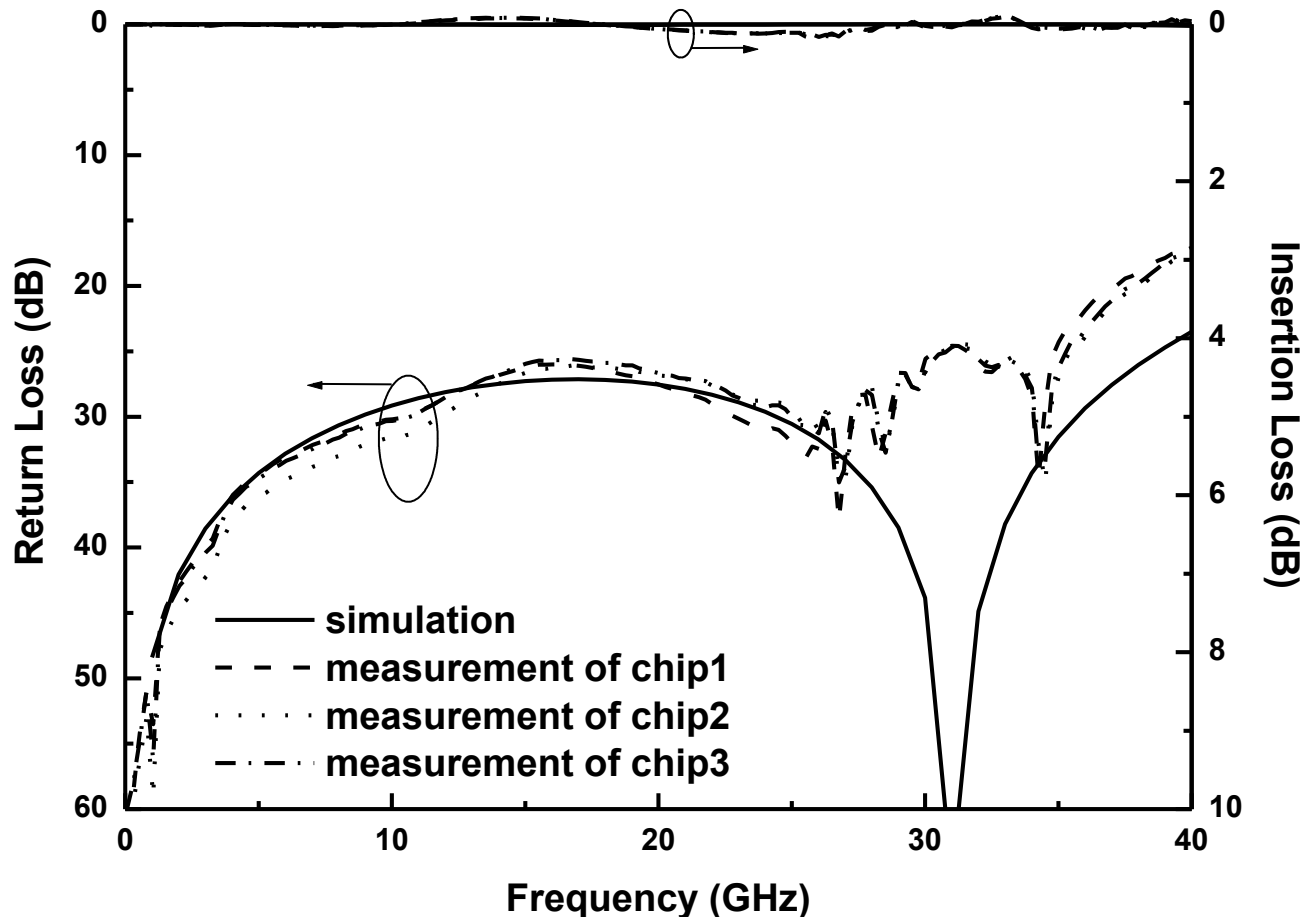- Ground Retreat on Both Sides — $\Delta_M=75\mu\text{m}$, $\Delta_C=50\mu\text{m}$
 - Measured Based on $Z_f=Z_p=54\Omega$



On Chip Design and Measurement Correction

- Summary

- Simulation

- zero conductor thickness based on $Z'_f=Z'_p=52\Omega$ is adopted

- Measurement

- Original measurement based on $Z_f=Z_p=50\Omega$ is calibrated to $Z_f=Z_p=54\Omega$
 - 4 to 10 dB error in RL is corrected

- Ground Retreat on Mother Board Only

- 15 dB RL up to 35 GHz

- Ground Retreats on Both Sides

- 25 dB RL up to 35 GHz

Conclusions

- **Conclusions**
 - **Conventional Flip-chip Transition**
 - This possesses a capacitive effect
 - **Resonant Flip-chip Transition**
 - The resonant length is controlled to result in a resonant dip in the desired frequency band
 - Discrete equivalent circuit could be optimized up to millimeter-wave frequencies
 - Chip areas are sacrificed in the longitudinal direction
 - **Inductive Compensation Flip-chip Transition**
 - Lumped inductance could well compensate the capacitive effect
 - High impedance line with higher impedance and thin strip could result in the best performance and smallest size
 - This saves chip areas
 - This could only enhance the performance up to millimeter-wave frequencies

Conclusions

- Conclusions
 - Locally Matching Flip-chip Transition
 - Ground retreat on mother board could substantially improve the performance
 - Ground retreat on both sides could greatly improve the performance
 - Wide band performance are obtained with chip areas sacrificed in the transverse direction
 - On Chip Design
 - Simulation considering conductor thickness with zero conductor thickness and somewhat higher impedance is adopted
 - Measurement correction procedures are required to calibrate the return loss level due to fabrication error