

# Architecture of Radio Receivers and Transmitters (BE2M37ART)

## Sensitivity Analysis, Distributed Amplifier, MMIC

Josef Dobeš

Sunday, May 12, 2019



*Outline*

*Algorithm in General*

*Standard Sensitivity...*

*Noise Sensitivity Analysis*

*Noise-Figure Sensitivity...*

*Distributed Amplifier*

*Monolithic Microwave...*

*-- Impedance Matching*

*-- Sensitivity Analysis*

*Home Page*



*Page 1 of 14*

*Go Back*

*Full Screen*

*Close*

*Quit*

## 1. Outline

- Algorithm in General
- Standard Sensitivity Analysis
- Noise Sensitivity Analysis
- Noise-Figure Sensitivity Analysis
- Distributed Amplifier
  - Frequency Characteristic
  - Sensitivity Analysis
  - Assessing Results
- MMIC
  - Impedance Matching
  - Sensitivity Analysis
  - Optimizing Noise Figure



### Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 2 of 14

Go Back

Full Screen

Close

Quit

## 2. Algorithm in General

A parametric system of the circuit linear equations can be written in the form

$$A(p) \mathbf{x}(p) = \mathbf{b}(p),$$

where  $p$  is one of the circuit parameters on which the sensitivities are requested.



*Outline*

*Algorithm in General*

*Standard Sensitivity...*

*Noise Sensitivity Analysis*

*Noise-Figure Sensitivity...*

*Distributed Amplifier*

*Monolithic Microwave...*

*-- Impedance Matching*

*-- Sensitivity Analysis*

*Home Page*



*Page 3 of 14*

*Go Back*

*Full Screen*

*Close*

*Quit*

## 2. Algorithm in General

A parametric system of the circuit linear equations can be written in the form

$$A(p) \mathbf{x}(p) = \mathbf{b}(p),$$

where  $p$  is one of the circuit parameters on which the sensitivities are requested.

The vector of the derivatives with respect to this parameter  $\partial \mathbf{x}(p) / \partial p$  marked by  $\mathbf{x}'(p)$  can be obtained by differentiating

$$A'(p) \mathbf{x}(p) + A(p) \mathbf{x}'(p) = \mathbf{b}'(p),$$

which gives the basic system of the complex linear equations

$$A(p) \mathbf{x}'(p) = \mathbf{b}'(p) - A'(p) \mathbf{x}(p).$$



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 3 of 14

Go Back

Full Screen

Close

Quit

### 3. Standard Sensitivity Analysis

The circuit contains an independent input source and no other internal sources in this case. Therefore, the first part of the right side is equal to zero and the system is simpler

$$A(p) \mathbf{x}'(p) = -A'(p) \mathbf{x}(p).$$



*Outline*

*Algorithm in General*

*Standard Sensitivity ...*

*Noise Sensitivity Analysis*

*Noise-Figure Sensitivity ...*

*Distributed Amplifier*

*Monolithic Microwave ...*

*-- Impedance Matching*

*-- Sensitivity Analysis*

*Home Page*



*Page 4 of 14*

*Go Back*

*Full Screen*

*Close*

*Quit*

### 3. Standard Sensitivity Analysis

The circuit contains an independent input source and no other internal sources in this case. Therefore, the first part of the right side is equal to zero and the system is simpler

$$A(p) \mathbf{x}'(p) = -A'(p) \mathbf{x}(p).$$

If simulator procedures are unable to determine the parametric derivatives  $\partial A \dots / \partial p$  in a symbolic way, they must be computed numerically. For example, the simplest approximation of the derivatives

$$A'(p) \approx \frac{A(p + \Delta p) - A(p)}{\Delta p}$$

can be used, and using this formula gives the final system

$$A(p) \mathbf{x}'(p) = \frac{\mathbf{b}(p) - A(p + \Delta p) \mathbf{x}(p)}{\Delta p}.$$



[Outline](#)

[Algorithm in General](#)

[Standard Sensitivity ...](#)

[Noise Sensitivity Analysis](#)

[Noise-Figure Sensitivity ...](#)

[Distributed Amplifier](#)

[Monolithic Microwave ...](#)

[-- Impedance Matching](#)

[-- Sensitivity Analysis](#)

[Home Page](#)



Page 4 of 14

[Go Back](#)

[Full Screen](#)

[Close](#)

[Quit](#)

## 4. Noise Sensitivity Analysis

The circuit contains  $n_n$  internal noise sources and no independent input source in this case. A  $j^{\text{th}}$  output of the noise analysis is determined by solving the system

$$\mathbf{A}(p)_j \mathbf{x}(p) = \mathbf{b}(p), \quad j = 1, \dots, n_n,$$

which is of the same type as that in the standard analysis. Therefore, the complex LU factorization of  $\mathbf{A}$  must be executed only once  $\forall f$ .



*Outline*

*Algorithm in General*

*Standard Sensitivity...*

***Noise Sensitivity Analysis***

*Noise-Figure Sensitivity...*

*Distributed Amplifier*

*Monolithic Microwave...*

*-- Impedance Matching*

*-- Sensitivity Analysis*

*Home Page*



*Page 5 of 14*

*Go Back*

*Full Screen*

*Close*

*Quit*

## 4. Noise Sensitivity Analysis

The circuit contains  $n_n$  internal noise sources and no independent input source in this case. A  $j^{\text{th}}$  output of the noise analysis is determined by solving the system

$$\mathbf{A}(p)_j \mathbf{x}(p) = {}_j \mathbf{b}(p), \quad j = 1, \dots, n_n,$$

which is of the same type as that in the standard analysis. Therefore, the complex LU factorization of  $\mathbf{A}$  must be executed only once  $\forall f$ .

Similarly, the sensitivity of the  $j^{\text{th}}$  output is determined by solving

$$\mathbf{A}(p)_j \mathbf{x}'(p) = {}_j \mathbf{b}'(p) - \mathbf{A}'(p)_j \mathbf{x}(p).$$



Outline

Algorithm in General

Standard Sensitivity...

**Noise Sensitivity Analysis**

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 5 of 14

Go Back

Full Screen

Close

Quit



## 4. Noise Sensitivity Analysis

The circuit contains  $n_n$  internal noise sources and no independent input source in this case. A  $j^{\text{th}}$  output of the noise analysis is determined by solving the system

$$A(p)_j \mathbf{x}(p) = {}_j \mathbf{b}(p), \quad j = 1, \dots, n_n,$$

which is of the same type as that in the standard analysis. Therefore, the complex LU factorization of  $A$  must be executed only once  $\forall f$ .

Similarly, the sensitivity of the  $j^{\text{th}}$  output is determined by solving

$$A(p)_j \mathbf{x}'(p) = {}_j \mathbf{b}'(p) - A'(p)_j \mathbf{x}(p).$$

If the procedure is unable to compute the parametric derivatives  $\partial A_{...}/\partial p$  in a symbolical way, they must be determined numerically using above approximation of  $A'(p)$  and the analogy is used

$${}_j \mathbf{b}'(p) \approx \frac{{}_j \mathbf{b}(p + \Delta p) - {}_j \mathbf{b}(p)}{\Delta p}, \quad j = 1, \dots, n_n,$$

which gives the final system

$$A(p)_j \mathbf{x}'(p) = \frac{{}_j \mathbf{b}(p + \Delta p) - A(p + \Delta p)_j \mathbf{x}(p)}{\Delta p}, \quad j = 1, \dots, n_n.$$



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 5 of 14

Go Back

Full Screen

Close

Quit

## 5. Noise-Figure Sensitivity Analysis

General formulae for computing the noise factor  $F_n$  and the noise figure  $F_n^{\text{dB}}$  are the following<sup>1</sup>

$$F_n = \frac{V_n^2 - V_{n,R_{\text{load}}}^2}{A_V^2 4kT_0 R_{\text{source}}}, \quad F_n^{\text{dB}} = 10 \log(F_n),$$

where  $V_n$ ,  $A_V$ ,  $k$ ,  $R_{\text{source}}$ , and  $T_0$  are the spectral density of the total output noise voltage, voltage gain, Boltzman constant, internal resistance of the input source, and standard temperature ( $T_0 = 290$  K).



[Outline](#)

[Algorithm in General](#)

[Standard Sensitivity...](#)

[Noise Sensitivity Analysis](#)

[Noise-Figure Sensitivity...](#)

[Distributed Amplifier](#)

[Monolithic Microwave...](#)

[-- Impedance Matching](#)

[-- Sensitivity Analysis](#)

[Home Page](#)



Page 6 of 14

[Go Back](#)

[Full Screen](#)

[Close](#)

[Quit](#)

## 5. Noise-Figure Sensitivity Analysis

General formulae for computing the noise factor  $F_n$  and the noise figure  $F_n^{\text{dB}}$  are the following<sup>1</sup>

$$F_n = \frac{V_n^2 - V_{n,R_{\text{load}}}^2}{A_V^2 4kT_0 R_{\text{source}}}, \quad F_n^{\text{dB}} = 10 \log(F_n),$$

where  $V_n$ ,  $A_V$ ,  $k$ ,  $R_{\text{source}}$ , and  $T_0$  are the spectral density of the total output noise voltage, voltage gain, Boltzman constant, internal resistance of the input source, and standard temperature ( $T_0 = 290$  K).

However, the procedure should be improved in the following ways:

- The circuit must be matched in advance because the Friis definition of the noise factor assumes **available** signal and noise powers.
- The subtraction is performed manually for each frequency in the original work. However, if the load resistor is created artificially as a current source controlled by its voltage, then the noise of the load resistor will **not** be generated.



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 6 of 14

Go Back

Full Screen

Close

Quit

<sup>1</sup>J. Ortiz and C. Denig, "Noise figure analysis using Spice," *Microwave Journal*, pp. 89–94, Apr. 1992.

By differentiating, the requested sensitivity of  $F_n^{\text{dB}}$  on the parameter  $p$  marked  $F_n^{\text{dB}'}$  can be obtained:

$$F_n^{\text{dB}'} \Big|_{V_n, R_{\text{load}} = 0} = \frac{10}{\ln(10)} \frac{1}{\frac{V_n^2}{A_V^2 4kT_0 R_{\text{source}}}} \times \frac{2V_n V_n' A_V^2 4kT_0 R_{\text{source}} - 2A_V A_V' 4kT_0 R_{\text{source}} V_n^2}{(A_V^2 4kT_0 R_{\text{source}})^2}$$

$$= \frac{20}{\ln(10)} \left( \frac{V_n'}{V_n} - \frac{A_V'}{A_V} \right).$$



[Outline](#)

[Algorithm in General](#)

[Standard Sensitivity...](#)

[Noise Sensitivity Analysis](#)

[Noise-Figure Sensitivity...](#)

[Distributed Amplifier](#)

[Monolithic Microwave...](#)

[-- Impedance Matching](#)

[-- Sensitivity Analysis](#)

[Home Page](#)



Page 7 of 14

[Go Back](#)

[Full Screen](#)

[Close](#)

[Quit](#)

By differentiating, the requested sensitivity of  $F_n^{\text{dB}}$  on the parameter  $p$  marked  $F_n^{\text{dB}'}$  can be obtained:

$$F_n^{\text{dB}'} \Big|_{V_n, R_{\text{load}} = 0} = \frac{10}{\ln(10)} \frac{1}{\frac{V_n^2}{A_V^2 4kT_0 R_{\text{source}}}} \times \frac{2V_n V_n' A_V^2 4kT_0 R_{\text{source}} - 2A_V A_V' 4kT_0 R_{\text{source}} V_n^2}{(A_V^2 4kT_0 R_{\text{source}})^2}$$

$$= \frac{20}{\ln(10)} \left( \frac{V_n'}{V_n} - \frac{A_V'}{A_V} \right).$$

Let us emphasize that the resulting formula is unusual—most of the CAD tools are not able to determine the sensitivity  $V_n'$  and therefore  $F_n^{\text{dB}'}$ , too.



[Outline](#)

[Algorithm in General](#)

[Standard Sensitivity...](#)

[Noise Sensitivity Analysis](#)

[Noise-Figure Sensitivity ...](#)

[Distributed Amplifier](#)

[Monolithic Microwave ...](#)

[-- Impedance Matching](#)

[-- Sensitivity Analysis](#)

[Home Page](#)



Page 7 of 14


[Go Back](#)

[Full Screen](#)

[Close](#)

[Quit](#)

## 6. Distributed Amplifier

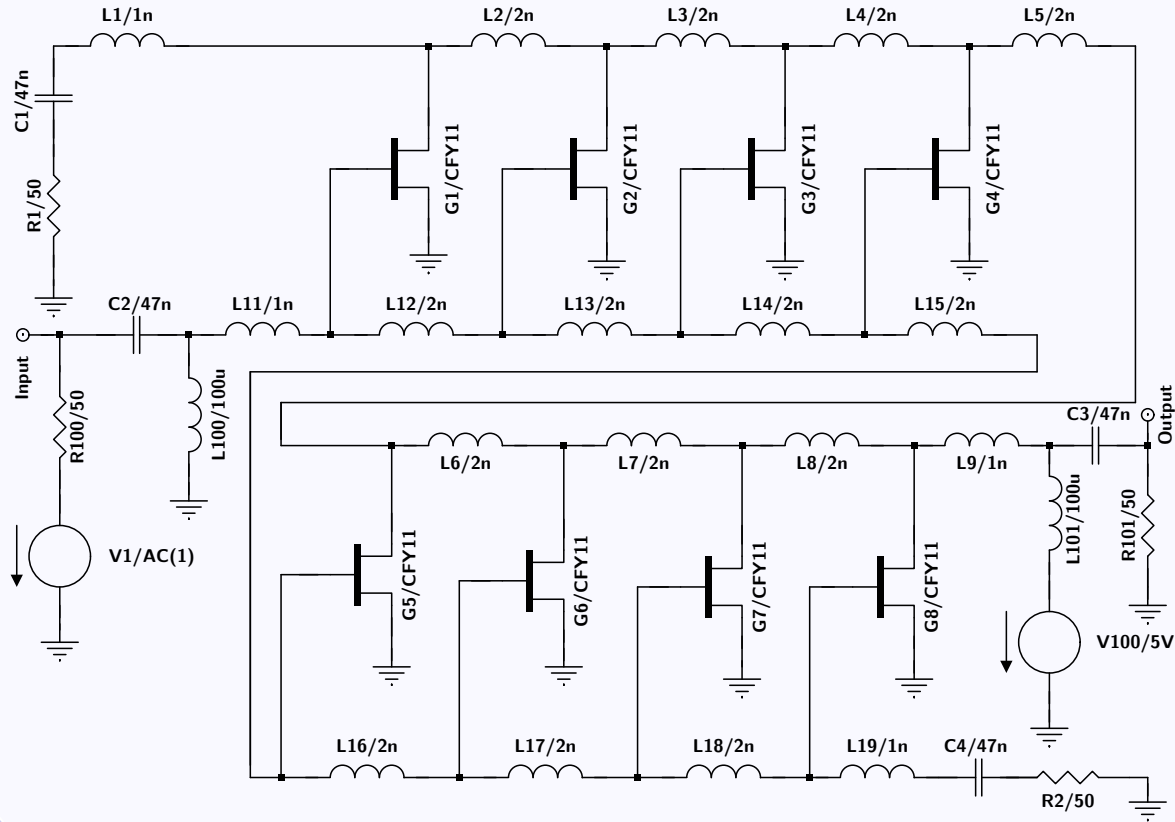

Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

**Distributed Amplifier**

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 8 of 14


Go Back

Full Screen

Close

Quit

## 6.1. Frequency Characteristic

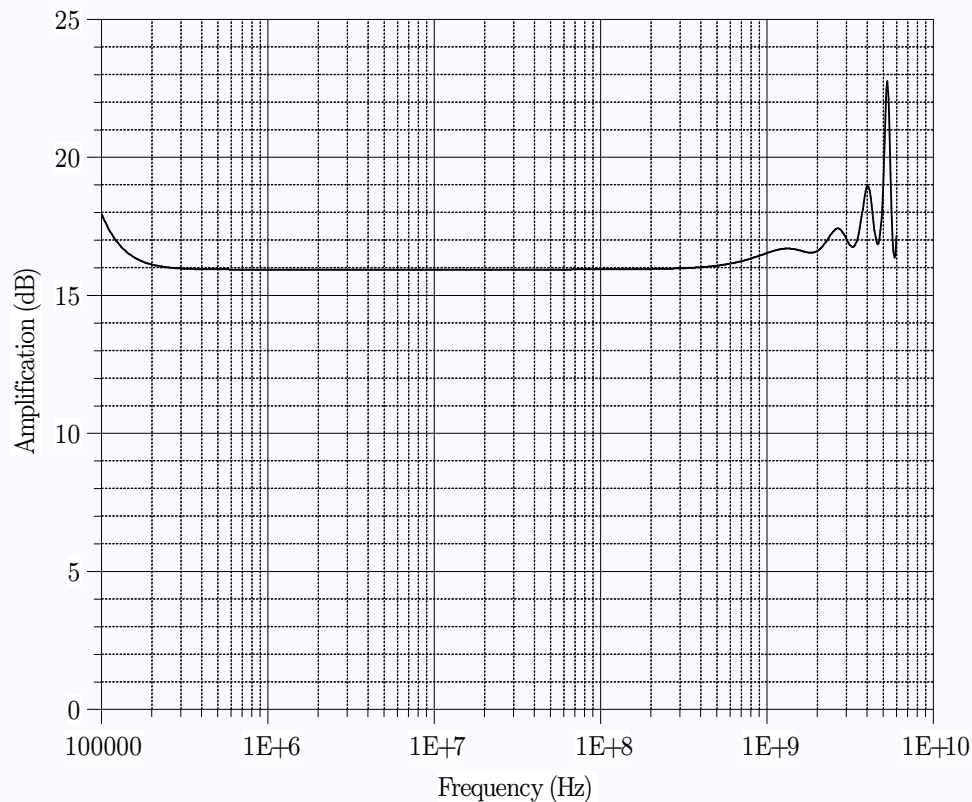

Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

**Distributed Amplifier**

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 9 of 14


Go Back

Full Screen

Close

Quit

## 6.2. Sensitivity Analysis

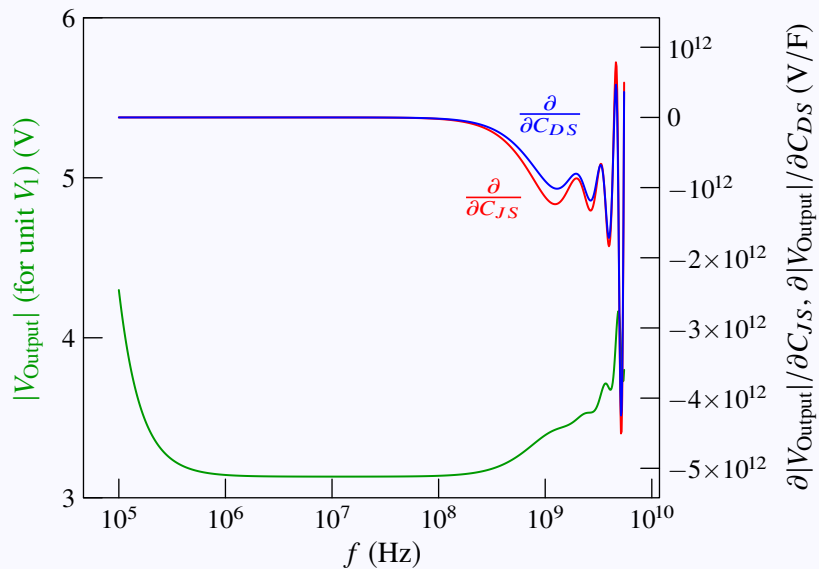

Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

**Distributed Amplifier**

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 10 of 14

Go Back


Full Screen

Close

Quit



## 6.2. Sensitivity Analysis

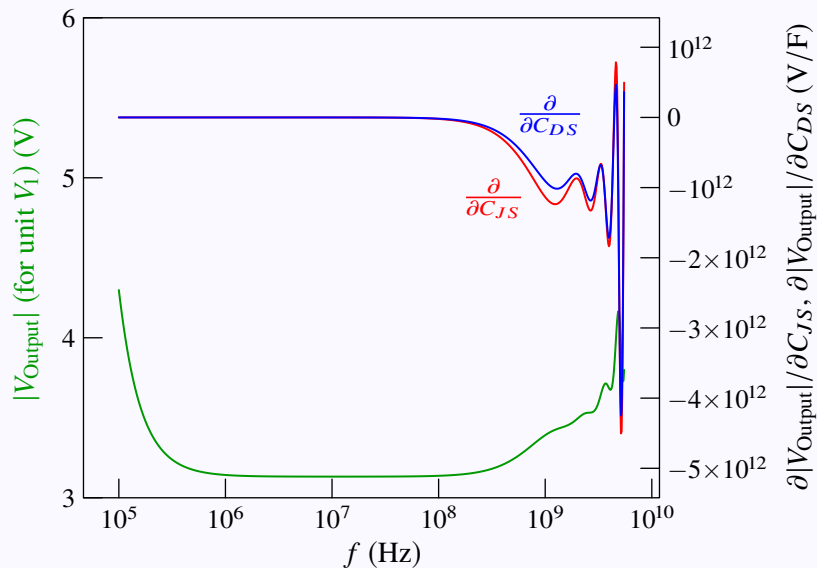

Nominally  $C_{JS} = 0.75$  pF, which is the output for  $C_{JS} = 0.751$  pF?

- Using the sensitivity analysis: 4.098543 V,
- Using the direct computation: 4.098516 V.



Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

**Distributed Amplifier**

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 10 of 14


Go Back

Full Screen

Close

Quit
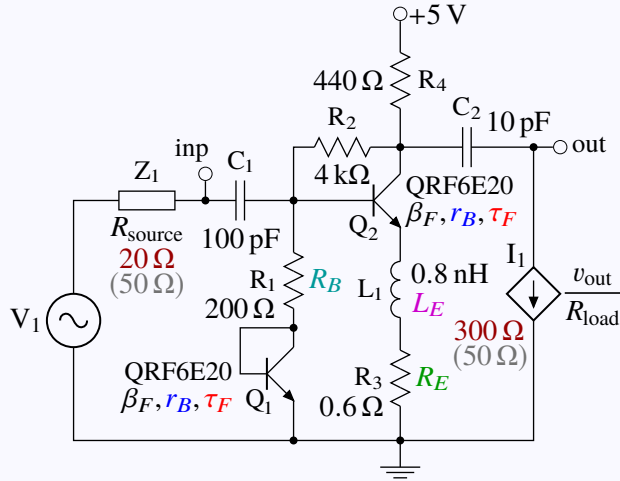
## 7. Monolithic Microwave Integrated Circuit (MMIC)



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 11 of 14

Go Back

Full Screen


Close

Quit

## 7.1. Optimizing Noise Figure

There are two possible improvements of the noise figure:

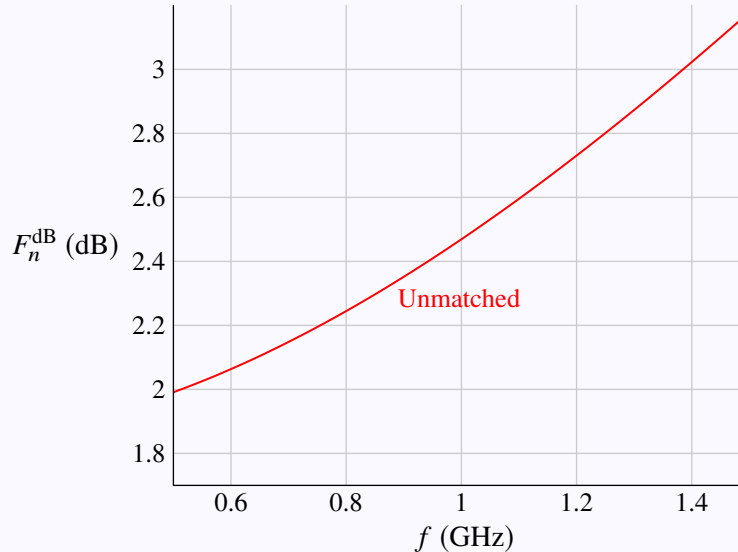1. Matching at the input and output
2. Updating a circuit parameter after the sensitivity analysis



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 12 of 14

Go Back

Full Screen


Close

Quit

## 7.1. Optimizing Noise Figure

There are two possible improvements of the noise figure:

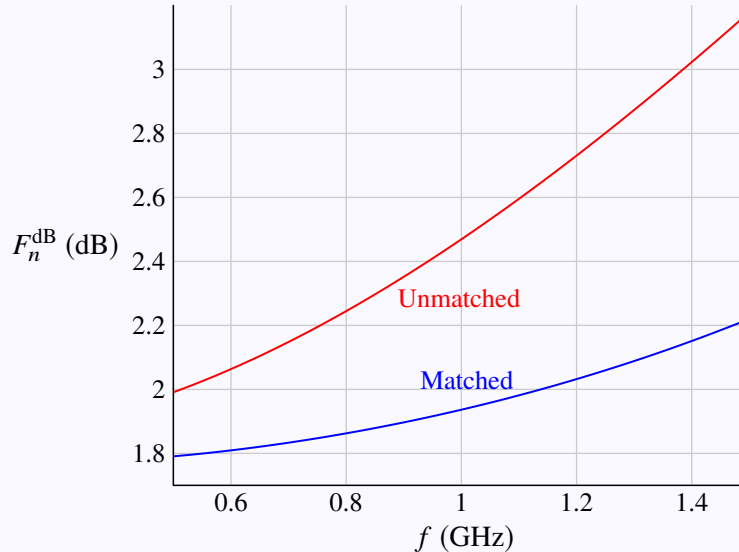1. Matching at the input and output
2. Updating a circuit parameter after the sensitivity analysis



Outline

Algorithm in General

Standard Sensitivity...

Noise Sensitivity Analysis

Noise-Figure Sensitivity...

Distributed Amplifier

Monolithic Microwave...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 12 of 14

Go Back

Full Screen


Close

Quit

## 7.1. Optimizing Noise Figure

There are two possible improvements of the noise figure:

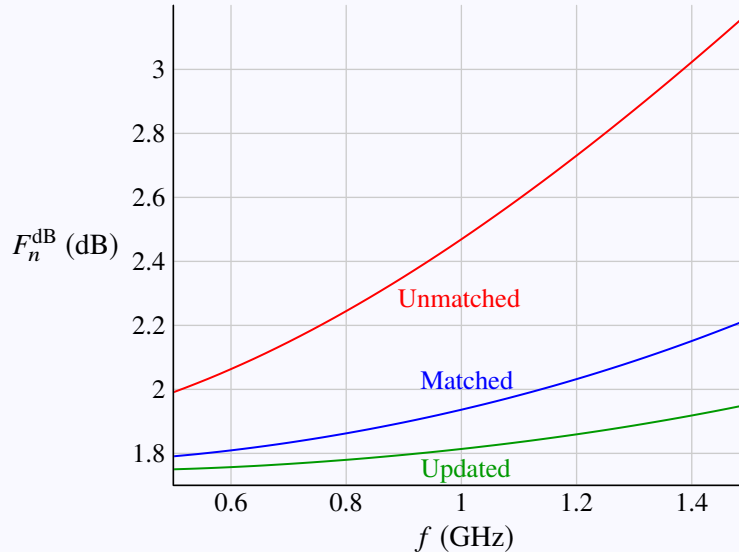1. Matching at the input and output
2. Updating a circuit parameter after the sensitivity analysis



Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

Distributed Amplifier

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 12 of 14


Go Back

Full Screen

Close

Quit

### 7.1.1. Impedance Matching

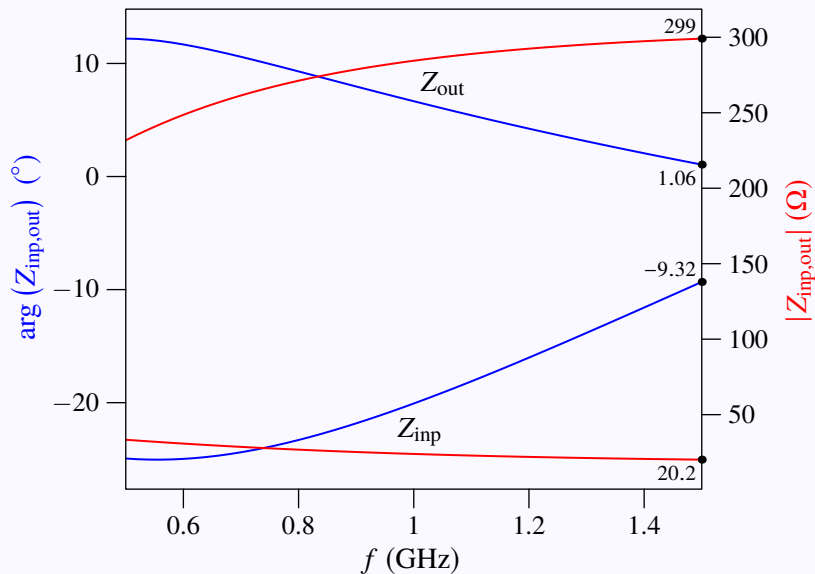

As the noise figure is the worst problem at 1.5 GHz, the impedance matching at this frequency was used. (And after that, we obtain “Matched” noise figure.)



Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

Distributed Amplifier

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 13 of 14


Go Back

Full Screen

Close

Quit

## 7.1.2. Sensitivity Analysis

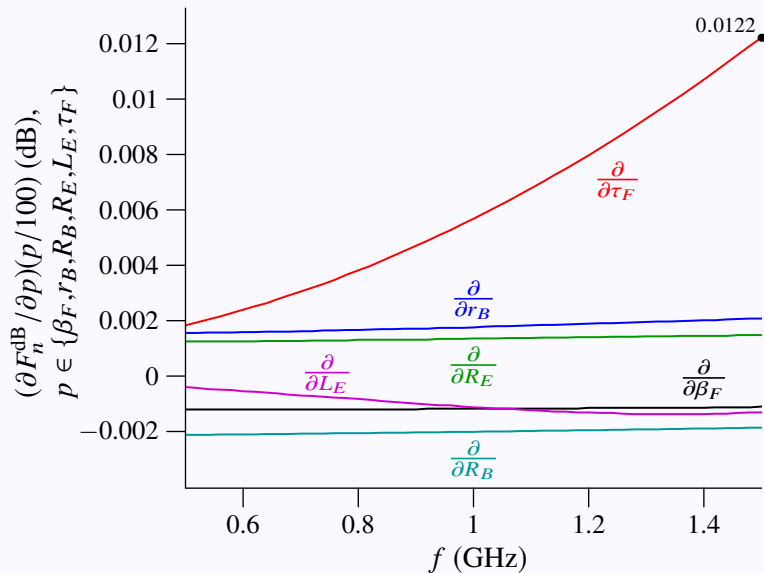

The transit time  $\tau_F$  of QRF6E20 was 28 ps. Therefore, it is now possible to use the transistors with  $\tau_F = 21$  ps (i.e., - 25 %). (And after that, we obtain “Updated” noise figure.)



Outline

Algorithm in General

Standard Sensitivity ...

Noise Sensitivity Analysis

Noise-Figure Sensitivity ...

Distributed Amplifier

Monolithic Microwave ...

-- Impedance Matching

-- Sensitivity Analysis

Home Page



Page 14 of 14

Go Back

Full Screen

Close

Quit