

## *Chapter 10*

# **Connectors, Packages, and Vias**

National Taiwan University of  
Science and Technology

Chun-Long Wang

# Outline

- Vias
- Connectors
- Chip Packages

# Vias

- Components of Vias

- Barrel


- The *barrel* is a conductive material that fills the hole to allow an electrical connection between layers.

- Pad

- The *pad* is used to connect the barrel to the component or trace.

- Antipad

 - The *antipad* is a clearance hole between the pad and the metal on a layer to which no connection is required.




# Vias

- Equivalent Circuit of Vias

- $\pi$  Network

- This is valid when **delay of the via** is smaller than **one-tenth** of the edge rate.
    - The **capacitors** represent the **via pad capacitance** on layers 1 and 2.
    - The **series inductance** represents the **barrel**.
    - The **via capacitance** will **slow down** the signal edge rate.
    - If several consecutive **vias** are placed in close **proximity** it will **lower** the effective characteristic impedance.

 

# Vias

- Equivalent Circuit of Vias

- $\pi$  Network

- The approximate value of the pad capacitance is

$$C_{\text{via}} \approx \frac{1.41 \epsilon_r D_1 T}{D_2 - D_1} \quad \text{picofarads}$$


- where  $D_2$  is the diameter of the antipad,  $D_1$  the diameter of the via pad,  $T$  the thickness of the PCB.
    - The inductance of the vias is usually more important than the capacitance, which will degrade the signal integrity and decrease the effect of decoupling capacitors.
    - The via inductance can be approximated by

$$L \approx 5.08h \left[ \ln \left( \frac{4h}{d} \right) + 1 \right] \quad \text{nano henries}$$
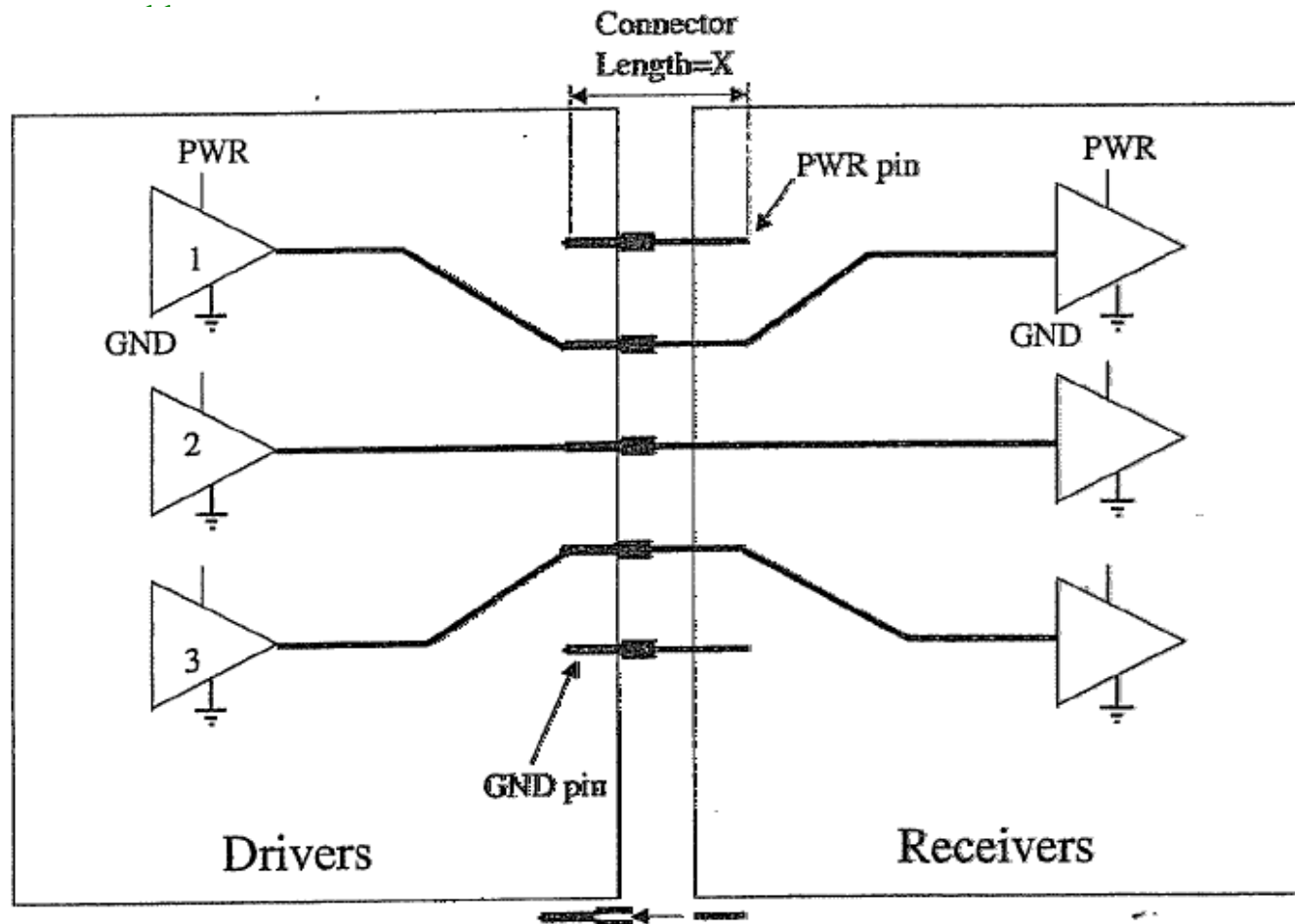
# Connectors

- Equivalent Circuit

- Series Inductance, Shunt Capacitance,  $C_r$



# Connectors

- Equivalent Circuit

- Series Inductance

- A series inductance can be estimated to a first-order level with the use of simple straight-wire formulas.
    - Estimates for the series inductance of round and rectangular wire, respectively, are

$$L \approx \frac{\mu_0}{2\pi} l \left[ \ln \left( \frac{2l}{r} \right) - \frac{3}{4} \right] \quad \text{nanohenries} \quad \text{for } r \ll l$$

$$L \approx \frac{\mu_0}{2\pi} l \left[ \ln \left( \frac{4l}{p} \right) + \frac{1}{2} \right] \quad \text{nanohenries}$$

- where  $l$  the length,  $r$  the radius of the wire, and  $p$  the perimeter.

# Connectors

- Equivalent Circuit

- Shunt Capacitance

- It can usually be ignored in the initial design.
    - It will slow down the system edge rate.
    - The addition of extra capacitance is sometimes used to mitigate the impedance discontinuity seen at the connector.
    - Extra capacitance can be added by using a wider pad, adding a small tab or widening out the connector pins.



# Connectors

- Equivalent Circuit

- Connector Crosstalk

- Typically, **the mutual inductance** plays a larger role than mutual capacitance.
    - **The mutual inductance** between two connector pins can be approximated as

$$L_M \approx \frac{\mu_0}{2\pi} l \left[ \ln \left( \frac{l}{s} + \sqrt{1 + \left( \frac{l}{s} \right)^2} \right) - \sqrt{1 + \left( \frac{s}{l} \right)^2} + \frac{s}{l} \right] \quad \text{nanohenries} \quad (5.)$$


$$L_M \approx \frac{\mu_0}{2\pi} l \left[ \ln \left( \frac{2l}{s} \right) - 1 \right] \quad \text{nanohenries} \quad \text{for } s \ll l \quad (5.)$$

- where  $l$  the length, and  $s$  the center-to-center spacing between the wires
      - **The mutual inductance** is largely independent on the **cross-sectional area** and the **shape of the conductor**.

# Connectors

- Effects of Inductively Coupled Connector Pin Fields

- Ground Effects Excluded

 

- The total induced voltage on pin 2 due to current changes in itself and pins 1 and 3 is


$$v_2 = L_{22}\dot{I}_2 + L_{21}\dot{I}_1 + L_{23}\dot{I}_3$$

- Assuming that the currents and the slew rates for each buffer are the same, a single-line equivalent model can be created

$$v_2 = \begin{cases} (L_{22} + L_{21} + L_{23})\dot{I} & \text{(all bits switching in phase)} \\ (L_{22} - L_{21} - L_{23})\dot{I} & \text{(bit 2 switching out of phase with bits 1 and 3)} \end{cases}$$
 
# Connectors

- Effects of Inductively Coupled Connector Pin Fields
  - Ground Effects Included



# Connectors

- Effects of Inductively Coupled Connector Pin Fields

- Ground Effects Included

- The response of the system is shown as

$$V_2 = L_{22}\dot{I}_2 + L_{21}\dot{I}_1 + L_{23}\dot{I}_3 + L_{2g}\dot{I}_g$$

$$V_{\text{gnd}} = L_{gg}\dot{I}_g + L_{g1}\dot{I}_1 + L_{g2}\dot{I}_2 + L_{g3}\dot{I}_3$$

$$\xrightarrow{\dot{I}_g = -(\dot{I}_1 + \dot{I}_2 + \dot{I}_3)} V'_2 = V_2 - V_{\text{gnd}}$$

$$V'_2 = \dot{I}_1(L_{21} - L_{2g} - L_{g1} + L_{gg}) + \dot{I}_2(L_{22} - L_{2g} - L_{g2} + L_{gg}) + \dot{I}_3(L_{23} - L_{2g} - L_{g3} + L_{gg})$$

$$\xrightarrow{\quad} V'_2 = L'_{22}\dot{I}_2 + L'_{21}\dot{I}_1 + L'_{23}\dot{I}_3$$

- For a group of  $n$  conductors with a single current return path:  $L'_{ij} = L_{ij} - L_{ig} - L_{gj} + L_{gg}$

# Connectors

- Effects of Inductively Coupled Connector Pin Fields

- Ground Effects Included

- The equations above are valid only for a coupled array of pins.
    - The total loop inductance of loop  $A$  has the largest total inductance, and loop  $C$  is the smallest.
    - Ways to reduce crosstalk effects:
      - maximize the total number of power and ground pins to decrease the total inductive path. It will effectively decrease  $L_{gg}$ .
      - place power and ground pins adjacent to each other because the currents flows in opposite directions.

Also, the area of the loop is proportional to the emission radiated.

# Connectors

- Connector Design Guidelines

- Non-Differential Signals

- Minimize the physical length of the connector pins to reduce the total series inductance.
    - Maximize the power and ground to signal pin ratio.
    - Each signal pin should be placed in close proximity to a power and a ground pin.

- Differential Signals

- The number of power and ground pins required will probably be far less than those for a similar single-ended system.
    - Without power or ground pins separating them.

# Connectors

- Connector Design Guidelines

- Conclusions

- Each signal pin should be tightly coupled to a current return pin.
    - The power and ground pins should be placed adjacent to each other.
    - The ratio of power pins to signal pins and the ratio of ground pins to signal pins are greater or equal to 1.
    - To use the shortest connector.
    - To increase the connector pin capacitance. But connector capacitance tends to slow the edge rates.

# Connectors

- Connector Design Guidelines

G	S	S	S	S	S	S	S	S	P
---	---	---	---	---	---	---	---	---	---

- Example 5.1 Choosing a Connector Pin Pattern

- This will exhibit **the worst performance** because the power and ground pins are physically **very far apart** from the signal pins.
    - This pin-out will **maximize the inductive noise** since the **return current** will **travel through a single power or ground pin**.
    - Large current loops** can exacerbate connector-related **EMI** and **increase series inductance**.
    - Since all the **signal pins** are **adjacent to each other**, **pin-to-pin crosstalk noise** will be maximized.




# Connectors

- Connector Design Guidelines

 - Example 5.1 Choosing a Connector Pin Pattern

- An increased number of power and ground pins will provide for lower-inductance current return paths and provide better power delivery.
    - Pin-to-pin crosstalk is also reduced.
    - The crosstalk between pairs, however, can still be quite high.
    - Notice that the connector size has increased by 30%.




- This is the optimal for the differential signaling but not the optimal for a single-ended signaling.

# Connectors


- Connector Design Guidelines

 - Example 5.1 Choosing a Connector Pin Pattern

- Both a power and a ground pin surround each signal pin. This minimizes the return current path inductance through both the power and ground pins.
- Pin-to-pin crosstalk between signals is reduced.
- The size of the connector has increased by 70%.




 
- The power and ground pins are always adjacent to each other.
- The best one is



- where the power/ground-to-signal ratio is 9 : 8.
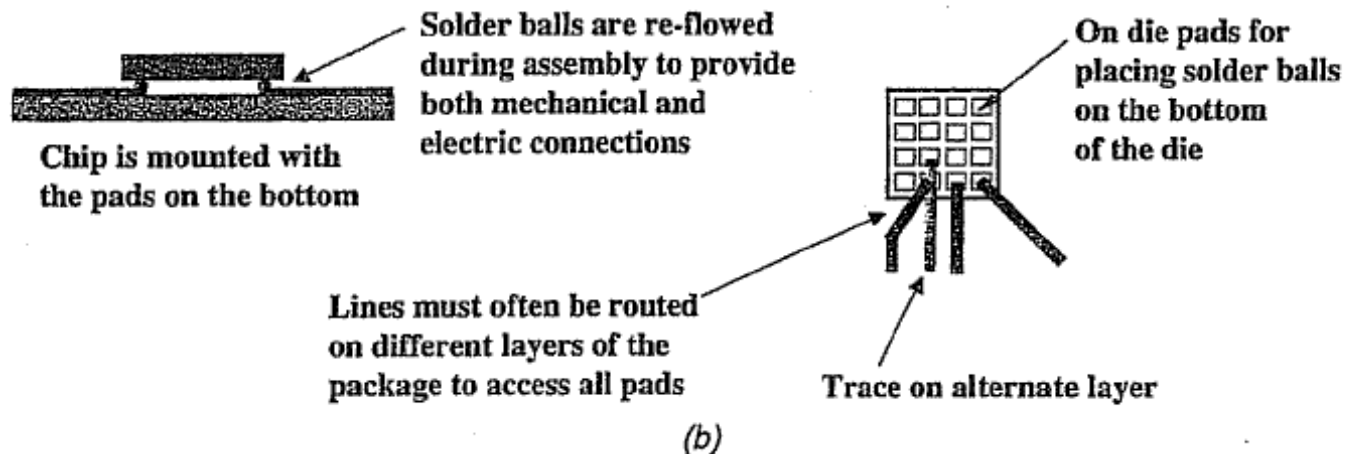 
# Chip Packages

- Common Types of Packages
  - Attachment of the Die to the Package
    - Wire bond and flip chip attachments




# Chip Packages

- Common Types of Packages

- Attachment of the Die to the Package—Wire Bond

 - A wire bond is simply a very small wire with a diameter on the order of 1 mil.
- Bond wire lengths vary from approximately 50 to 500 mils.



# Chip Packages

- Common Types of Packages
  - Attachment of the Die to the Package—Wire Bond
    - Section  $A$  is roughly perpendicular to the reference plane; subsequently, the reference plane will have a minimal effect.
    - Section  $B$  is roughly parallel to the reference plane with an approximate height of  $H_1$ . Subsequently, the inductance  $L_B$  must be calculated using the inductance of a straight wire in the presence of a ground plane. 
$$L = l(5.08 \times 10^{-9}) \ln \frac{4h}{d} \quad \text{nanohenries}$$
    - where  $l$  is the length in inches,  $h$  the height above the ground plane, and  $d$  the wire diameter.

# Chip Packages

- Common Types of Packages
  - Attachment of the Die to the Package—Wire Bond (Disadvantages)
    - Wire bonds also exhibit a large amount of crosstalk, which will cause pattern-dependent inductance values and ground return path problems.
    - The mutual inductance for two bond wires above a local ground plane is

$$L_M = L \frac{1}{1 + (s/h)^2} \quad \text{nanohenries}$$

- where  $L$  is the self-inductance of the two bond wires,  $s$  the center-to-center spacing, and  $h$  the height above the ground plane.

# Chip Packages

- Common Types of Packages
  - Attachment of the Die to the Package—Wire Bond (Advantages)
    - They are **inexpensive, mechanically simple**, and allow for some **changes in the bonding pad location** and **package routing**.
    - Furthermore, since the back of the chip is **attached directly to** the package substrate, it **maximizes heat transfer out** of the die.
    - (Disadvantage) **The I/O pads** tend to be limited to **the periphery of the die**, which will **inflate the die size** for a large number of I/O.

# Chip Packages

- Common Types of Packages
  - Attachment of the Die to the Package—Flip Chip (Advantages)
    - Flip-chip technology is also said to be *self-aligning*.
    - The series inductance of a flip-chip connection is much lower. The typical inductance is on the order of 0.1 nH.
    - Furthermore, the effect of crosstalk in a flip-chip connection can be ignored at low frequencies.
    - The bonding pads for a flip-chip connection can be placed over the entire die, not just on the periphery. This will help to minimize die size when a large number of I/O cells are required.



# Chip Packages

- Common Types of Packages

- Attachment of the Die to the Package—Flip Chip (Disadvantages)


- Mechanically and thermally, however, flip-chip technology is dismal.
    - The thermal coefficient of expansion must be very close between the die and the package substrate.
    - Furthermore, the physical tolerances must be very tight.
    - Cooling is also more difficult with flip-chip technology.

Table 5.1: Comparison of Wire Bond and Flip-Chip Technology

	Series Inductance (nH)	Minimum Pitch (mils)	I/O Placement	Cooling
Wire bond	1–5	4–6	Periphery only	Easy
Flip chip	0.1	2–3	Entire surface	Difficult


 
# Chip Packages

- Common Types of Packages
  - Routing of the Signals on the Package
    - *Controlled Impedance:*
    - For **high-speed digital designs**
    - This package typically resembles **a miniature PCB board** with different layers and power and ground planes with **a centered cavity used for die placement.**
    - **The chip** is usually attached with **flip-chip bonding**, although short wire bonds are often used.
    - **Small-dimensioned transmission lines** are used to route the signals **from the bond pad** on the package **to the board attachment.**


  
# Chip Packages

- Common Types of Packages
  - Routing of the Signals on the Package
    - *Noncontrolled Impedance:*
    - **Noncontrolled-impedance** packages usually **wire bond** the **die** directly to a **lead frame**, which is then soldered to the board.
    - This creates **a series inductance** that can wreak havoc on the signal integrity.




# Chip Packages

- Common Types of Packages
  - Attachment of the Package to the Board
    - *A Lead Frame:*
      - A *lead frame* is simply a **metal frame** that is integral to the package, which provides an **electrical connection** between the wire bonds and the PCB.
        - A **through-hole mount** is achieved by drilling a hole through the PCB, inserting the lead frame pins through the hole, and **re-flowing solder**.
        - A **surface-mount attachment** is achieved by soldering the lead frame pins onto pads **on the surface layer** of the PCB.
      - *A pin-grid array:*
        - A *pin-grid array* (PGA) consists of an **array of pins** that stick out of the bottom part of the package.

 
# Chip Packages

- Creating a Package Model
  - Example 5.2 Controlled-Impedance Package
    - Step 1: Attachment of the die to the package
    - Step 2: Routing of the signals on the package
    - Step 3: Attachment of the package to the PCB



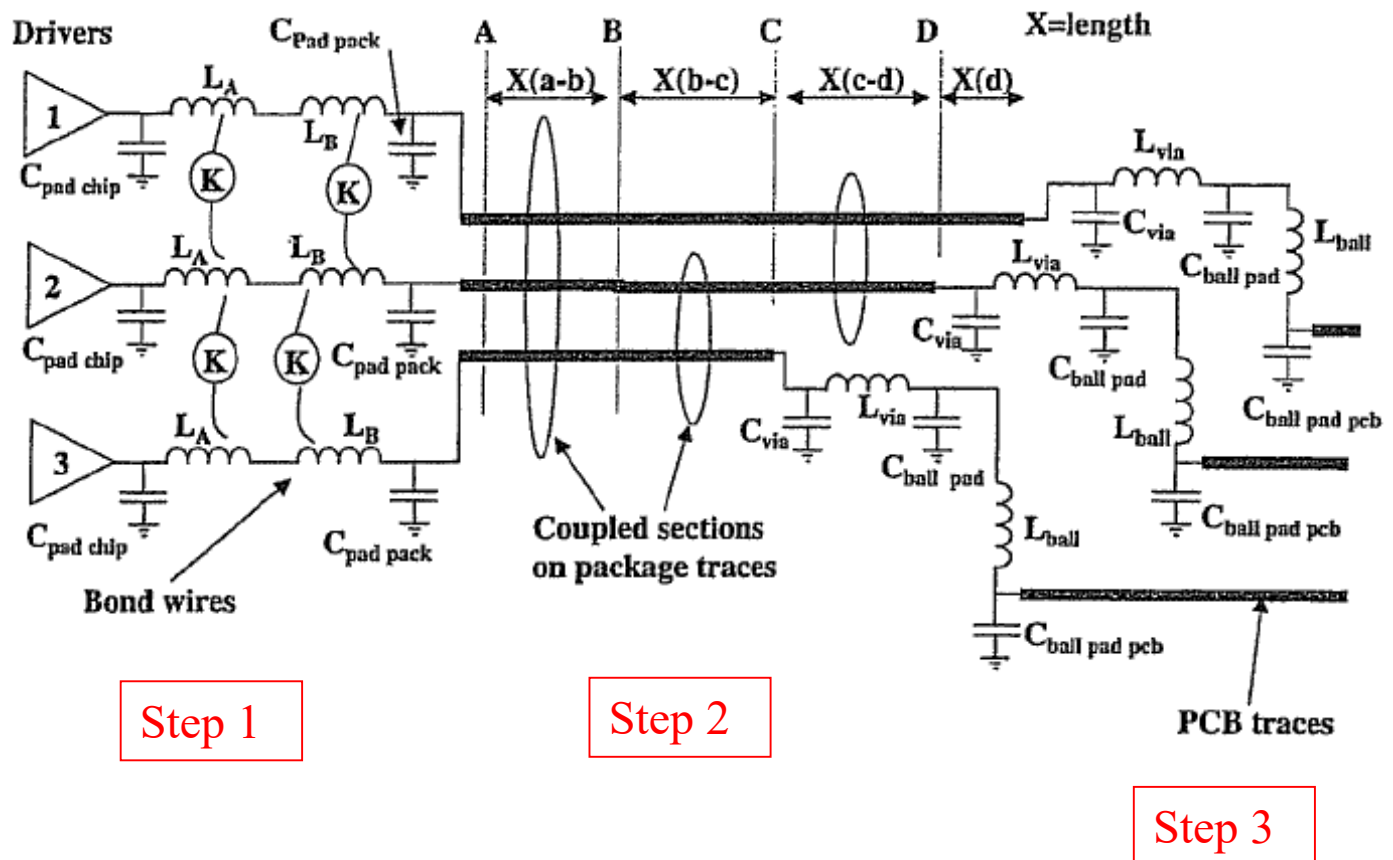
# Chip Packages

- Creating a Package Model
  - Example 5.2 Controlled-Impedance Package
    - The equivalent circuit is shown below.


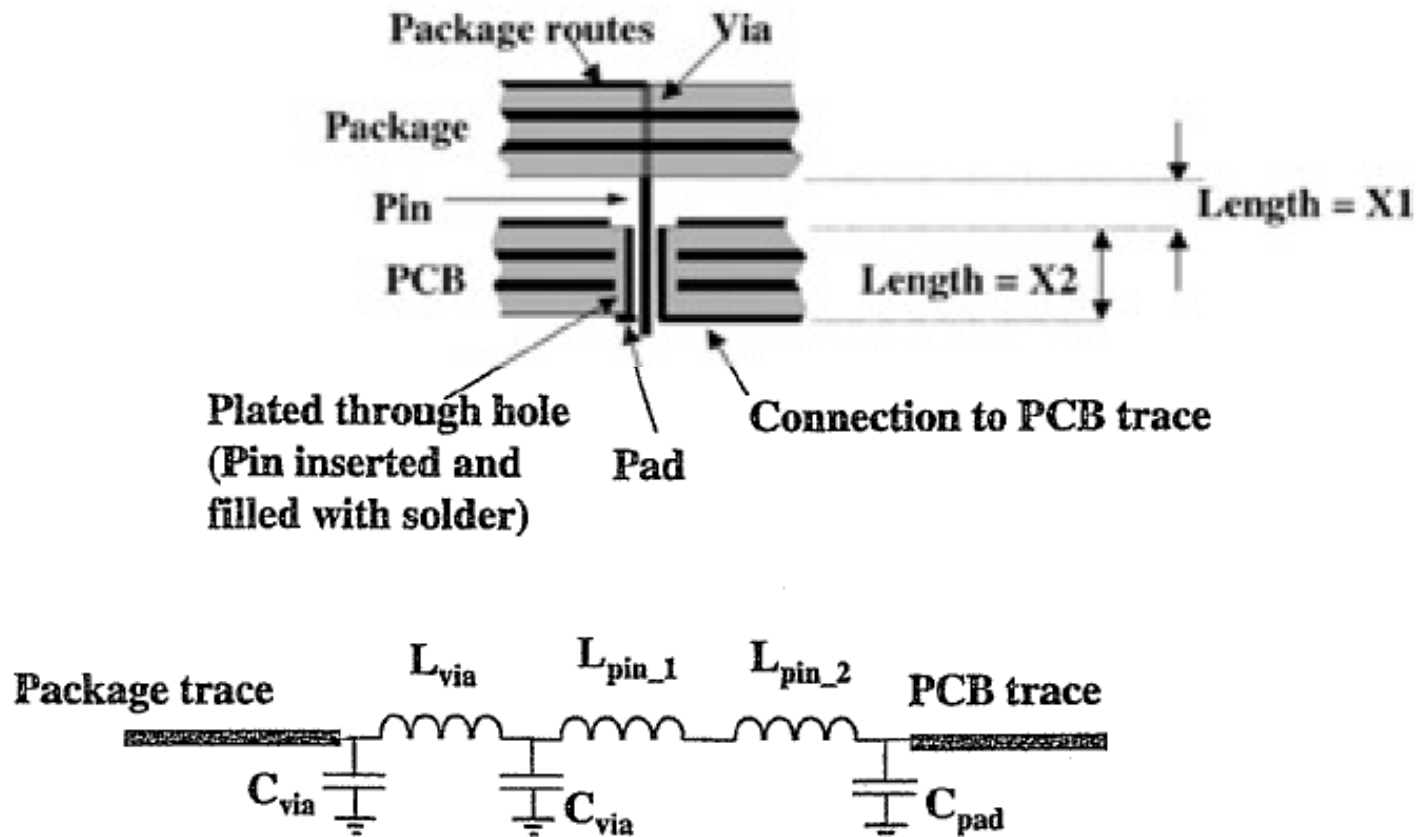
# Chip Packages

- Creating a Package Model
  - Example 5.2 Pin-Grid-Array Attachment




# Chip Packages


- Effect of a Package

- Point-to-Point Bus Topology

 
- *Case 1:* noncontrolled-impedance package with a total bond length (bond wire plus lead frame) of 0.75 in.



 - *Case 2:* controlled-impedance package with 0.25-in. bond wires and a 40- $\Omega$  transmission line on the package.




 
- *Case 3:* controlled-impedance package with die flip-chip attached to the package and 40- $\Omega$  package routing.




  
# Chip Packages

- Effect of a Package
  - Point-to-Point Bus Topology



	$Z_{0\_package}$	$L_{bond}$	$L_{gnd}$
Case1	50 ohm	15nH	1.5nH
Case2	40 ohm	5nH	0.5nH
Case3	40 ohm	0.1nH	0.01nH

# Chip Packages

- Effect of a Package

- Point-to-Point Bus Topology


- The edge rate has been slowed significantly due to the extra inductance. This is because the inductance will act as a low-pass filter, which will attenuate the high-frequency components.
    - Case3 is the best one, case 2 is the secondary one and case 1 is the worst one. ( $L_{\text{case3}} < L_{\text{case2}} < L_{\text{case1}}$ )
    - Also, the crosstalk between bond wires and leads in case 1 cause significant pattern-dependent inductance values (due to the mutual inductance), which will cause edge-rate differences and degrade timing margins further.

# Chip Packages

- Effect of a Package

- Multidrop or Daisy Chain Topologies

 - The effect of packaging on such bus topologies is largely dependent on the package stub length:
      - If the package stub is long, it will induce transmission line reflections that degrade the signal quality.
      - If the package length is short, it will produce significant filtering effects that degrade the edge rate and change the effective characteristics of the transmission line.




# Chip Packages

- Effect of a Package

- Long Package Stub Effect

 - A package stub is considered to be long if  $TD_{\text{stub}} > \frac{1}{2}T_{10-90\%}$
    - where  $TD_{\text{stub}}$  is the electrical delay of the unloaded package stub and  $T_{10-90\%}$  is the rise or fall time of the signal edge.




# Chip Packages

- Effect of a Package

- Long Package Stub Effect


- Effect of package stub length:

 

The capacitive loading at the end of the stub will increase the effective electrical delay of the stub by approximately 1 time constant ( $Z_0C$ ).

The length of the ledge depends on the electrical delay of the stub.

- Effect of package stub impedance

 

The impedance of the stub influences the level of the ledge (path 1).


# Chip Packages

- Effect of a Package

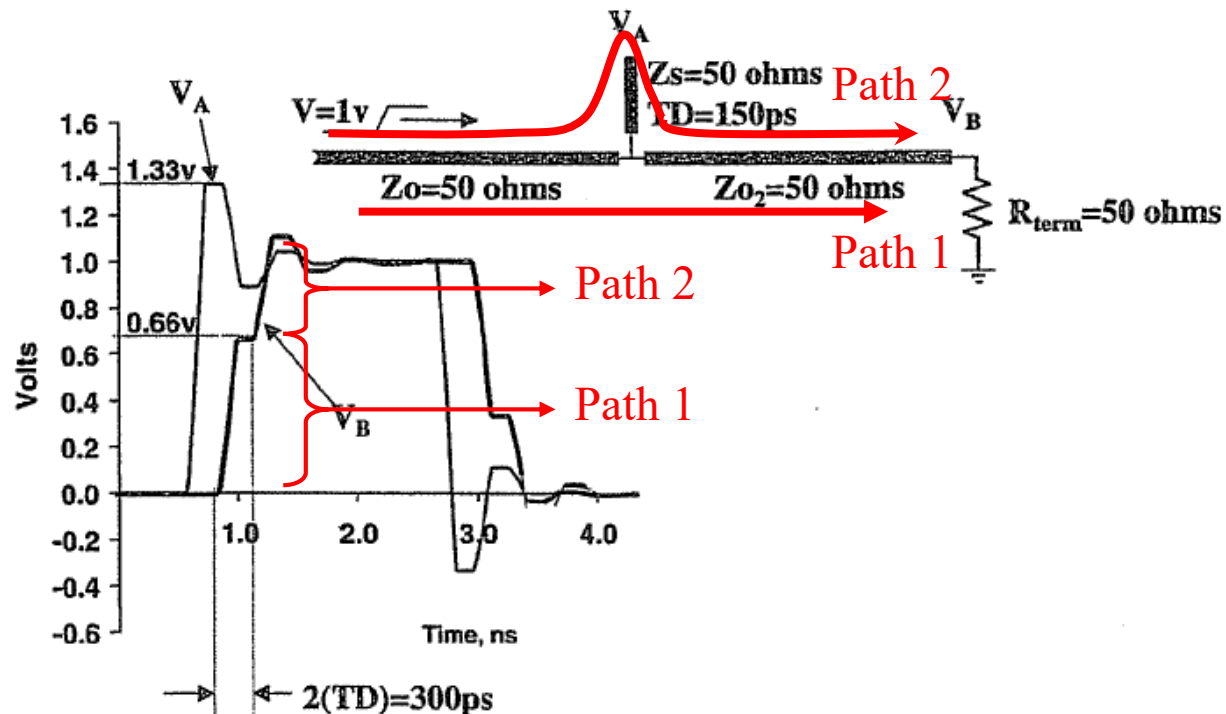- Example 5.4 Effects of a Long Package Stub

- The reflection coefficient looking into the stub junction is

$$\rho_{\text{at stub}} = \frac{Z_s \parallel Z_{o_2} - Z_o}{Z_s \parallel Z_{o_2} + Z_o} = -\frac{1}{3} \longrightarrow \boxed{T = 1 + \rho_{\text{at stub}} = 2/3}$$



# Chip Packages

- Effect of a Package

- Example 5.4 Effects of a Long Package Stub

- The transmission coefficient down the stub and the second half of the trunk is

$$T = 1 + \rho_{\text{at stub}} = 1 + \frac{Z_s \parallel Z_{o_2} - Z_o}{Z_s \parallel Z_{o_2} + Z_o} = \frac{2}{3}$$

- Subsequently, the voltage arrived first at node *B* (path 1) is

$$V_B = VT = 1.0 \left( \frac{2}{3} \right) = 0.666 \text{ V}$$

- The voltage arrived secondly at node *B* (path 2) is

$$0.66\text{V} \cdot (2/3) = 0.44 \text{ V}$$

- The voltage from the first reflection at node *A* is

$$V_A = 2VT = 1.33 \text{ V}$$


The timing push-out caused by the stub at node B depends on twice the total delay of the stub.

# Chip Packages

- Effect of a Package

- Widely Spaced Short Package Stub Effect

 - A package stub is considered to be short if  $TD_{\text{stub}} < \frac{1}{2}T_{10-90\%}$
- where  $TD_{\text{stub}}$  is the electrical delay of the unloaded package stub and  $T_{10-90\%}$  is the rise or fall time of the signal edge.
- When a package stub is sufficiently short, the load will look like a capacitor.





# Chip Packages

- Effect of a Package

- Widely Spaced Short Package Stub Effect

- The reflection and transmission coefficients are

$$\rho_{\text{cap}} = \frac{Z_o \parallel (1/j\omega C) - Z_o}{Z_o \parallel (1/j\omega C) + Z_o} = \frac{-Z_o(j\omega C)}{2 + Z_o(j\omega C)} \approx \frac{-Z_o(j\omega C)}{2}$$

$$T_{\text{cap}} = 1 + \rho_{\text{cap}} \approx 1 - \frac{Z_o(j\omega C)}{2}$$

- As the capacitance increases, the transmission coefficient decreases for a given frequency.
    - Assuming a very fast input edge rate, the transmitted edge will have an edge rate approximately equal to

$$T_{\text{edge}} \approx \frac{2.2(Z_o C)}{2}$$


- The rise or fall time of the signal after it passes though the capacitive load is  $T_{\text{system}} \approx \sqrt{T_{\text{edge}}^2 + T_{\text{input}}^2}$

# Chip Packages

- Effect of a Package

- Distributed Capacitive Loading on a bus (Narrow Spacing)

- RIMM memory module:

 

- The equivalent impedance and delay parameters for a uniformly capacitive loaded are

$$Z'_o = \sqrt{\frac{L}{C + NC_L/X}} \quad \downarrow \quad TD' = \sqrt{L \left( C + \frac{NC_L}{X} \right)} \quad \uparrow$$

Per unit length delay


- where  $L$  and  $C$  are the distributed transmission line parasitics,  $N$  the number of loads, and  $X$  the line length.

# Chip Packages

- Optimal Pin-Outs

- Square v.s. Rectangular Shape

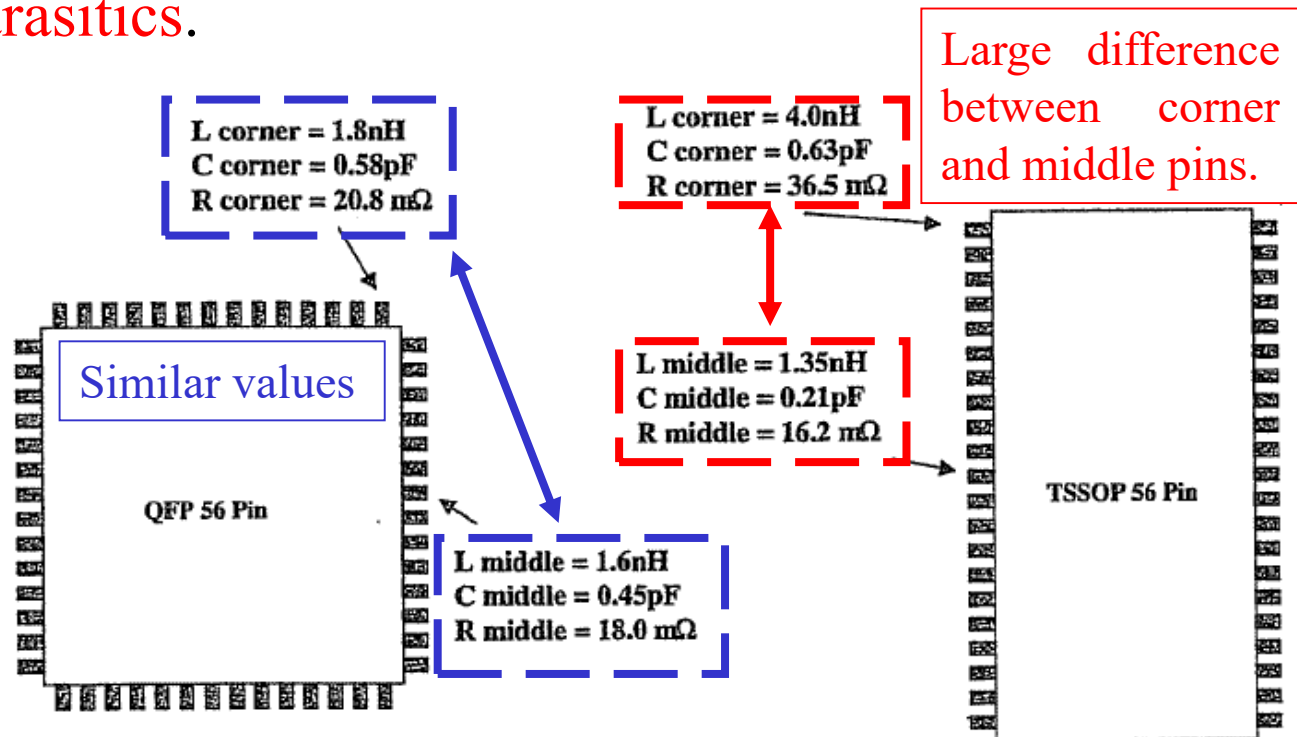- In some applications, pin-to-pin parasitic matching is more important than minimizing total pin parasitics.



# Chip Packages

- Package Design

- Rules of Thumb

- Use controlled packaging for a high-speed design.
    - Minimize inductance by using flip-chip or the shortest possible bond wire lengths for die attachment.
    - Follow all the same pin-out rules of thumb as described for connector design when choosing power and ground pin ratios.
    - Use the shortest possible package interconnect lengths to minimize impedance discontinuities and stub effects.

# Chip Packages

- Package Design

- Rules of Thumb

- On a multidrop bus, stub length is often the primary system performance inhibitor.
    - In a multidrop bus design, never use long stubs that are narrowly spaced.
    - Pin-to-pin package parasitic mismatch, which is strongly affected by the physical aspect ratio of the package, should be considered.