

# Microwave Circuits and Sub-Systems

## A2M17MOS

### Narrow-Band Amplifier Design – Part B

**Přemysl Hudec**  
**CTU Prague, Faculty of Electrical Engineering**

**hudecp@fel.cvut.cz**

version 2014



# Contents

- Stability conditions
- Design of amplifiers with absolutely stable transistors
- Design of amplifiers with potentially unstable transistors
- Design of amplifiers with stabilized transistors
- Definition of noise parameters
- Cascade of noisy 2-ports
- Noise figure of passive 2-ports
- LNA design steps

# Absolute Stability Conditions

- **Absolute stability** conditions:

$$|\Gamma_1| \leq 1 \quad \text{for all passive loads} \quad |\Gamma_L| \leq 1$$


$$|\Gamma_2| \leq 1 \quad \text{for all passive sources} \quad |\Gamma_G| \leq 1$$

- Stability factor 
$$k = \frac{1 - |s_{11}|^2 - |s_{22}|^2 + |D|^2}{2|s_{12}s_{21}|} \quad D = s_{11}s_{22} - s_{12}s_{21}$$

- Absolutely stable transistor  $k \geq 1 \rightarrow$  **ideal amplifier** can be designed:

- Input reflections  $|\Gamma_{in}| \rightarrow 0$       output reflections  $|\Gamma_{out}| \rightarrow 0$
- Gain  $G_t = G_{a \max}$

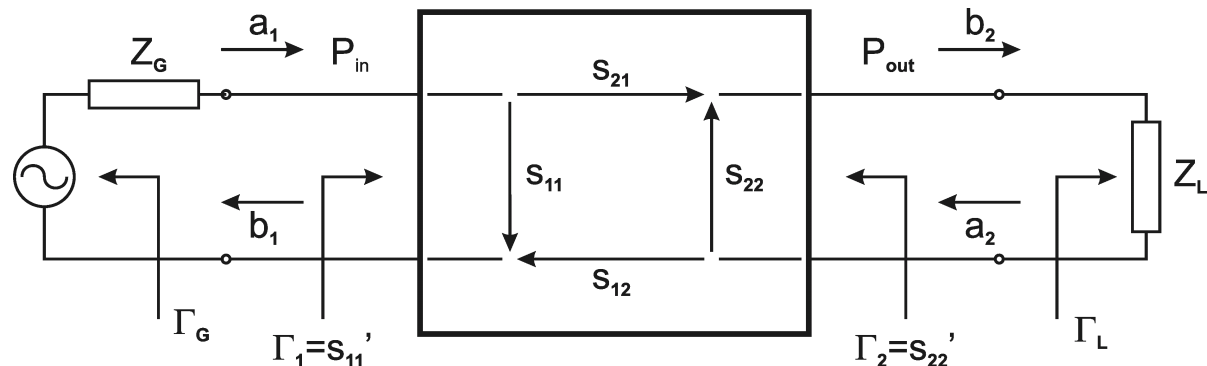- **Resulting amplifier**  $\rightarrow$  ideally matched, highest possible gain (at the given frequency and transistor biasing point)




# Amplifier with Absolutely Stable Transistor

- Basic impedance matching conditions:

$$\Gamma_{Gopt}^* = \Gamma_1 = s_{11} + \frac{s_{12}s_{21}\Gamma_{Lopt}}{1 - s_{22}\Gamma_{Lopt}}$$

$$\Gamma_{Lopt}^* = \Gamma_2 = s_{22} + \frac{s_{12}s_{21}\Gamma_{Gopt}}{1 - s_{11}\Gamma_{Gopt}}$$

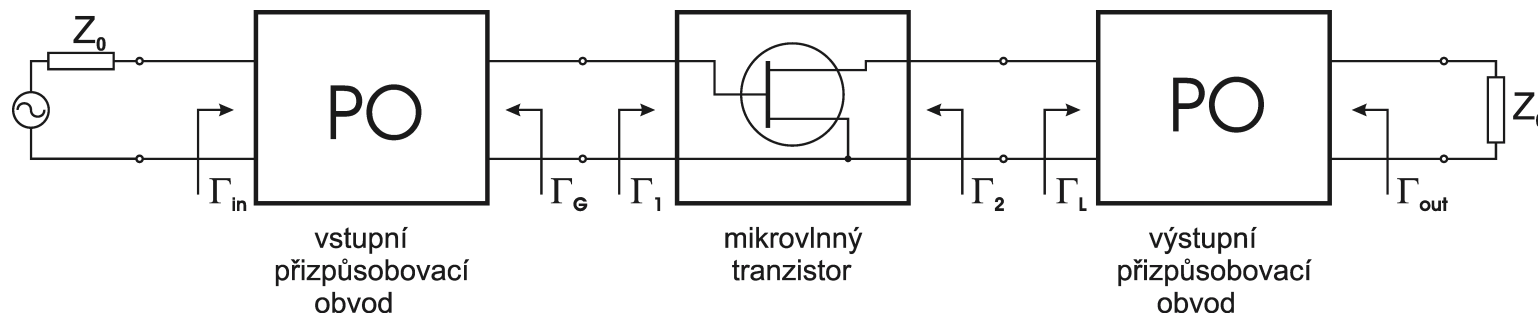- Set of two equations with two unknowns  $\rightarrow \Gamma_{Gopt}, \Gamma_{Lopt}$



# Amplifier with Absolutely Stable Transistor

- Solution:

$$\Gamma_{Gopt} = C_1^* \left[ B_1 \pm \left( B_1^2 - 4|C_1|^2 \right)^{\frac{1}{2}} \right] \frac{1}{2|C_1|^2}$$

$$\Gamma_{Lopt} = C_2^* \left[ B_2 \pm \left( B_2^2 - 4|C_2|^2 \right)^{\frac{1}{2}} \right] \frac{1}{2|C_2|^2}$$
- Auxiliary variables:

$$B_1 = 1 + |s_{11}|^2 - |s_{22}|^2 - |D|^2$$

$$B_2 = 1 - |s_{11}|^2 + |s_{22}|^2 - |D|^2$$

$$C_1 = s_{11} - D.s_{22}^*$$

$$C_2 = s_{22} - D.s_{11}^*$$



$$D = s_{11}s_{22} - s_{12}s_{21}$$
- Signs:

+ if  $B_j < 0$

- if  $B_j > 0$
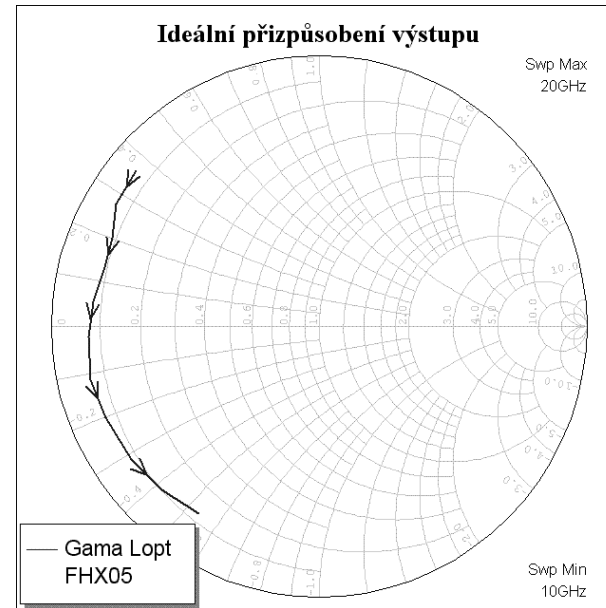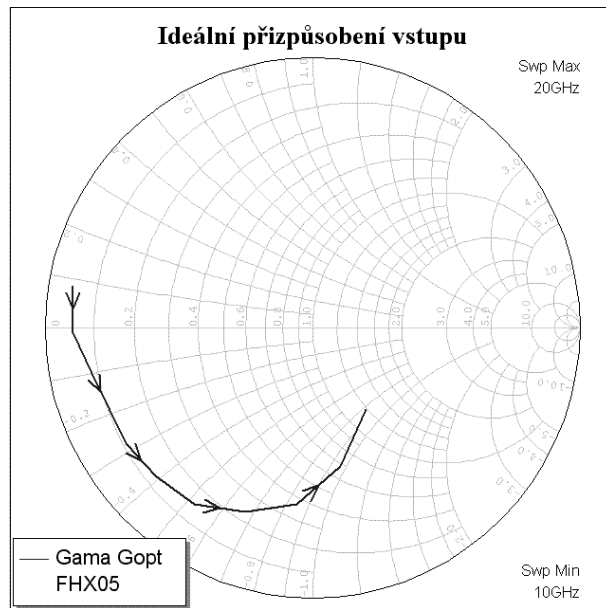
# Wideband Impedance Matching

- **AWR-MO:**  $\Gamma_{Gopt} = GM1$      $\Gamma_{Lopt} = GM2$





- Frequency plots of  $\Gamma_{Gopt}$  and  $\Gamma_{Lopt}$  run **counter-clockwise**
- Frequency plot of ANY matching circuit run clockwise
- Ideal impedance matching can be reached only at 1 frequency, or at several discrete and distant frequencies
- It is NOT possible to design wideband amplifiers with ideal impedance matching

# Design Steps – Example 1




- With the  $\Gamma_{Gopt}$  and  $\Gamma_{Lopt}$  values known (GM1, GM2 provided by AWR-MO) it is possible to synthesize the whole **absolutely stable amplifier**:
  - Input MC  $\rightarrow$  transforms  $Z_0$  to  $\Gamma_{Gopt}$
  - Output MC  $\rightarrow$  transforms  $Z_0$  to  $\Gamma_{Lopt}$
  - Input reflection coeff.  $\Gamma_{in} \rightarrow 0$
  - Output reflection coeff.  $\Gamma_{out} \rightarrow 0$
  - Gain is equal to  $G_{amax}$

## Example: FHX05, 12 GHz

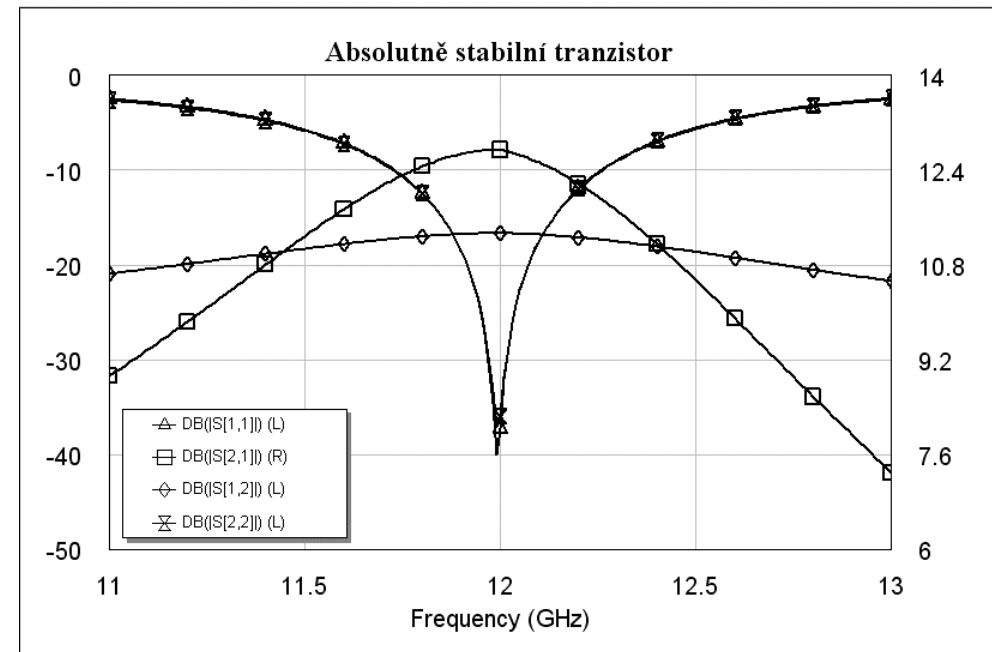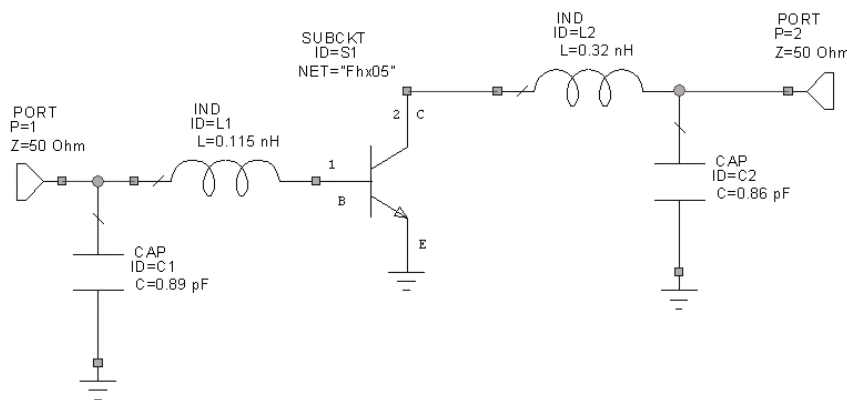

# Example 2

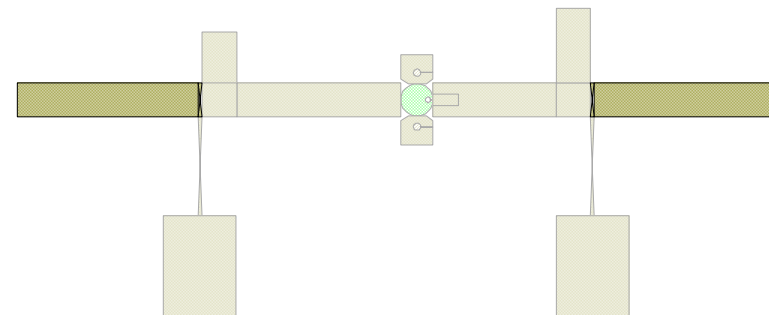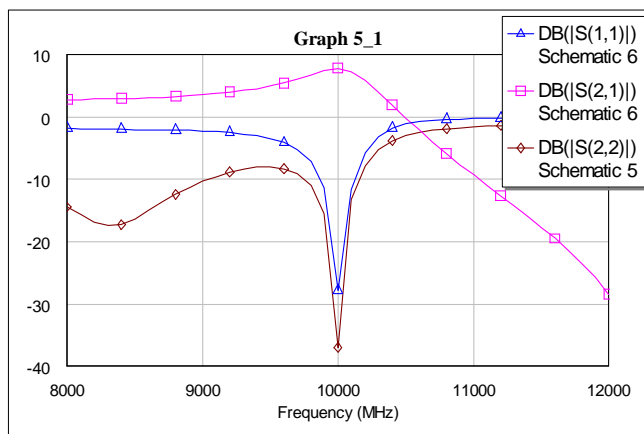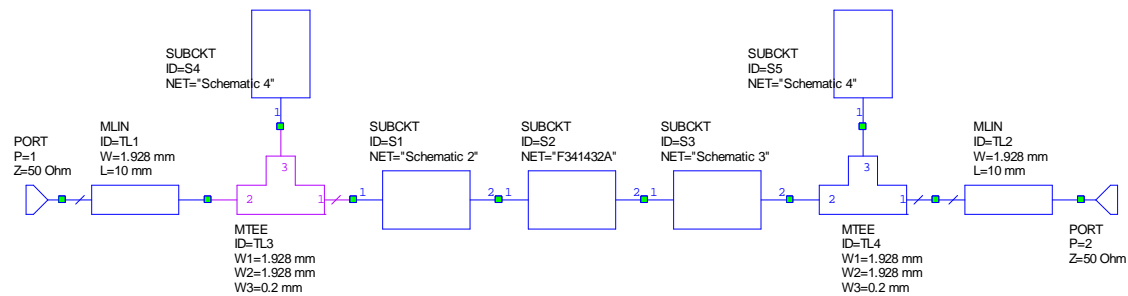- Task No.2 – amplifier with absolutely stable transistor
  - ATF-34143 (file F341432A.S2P), FET, 2V/20mA
  - $f=10\text{GHz}$
  - $k>1$
  - $GM1= 0,821 / -36^\circ$
  - $GM2=0,4975 / -85^\circ$







# Amplifier with Potentially Unstable Transistor

- **More complicated design:**

- Definite  $\Gamma_G$  and  $\Gamma_L$  values can cause the amplifier to oscillate
- The  $G_{a\max}$  parameter is not defined,  $G_{ms}$  must be used
- Stability must be treated


- **Worse attainable parameters:**

- Cannot be simultaneously matched both at input and output
- If matched at input  $\Gamma_{in} \rightarrow 0$  there appears reflection at output  $|\Gamma_{out}| > 0$
- If matched at output  $\Gamma_{out} \rightarrow 0$  there appears reflection at input  $|\Gamma_{in}| > 0$
- There can be reflections both at input  $|\Gamma_{in}| > 0$  and output  $|\Gamma_{out}| > 0$
- Gain must be lower than  $G_{ms}$  (by 1 – 2 dB)
- Amplifier is only **CONDITIONALLY stable**

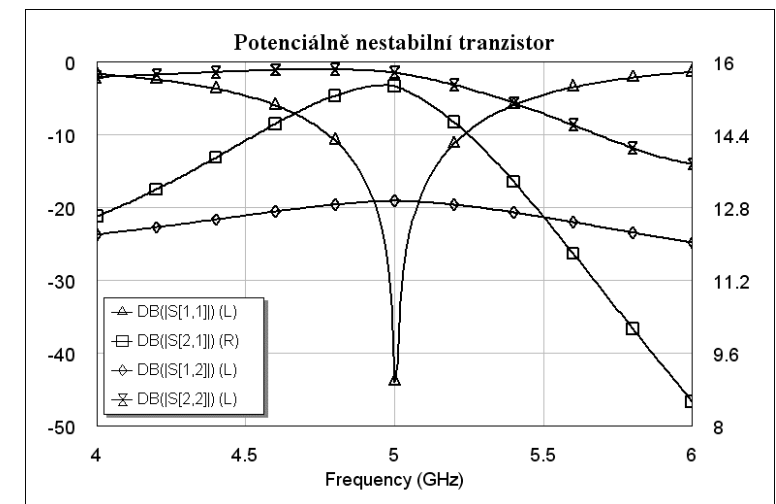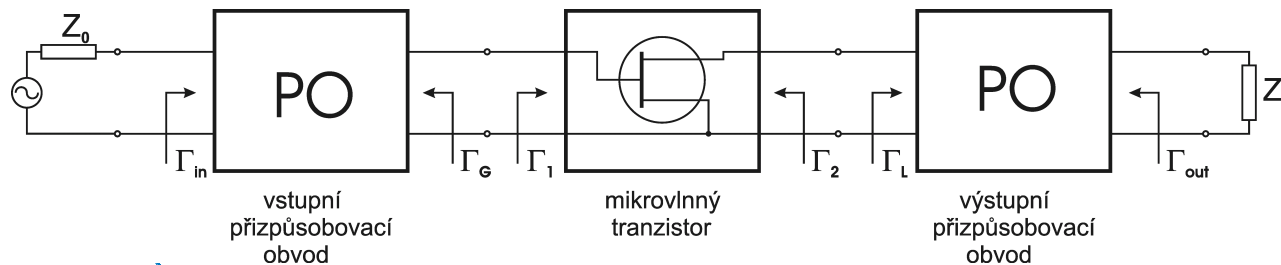

# Amplifier with Potentially Unstable Transistor

- Design with **ideal impedance matching at the input**  $\Gamma_{in} \rightarrow 0$  :
- Resulting parameters:
  - Ideal impedance matching at input  $\Gamma_{in} \rightarrow 0$
  - General reflection at output  $|\Gamma_{out}| \leq 1$  (example: dBs22 $\approx$ -3dB)
  - Operational gain is by 1-2 dB lower than  $G_{ms}$
- Design steps:
  - Ensuring of stability
  - Impedance matching

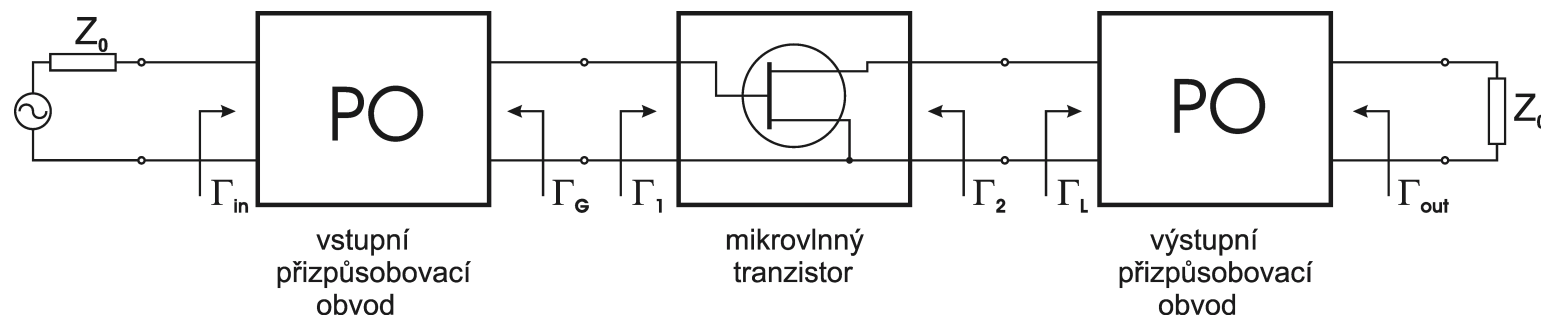

# Stability Circles

- **Stability** → will be treated in the  $\Gamma_L$  plane (due to the required imp. matching at input)
- Stability circles can be used
- Equation of the output stability circle in the  $\Gamma_L$  plane:

$$|\Gamma_1| = 1 \quad \Gamma_1 = s_{11} + \frac{s_{12}s_{21}\Gamma_L}{1 - s_{22}\Gamma_L} \quad 1 = \left| s_{11} + \frac{s_{12}s_{21}\Gamma_L}{1 - s_{22}\Gamma_L} \right|$$



- Solution → circle  $|\Gamma_1| = 1$  in the  $\Gamma_L$  plane

- Centers 
$$C_L = \frac{s_{22}^* - s_{11}D^*}{|D|^2 - |s_{22}|^2}$$

- Radiuses 
$$r_L = \frac{|s_{12}s_{21}|}{|D|^2 - |s_{22}|^2}$$




- Stable/unstable region → can be differentiated according to  $s_{11}$  of the given transistor

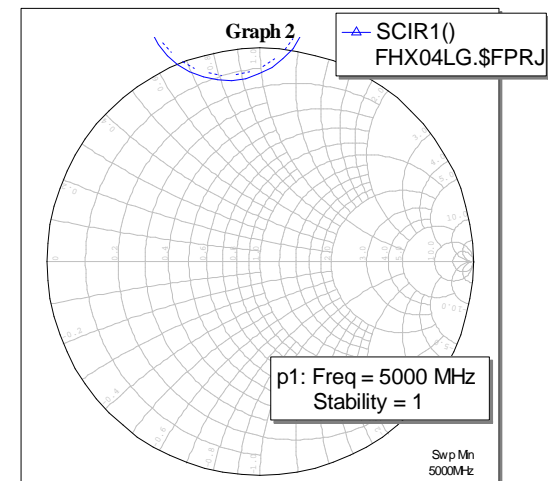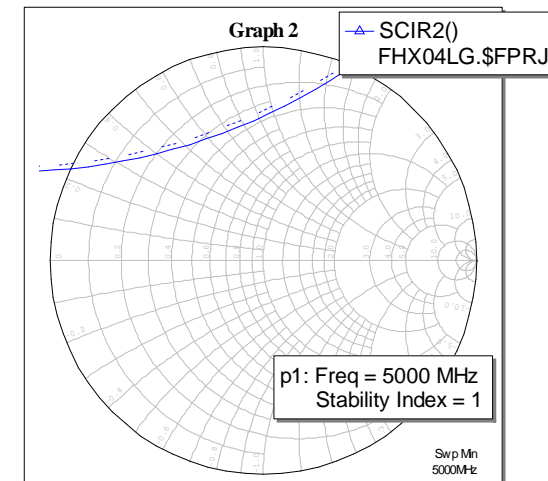- **AWR-MO:** **SCIR1** (in the  $\Gamma_G$  plane)  
**SCIR2** (in the  $\Gamma_L$  plane)



# Conditional Stability

- Ensuring **conditional amplifier stability** → the selected  $\Gamma_{Lz}$  must lie in the STABLE region
- AWR-MO** → the **SCIR2** plot, the UNSTABLE region is marked by the dashed circle
- The  $\Gamma_{Lz}$  chosen from the stable region – lead to  $|\Gamma_1| < 1$
- The  $\Gamma_{Lz}$  chosen from the unstable region – lead to  $|\Gamma_1| > 1$
- Example:** FHX04LG @ 5 GHz
- Stable region:  
 $\Gamma_{Lz} = 0,9 / -90^\circ$  lead to  $\Gamma_1 = 0,79 / -80^\circ$
- Unstable region:  
 $\Gamma_{Lz} = 0,9 / 90^\circ$  lead to  $\Gamma_1 = 1,1 / -98^\circ$
- AWR-MO** calculations → use the **LTUNER** model

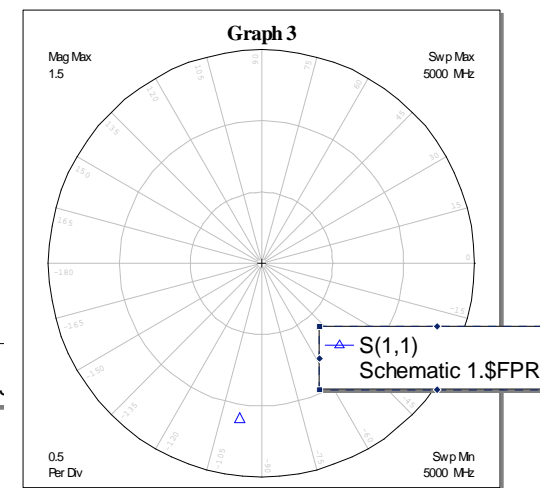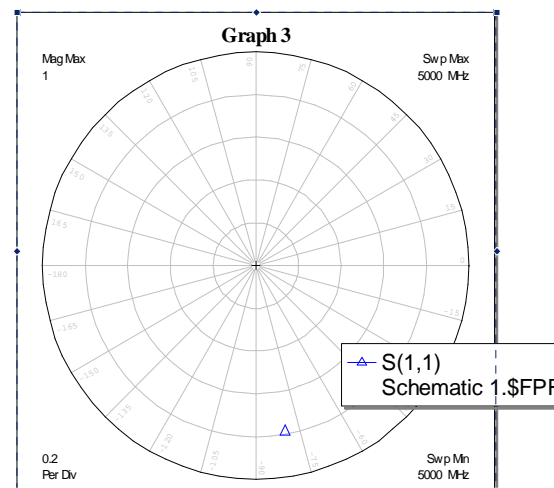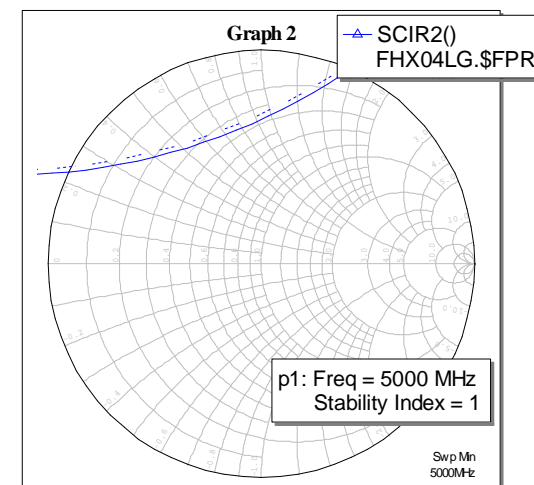

# Constant $G_p$ Circles

- Operational gain  $\rightarrow$  must be by 1-2 dB lower than  $G_{ms}$
- Can be ensured by using constant power gain  $G_p$  circles
- Power gain  $G_p \rightarrow$  depends on s-parameters and  $\Gamma_L$  (+ input impedance matching)
- Power gain circles**  $\rightarrow$  solution  $G_p = const.$  in the  $\Gamma_L$  plane

$$G_p = const = \frac{(1 - |\Gamma_L|^2) |s_{21}|^2}{|1 - s_{22}\Gamma_L|^2 (1 - |\Gamma_1|^2)} \quad \Gamma_1 = s_{11} + \frac{s_{12}s_{21}\Gamma_L}{1 - s_{22}\Gamma_L}$$

- Solution:**

- Centers


$$C_P = \frac{g(s_{22}^* - D^* s_{11})}{1 + g(|s_{22}|^2 - |D|^2)}$$

- Radiuses

$$r_P = \frac{(1 - 2k|s_{12}s_{21}|g + |s_{12}s_{21}|^2 g^2)^{\frac{1}{2}}}{|1 + g(|s_{22}|^2 - |D|^2)|}$$

$$g = \frac{G_P}{|s_{21}|^2} \quad D = s_{11}s_{22} - s_{12}s_{21}$$

- AWR-MO: GPCIR**

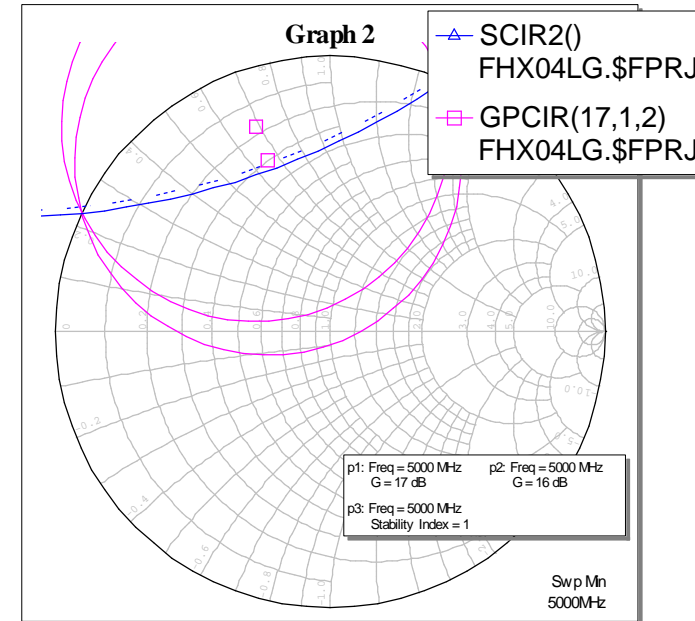

# Optimum Transistor Loading - $\Gamma_{Lz}$

- The selected  $\Gamma_{Lz}$  load:
  - Lies in the stable region
  - Lies on the required constant power gain circle
  - Close to the SD centre
- Often – the  $\Gamma_{Lz} = 0$  value can be chosen  $\rightarrow$  amplifier has no output matching circuit

- Input impedance matching  $\rightarrow$  **must be ideal**


$$\Gamma_G = \Gamma_1^*$$

- Calculation of  $\Gamma_1$ :

- Formula 
$$\Gamma_1 = s_{11} + \frac{s_{12}s_{21}\Gamma_{Lz}}{1 - s_{22}\Gamma_{Lz}}$$



- AWR-MO:**

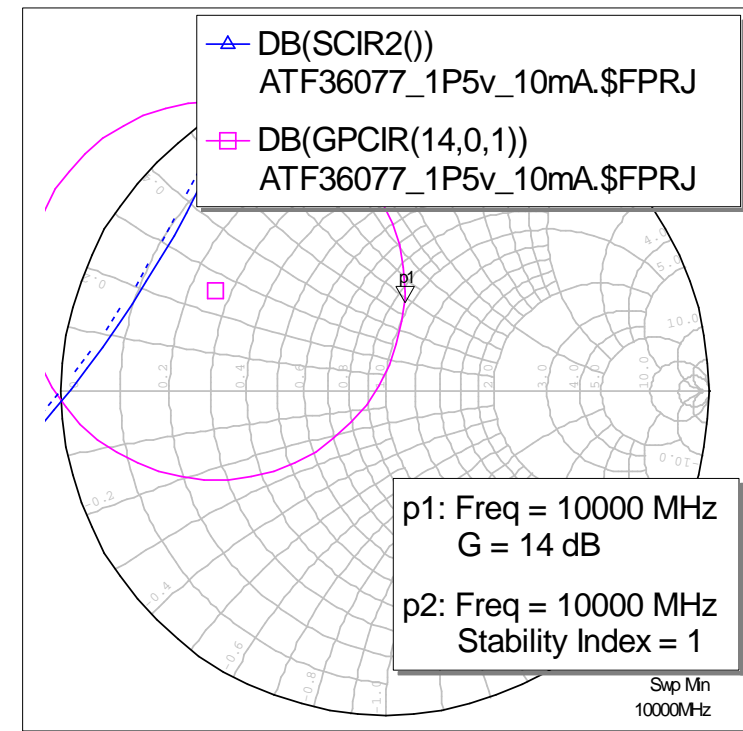- transistor
- LTUNER** at output simulates  $\Gamma_{Lz}$
- $S_{11} = \Gamma_1$


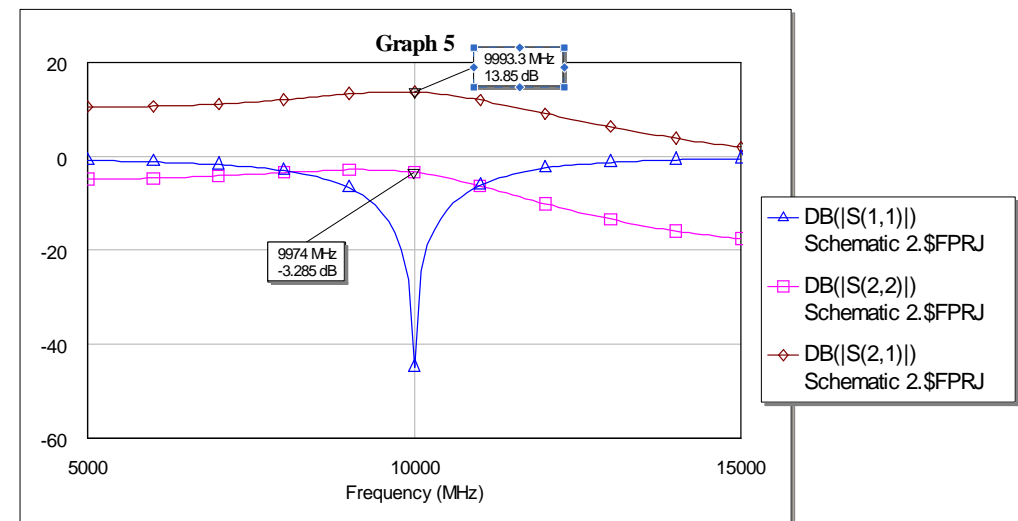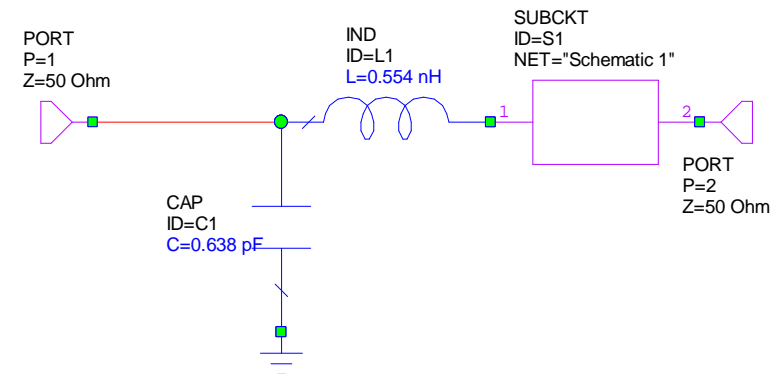
# Example – Task No. 3

- With the  $\Gamma_{Lz}$  and  $\Gamma_G = \Gamma_1^*$  values known  $\rightarrow$  input and output MCs can be synthesized
- **Example:** ATF36077 @ 10GHz
  - FET 1,5V / 10mA
  - $k=0,74$
  - MSG=16,38dB
  - Chosen  $G_p=14$ dB,  $\Gamma_{Lz} = 0$
- Lumped input matching circuit
- Obtained parameters @10GHz:
  - Gain  $G_t = G_p = 13,85$  dB
  - Input matching  $RL_{in} = -dBs11 = 42$ dB
  - Output matching  $RL_{out} = -dBs22 = 3,2$ dB
  - **Conditionally stable**





# Problems

- **Amplifiers based on potentially un-stable transistors show several significant disadvantages:**
- High reflection at output, commonly  $|\Gamma_{out}| \approx 0,8 \div 0,9$
- Conditional stability
  - Under definite circumstances → the amplifier can **start to oscillate**:
    - When disconnecting the input 50Ω source with active transistor biasing
    - When disconnecting the output 50Ω load with active transistor biasing
- Reason:
  - $\Gamma_L$  is realized from the  $|\Gamma| = 0$  load by the output MC
  - If  $|\Gamma| = 1 \rightarrow$  the real  $\Gamma_L$  can fall into the unstable region
  - The amplifier can start to oscillate
  - The same is valid for  $\Gamma_G$
  - Only hardly acceptable in the technical praxis






# Stabilization

- Possible solutions:
  - Balanced amplifier structure
  - Stabilization of the transistor used
- Transistor stabilization – connection of 1 or 2 **stabilizing resistors**
  - Low-noise amplifiers  $\rightarrow R_{p2}, R_{s2}$
  - Power amplifiers  $\rightarrow R_{s1}, R_{p1}$
  - Increase the stability coefficient from  $k < 1$  to  $k \cong 1,1$
- Combination transistor + stabilizing resistor = **new absolutely stable transistor**
- Design amplifier with absolutely stable transistor
- Resulting parameters:
  - $|\Gamma_{in}| \rightarrow 0$
  - $|\Gamma_{out}| \rightarrow 0$
  - $G_t \approx G_{ms} - 2dB$
  - Professional solution

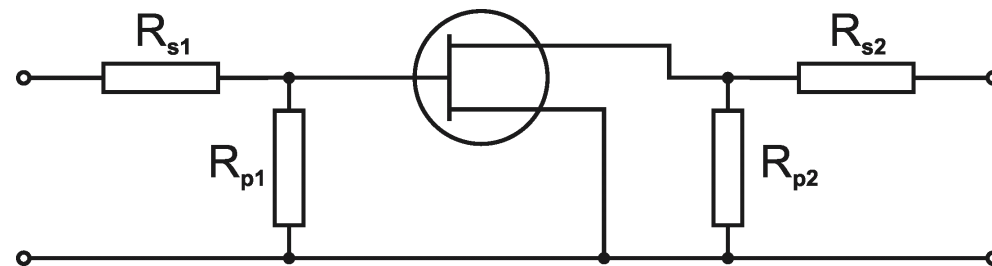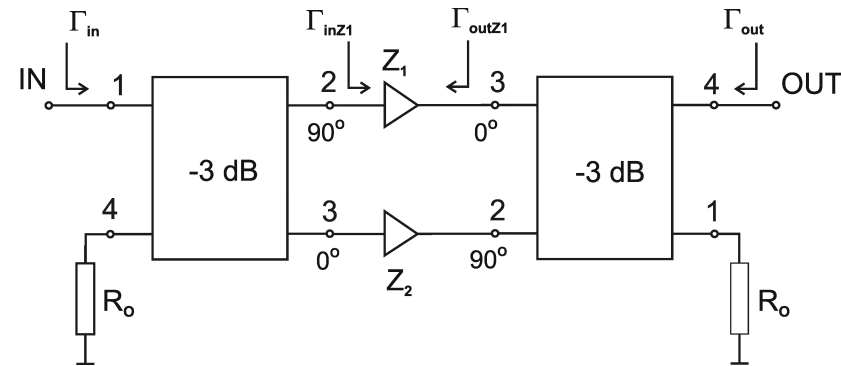

# Stabilization - Example

- **Example:** ATF36077 @10GHz
  - Stability coeff.  $k = 0,74$
  - Stabilized using  $R_{s1} = 5,3\Omega$
  - Resulting parameters:
    - Stability  $k = 1,2$
    - Gain  $G_t = 13,77 \text{ dB}$
    - Input matching  $|\Gamma_{in}|_{dB} > 42$
    - Output matching  $|\Gamma_{out}|_{dB} > 45$

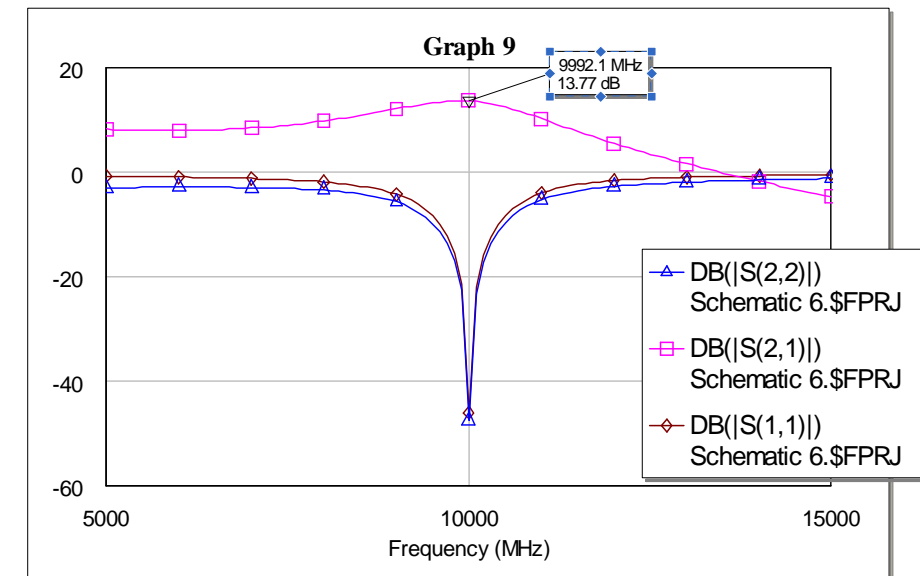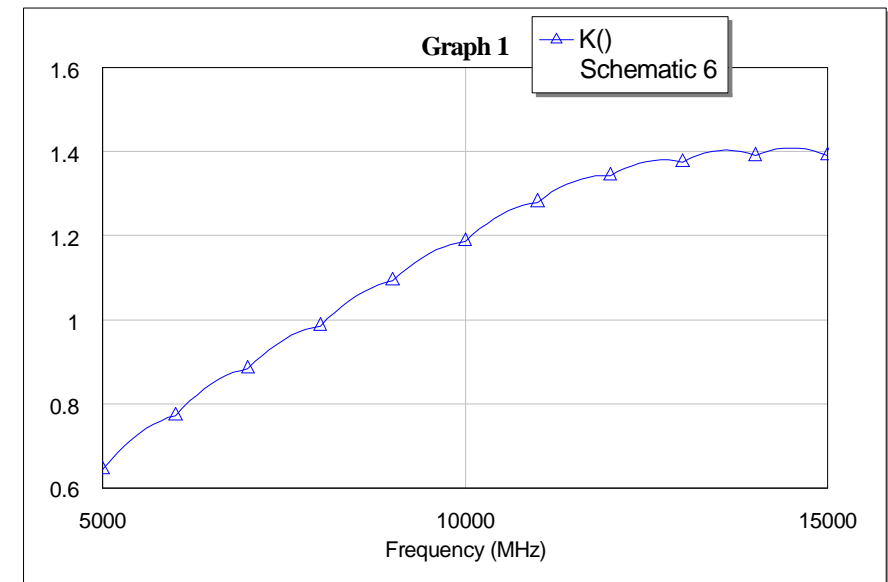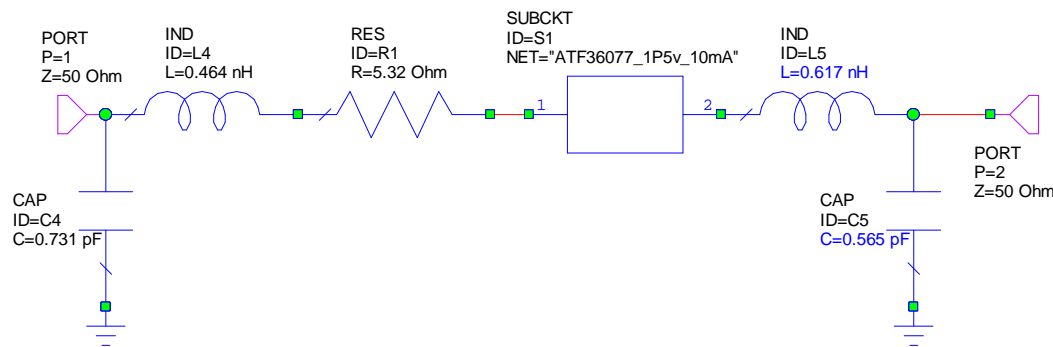

# Low-Noise Amplifiers


- **LNAs**
- Important at inputs of circuits or sub-systems processing very low-level signals
- Usually, at inputs of communication, satellite or radar receivers
- Input signal levels are lower than -100dBm often
- The receiver must ensure sufficient S/N ratio → in order to:
  - Ensure the required communication quality e.g. BER
  - Ensure the required radar detection range
- Basic noise parameters:
  - **Noise figure**
  - **Equivalent noise temperature**
  - **Design noise parameters**
- The above stated parameters are important for the LNA design

# S/N Definition of F

- Noise figure → the S/N definition:

$$F = \frac{\frac{S_1}{N_1}}{\frac{S_2}{N_2}}$$


- $S_1$  power of signal at the 2-port input
- $N_1$  power of noise at the 2-port input  $N_1 = k_B T_0 B$
- $S_2$  power of signal at the 2-port output
- $N_2$  power of noise at the 2-port output
- Important: **The definition is valid only if:**  $N_1 = k_B T_0 B$ 
  - $N_1$  Available noise power generated by the ideal  $Z_0$  impedance termination (black-body)
  - $k_B$  Boltzman's constant  $k_B = 1,38 \cdot 10^{-23} \text{ J / K}$
  - $T_0$  Definition temperature  $T_0 = 290K$
  - $B$  Frequency bandwidth

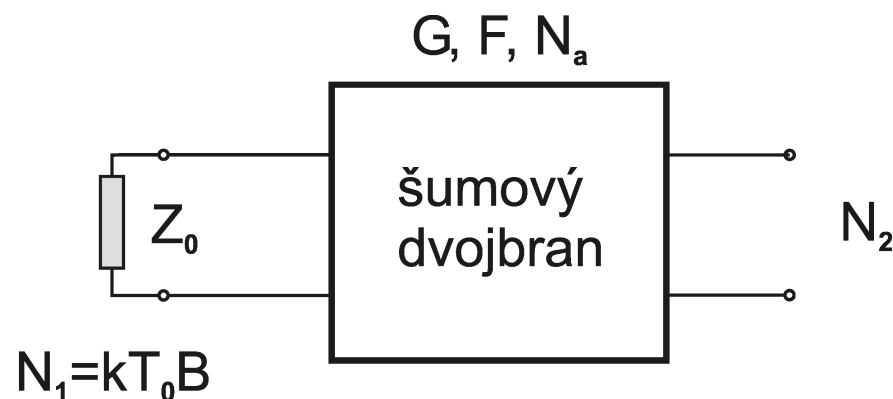

# S/N Definition of F

- Noise figure - the S/N definition:
  - Important for the communication, radar,... system design
  - S/N is one of the parameters decisive for BER
  - Cannot be used easily in cascades  $\rightarrow N_1$  is no more  $k_B T_0 B$
  - More complex formulas must be used for analysis of the cascaded noise 2-ports
- All powers = **available powers from the generator**  $P_{AL}$  (into the conjugate load)
- If all components are well matched  $\rightarrow$  insertion gain can be used
- Amplifier design  $\rightarrow S_1$  is not known usually
- That is why the **power F definition** can be more suitable
- F often stated in dB:

$$F_{dB} = 10 \log(F)$$

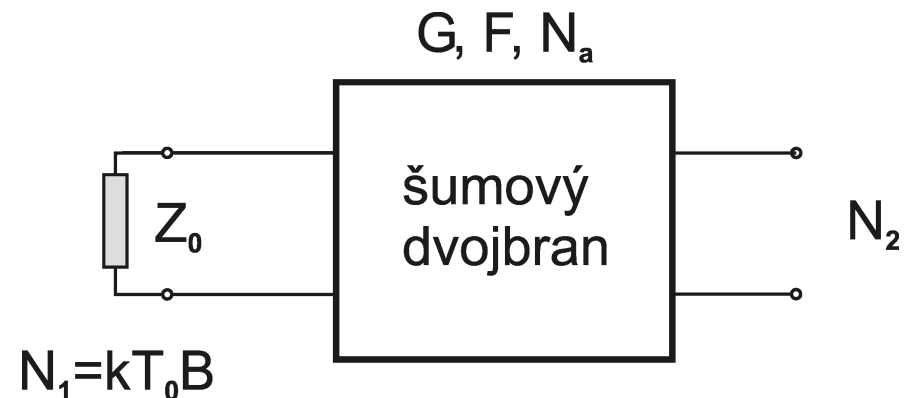

# Power Definition of F


- Power F definition:**

$$F = \frac{N_2}{GN_1} = \frac{GN_1 + N_a}{GN_1} = \frac{kT_0BG + N_a}{kT_0BG} = 1 + \frac{N_a}{kT_0BG}$$

- Total output noise power divided by the amplified noise  $N_1 = k_B T_0 B$  from the input  $Z_0$  impedance termination
- $N_2$  consists of the amplified  $N_1$  noise and the  $N_a$  noise added by the 2-port itself (referred to output)
- Can be derived from the S/N definition using the (available) gain  $G = S_2 / S_1$

$$F = \frac{S_1 N_2}{S_2 N_1} = \frac{N_2}{GN_1}$$


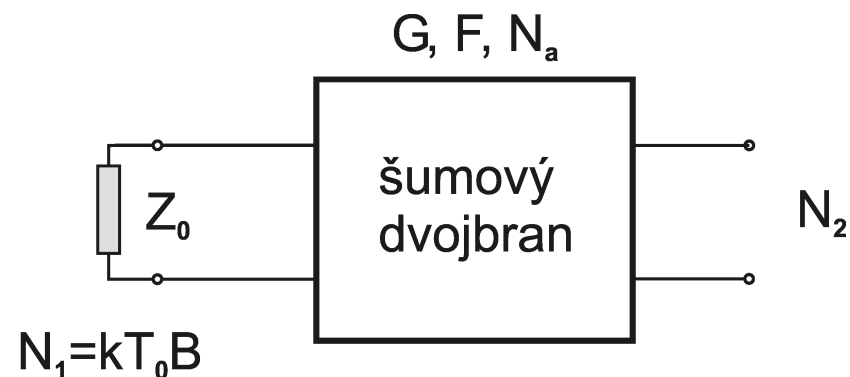
- Noise added** ref. to input  $N_a = (F - 1)k_B T_0 B$
- Noise added** ref. to output  $N_a = (F - 1)k_B T_0 BG$
- Suitable for calculations of cascades


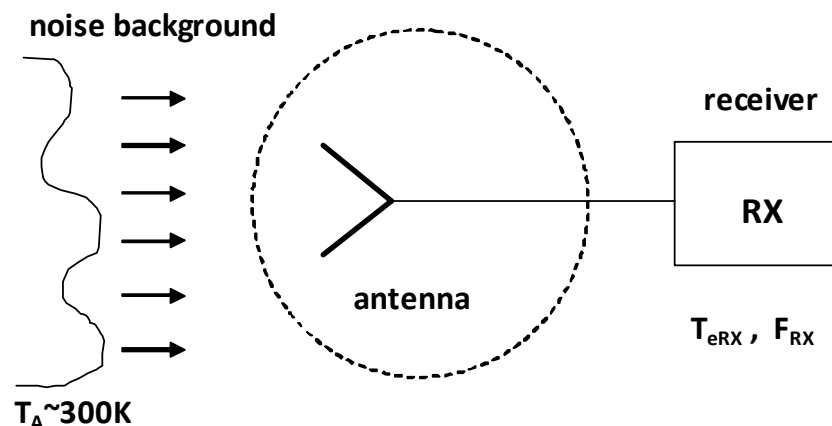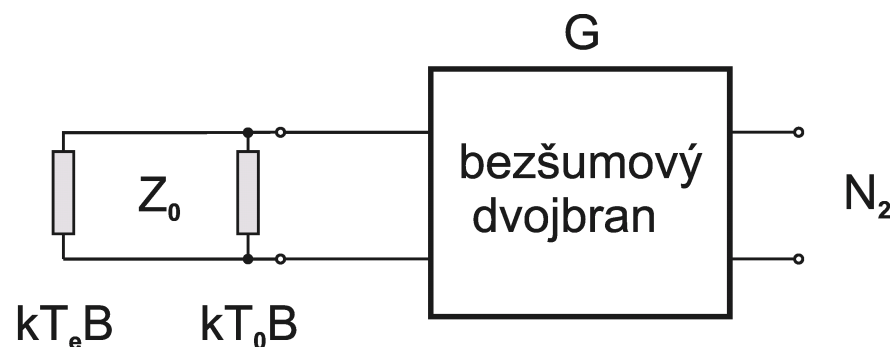
# Equivalent Noise Temperature - $T_e$

- All noise sources are removed from the 2-port and replaced by an additional virtual impedance termination kept at equivalent temperature  $T_e$
- Corresponding output noise power:  $N_2 = k_B T_0 B G + k_B T_e B G$
- From the F definition:  $N_2 = k_B T_0 B G + N_a = k_B T_0 B G + (F - 1) k_B T_0 B G$
- Comparison:  $k_B T_e B G = (F - 1) k_B T_0 B G$
- **Definition:**  $T_e = (F - 1) T_0$
- **Applications:**
  - Low F values (radio-astronomy)
    - $F=1,1$  (0,41dB)  $T_e=29K$
    - $F=1,15$  (0,61dB)  $T_e=43,5K$
  - Noise description of receiver input circuits
  - Enable to take into account the noise background „seen“ by the antenna

$$T_{sys} = T_A + T_{eRX} \quad F_{sys} = T_{sys} / T_0 + 1$$




# Design Noise Parameters

- Design noise parameters → necessary for LNA design
- 1 complex number + 2 scalar numbers → together **4 scalar numbers + frequency**
- Can be derived from the noisy 2-port equivalent circuit
- All 2-port inner noise sources are replaced with 2 noise sources in the input circuit
- The solution can be derived in the 1-1' plane → the rest of circuit is noise-less

- Noise figure 
$$F = \frac{P_{na1}}{P_{ng}}$$

- $P_{na1}$  total available noise power in the 1-1' plane

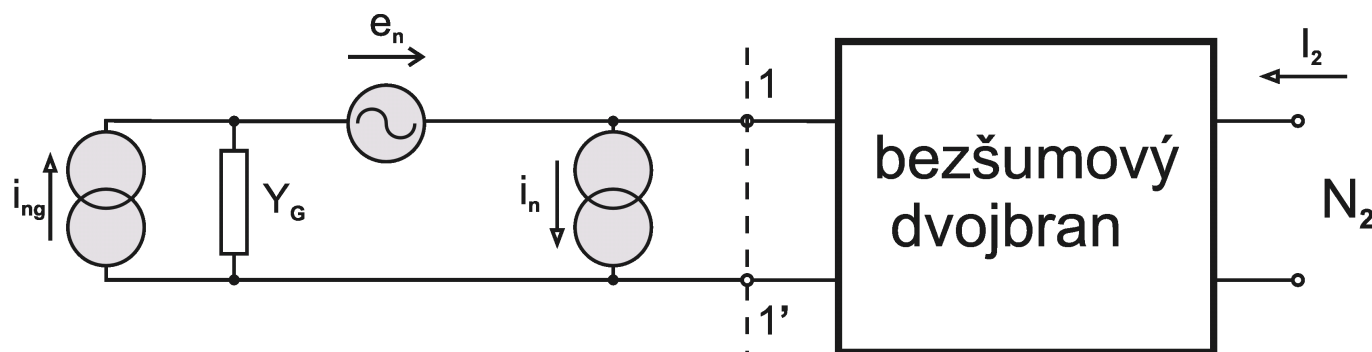- $P_{ng}$  noise power of the  $Y_G$  (general admittance) generator at  $T_0 = 290 K$





# Noise Equivalent Circuit

- The  $P_{na1}$  noise power can be calculated from the  $i_{nc}$  total **noise current in the short-circuited 1-1' plane**
- Using superposition and the Thevenin rules:


$$i_{nc1} = i_{ng} \quad i_{nc2} = -e_n Y_G \quad i_{nc3} = -i_n \quad i_{nc} = i_{ng} - (i_n + e_n Y_G)$$

- Noise power  $\rightarrow$  corresponds to the mean-square value

$$E[|i_{nc}|^2] = E[(i_{ng} - (i_n + e_n Y_G))(i_{ng} - (i_n + e_n Y_G))^*] = E[|i_{ng}|^2] - 2 \operatorname{Re} E[i_{ng} (i_n + e_n Y_G)^*] + E[|i_n + e_n Y_G|^2]$$

- Uncorrelated variables:  $E[x.y] = E[x]E[y]$


- White noise  $E[i_{ng}] = 0$

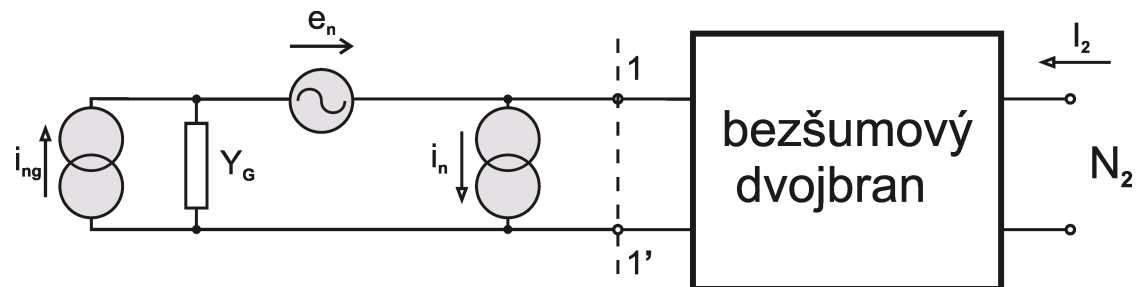

# Correlated Noise Sources


- From that 
$$E[|i_{nc}|^2] = E[|i_{ng}|^2] + E[|i_n + e_n Y_G|^2]$$
- Inner noise sources  $i_n$  and  $e_n$  can be **partially correlated**
- The correlation can be described using:  $i_n = i_{nn} + Y_{cor} e_n$
- $Y_{cor}$  = **correlation admittance**  $Y_{cor} = G_{cor} + jB_{cor}$
- $i_{nn}$  = 100% **uncorrelated component**
- $Y_{cor} e_n$  = 100% **correlated component**
- From that: 
$$i_{nc} = i_{ng} - (i_{nn} + Y_{cor} e_n + Y_G e_n) = i_{ng} - i_{nn} - e_n (Y_{cor} + Y_G)$$
- All 3 components are non-correlated → the mean-square value can be expressed as:

$$E[|i_{nc}|^2] = E[|i_{ng}|^2] + E[|i_{nn}|^2] + |Y_{cor} + Y_G|^2 E[|e_n|^2]$$

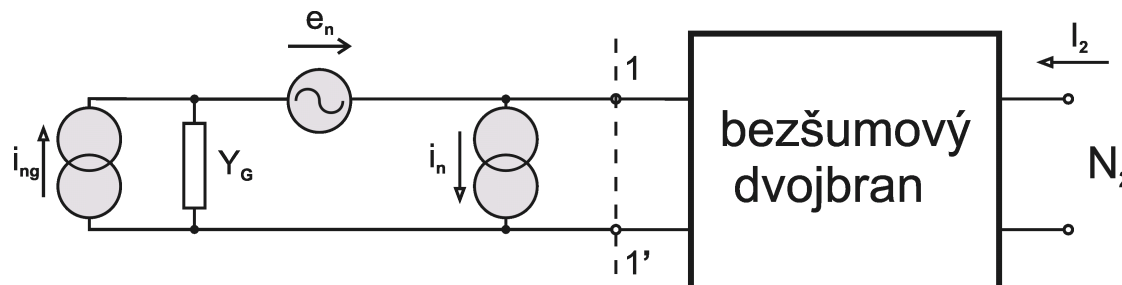


# Noise Parameter Set: $G_n$ , $R_n$ , $G_{cor}$ , $B_{cor}$

- Noise power  $P_{na1}$  :  $P_{na1} = E[|i_{nc}|^2] = E[|i_{ng}|^2] + E[|i_{nn}|^2] + |Y_{cor} + Y_G|^2 E[|e_n|^2]$
- Noise power  $P_{ng}$  :  $P_{ng} = E[|i_{ng}|^2]$
- Noise figure: 
$$F = \frac{E[|i_{nc}|^2]}{E[|i_{ng}|^2]} = 1 + \frac{E[|i_{nn}|^2]}{E[|i_{ng}|^2]} + \frac{E[|e_n|^2]}{E[|i_{ng}|^2]} |Y_{cor} + Y_G|^2$$
- Equivalent expressions:  $E[|e_n|^2] = 4kT_0 B R_n$     $E[|i_{nn}|^2] = 4kT_0 B G_n$     $E[|i_{ng}|^2] = 4kT_0 B G_G$
- From that: 
$$F = 1 + \frac{G_n}{G_G} + \frac{R_n}{G_G} |Y_{cor} + Y_G|^2$$
- 4 noise parameter set:**  $G_n$     $R_n$     $Y_{cor} = G_{cor} + jB_{cor}$

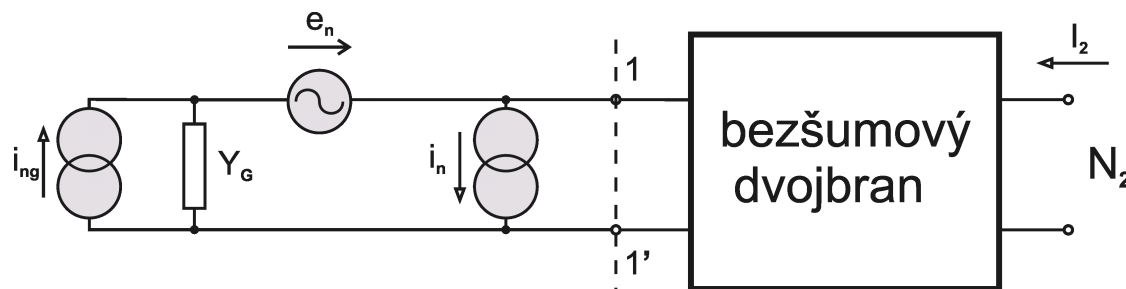

# Noise Parameter Set: $G_n$ , $R_n$ , $G_{cor}$ , $B_{cor}$

- **Noise figure:** 
$$F = 1 + \frac{G_n}{G_G} + \frac{R_n}{G_G} |Y_{cor} + Y_G|^2$$
- Set of 4 design noise parameters:  $G_n$ ,  $R_n$ ,  $Y_{cor} = G_{cor} + jB_{cor}$
- Describe dependence of F on  $Y_G = G_G + jB_G$
- This set of noise parameters → often used in **calculation cores of noise analysis programs**
- But  $Y_{cor}$  is **difficult to be measured**
- That is why another sets of design noise parameters are also used
- The most frequently used set can be derived from the above presented noise parameters by finding minimum value of the noise figure  $F$  as a function of  $Y_G = G_G + jB_G$

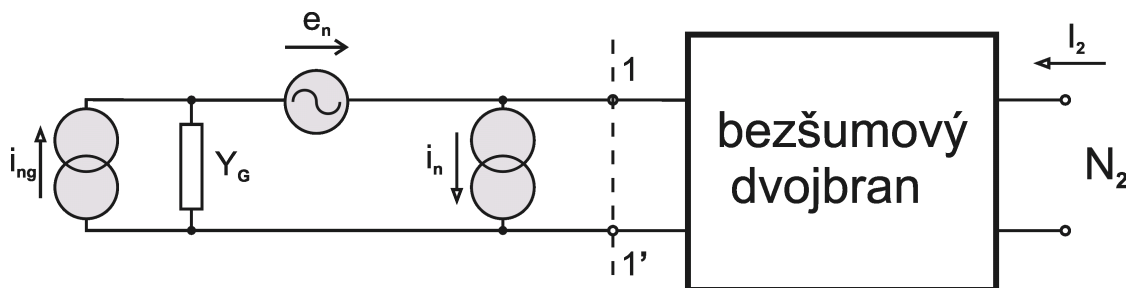

# Noise Parameter Set: $F_{\min}$ , $R_n$ , $G_{\text{opt}}$ , $B_{\text{opt}}$


- Noise figure: 
$$F = 1 + \frac{G_n}{G_G} + \frac{R_n}{G_G} |Y_{\text{cor}} + Y_G|^2$$
- Minimum of F: 
$$\frac{\partial F}{\partial B_G} = \frac{R_n}{G_G} 2(B_G + B_{\text{cor}}) = 0$$
  

$$\frac{\partial F}{\partial G_G} = -\frac{G_n}{G_G^2} + \left\{ -\frac{R_n}{G_G^2} [(G_G + G_{\text{cor}})^2 + (B_G + B_{\text{cor}})^2] + 2 \frac{R_n}{G_G} (G_G + G_{\text{cor}}) \right\} = 0$$
- From that → the **optimum generator conductance**  $G_{\text{Gopt}}$  and the **optimum generator susceptance**  $B_{\text{Gopt}}$  providing the **lowest achievable**  $F = F_{\min}$  value can be derived:

$$B_{\text{Gopt}} = -B_{\text{cor}}$$

$$G_{\text{Gopt}} = \left( \frac{G_n}{R_n} + G_{\text{cor}} \right)^{\frac{1}{2}}$$
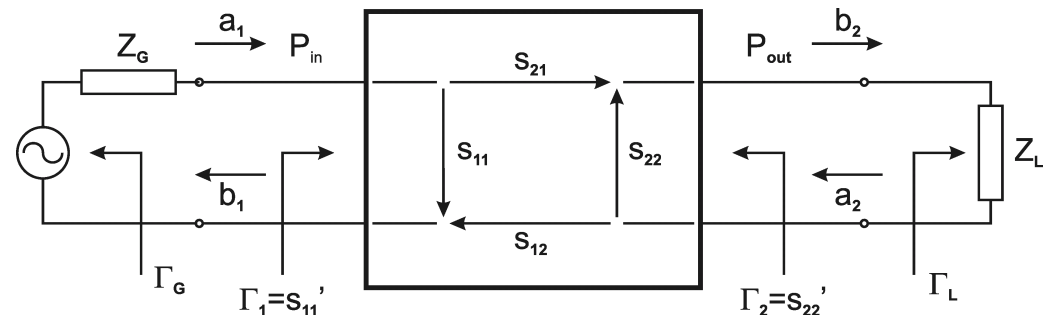
$$F_{\min} = 1 + 2R_n (G_{\text{Gopt}} + G_{\text{cor}})$$




# Noise Parameter Set: $F_{\min}$ , $R_n$ , $|\Gamma_{Gopt}|$ , $\Phi_{Gopt}$

- **Noise figure:** 
$$F = F_{\min} + \frac{R_n}{G_G} \left[ (G_G - G_{Gopt})^2 + (B_G - B_{Gopt})^2 \right] = F_{\min} + \frac{R_n}{G_G} |Y_G - Y_{Gopt}|^2$$
- If gate or base of the transistor used „sees“  $Y_{Gopt} = G_{Gopt} + jB_{Gopt}$  the **optimum generator admittance** → its noise figure  $F = F_{\min}$
- If not, the resulting noise figure increases
- The  $R_n$  **noise resistance** → defines how fast F increases
- Low  $R_n$  values are advantageous
- For design of RF & microwave amplifiers → noise parameters based on  $\Gamma_G$  and  $\Gamma_{Gopt}$  are beneficial


$$F = F_{\min} + 4 \frac{R_n}{Z_0} \frac{|\Gamma_G - \Gamma_{Gopt}|^2}{|1 + \Gamma_{Gopt}|^2 (1 - |\Gamma_G|^2)}$$

- Corresponding design noise parameters:  $R_n$   $F_{\min}$   $\Gamma_{Gopt} = |\Gamma_{Gopt}| e^{j\Phi_{Gopt}}$

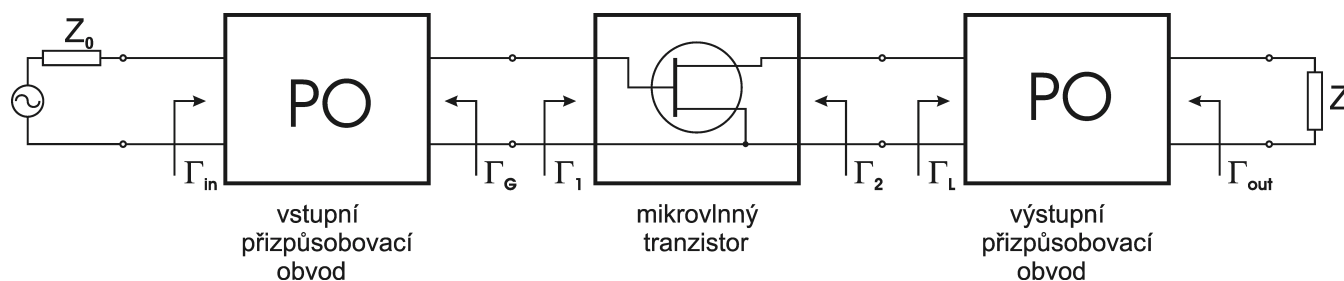

# Noise Parameter Set: $F_{\min}$ , $R_n$ , $|\Gamma_{\text{Gopt}}|$ , $\Phi_{\text{Gopt}}$

- Measurement:
  - Using the **variable impedance transformer** (IT) and the **noise figure measurement device** (NF)
  - Closer description in A0M17MMS
  - Using the variable IT  $\rightarrow$  the minimum noise figure  $F = F_{\min}$  of the DUT is found
  - The corresponding  $\Gamma_G = \Gamma_{\text{Gopt}}$  is measured using the VNA
  - The  $R_n$  value can be calculated from the additional  $\Gamma_G = 0$  measurement
  - In practice:
    - Measurement of  $F$  for more  $\Gamma_G$  values
    - Solution of set of equations
  - Measurement of design noise parameters  $\rightarrow$  **demanding**
- For the LNA design  $\rightarrow$  noise parameters appended to the s-parameter file
- Signal and noise analysis run in parallel

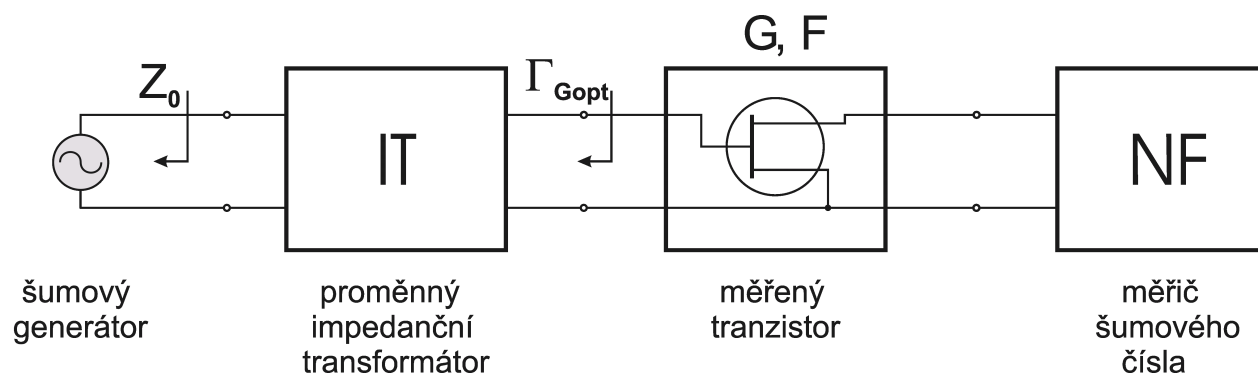

# Example: AWR-MO transistor data file

!fhx04lg.s2p

!8/88

!FHX04/05/06LG

!@2V-10mA

!.1GHZ 20GHZ 22

# GHZ S MA R 50

! S-parameter data

1.0	.990	-19.3	4.232	162.1	.016	75.1	.576	-14.3
2.0	.965	-37.5	4.115	144.1	.030	64.8	.563	-28.1
3.0	.928	-55.2	3.923	127.4	.042	53.3	.546	-41.2

16.0	.557	151.8	2.151	-43.2	.066	-22.2	.642	177.8
17.0	.522	140.9	2.142	-56.9	.067	-29.4	.673	169.5
18.0	.480	128.4	2.136	-71.2	.068	-39.2	.694	159.7

! Noise data 4/90

2	0.33	0.99	29.0	.43
4	0.35	0.97	53.0	.30
6	0.45	0.93	77.0	.20

14	0.88	0.63	178.0	.03
16	1.05	0.53	-156.0	.05
18	1.30	0.42	-129.0	.09

Transistor Fujitsu

FHX04LG, FHX05LG, FX06LG

2V/10mA

f [GHz] s11 s21 s12 s22

Design noise parameters

f [GHz]  $F_{\min}$  dB  $|\Gamma_{\text{opt}}|$   $\arg(\Gamma_{\text{opt}})$   $R_n/Z_0$




# Cascade of Noisy 2-Ports

- Each circuit or system contain more noisy elements always
- In case of their cascade connection → the Frii's formula can be used
- The cascade noise figure → can be derived using the  **$N_a$  added noise powers**:

$$N_{a1} = (F_1 - 1)kT_0B \quad N_{a2} = (F_2 - 1)kT_0B \quad N_{a3} = (F_3 - 1)kT_0B$$

$$\begin{aligned} N_2 &= kT_0BG_1G_2G_3 + N_{a1}G_1G_2G_3 + N_{a2}G_2G_3 + N_{a3}G_3 = \\ &= kT_0B[G_1G_2G_3 + (F_1 - 1)G_1G_2G_3 + (F_2 - 1)G_2G_3 + (F_3 - 1)G_3] \end{aligned}$$

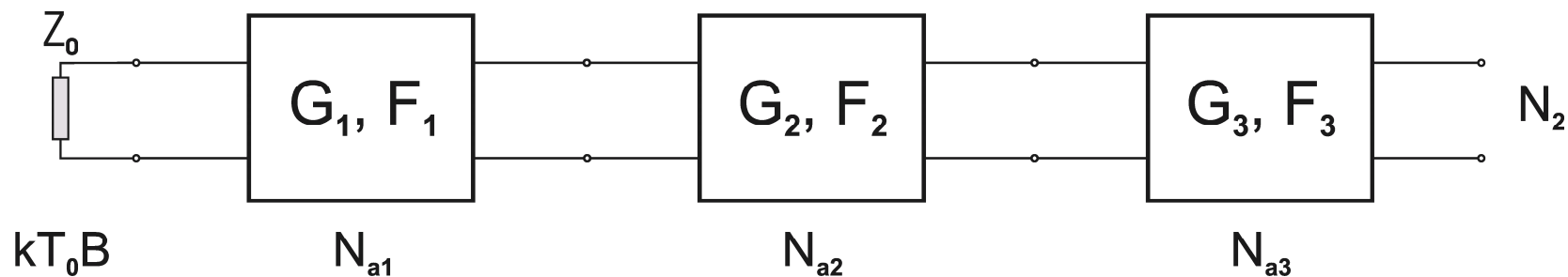- **The Frii's formula:** 
$$F = \frac{N_2}{kT_0BG_1G_2G_3} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1G_2}$$



# Noise Figure of Passive 2-Ports

- Noise of any **passive lossy matched 2-port** (e.g. attenuator):
  - Behaves as the  $Z_0$  impedance termination  $N_2 = k_B T_0 B$
  - The signal is amplified by:  $G = 1/L$
- **Noise figure:** 
$$F = \frac{N_2}{GN_1} = \frac{kT_0 B}{\frac{kT_0 B}{L}} = L$$
- The same applies to all lossy 2-ports with very good impedance matching: **Attenuators, cables, inter-connecting lines, RF filters (in the pass-band), RF switches, ...**
- But also to multi-ports with only 2 ports considered: **Splitters, directional couplers, ...**
- **Consequences** of the Frii's formula:
  - LNAs must show high associate gain
  - Cascade connection of the attenuator  $L$  and amplifier  $F_2$ :  $F = L + (F_2 - 1)L = L + LF_2 - L = LF_2$
  - Any attenuation  $L$  at input increases the overall noise figure:  $F_{dB} = L_{dB} + F_{2dB}$
  - This also concerns input matching circuits → their loss directly increase  $F$


# Recommended LNA Design Steps

## 1. Choice of the suitable transistor

- Specialized low-noise transistors (HEMT) → acceptable  $F_{\min}$  and  $G_{as}$ , low  $R_n$  = advantage
- Proper biasing →  $F_{\min}$  depends upon  $I_{CE}$  or  $I_{DS}$
- Design noise parameters:  $R_n$   $F_{\min}$   $\Gamma_{Gopt} = |\Gamma_{Gopt}| e^{j\phi_{Gopt}}$  → from the catalog or by measurement
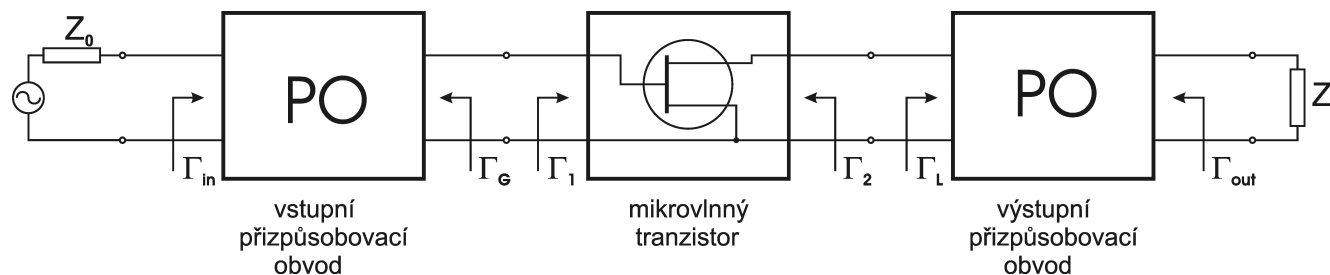
## 2. Noise matching

- Performed in the  $\Gamma_G$  plane
- Optimum noise matching  $\Gamma_G = \Gamma_{Gopt}$
- Absolutely stable transistor → output impedance matching  $\Gamma_L = \Gamma_2^*$
- Potentially unstable transistor
  - o Both  $\Gamma_G = \Gamma_{Gopt}$  and  $\Gamma_L = \Gamma_2^*$  must lie in the stable regions
  - o Or stabilization of the transistor by using  $R_{p2}$  or  $R_{s2}$
- Since  $\Gamma_{Goptnoise} \neq \Gamma_{Goptpower}$ , the LNAs show high input reflection



# LNA design

## 3. Possible compromise → noise matching versus input reflection:


- **Constant noise figure**  $F_i$  **circles** can be plotted into the  $\Gamma_G$  plane

Centers  $C_F = \frac{\Gamma_{Gopt}}{1 + N_i}$

Diameters  $r_F = \frac{1}{1 + N_i} \left[ N_i^2 + N_i \left( 1 - |\Gamma_{Gopt}|^2 \right) \right]^{\frac{1}{2}}$

$$N_i = \frac{(F_i - F_{min})Z_0}{4R_n} |1 + \Gamma_{Gopt}|^2$$

- **AWR-MO: NFCIR**

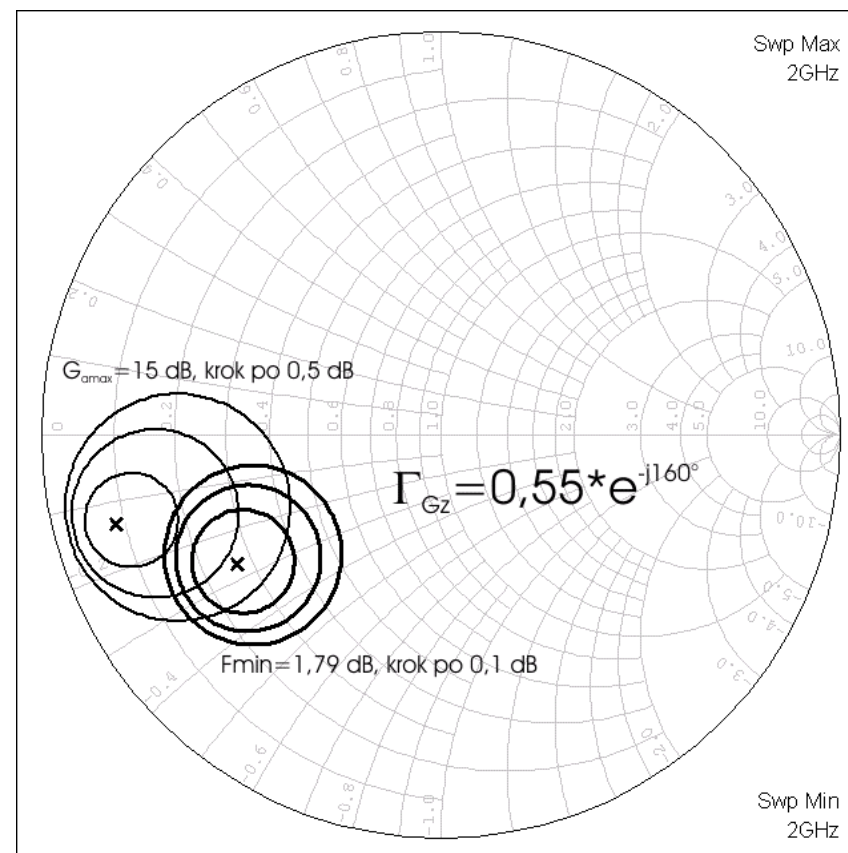

# LNA design

- **Constant available gain circles** can also be plotted into the  $\Gamma_G$  plane:


Centers 
$$C_a = \frac{g_a (s_{11}^* - D^* s_{22})}{1 + g_a (|s_{11}|^2 - |D|^2)}$$

Diameters 
$$r_a = \frac{\left(1 - 2k |s_{12} s_{21}| g_a + |s_{12} s_{21}|^2 g_a^2\right)^{\frac{1}{2}}}{1 + g_a (|s_{11}|^2 - |D|^2)}$$

Norm. gains 
$$g_a = \frac{G_a}{|s_{21}|^2}$$

- **AWR-MO: GACIR**

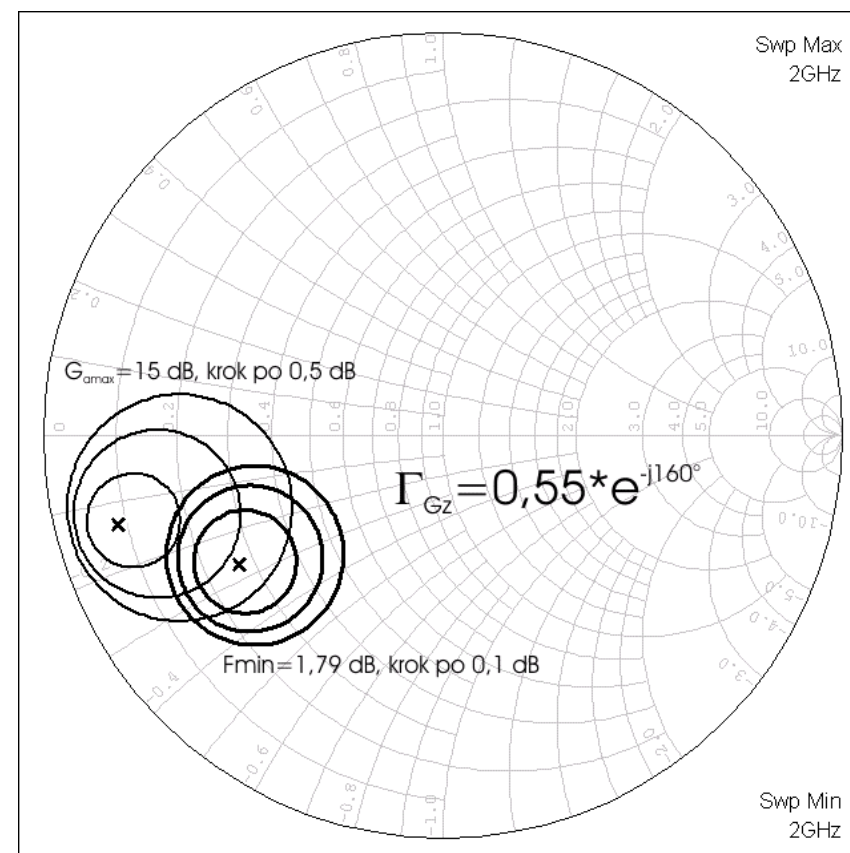- The compromise  $\Gamma_G = \Gamma_{Gz}$  can be found
- Higher  $F$  but lower  $\Gamma_{in}$
- Not much recommended
- Lower  $\Gamma_{in}$  can be obtained by  $R_{s2}$



# LNA design

## 4. Output impedance matching is beneficial

$$\Gamma_L = \Gamma_2^* \quad \Gamma_2 = s_{22} + \frac{s_{12}s_{21}\Gamma_{Gz}}{1 - s_{11}\Gamma_{Gz}}$$


**AWR-MO: LTUNER**

With  $\Gamma_{Gz}$  and  $\Gamma_L$  known, the input and output matching circuits can be synthesized

- Input MC transforms  $Z_0$  to  $\Gamma_{Gz}$  or  $\Gamma_{Gopt}$
- Output MC transforms  $Z_0$  to  $\Gamma_L$

## 5. Resulting amplifier parameters:




- Since  $\Gamma_{Goptnoise} \neq \Gamma_{Goptpower} \rightarrow$  significant input reflections appear  $|\Gamma_{in}| \approx 0,6 \div 0,9$
- Output can be ideally matched  $|\Gamma_{out}| \rightarrow 0$
- Gain is equal to associate gain  $G_{as}$

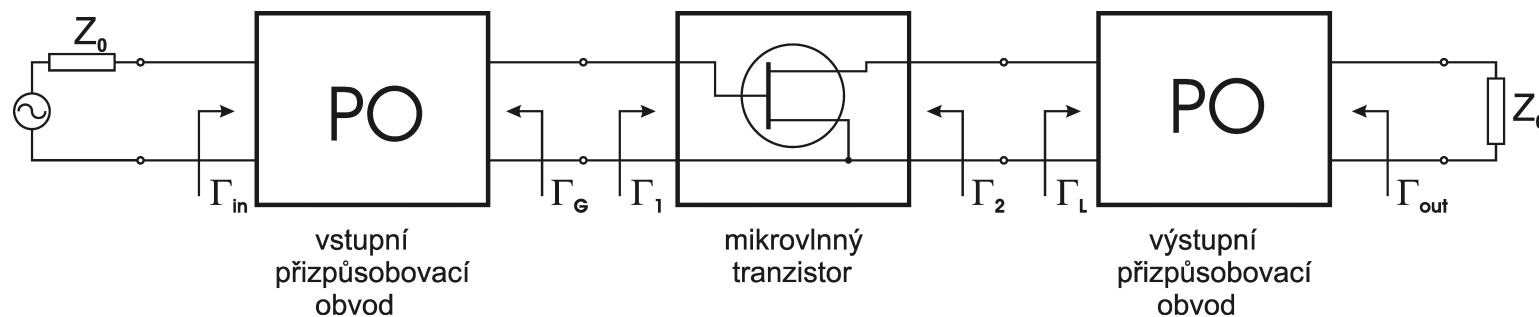

# LNA Example 1
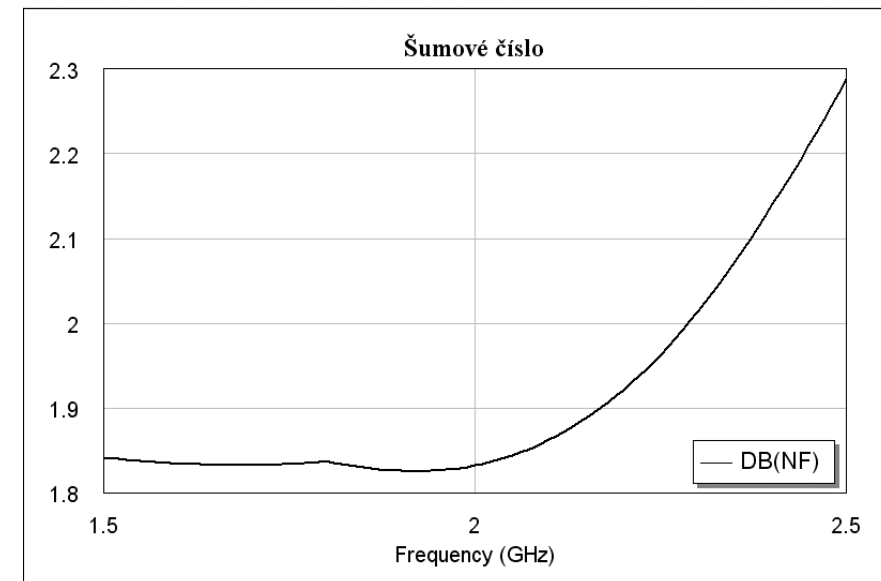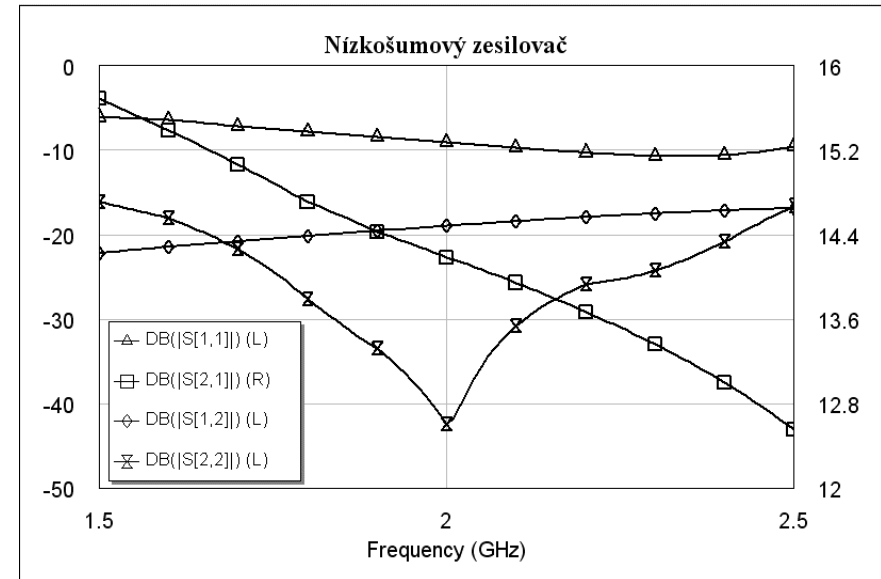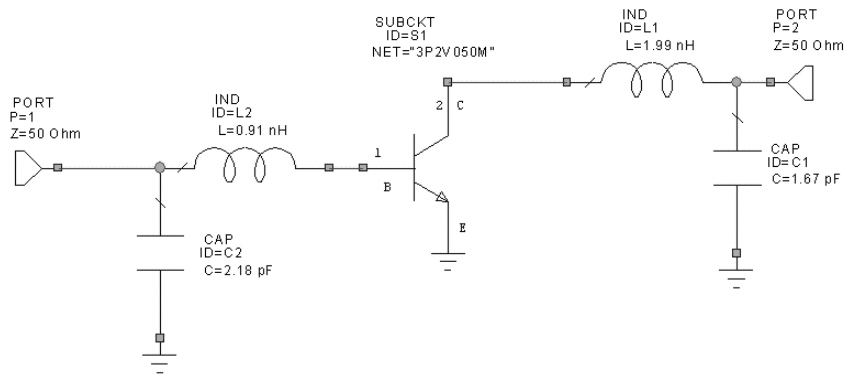
## 6. Example:

- BJT BFP450
- Frequency 2 GHz
- Chosen generator  $\Gamma_G = \Gamma_{Gz} = 0,55 e^{-j160^\circ}$



# LNA Example 2

## 6. Example: ATF-34143, FET 2V / 20mA

- $f=8\text{GHz}$  ,  $k=1,1$  ,  $F_{\min}=0,95\text{dB}$
- $\text{GMN}=0,47$  /  $-86^\circ$
- Minimum F design
- Optimum output matching
- Resulting parameters:
  - o  $F=1,05\text{dB}$
  - o Input matching
  - o Output matching

